


5

BUILDING

LOW ENTROPY EXPRESSIONS

WITH MINIMUM WORK

Double-pole low-pass LC filter

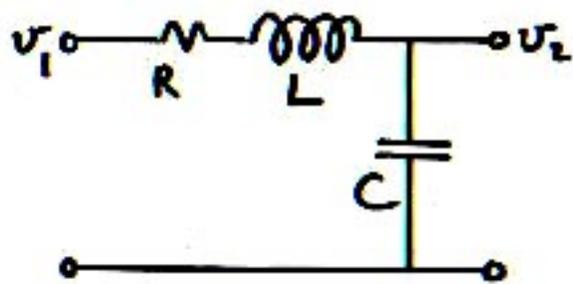

$$\frac{v_2}{v_1} = \frac{1}{1 + sRC + s^2LC}$$

$$= \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2}$$

in which

$$\omega_0 \equiv \frac{1}{\sqrt{LC}} \quad \leftarrow \text{corner (resonant) frequency}$$

$$= \frac{1}{\left(1 + \frac{s}{\omega_1} \right) \left(1 + \frac{s}{\omega_2} \right)}$$

↑ roots ↑

$$Q \equiv \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR} = \frac{R_0}{R} \quad \text{where } R_0 \equiv \sqrt{\frac{L}{C}}$$

↑ characteristic resistance

$Q < 0.5$: roots ω_1 and ω_2 are real

$Q > 0.5$: roots ω_1 and ω_2 are complex

$$\frac{Z_2}{Z_1} = \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$


$$\left| \frac{Z_2}{Z_1} \right| \xrightarrow{\omega \rightarrow 0} 1 \Rightarrow 0 \text{ dB}$$

$$\xrightarrow{\omega \rightarrow \infty} \left(\frac{\omega_0}{\omega}\right)^2$$

Asymptotes intersect at ω_0

Asymptotes are independent of Q ;

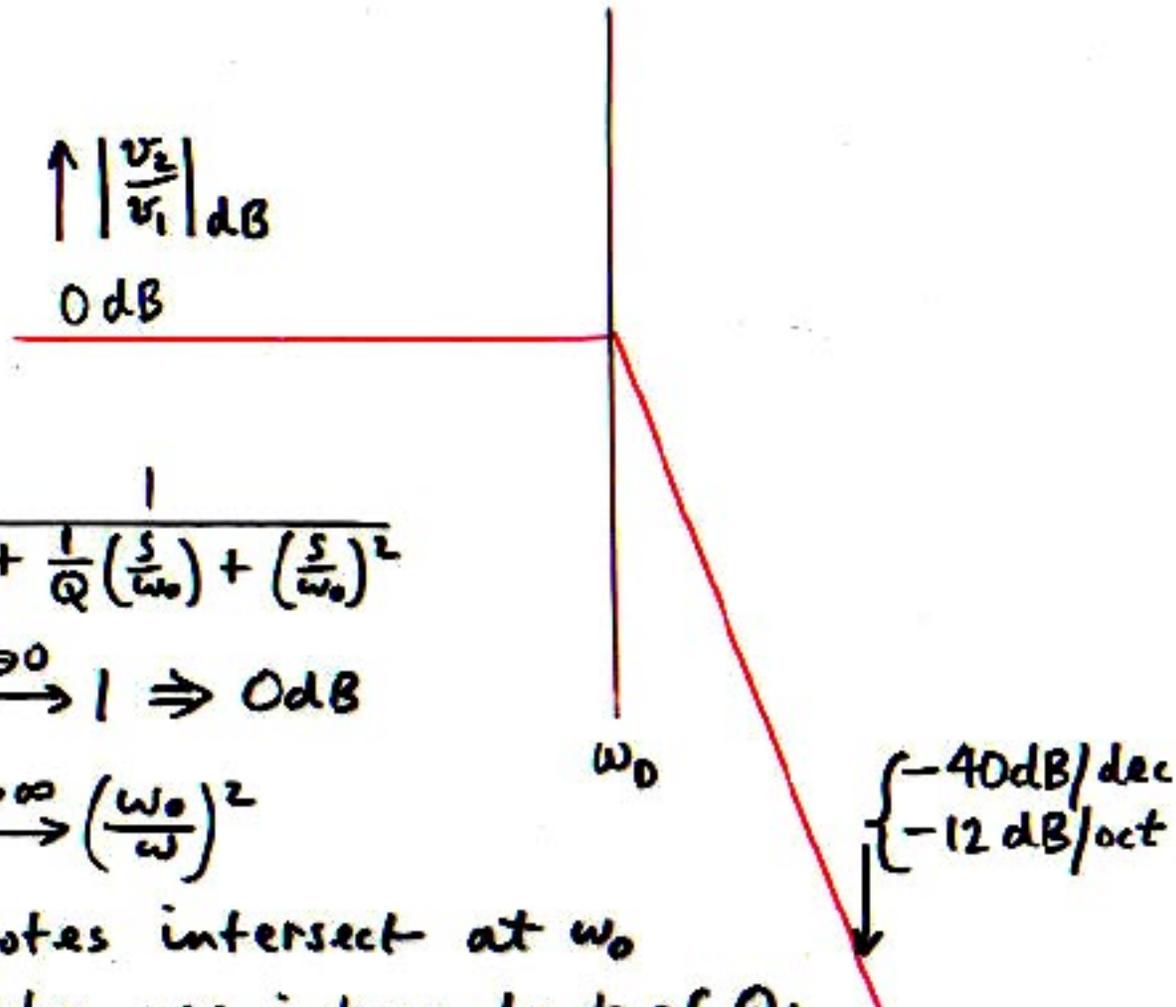Q affects shape only in neighborhood of ω_0





$$\frac{v_2}{v_1} = \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2}$$


$$\left| \frac{v_2}{v_1} \right| \xrightarrow{\omega \rightarrow 0} 1 \Rightarrow 0 \text{ dB}$$

$$\xrightarrow{\omega \rightarrow \infty} \left(\frac{\omega_0}{\omega} \right)^2$$

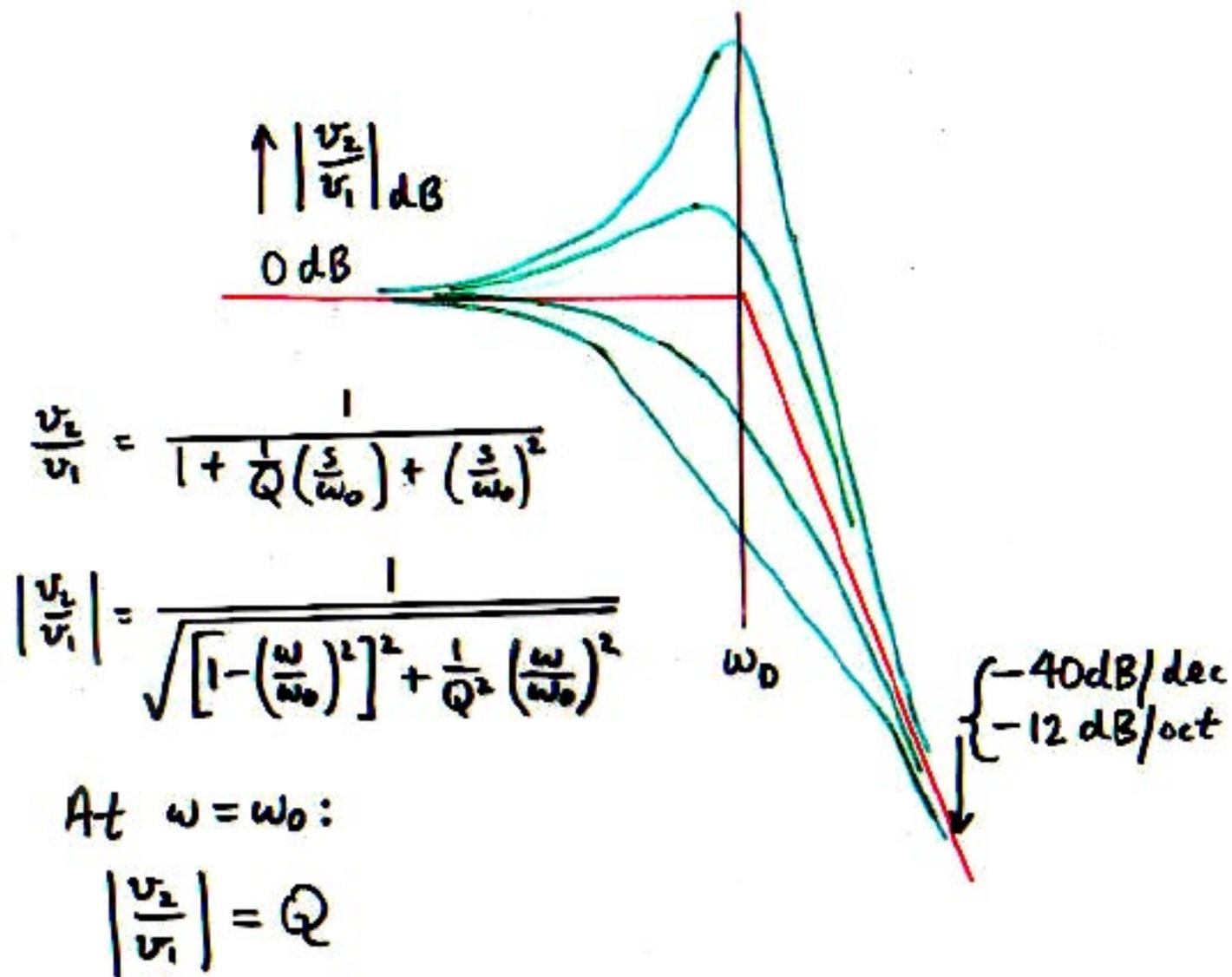Asymptotes intersect at ω_0
 Asymptotes are independent of Q ;
 Q affects shape only in neighborhood of ω_0



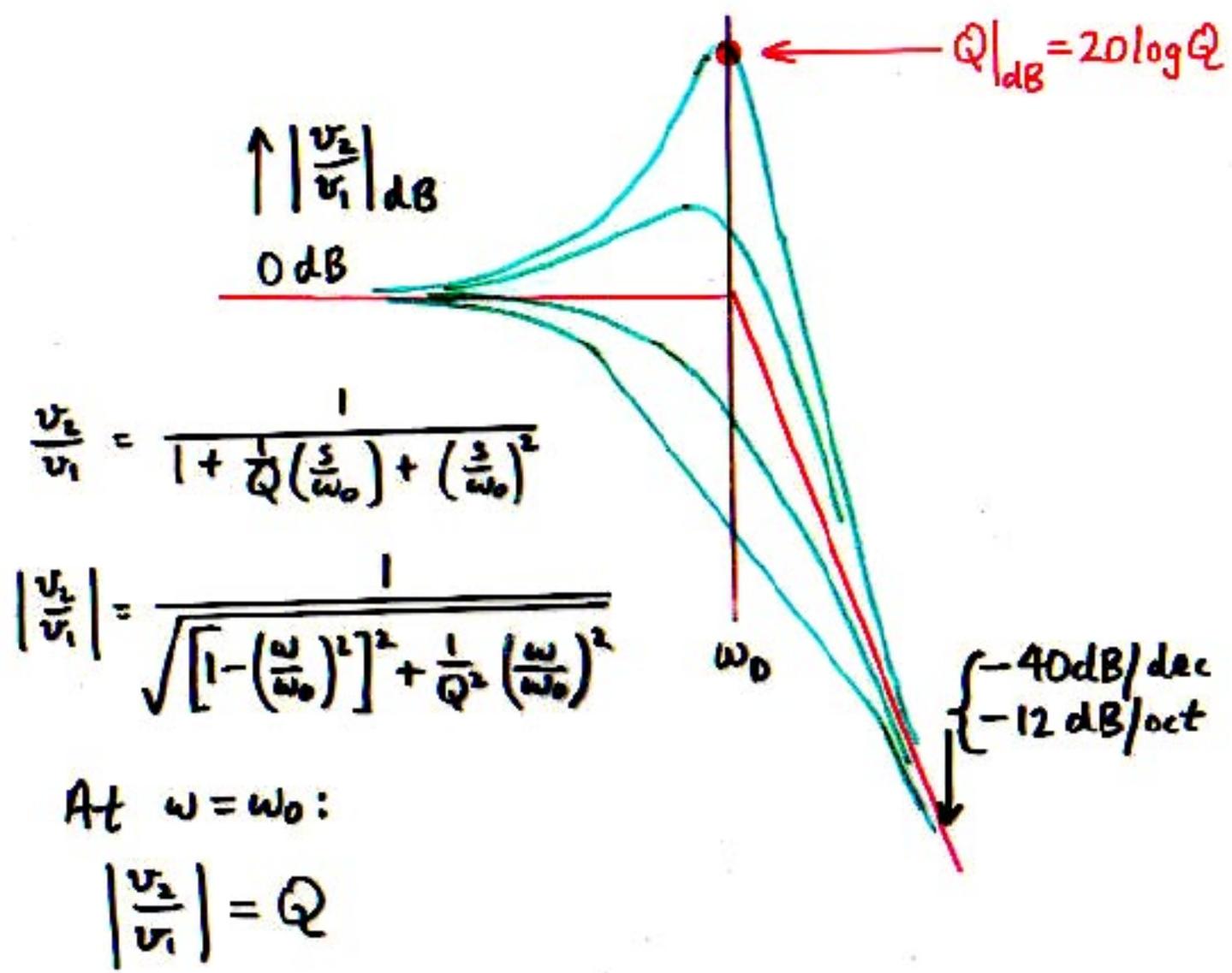

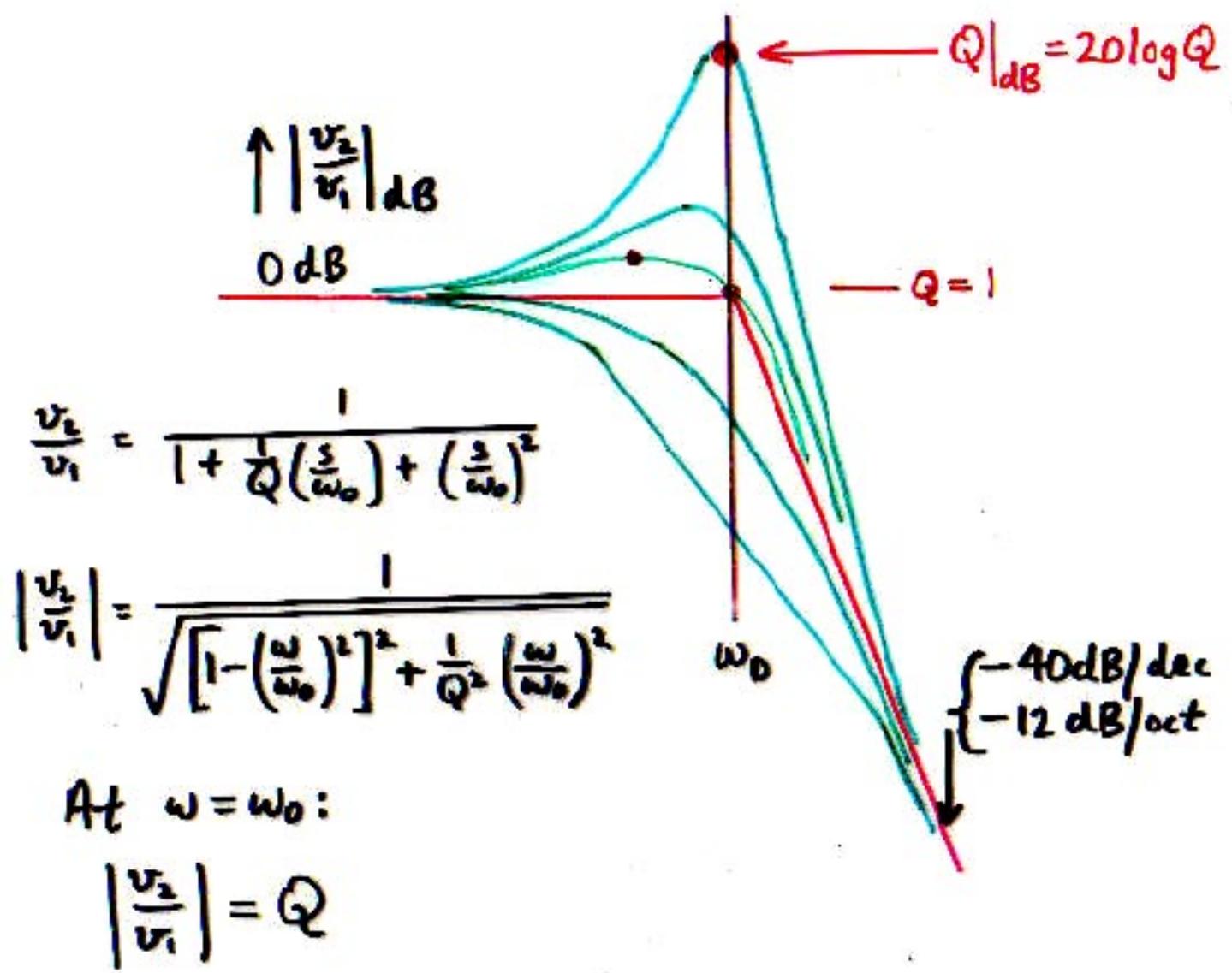


$$\frac{v_2}{v_1} = \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2}$$

$$\left| \frac{v_2}{v_1} \right| = \frac{1}{\sqrt{\left[1 - \left(\frac{\omega}{\omega_0} \right)^2 \right]^2 + \frac{1}{Q^2} \left(\frac{\omega}{\omega_0} \right)^2}}$$

At $\omega = \omega_0$:

$$\left| \frac{v_2}{v_1} \right| = Q$$

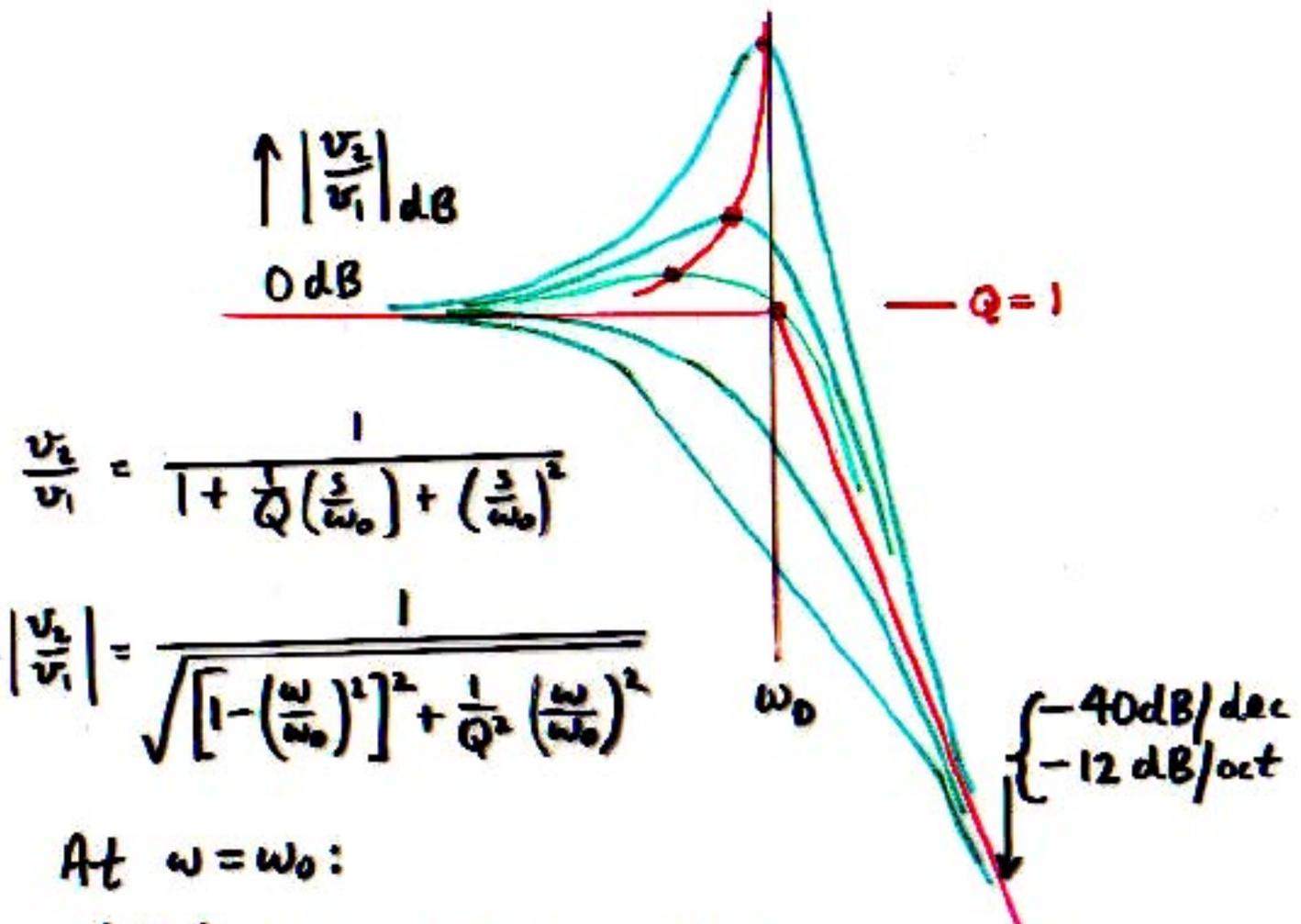


$$\frac{v_2}{v_1} = \frac{1}{1 + \frac{1}{Q} \left(\frac{\omega}{\omega_0} \right) + \left(\frac{\omega}{\omega_0} \right)^2}$$

$$\left| \frac{v_2}{v_1} \right| = \frac{1}{\sqrt{\left[1 - \left(\frac{\omega}{\omega_0} \right)^2 \right]^2 + \frac{1}{Q^2} \left(\frac{\omega}{\omega_0} \right)^2}}$$

At $\omega = \omega_0$:

$\left| \frac{v_2}{v_1} \right| = Q$ which is not the maximum;
 the maximum moves to the left for
 lower Q .

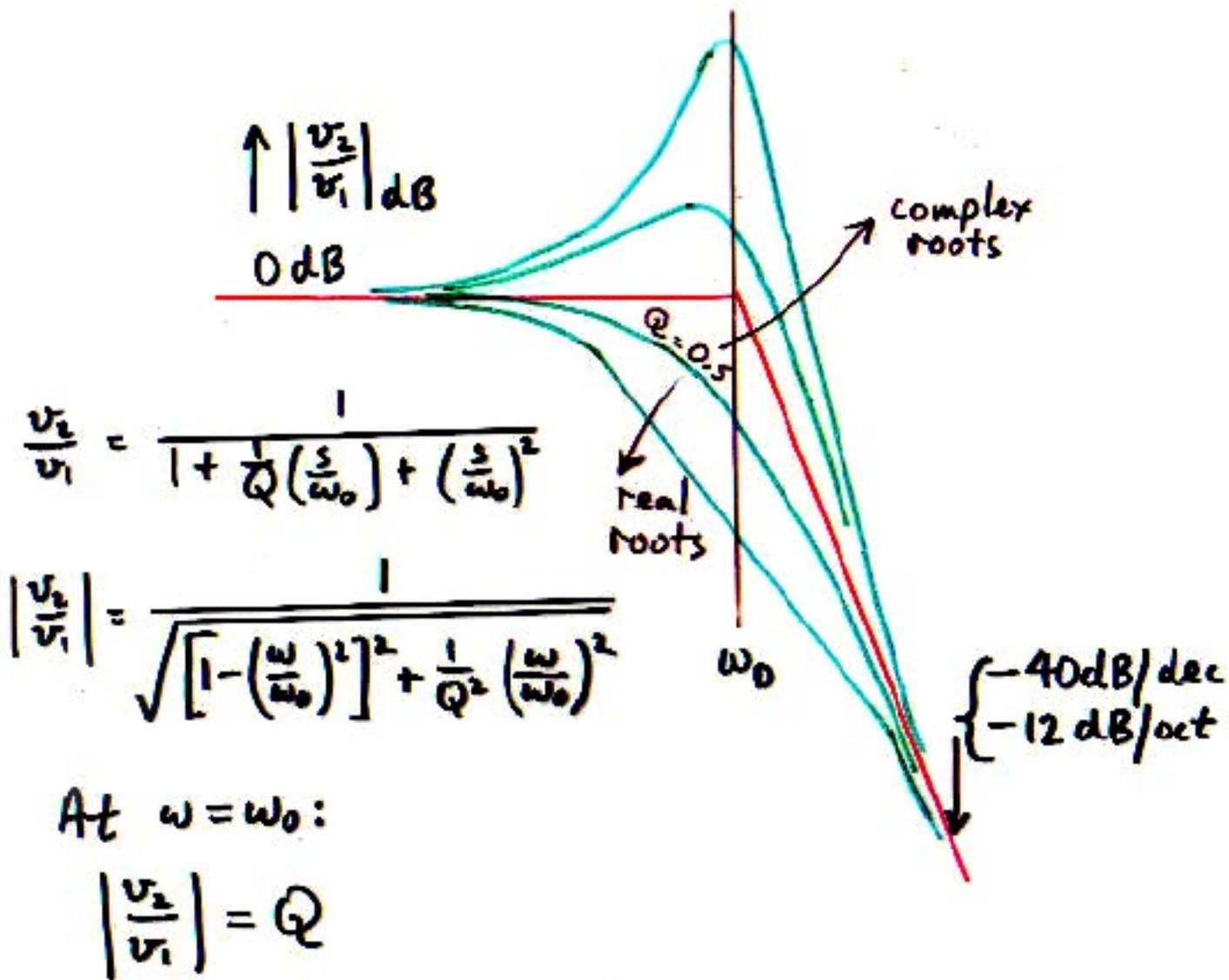


Phase shape:

$$\angle \frac{v_2}{v_1} = - \tan^{-1} \left[\frac{\frac{1}{Q} \left(\frac{\omega}{\omega_0} \right)}{1 - \left(\frac{\omega}{\omega_0} \right)^2} \right]$$

$\omega \rightarrow 0$	0°
$\omega = \omega_0$	-90°
$\omega \rightarrow \infty$	-180°

} independent of Q

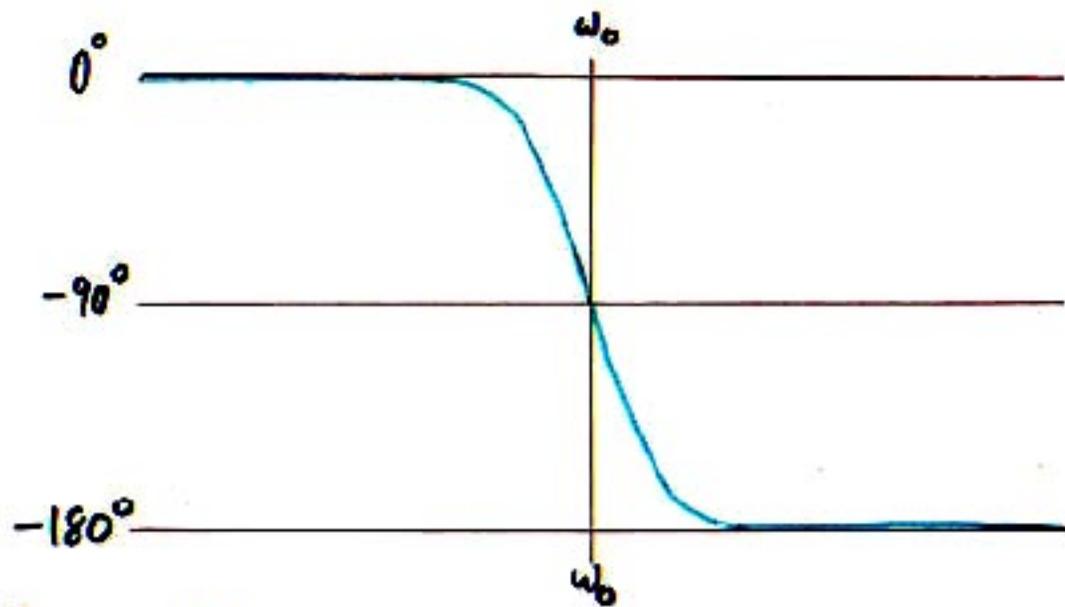


Phase shape:

$$\angle \frac{v_2}{v_1} = -\tan^{-1} \left[\frac{\frac{1}{Q} \left(\frac{\omega}{\omega_0} \right)}{1 - \left(\frac{\omega}{\omega_0} \right)^2} \right]$$


$\omega \rightarrow 0$	\rightarrow	0°	}
$\omega = \omega_0$	\rightarrow	-90°	
$\omega \rightarrow \infty$	\rightarrow	-180°	

independent
of Q

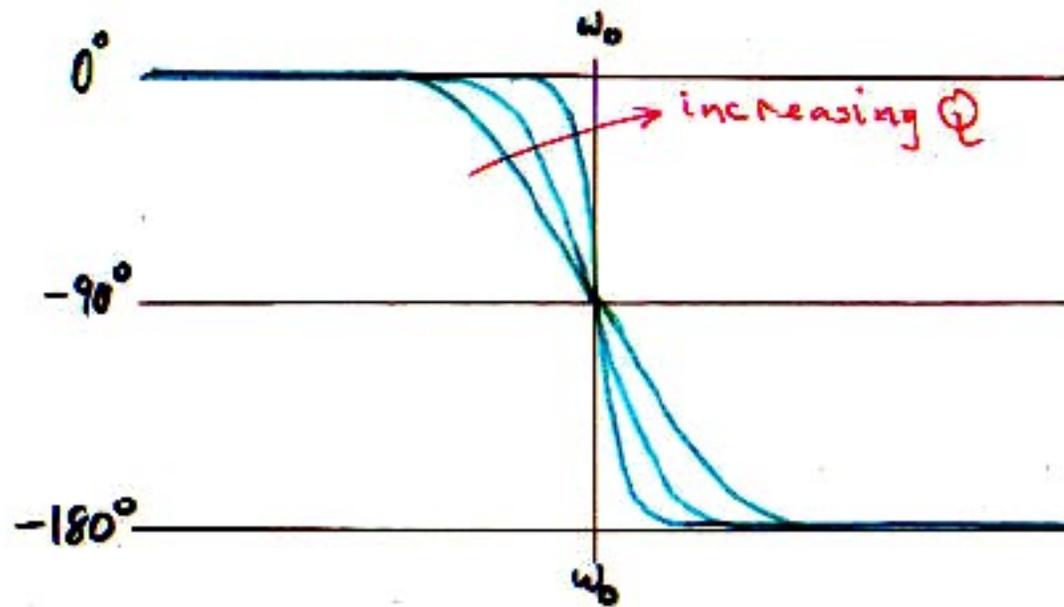


Increased Q causes sharper phase change between the 0° and -180° asymptotes.

Need: a straight-line approximation.

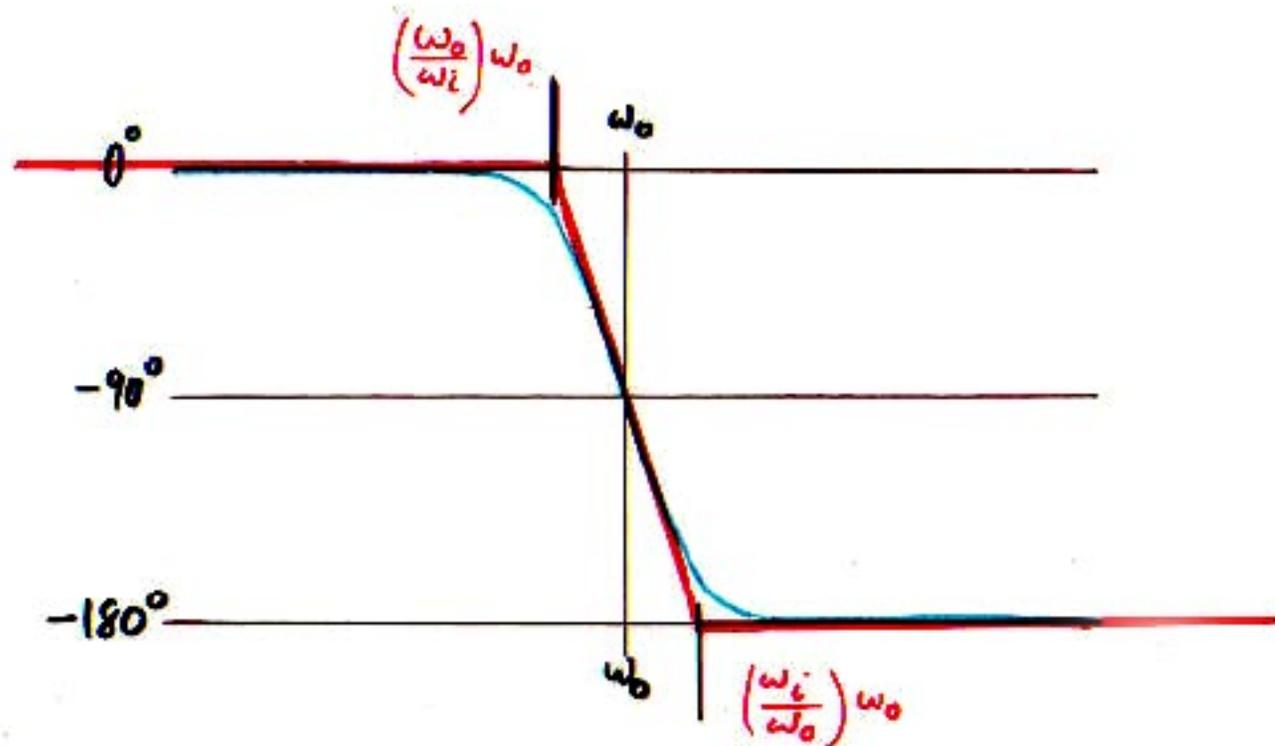

Choose same slope at $\omega = \omega_0$:
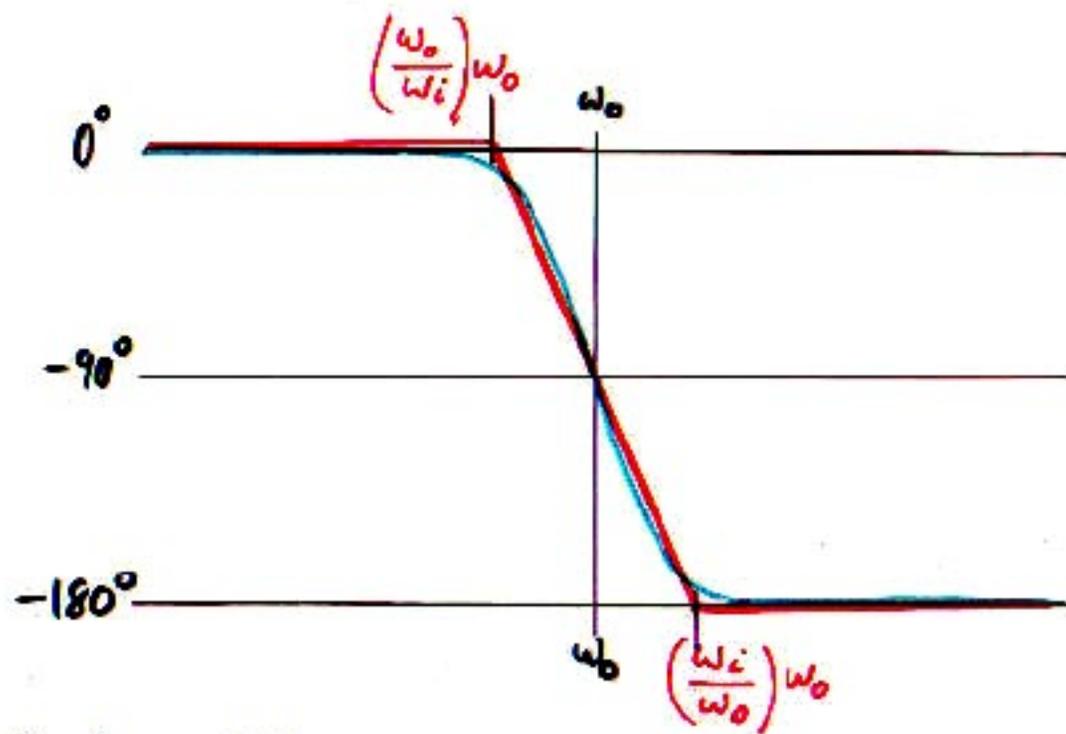
$$\frac{\omega_i}{\omega_0} = \left(e^{\frac{\pi}{2}} \right)^{\frac{1}{2Q}} = (4.81)^{\frac{1}{2Q}}$$



Better choice :

$$\frac{\omega_i}{\omega_0} \approx 5^{\frac{1}{2Q}}$$

Second-order response:

$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$

$$x = \frac{s}{\omega_0}$$


$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$

$$x = s$$


$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$

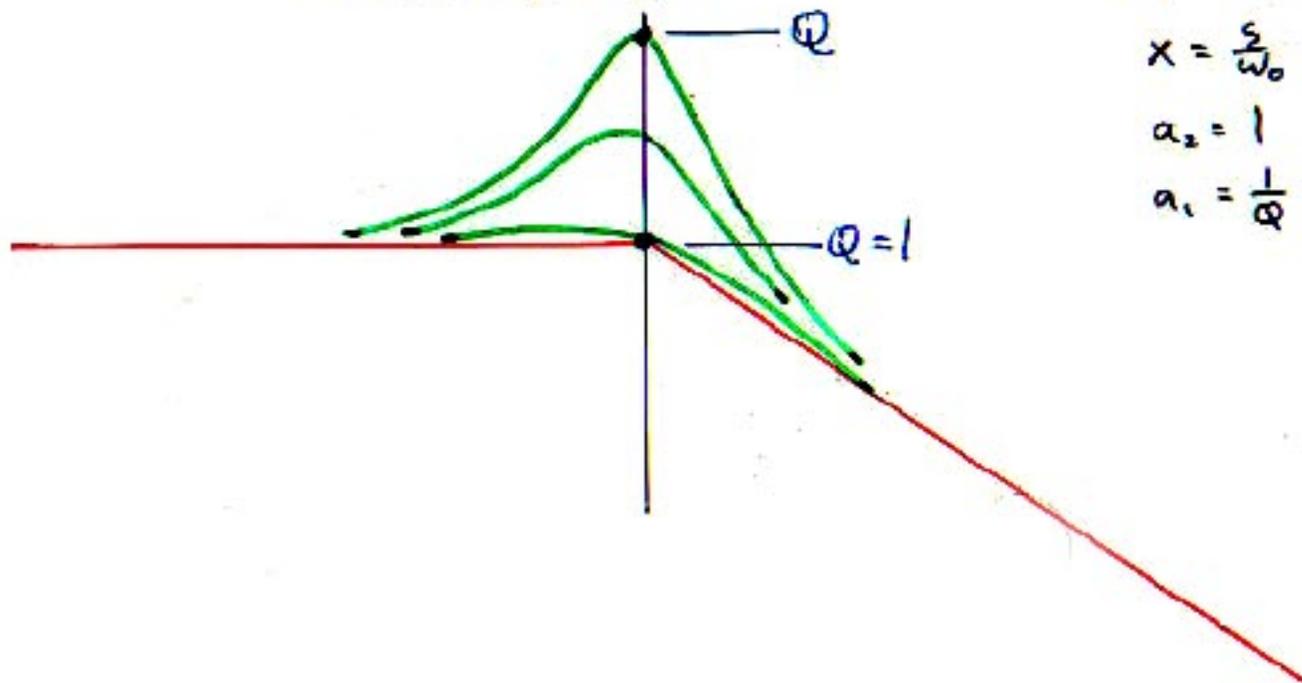

Second-order response:
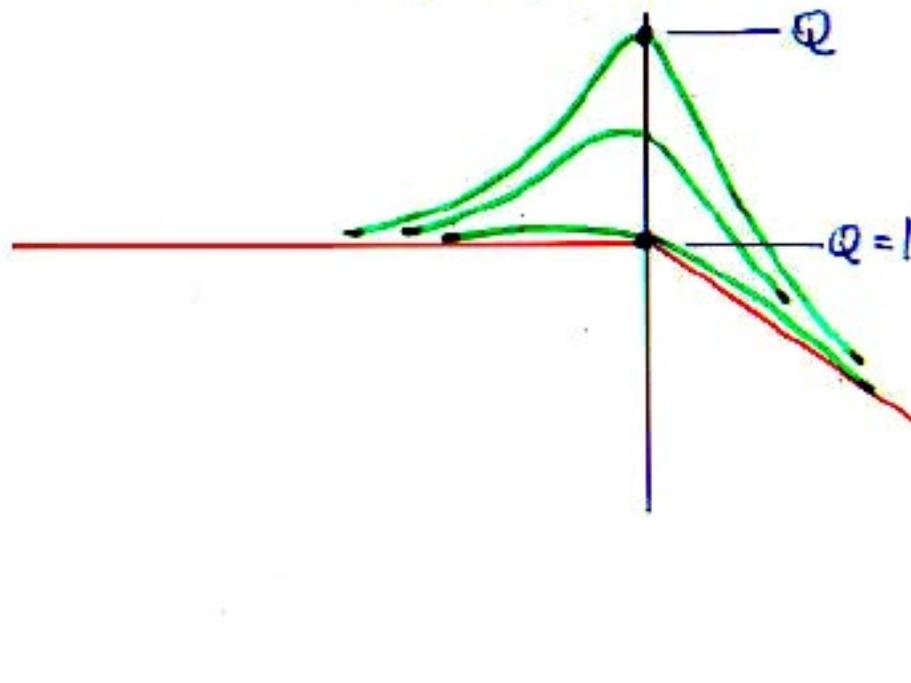
$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$



$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$

$$x = \frac{s}{\omega_0}$$

$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$

$$x = s$$

$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$


$$F \equiv \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4a_2/a_1^2}$$

$$F \equiv \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}$$

$$A = A_1 \frac{1}{(1 + a_1 F x) \left(1 + \frac{a_2}{a_1 F} x\right)}$$

Second-order response:
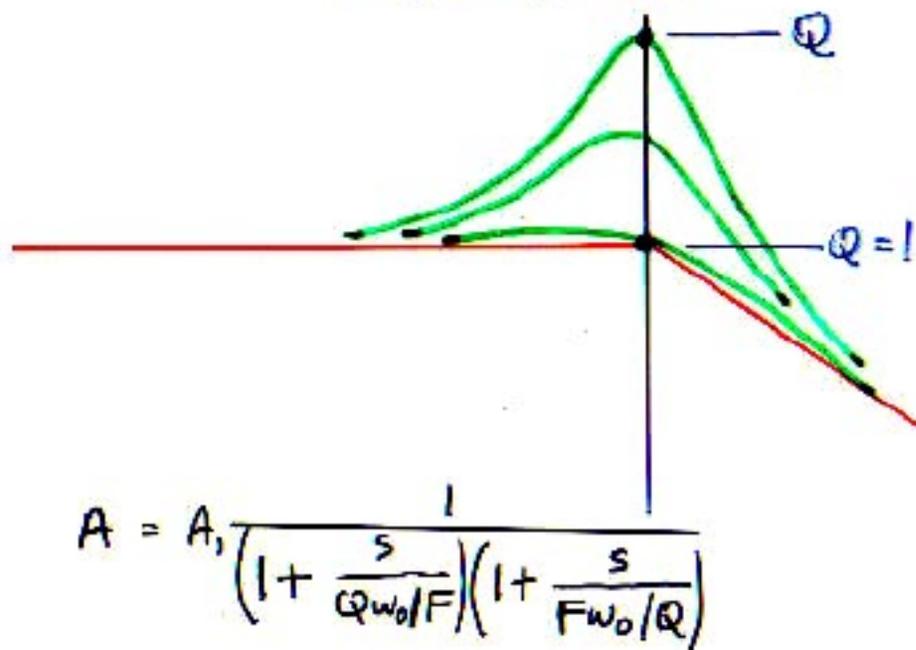
$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$



$$A = A_1 \frac{1}{\left(1 + \frac{s}{Q\omega_0/F}\right) \left(1 + \frac{s}{F\omega_0/Q}\right)}$$

$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$

$$x = \frac{s}{\omega_0}$$

$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$

$$x = s$$

$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4a_2/a_1^2}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}$$

$$A = A_1 \frac{1}{(1 + a_1 F x) \left(1 + \frac{a_2}{a_1 F} x\right)}$$

Second-order response:

$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$

$$x = \frac{s}{\omega_0}$$

$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$

$$x = s$$


$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4a_2/a_1^2}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}$$
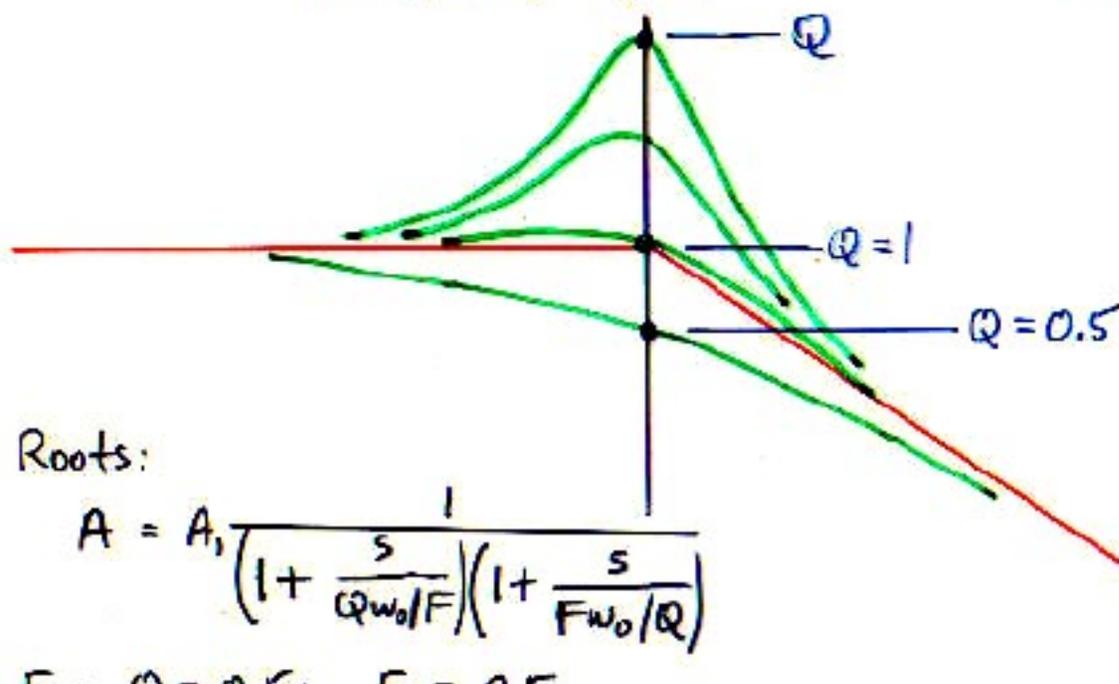
$$A = A_1 \frac{1}{(1 + a_1 F x)(1 + \frac{a_2}{a_1 F} x)}$$



Roots:

$$A = A_1 \frac{1}{\left(1 + \frac{s}{Q\omega_0/F}\right) \left(1 + \frac{s}{F\omega_0/Q}\right)}$$

For $Q = 0.5$: $F = 0.5$

$$A = A_1 \frac{1}{\left(1 + \frac{s}{\omega_0}\right)^2}$$

Second-order response:

$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$

$$x = \frac{s}{\omega_0}$$

$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$


$$x = s$$

$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4a_2/a_1^2}$$
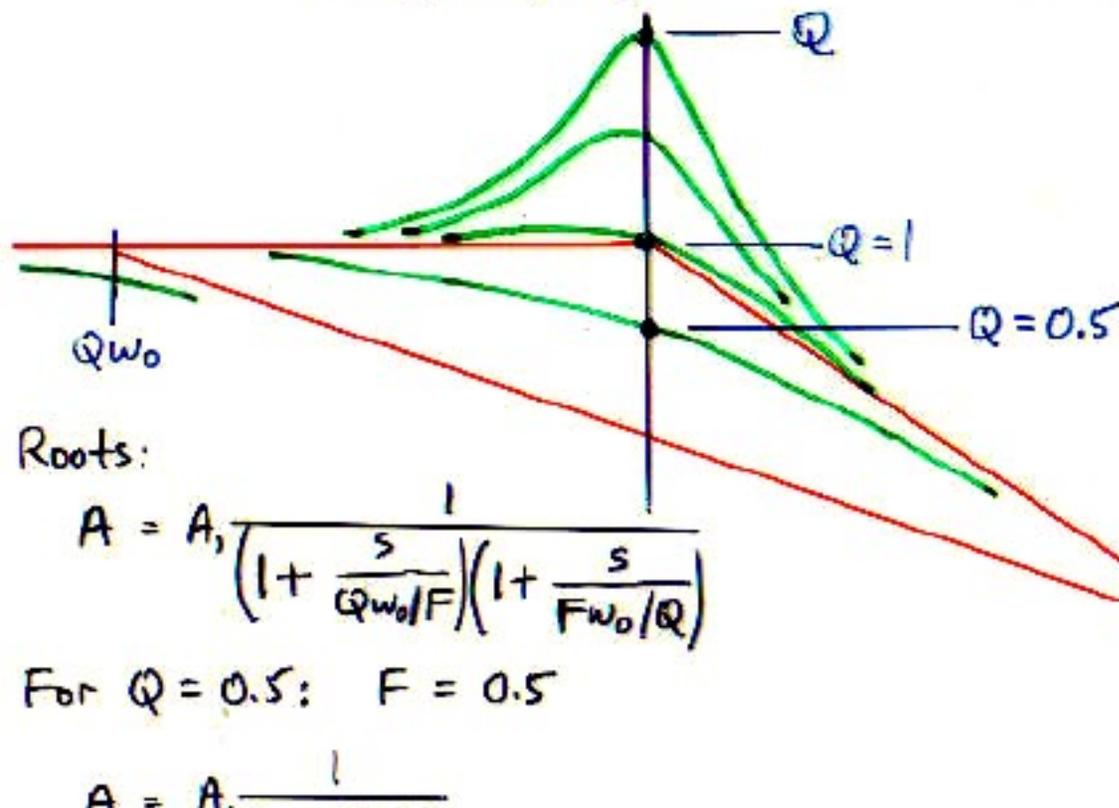
$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}$$



Roots:

$$A = A_1 \frac{1}{\left(1 + \frac{s}{Q\omega_0/F}\right) \left(1 + \frac{s}{F\omega_0/Q}\right)}$$

For $Q = 0.5$: $F = 0.5$

$$A = A_1 \frac{1}{\left(1 + \frac{s}{\omega_0}\right)^2}$$

For $Q \ll 0.5$: $F \approx 1$


$$A = A_1 \frac{1}{\left(1 + \frac{s}{Q\omega_0}\right) \left(1 + \frac{s}{\omega_0/Q}\right)}$$


$$A = A_1 \frac{1}{\left(1 + a_1 F x\right) \left(1 + \frac{a_2}{a_1 F} x\right)}$$

$$\frac{\omega_0}{Q}$$


$$A = A_1 \frac{1}{\left(1 + a_1 x\right) \left(1 + \frac{a_2}{a_1} x\right)}$$

Low-pass 2-pole characteristic:







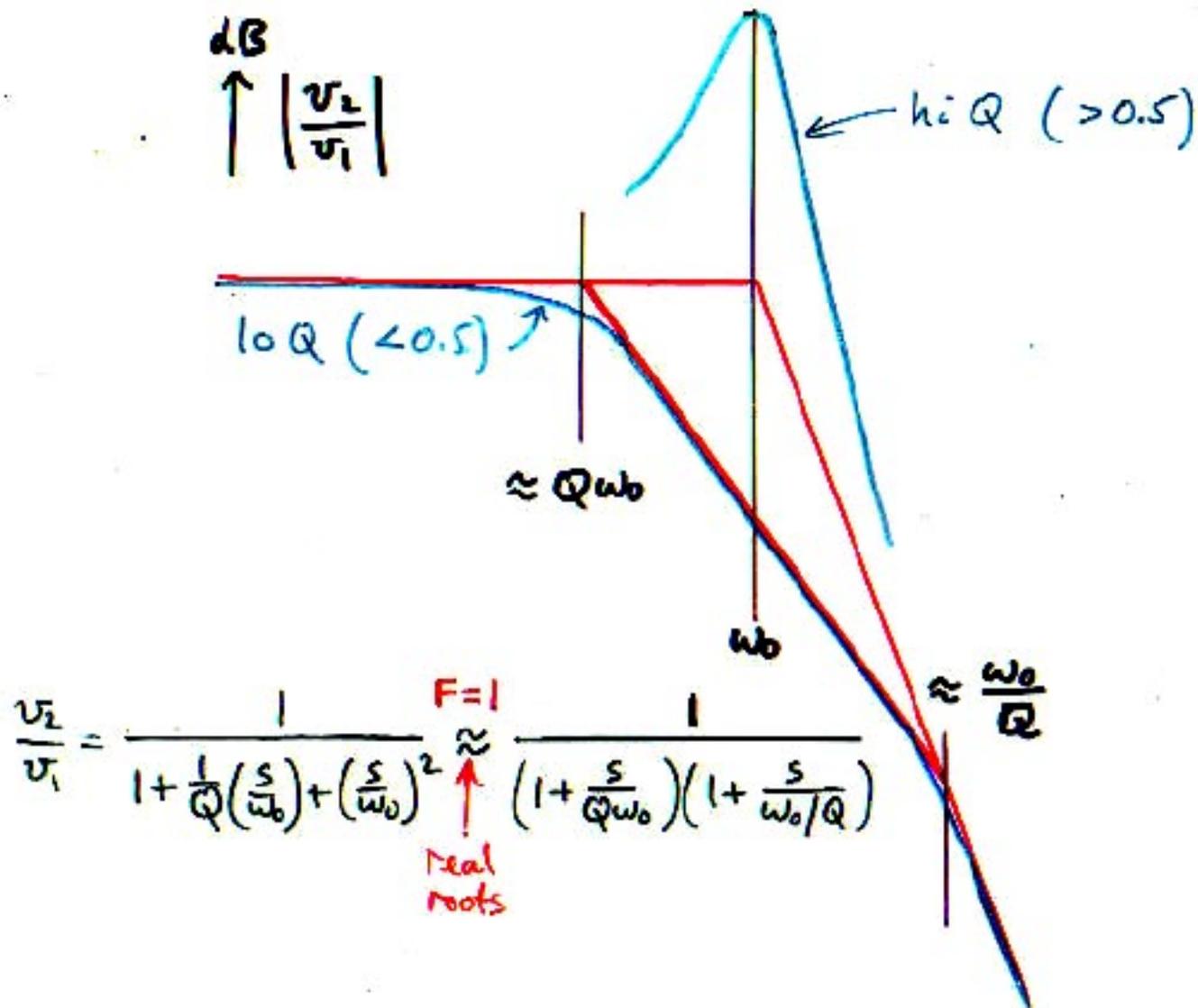


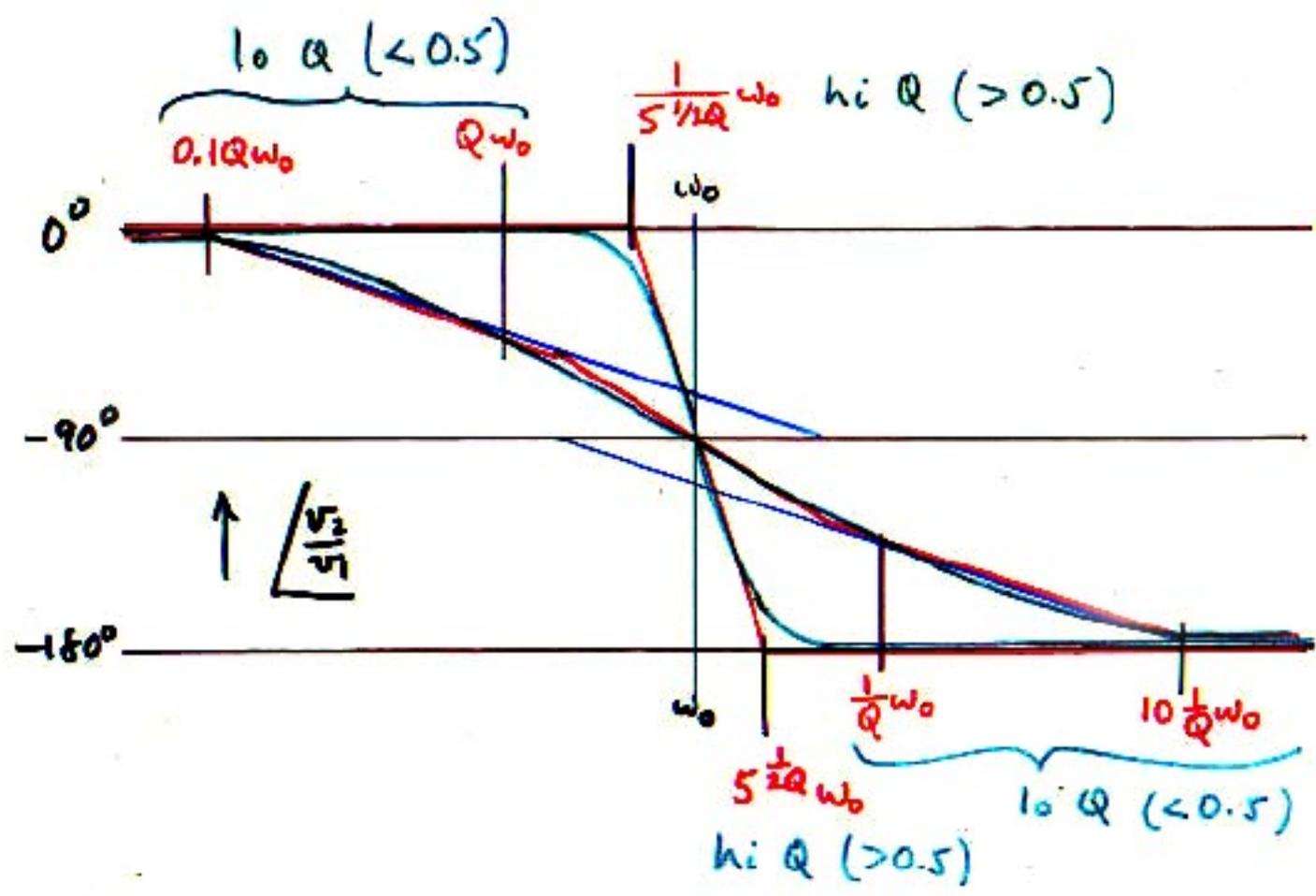


Normal and inverted poles and zeros:

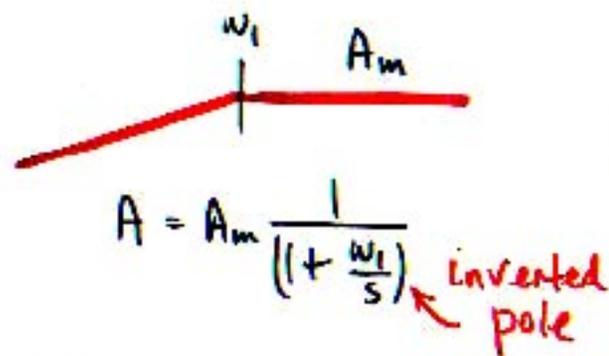

$|A|$ dB
 \uparrow
 ω (log)

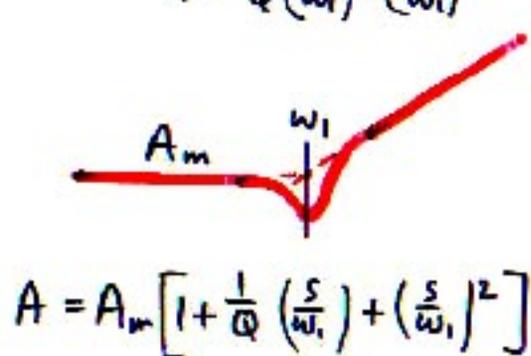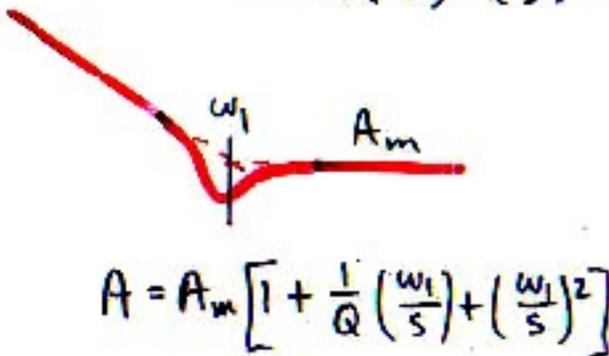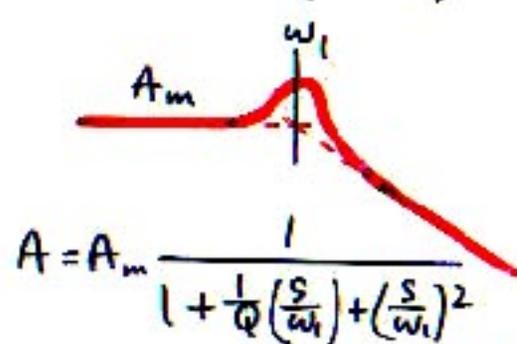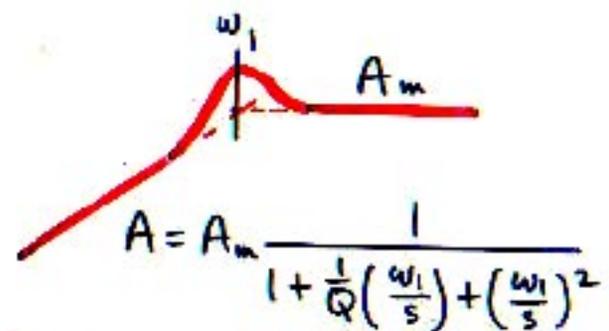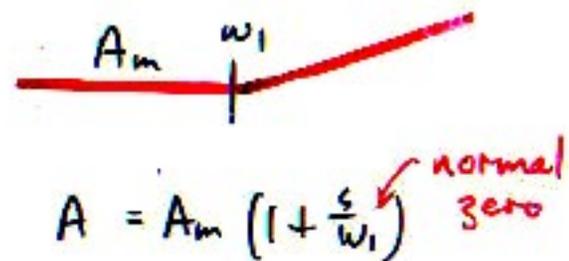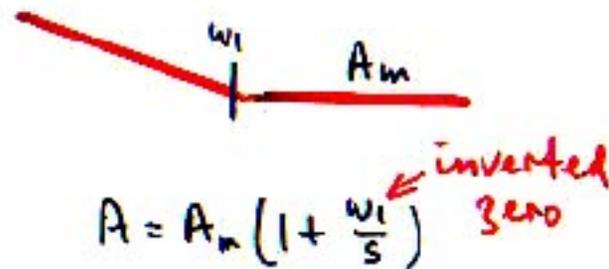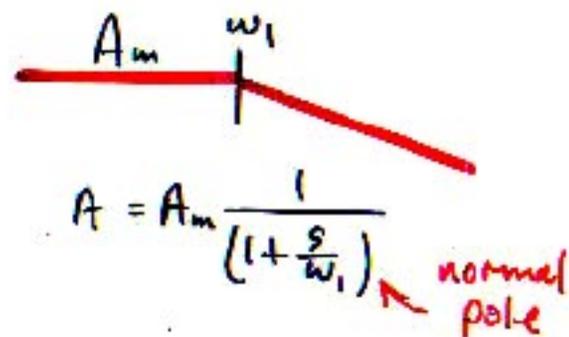

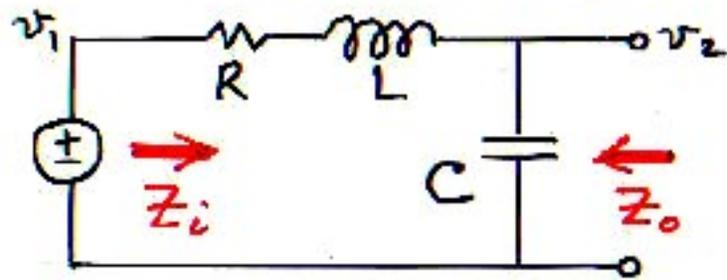Input and Output Impedances of low-pass filter



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$R_0 = \sqrt{\frac{L}{C}} \quad Q = \frac{R_0}{R} = \frac{1}{\omega_0 CR} = \frac{\omega_0 L}{R}$$

$$Z_i = \frac{1}{sC} + R + sL$$

$$= \frac{1 + sCR + s^2LC}{sC}$$

$$Z_o = \frac{1}{sC} \frac{(R + sL)}{1 + sCR + s^2LC}$$

$$= \frac{R + sL}{1 + sCR + s^2LC}$$

Express in terms of ω_0 , Q , R_0 :


$$Z_i = \frac{1}{\omega_0 C} \frac{1 + \omega_0 CR \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)}$$

$$= R_0 \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)}$$

$$Z_o = \omega_0 L \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{R}{sL}\right)}{1 + \omega_0 CR \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

$$= R_0 \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

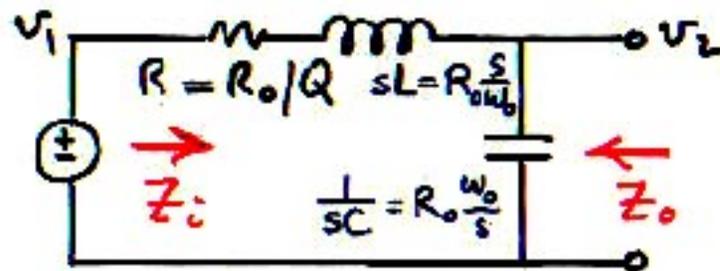Input and Output Impedances of low-pass filter



$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \frac{R_0}{R}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

$$Z_i = \frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}$$

$$= R_0 \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)}$$

$$Z_o = \frac{\left(\frac{R_0}{Q} + R_0 \frac{s}{\omega_0}\right) R_0 \frac{\omega_0}{s}}{\frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}}$$



$$= R_0 \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

Note how the algebra is shortened when the analysis starts with the normalized element values.


$$Z_i = R_o \times \left[1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2 \right] \times \left[\frac{1}{\frac{s}{\omega_o}} \right]$$

ref. value $\frac{1}{H}$ single slope


R_o

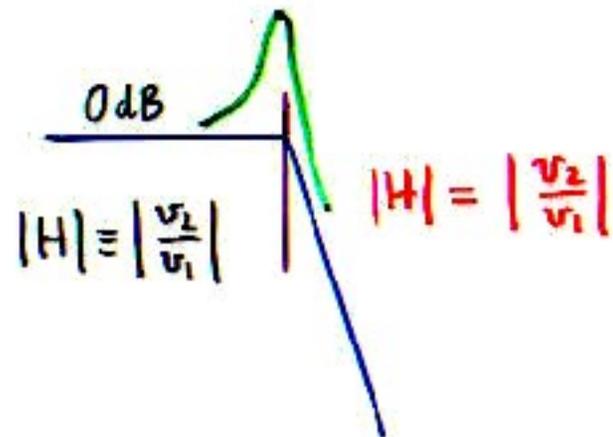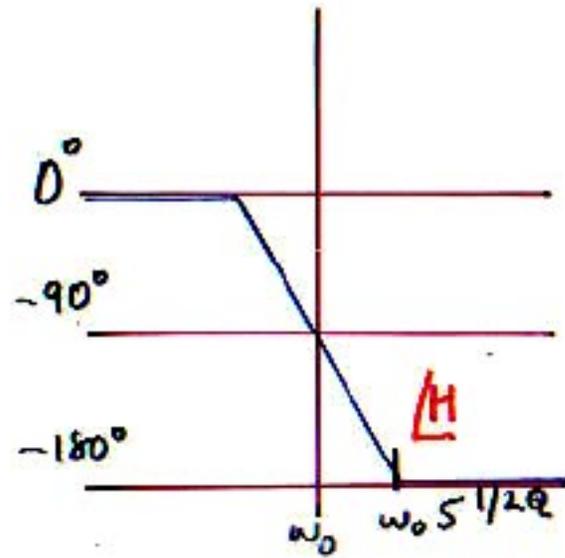


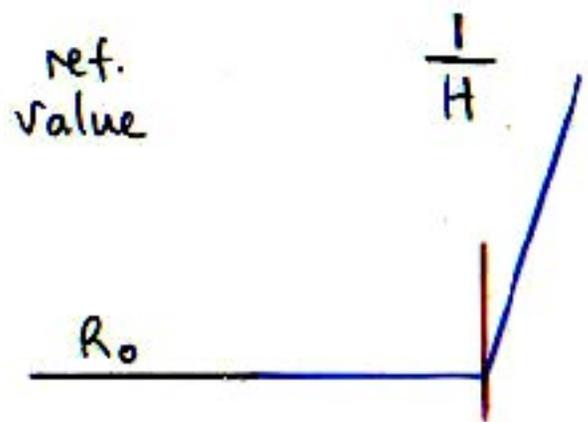
$$Z_i = R_o \times \left[1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2 \right] \times \left[\frac{1}{\frac{s}{\omega_o}} \right]$$





single slope

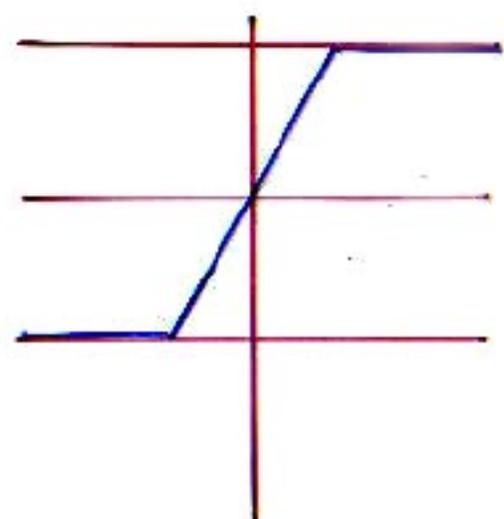

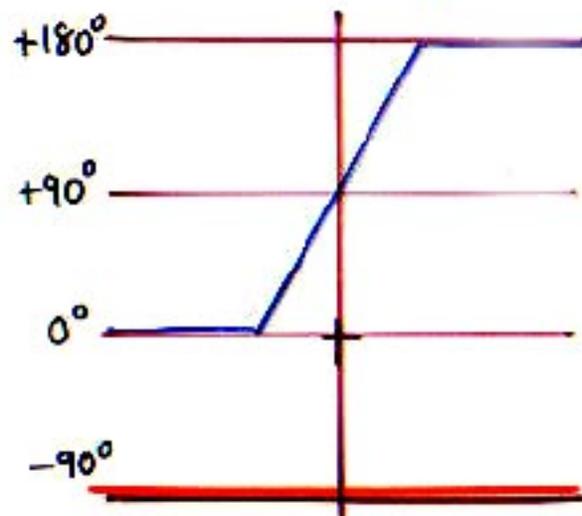
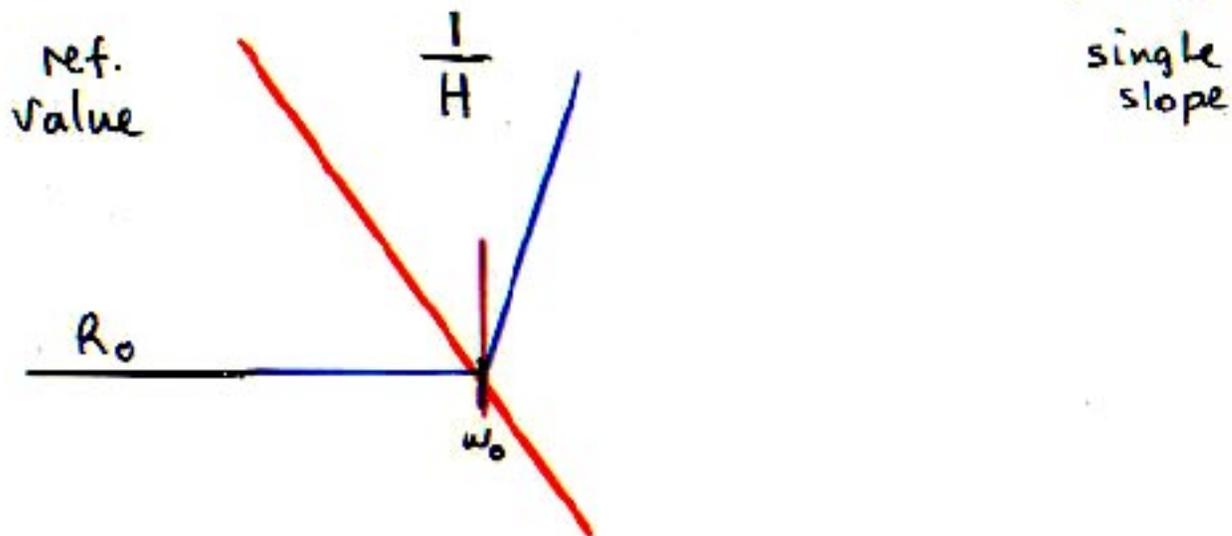
$$Z_i = R_o \times \left[1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2 \right] \times \left[\frac{1}{\frac{s}{\omega_o}} \right]$$



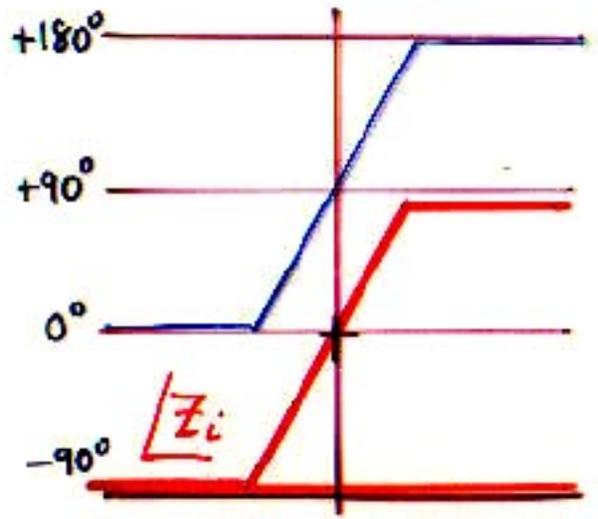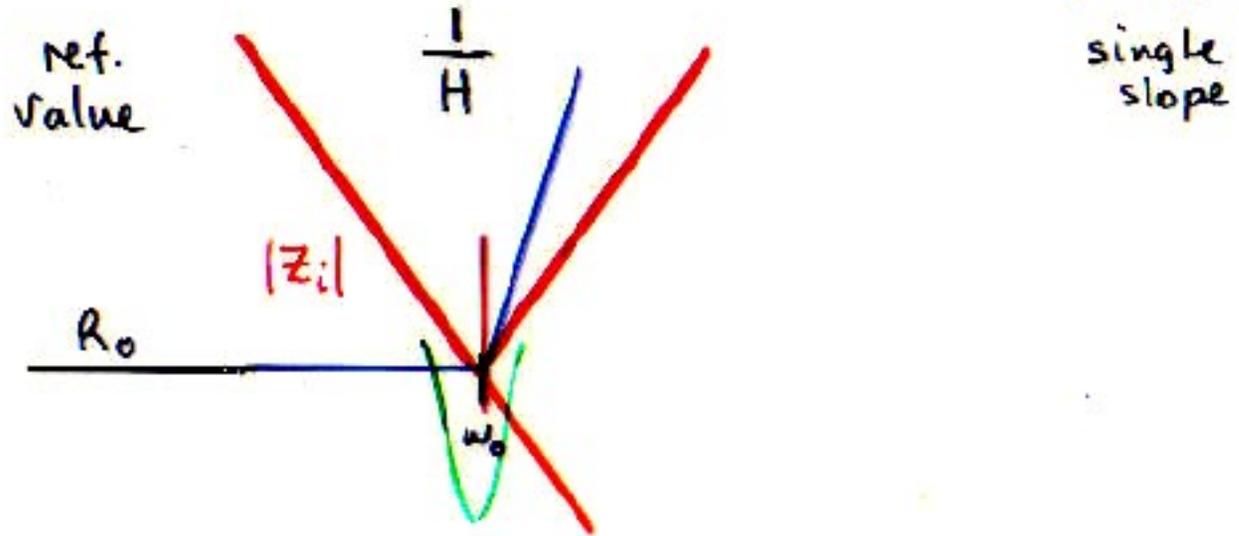
$$Z_i = R_o \times \left[1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2 \right] \times \left[\frac{1}{\frac{s}{\omega_o}} \right]$$



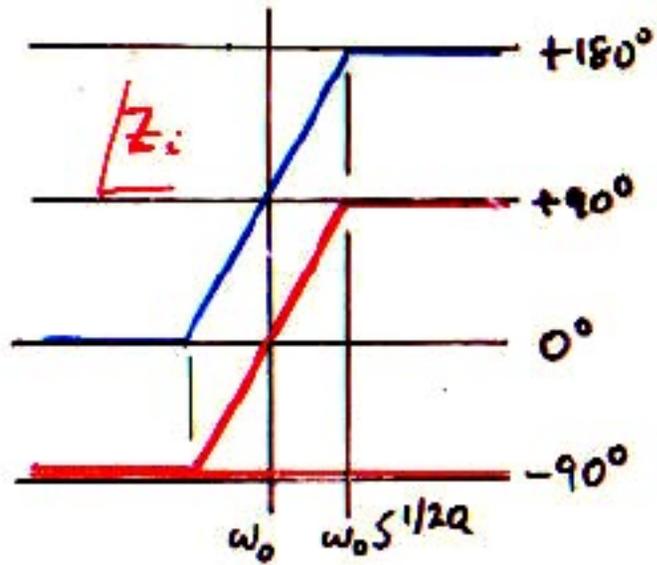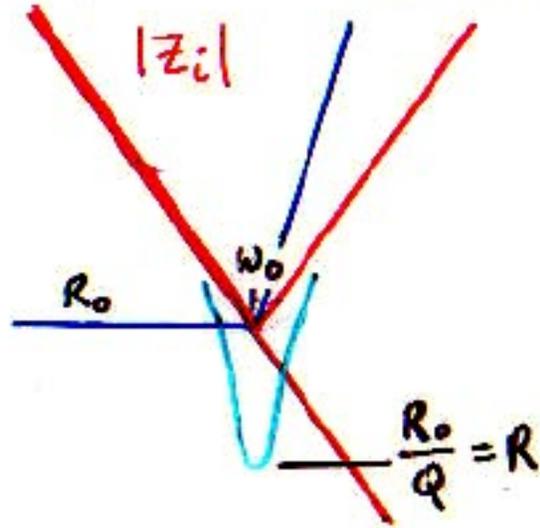Asymptote sketches for high Q ($\gg 0.5$)



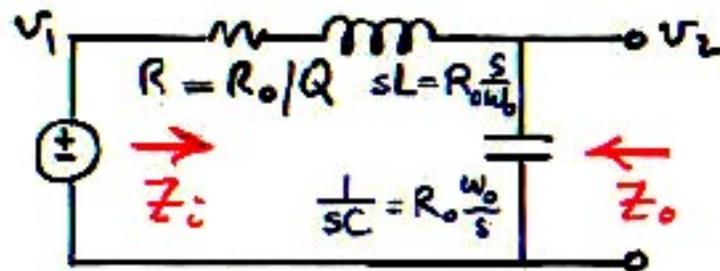Input and Output Impedances of low-pass filter



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$R_0 = \sqrt{\frac{L}{C}} \quad Q = \frac{R_0}{R}$$

$$Z_i = \frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}$$

$$= R_0 \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)}$$

$$Z_o = \frac{\left(\frac{R_0}{Q} + R_0 \frac{s}{\omega_0}\right) R_0 \frac{\omega_0}{s}}{\frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}}$$

$$= R_0 \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

Note how the algebra is shortened when the analysis starts with the normalized element values.



$$Z_o = R_o \times \left[\frac{\frac{s}{\omega_o}}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2} \right] \times \left(1 + \frac{\omega_o/Q}{s} \right)$$

ref.
value

$\frac{1}{Z_i}$

inverted
zero



R_o

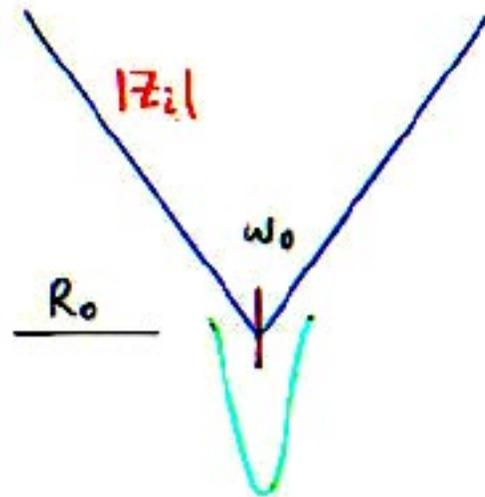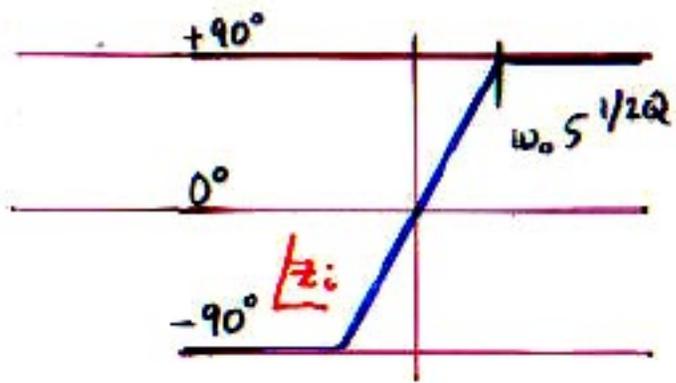

$$Z_o = R_o \times \left[\frac{\frac{s}{\omega_o}}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2} \right] \times \left(1 + \frac{\omega_o/Q}{s} \right)$$

ref. value
 $\frac{1}{Z_i}$
inverted zero

R_o

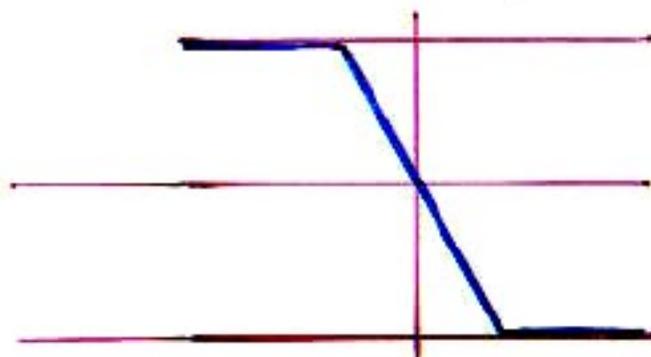
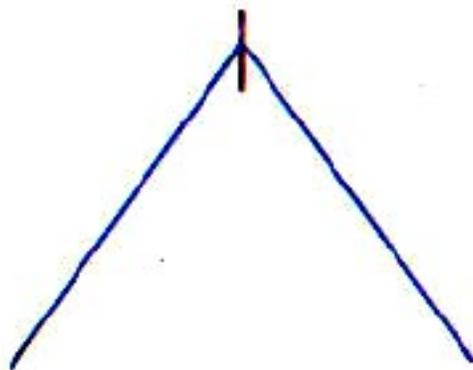


$$Z_o = R_o \times \left[\frac{\frac{\omega_o}{Q}}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2} \right] \times \left(1 + \frac{\omega_o/Q}{s} \right)$$

ref.
value

$\frac{1}{Z_i}$

inverted
zero

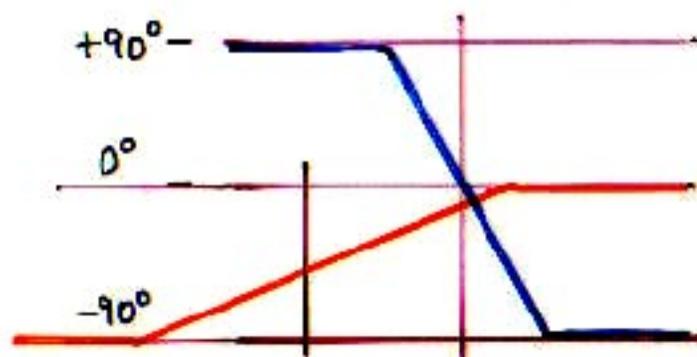
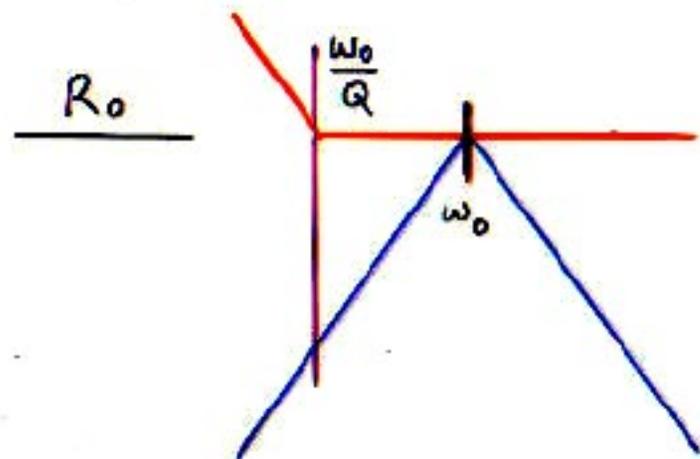


$$Z_o = R_o \times \left[\frac{\frac{2}{\omega_o}}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2} \right] \times \left(1 + \frac{\omega_o/Q}{s} \right)$$


ref.
value

$\frac{1}{Z_i}$


inverted
zero

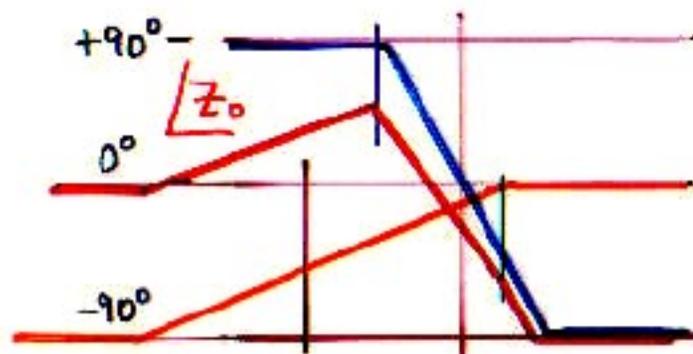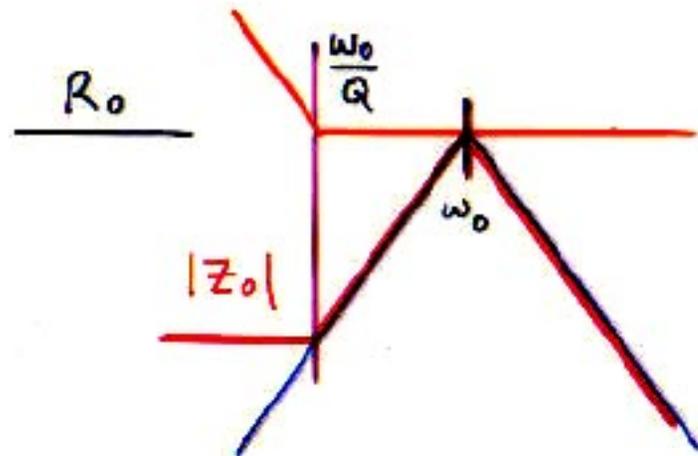

$|Z_0|$

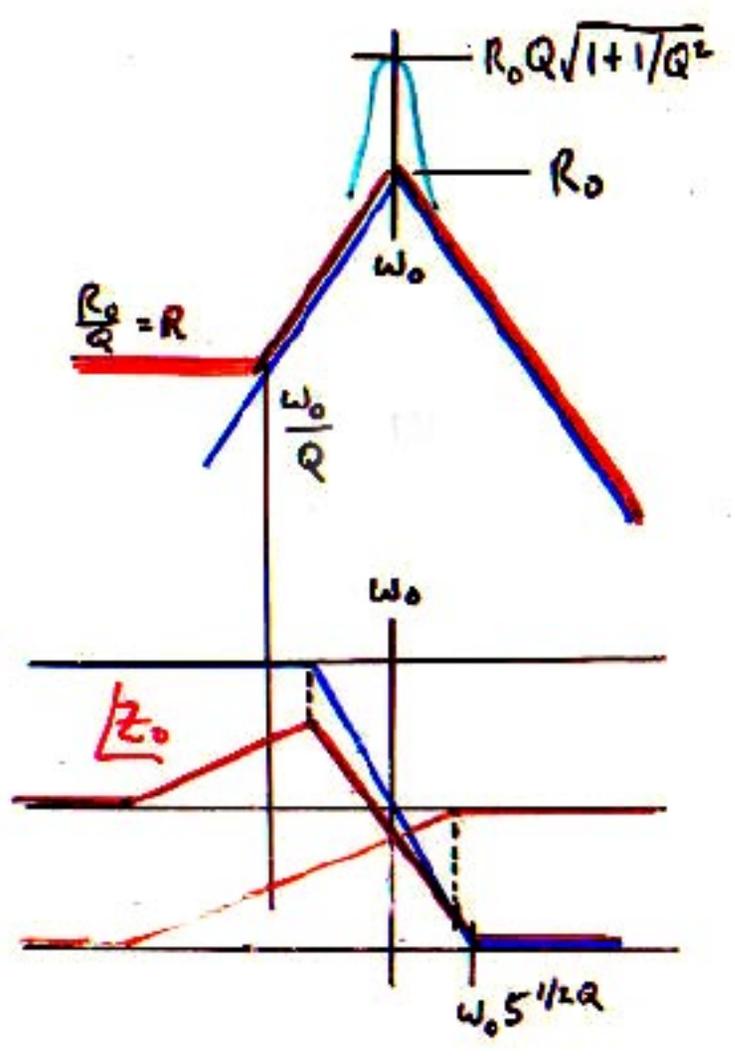

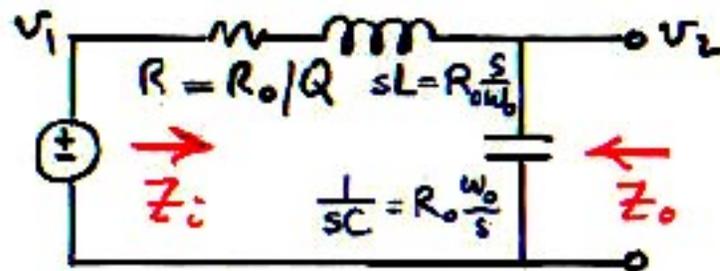Input and Output Impedances of low-pass filter



$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \frac{R_0}{R}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

$$Z_i = \frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}$$

$$= R_0 \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)}$$

$$Z_o = \frac{\left(\frac{R_0}{Q} + R_0 \frac{s}{\omega_0}\right) R_0 \frac{\omega_0}{s}}{\frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}}$$


$$= R_0 \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

Note how the algebra is shortened when the analysis starts with the normalized element values.

Exercise

For the two-pole low-pass LC filter,
sketch the magnitude and phase asymptotes
of Z_i and Z_o for low Q ($\ll 0.5$).
(But take $Q > 0.1$)

Loaded low-pass LC filter

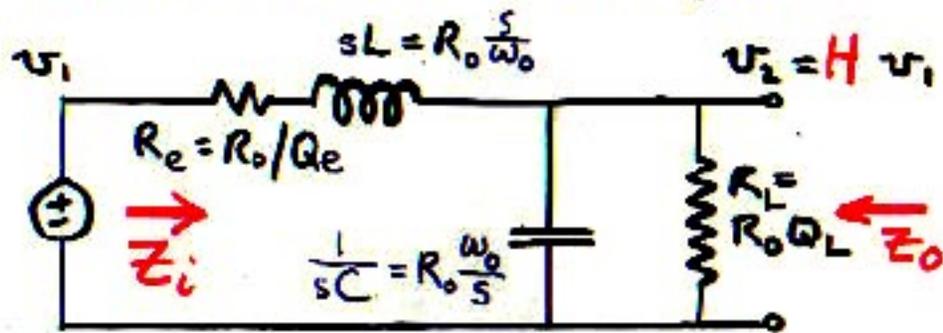


Note: $R \rightarrow R_e$, $Q \rightarrow Q_e$

$$\omega_0 \equiv \frac{1}{\sqrt{LC}} \quad R_o \equiv \sqrt{\frac{L}{C}}$$

$$Q_e \equiv \frac{R_o}{R_e} \quad Q_L \equiv \frac{R_L}{R_o}$$

Loaded low-pass LC filter

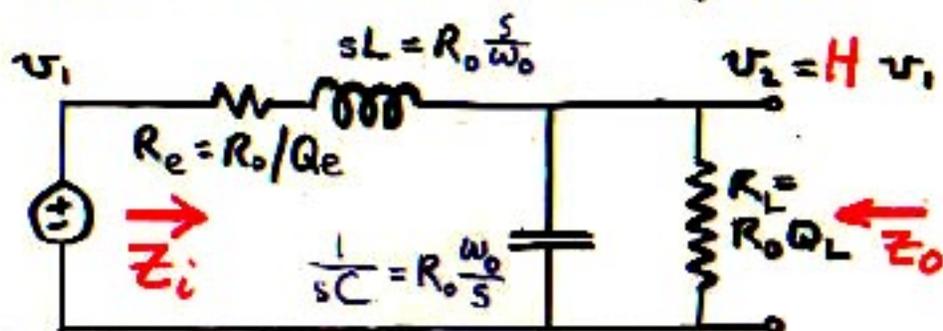

Note: $R \rightarrow R_e, Q \rightarrow Q_e$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad R_o = \sqrt{\frac{L}{C}}$$

$$Q_e = \frac{R_o}{R_e} \quad Q_L = \frac{R_L}{R_o}$$

$$H = \frac{\frac{R_o Q_L}{1 + Q_L \frac{s}{\omega_0}}}{\frac{R_o Q_L}{1 + Q_L \frac{s}{\omega_0}} + \frac{R_e}{Q_e} + R_o \frac{s}{\omega_0}} = \frac{Q_L}{Q_L + \frac{1}{Q_e} + \left(\frac{Q_L}{Q_e} + 1\right) \left(\frac{s}{\omega_0}\right) + Q_L \left(\frac{s}{\omega_0}\right)^2}$$

$$= \frac{1}{1 + 1/Q_e Q_L} \frac{1}{1 + \frac{\left(\frac{1}{Q_e} + \frac{1}{Q_L}\right)}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0}\right) + \frac{1}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0}\right)^2}$$

Result, compared with unloaded case:

1. Low-freq. asymptote is $\frac{1}{1+1/Q_e Q_L} = \frac{R_L}{R_L + R_e}$
(resistive divider)

2. The corner frequency is changed to
 $\sqrt{1+1/Q_e Q_L} \omega_0$

3. The damping coefficient is changed to
 $\frac{\frac{1}{Q_e} + \frac{1}{Q_L}}{\sqrt{1+1/Q_e Q_L}}$

For the high-Q case, $Q_e, Q_L \gg 0.5$, $Q_e Q_L \gg 1$ and the first two effects are negligible, and the damping coefficient becomes

$$\frac{1}{Q_e} + \frac{1}{Q_L}$$

Hence, for the high-Q case,


$$H \approx \frac{1}{1 + \frac{1}{Q_t} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

where Q_t is a "total" Q-factor given by the "parallel combination"

$$\frac{1}{Q_t} \equiv \frac{1}{Q_e} + \frac{1}{Q_L}$$

Loaded low-pass LC filter

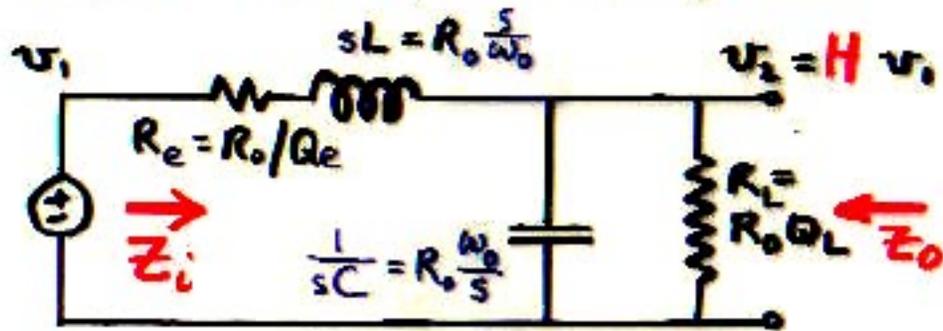Note: $R \rightarrow R_e$, $Q \rightarrow Q_e$



$$\omega_0 = \frac{1}{\sqrt{LC}} \quad R_0 = \sqrt{\frac{L}{C}}$$

$$Q_e = \frac{R_0}{R_e} \quad Q_L = \frac{R_L}{R_0}$$


$$H = \frac{\frac{R_L}{1+sCR_L}}{\frac{R_L}{1+sCR_L} + R_e + sL} = \frac{R_L}{R_L + R_e + s(CR_L R_e + L) + s^2 LCR_L}$$

$$= \frac{R_L}{R_L + R_e} \frac{1}{1 + s\left(CR_e + \frac{L}{R_L}\right) \frac{R_L}{R_L + R_e} + s^2 LC \frac{R_L}{R_L + R_e}}$$

$$= \frac{R_L}{R_L + R_e} \frac{1}{1 + s\sqrt{LC} \left(R_e \sqrt{\frac{C}{L}} + \frac{1}{R_L} \sqrt{\frac{L}{C}} \right) \frac{R_L}{R_L + R_e} + s^2 LC \frac{R_L}{R_L + R_e}}$$

$$= \frac{1}{1 + 1/Q_e Q_L} \frac{1}{1 + \frac{\left(\frac{L}{Q_e} + \frac{1}{Q_L}\right)}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0}\right) + \frac{1}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0}\right)^2}$$



Loaded low-pass LC filter

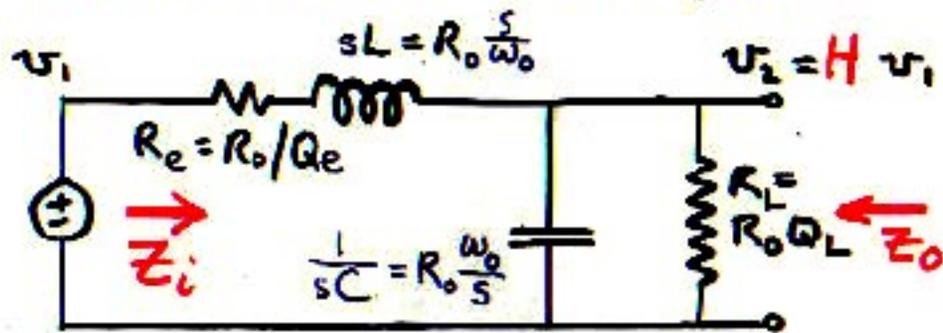


Note: $R \rightarrow R_e$, $Q \rightarrow Q_e$

$$\omega_o \equiv \frac{1}{\sqrt{LC}} \quad R_o \equiv \sqrt{\frac{L}{C}}$$
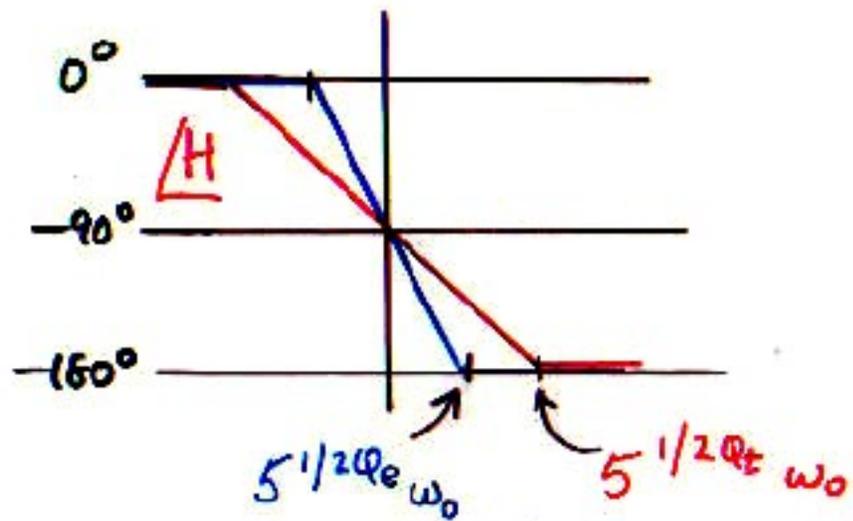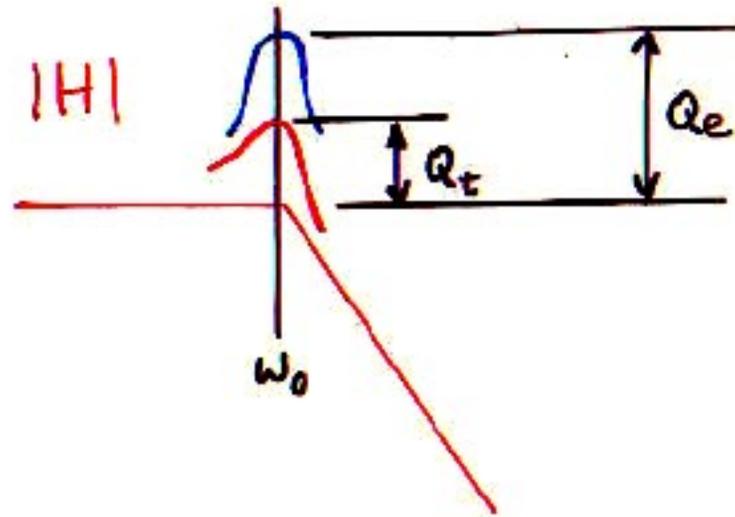
$$Q_e \equiv \frac{R_o}{R_e} \quad Q_L \equiv \frac{R_L}{R_o}$$



Loaded low-pass LC filter

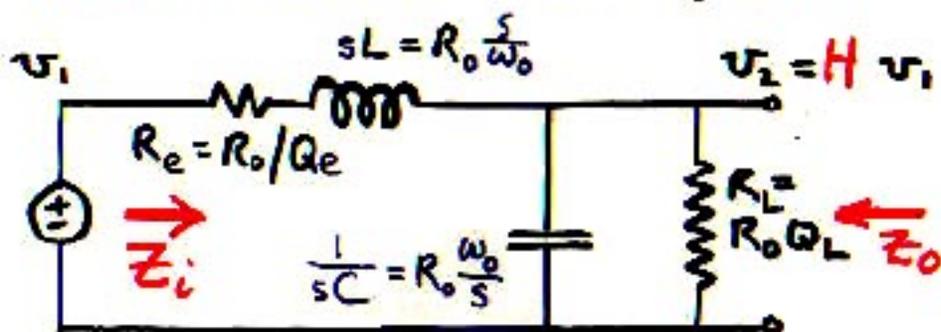

Note: $R \rightarrow R_e$, $Q \rightarrow Q_e$

$$\omega_0 \equiv \frac{1}{\sqrt{LC}} \quad R_o \equiv \sqrt{\frac{L}{C}}$$


$$Q_e \equiv \frac{R_o}{R_e} \quad Q_L \equiv \frac{R_L}{R_o}$$

$$Z_i = \frac{R_o Q_L}{1 + Q_L \left(\frac{s}{\omega_0}\right)} + \frac{R_o}{Q_e} + R_o \frac{s}{\omega_0} = R_o \frac{Q_L + \frac{1}{Q_e} + \left(\frac{Q_L}{Q_e} + 1\right) \left(\frac{s}{\omega_0}\right) + Q_L \left(\frac{s}{\omega_0}\right)^2}{1 + Q_L \left(\frac{s}{\omega_0}\right)}$$

$$= R_o \left(1 + \frac{1}{Q_e Q_L}\right) \frac{1 + \frac{\frac{1}{Q_e} + \frac{1}{Q_L}}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_0}\right) + \frac{1}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0 Q_L}{s}\right)}$$

Same three effects as for H , but with addition of an inverted pole at ω_0 / Q_L .

Loaded low-pass LC filter

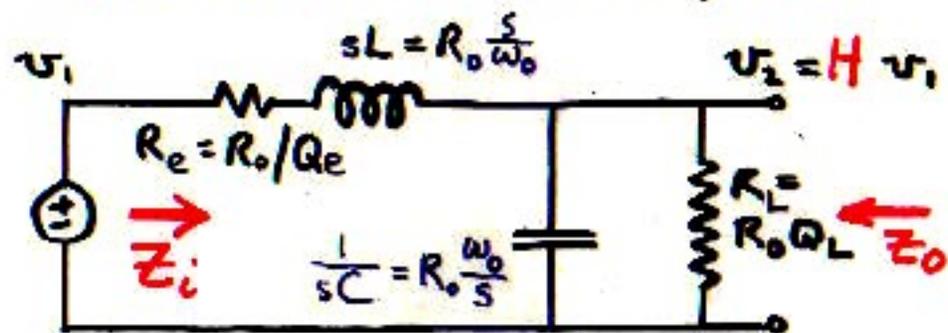

Note: $R \rightarrow R_e$, $Q \rightarrow Q_e$


$$\omega_o = \frac{1}{\sqrt{LC}} \quad R_o = \sqrt{\frac{L}{C}}$$

$$Q_e = \frac{R_o}{R_e} \quad Q_L = \frac{R_L}{R_o}$$


Hence, for the high- Q case,

$$Z_i \approx R_o \frac{1 + \frac{1}{Q_L} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}{\left(\frac{s}{\omega_o}\right) \left(1 + \frac{\omega_o / Q_L}{s}\right)}$$

For high-Q case:

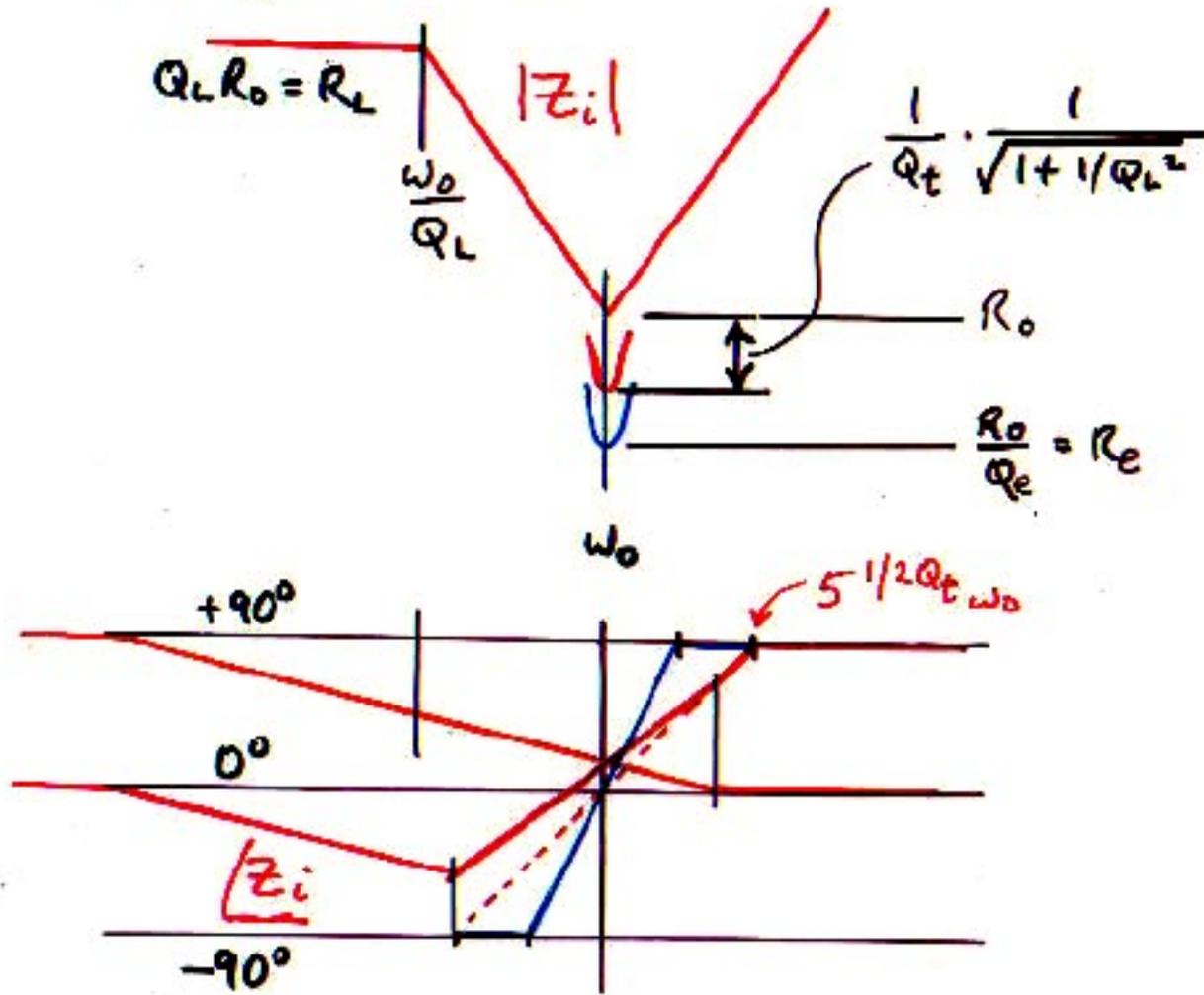

Loaded low-pass LC filter

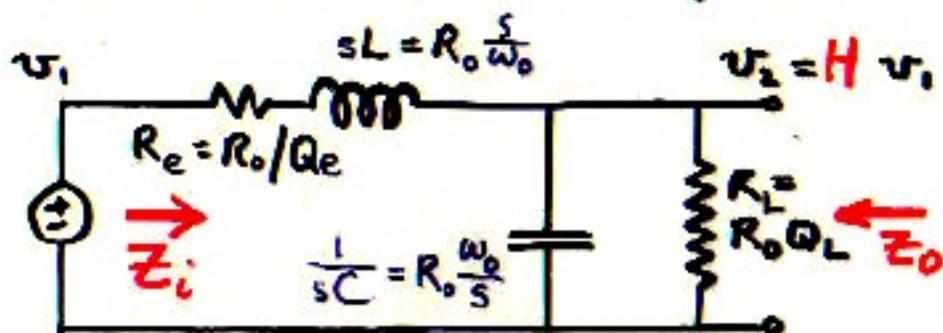

Note: $R \rightarrow R_e$, $Q \rightarrow Q_e$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad R_o = \sqrt{\frac{L}{C}}$$

$$Q_e = \frac{R_o}{R_e} \quad Q_L = \frac{R_L}{R_o}$$


$$Z_o = \frac{\frac{Q_L R_o}{1 + Q_L (\frac{s}{\omega_0})} \left(\frac{R_o}{Q_e} + R_o \frac{s}{\omega_0} \right)}{\frac{Q_L R_o}{1 + Q_L (\frac{s}{\omega_0})} + \frac{R_o}{Q_e} + R_o \frac{s}{\omega_0}} = R_o Q_L \frac{\frac{1}{Q_e} + \frac{s}{\omega_0}}{Q_L + \frac{1}{Q_e} + \left(\frac{Q_L}{Q_e} + 1 \right) \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2}$$

$$= R_o \cdot \frac{1}{1 + 1/Q_e Q_L} \cdot \frac{\left(\frac{s}{\omega_0} \right) \left(1 + \frac{\omega_0 / Q_e}{s} \right)}{1 + \frac{\left(\frac{1}{Q_e} + \frac{1}{Q_L} \right)}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0} \right) + \frac{1}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0} \right)^2}$$

Same three effects as for H , so for high- Q case

$$Z_o \approx R_o \frac{\left(\frac{s}{\omega_0} \right) \left(1 + \frac{\omega_0 / Q_e}{s} \right)}{1 + \frac{1}{Q_L} \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2}$$

Loaded low-pass LC filter

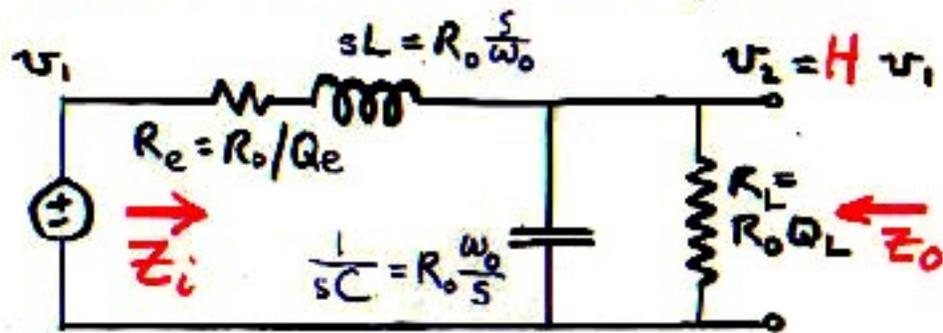


Note: $R \rightarrow R_e$, $Q \rightarrow Q_e$

$$\omega_o \equiv \frac{1}{\sqrt{LC}} \quad R_o \equiv \sqrt{\frac{L}{C}}$$

$$Q_e \equiv \frac{R_o}{R_e} \quad Q_L \equiv \frac{R_L}{R_o}$$

Loaded low-pass LC filter

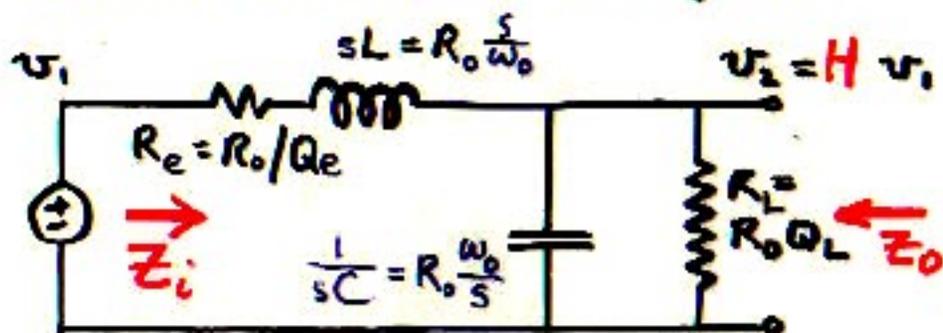

Note: $R \rightarrow R_e$, $Q \rightarrow Q_e$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad R_0 = \sqrt{\frac{L}{C}}$$

$$Q_e = \frac{R_0}{R_e} \quad Q_L = \frac{R_L}{R_0}$$


$$Z_0 = \frac{\frac{Q_L R_0}{1 + Q_L \left(\frac{s}{\omega_0}\right)} \left(\frac{R_0}{Q_e} + R_0 \frac{s}{\omega_0}\right)}{\frac{Q_L R_0}{1 + Q_L \left(\frac{s}{\omega_0}\right)} + \frac{R_0}{Q_e} + R_0 \frac{s}{\omega_0}} = R_0 Q_L \frac{\frac{1}{Q_e} + \frac{s}{\omega_0}}{Q_L + \frac{1}{Q_e} + \left(\frac{Q_L}{Q_e} + 1\right) \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

$$= R_0 \cdot \frac{1}{1 + 1/Q_e Q_L} \cdot \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q_e}{s}\right)}{1 + \frac{\left(\frac{1}{Q_e} + \frac{1}{Q_L}\right)}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0}\right) + \frac{1}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0}\right)^2}$$


Same three effects as for H , so for high- Q case

$$Z_0 \approx R_0 \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q_e}{s}\right)}{1 + \frac{1}{Q_L} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

For high-Q case:

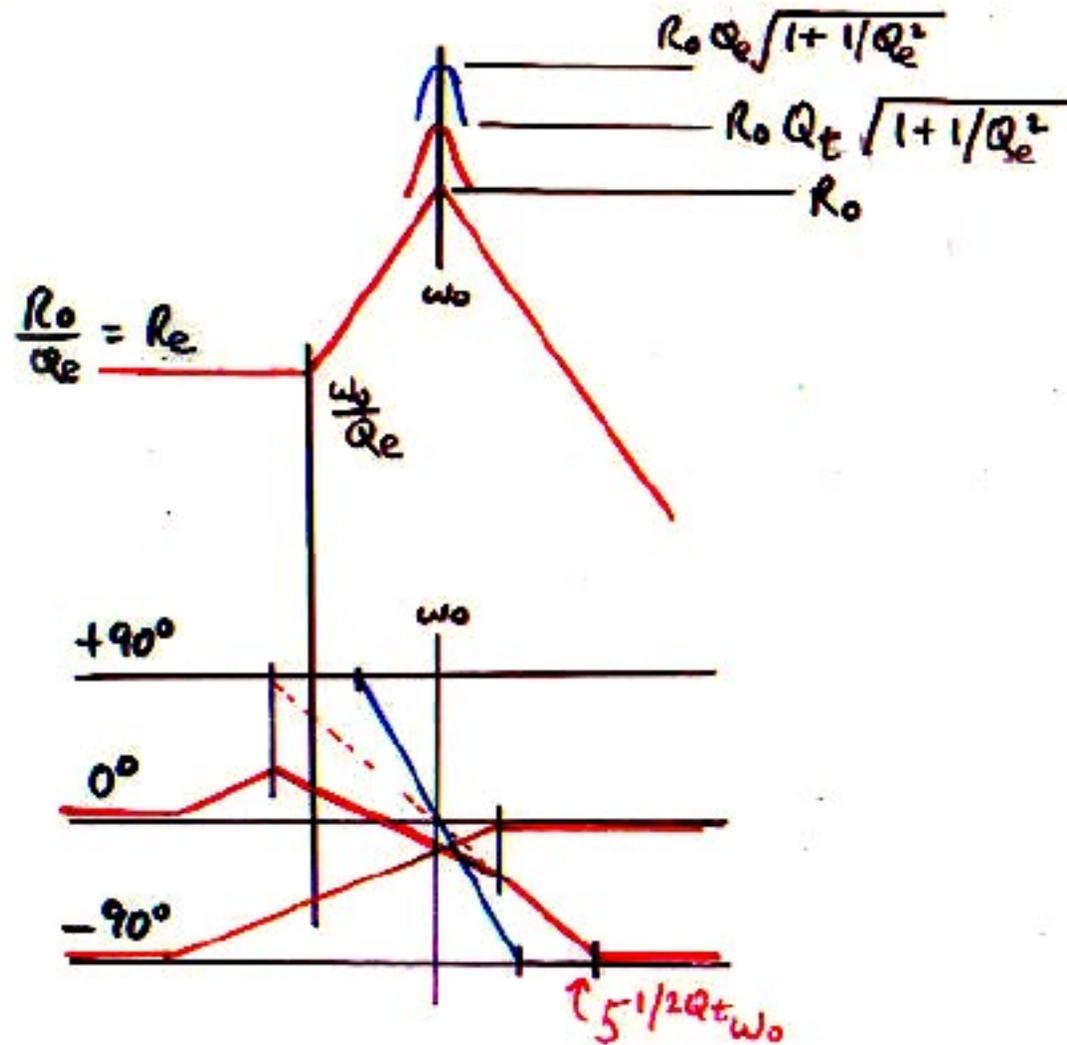

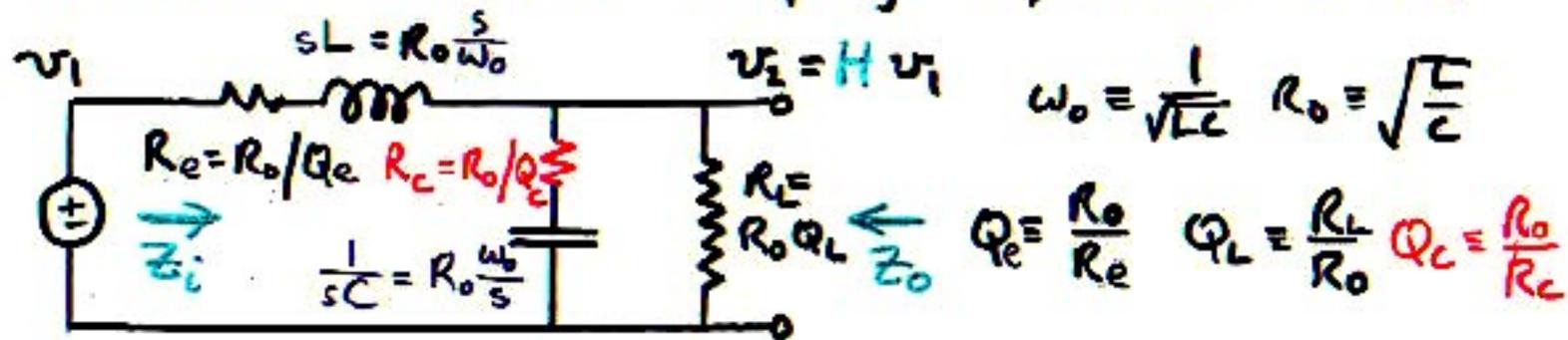Consider additional damping: Capacitor and R_c





For the high- Q case, the previous results can be extended by inspection:

$$H = \frac{1 + \frac{1}{Q_c} \left(\frac{s}{\omega_0} \right) \leftarrow 1 + sR_c C}{1 + \frac{1}{Q_t} \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2}$$

$$Z_i = R_0 \frac{1 + \frac{1}{Q_t} \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2}{\left(\frac{s}{\omega_0} \right) \left(1 + \frac{\omega_0 / Q_t}{s} \right)}$$
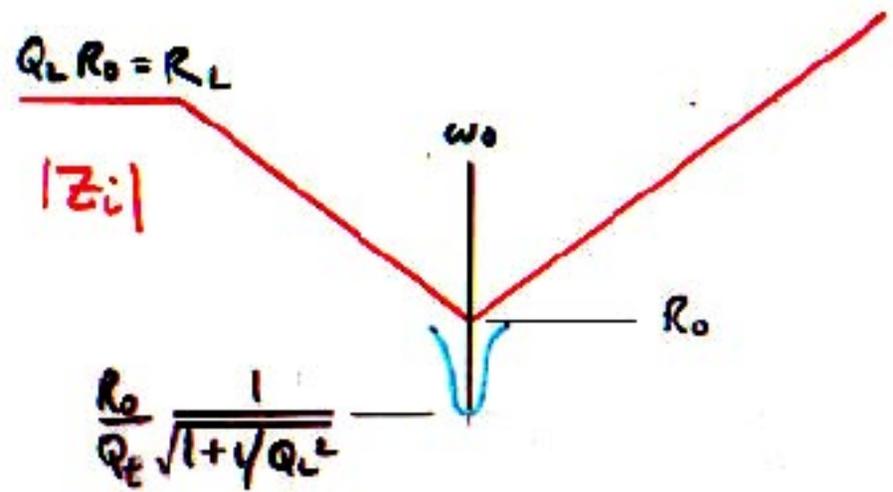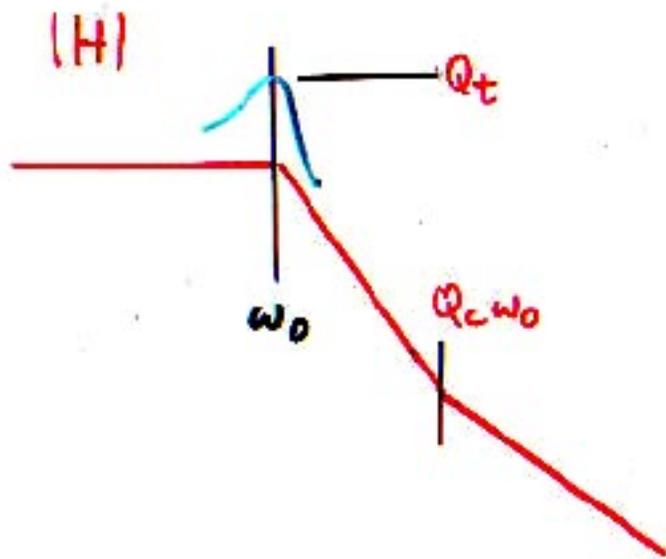
$$\frac{1}{Q_t} \equiv \frac{1}{Q_e} + \frac{1}{Q_L} + \frac{1}{Q_c}$$



Principle for extension of results to a more complicated case:

1. Determine the new total Q_t .
2. Add any additional pole or zero factors
(Is there any change in the $\omega \rightarrow 0$
or $\omega \rightarrow \infty$ asymptotes?)

Exercise:


Obtain the corresponding results for Z_0 .

Exercise solution:

$$Z_0 = R_0 \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q_e}{s}\right) \left(1 + \frac{1}{Q_e} \frac{s}{\omega_0}\right)}{1 + \frac{1}{Q_t} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

Check high-frequency limit:
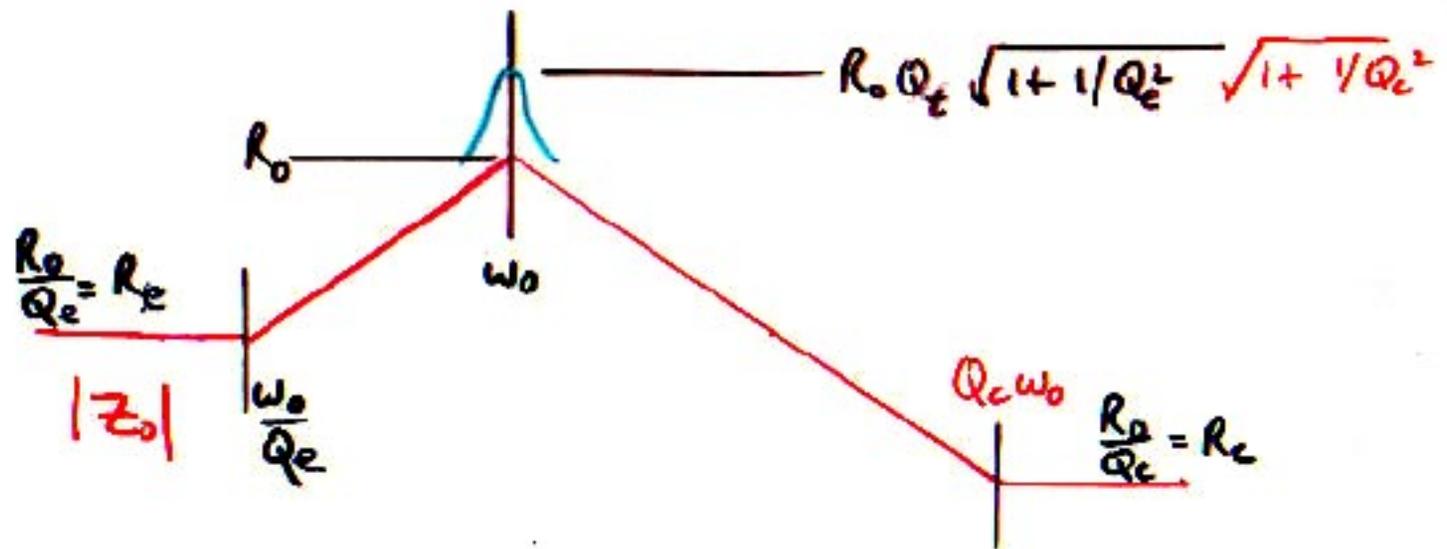
$$Z_0 \xrightarrow{\omega \rightarrow \infty} \frac{R_0}{Q_e} = R_c$$



The key step is now to determine T12 and T22 from the small signal model for the condition $\hat{v}_i = 0$:

$$T_{12} = \left[\frac{VO \times (RL - D^2 \times N^2 \times Z) \times (1 + sC \times RC)}{(D \times N \times \Delta)} \right] \quad [15]$$

$$T_{22} = \left[\frac{VO \times (RL - D^2 \times N^2 \times Z) \times (1 + sC \times RL)}{(D \times N \times RL \times \Delta)} \right] \quad [16]$$

where $(sL_1 + R_{L1})(sC_1 R_{C1} + 1)$

$$Z = \left[\frac{(s^2 L_1 \times C_1 \times R_{C1}) + (sC_1 \times R_{C1} \times R_{L1}) + sL_1 + R_{L1}}{(s^2 L_1 \times C_1) + sC_1 \times (R_{L1} + R_{C1}) + 1} \right] \quad [17]$$

$$\Delta = [a_1 + (D^2 \times N^2 \times Z) \times (1 + sC \times RL)] \quad [18]$$

$$a_1 = \left[(s^2 L \times C \times RL) + sC \times RL \times (R_I + RC + \frac{L}{(C \times RL)}) + RL \right] \quad [19]$$

At the resonant frequency of the input filter, the impedance Z will attain a very high value, limited only by the series resistances RL1 and RC1. The peaking in the value of Z will affect both the numerators and denominators of the transfer functions T12 and T22, as shown in equations 15 and 16. The net effect will be a reduction in the loop gain G_r and a corresponding phase margin reduction.

