


EXERCISE 5.1


SOLUTION

Exercise


For the two-pole low-pass LC filter,
sketch the magnitude and phase asymptotes
of Z_i and Z_o for low Q ($\ll 0.5$).
(But take $Q > 0.1$)

Low-pass 2-pole characteristic:

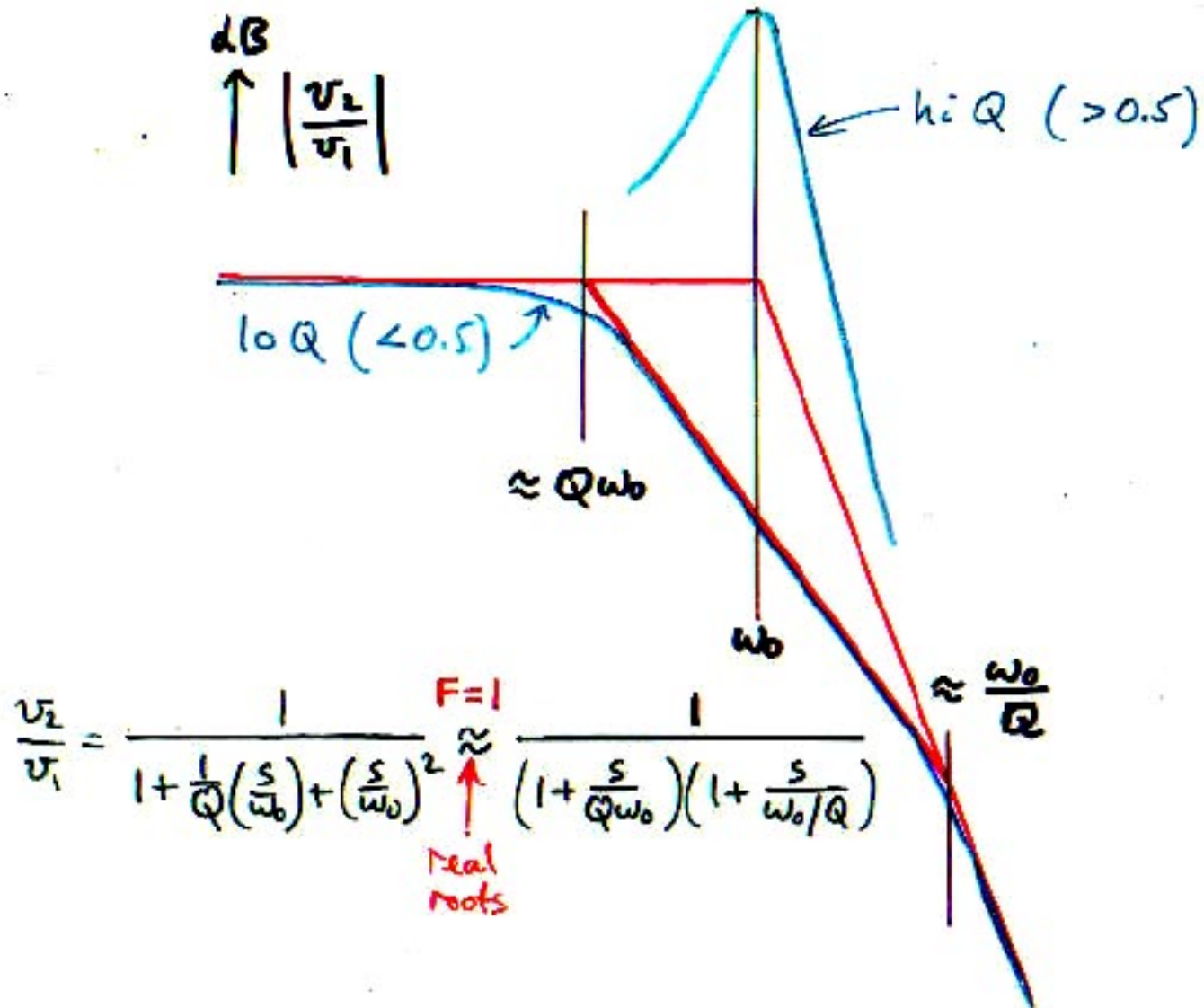

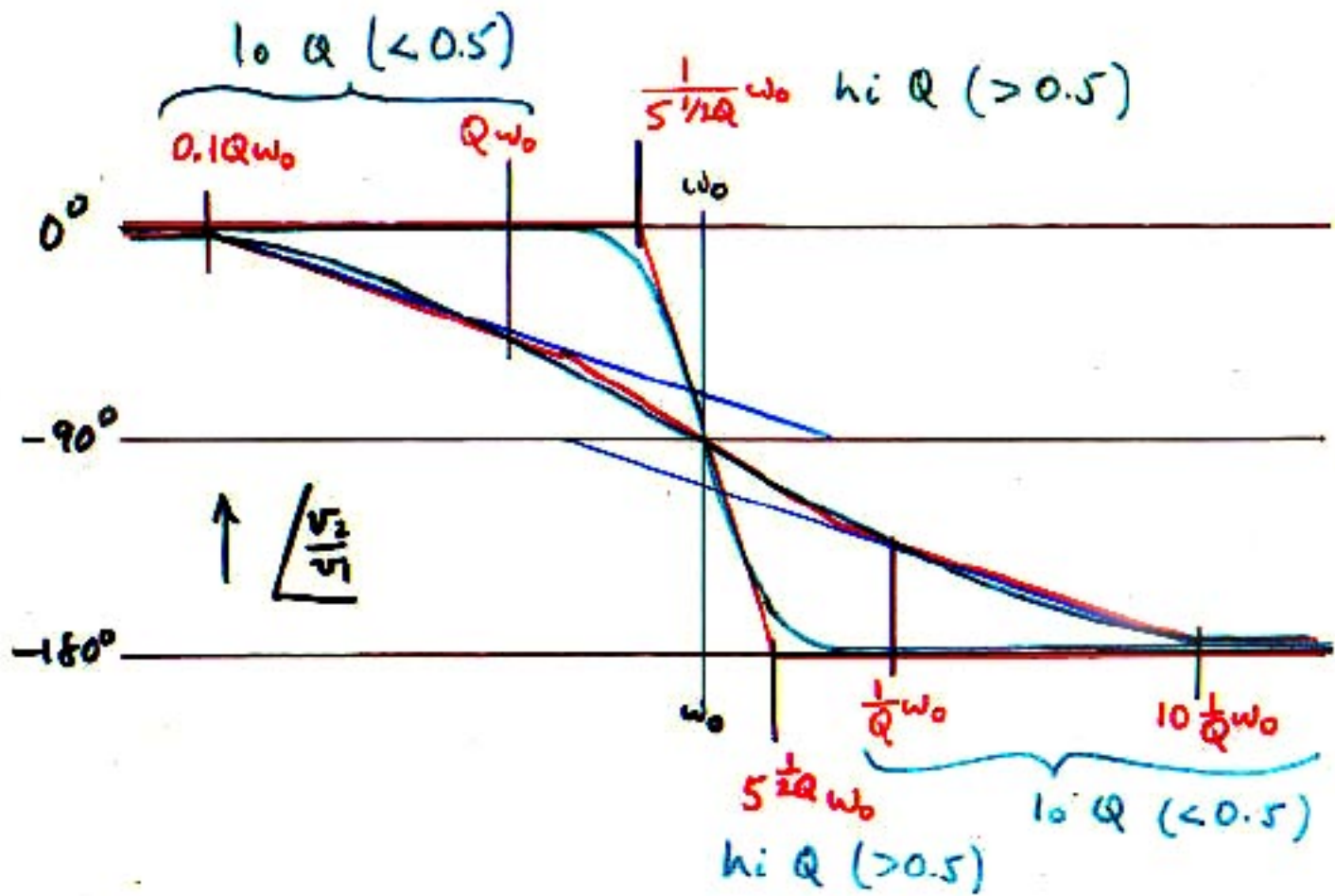

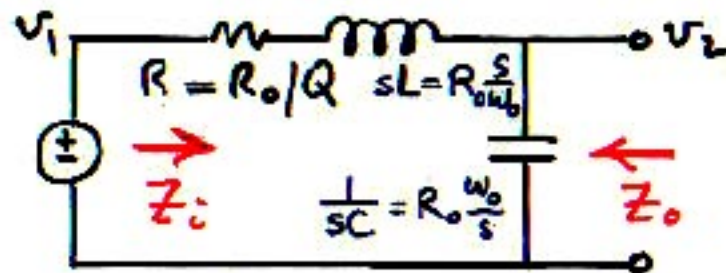Input and Output Impedances of low-pass filter



$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \frac{R_0}{R}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

$$Z_i = \frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}$$

$$= R_0 \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)}$$

$$Z_o = \frac{\left(\frac{R_0}{Q} + R_0 \frac{s}{\omega_0}\right) R_0 \frac{\omega_0}{s}}{\frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}}$$

$$= R_0 \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$


Note how the algebra is shortened when the analysis starts with the normalized element values.

$$Z_i = R_o \times \left[1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2 \right] \times \left[\frac{1}{\frac{s}{\omega_o}} \right]$$


ref. value $\frac{1}{H}$ single slope

R_o

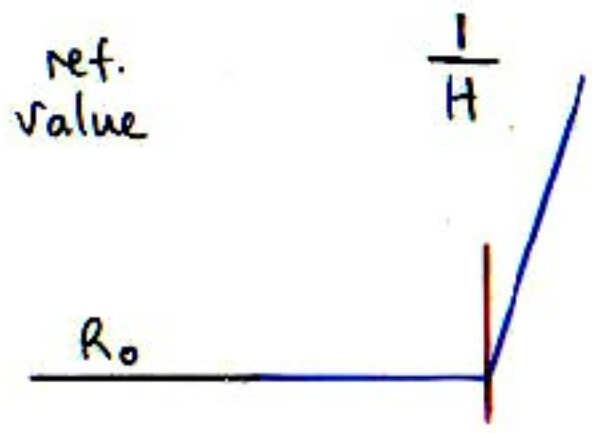
$$Z_i = R_o \times \left[1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2 \right] \times \left[\frac{1}{\frac{s}{\omega_o}} \right]$$




single slope

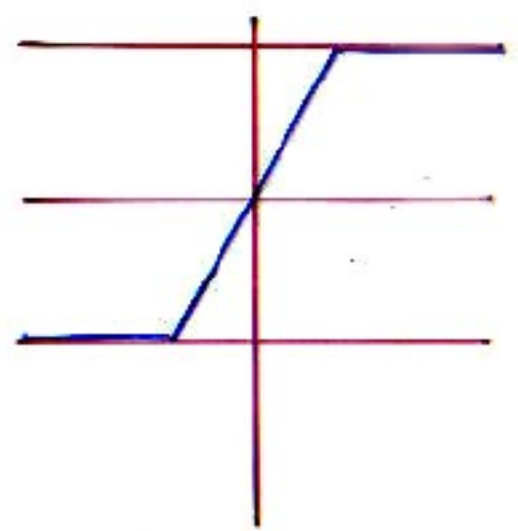

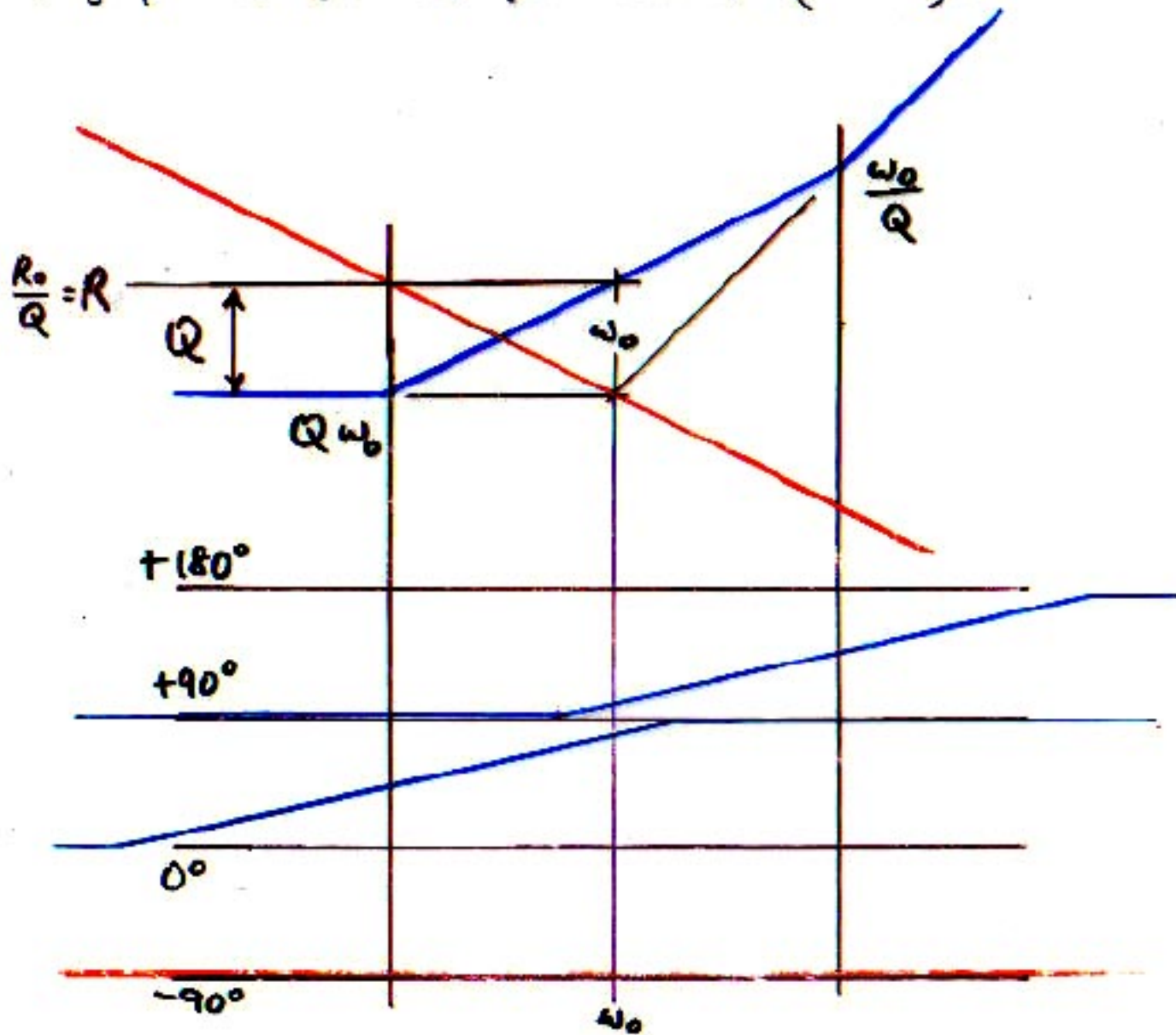Asymptotes for Z_i for low Q ($\ll 0.5$):



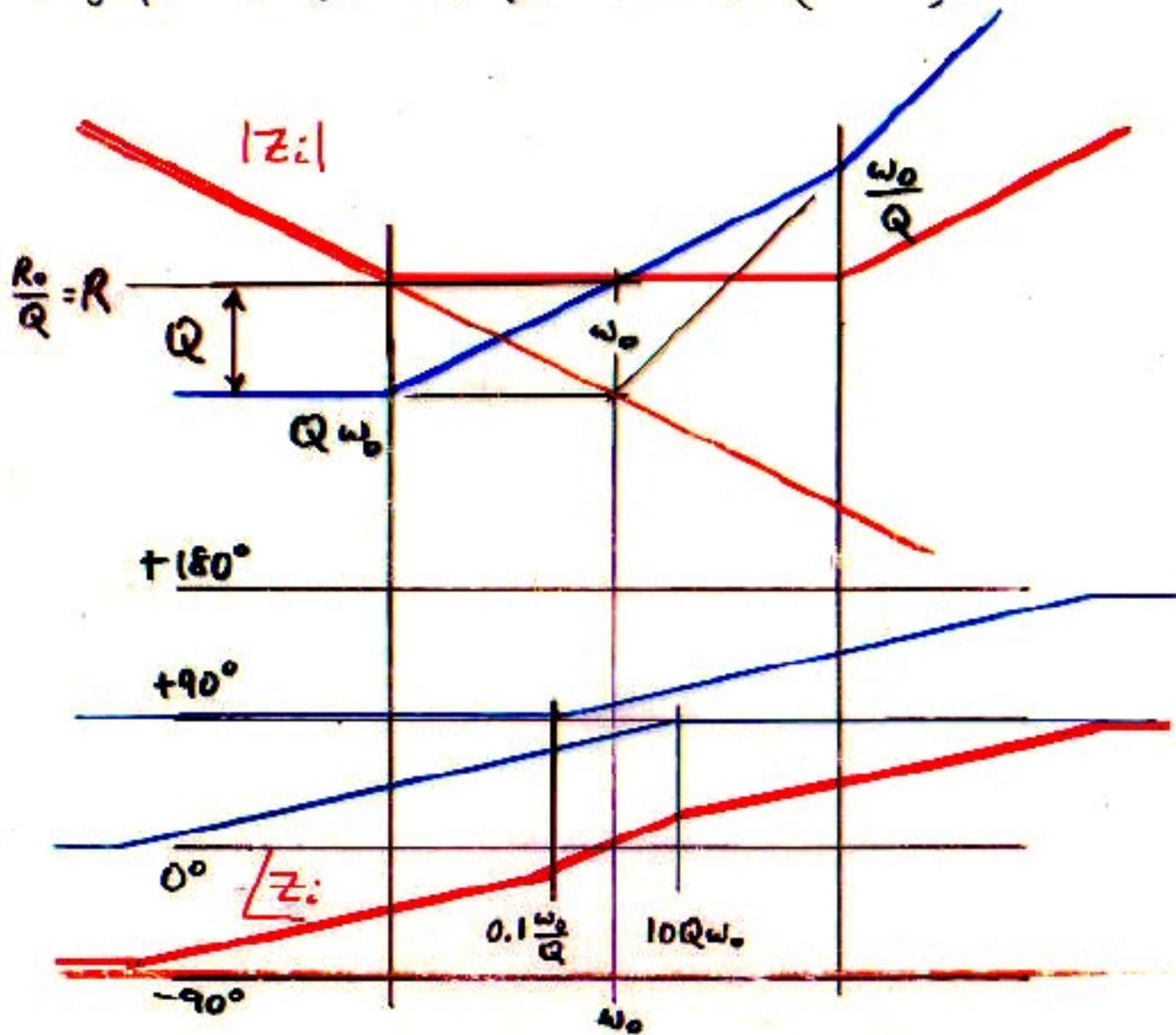Asymptotes for Z_i for low Q ($\ll 0.5$):



$$Z_o = R_o \times \left[\frac{\frac{s}{\omega_o}}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2} \right] \times \left(1 + \frac{\omega_o/Q}{s} \right)$$

ref.
value

$\frac{1}{Z_i}$


inverted
zero

R_o

$$Z_o = R_o \times \left[\frac{\frac{3}{\omega_o}}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2} \right] \times \left(1 + \frac{\omega_o/Q}{s} \right)$$

ref. value
 $\frac{1}{Z_i}$
inverted zero

R_o


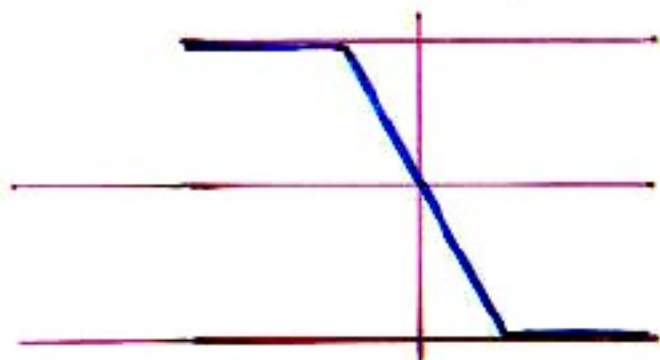


$$Z_o = R_o \times \left[\frac{\frac{\omega_o}{Q}}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o} \right) + \left(\frac{s}{\omega_o} \right)^2} \right] \times \left(1 + \frac{\omega_o/Q}{s} \right)$$


ref.
value

$\frac{1}{Z_i}$

inverted
zero

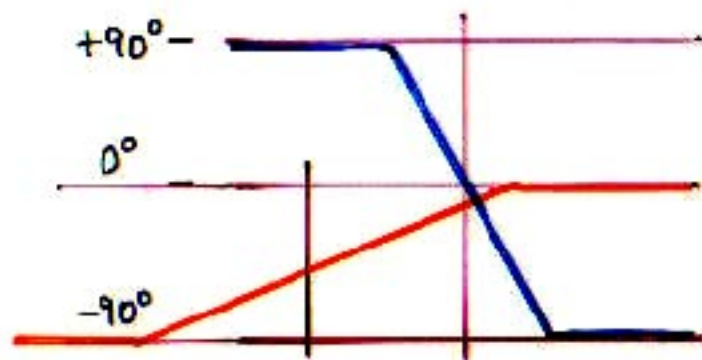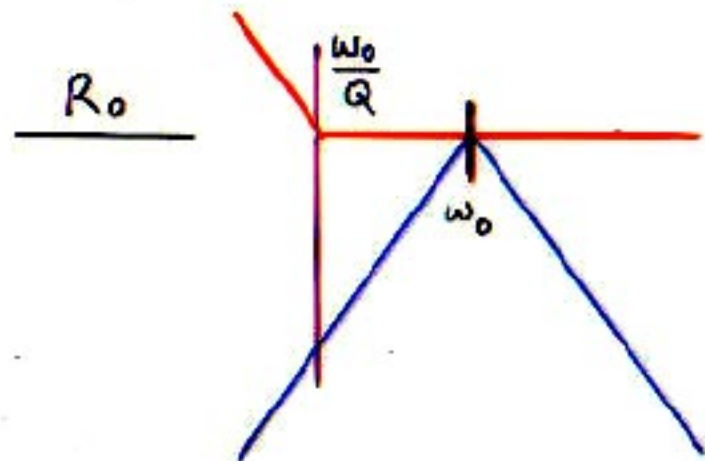

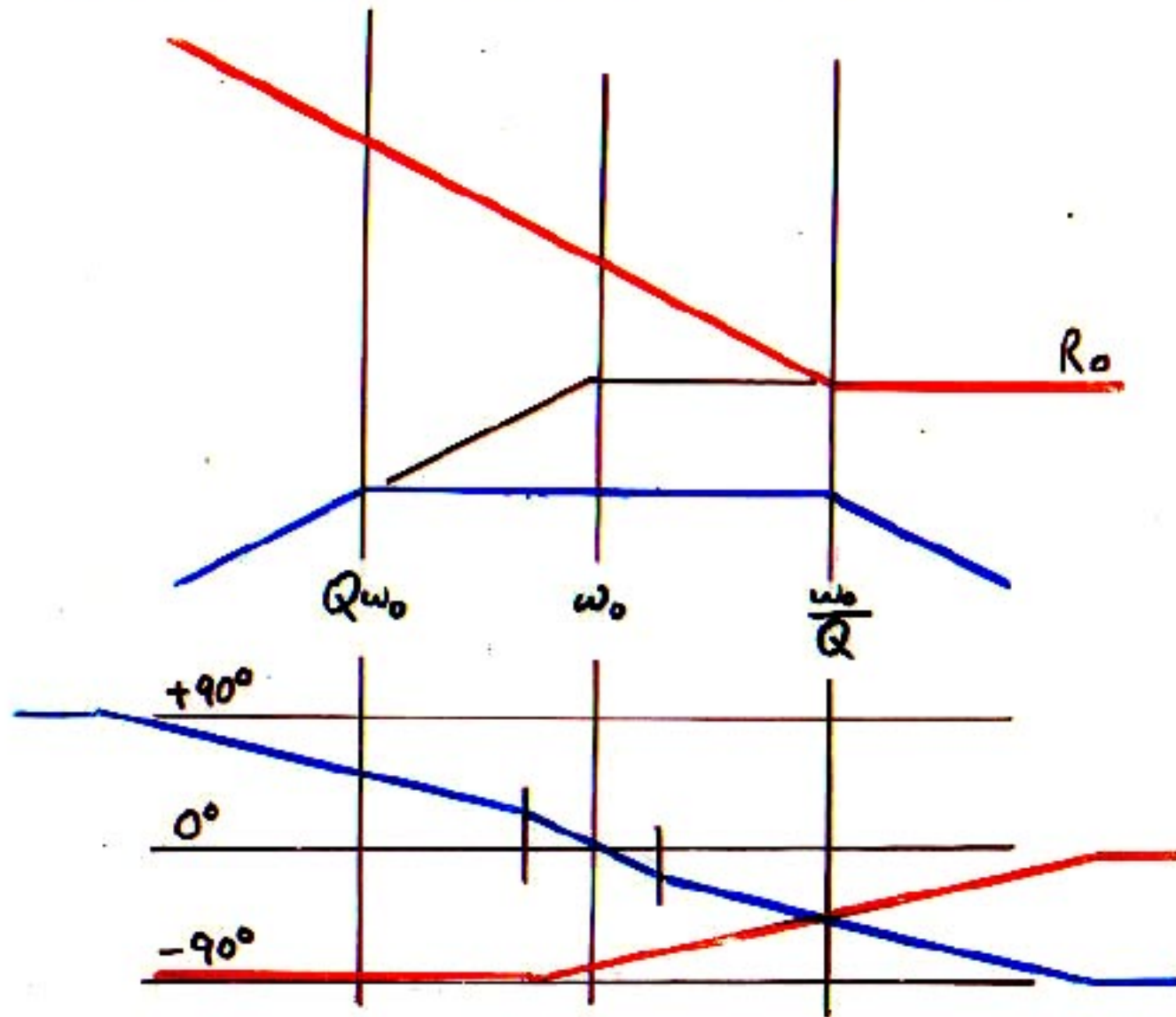Asymptotes for Z_o for low Q ($\ll 0.5$):



Asymptotes for Z_o for low Q ($\ll 0.5$):

