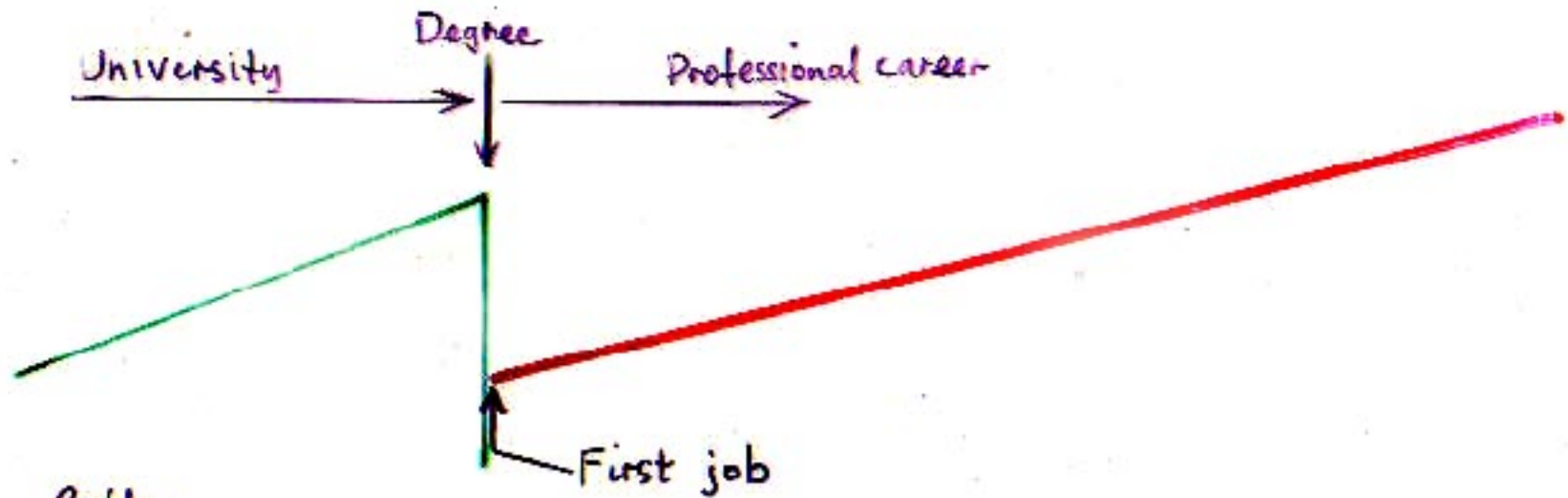


# 1



## **MOTIVATION AND BACKGROUND**






Problem:

New graduate engineers are unable to translate the principles and methods they have learned to the real world.

What can be done.?

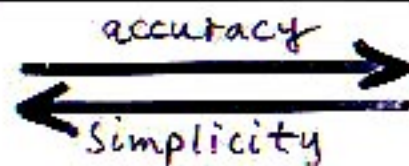
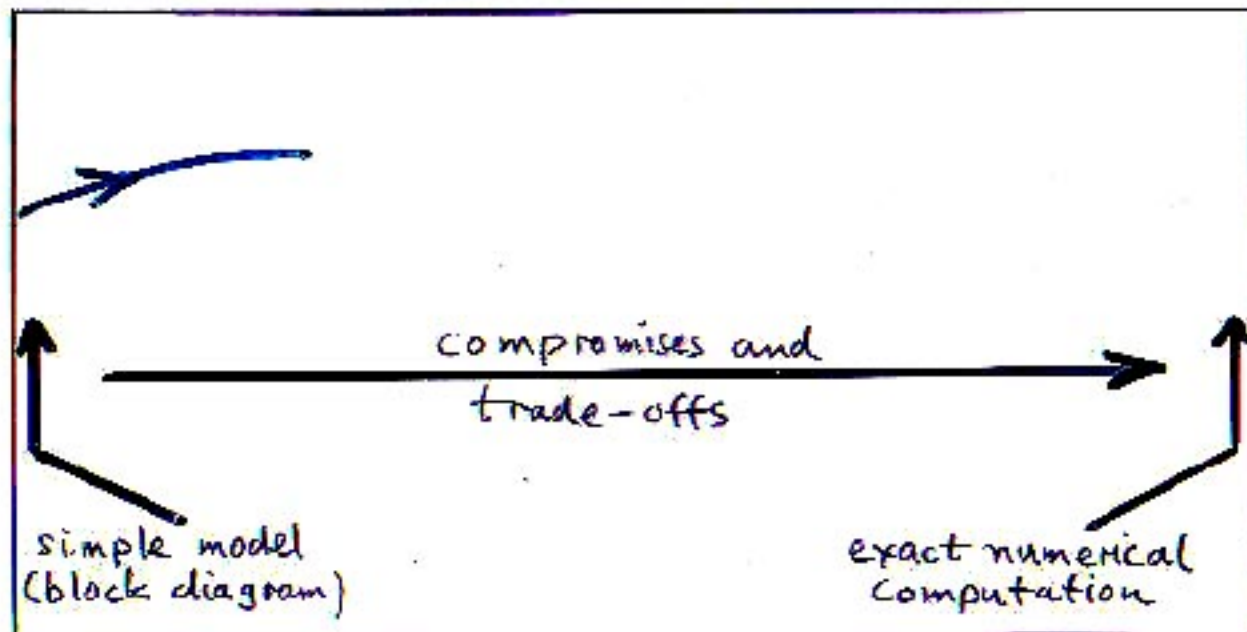


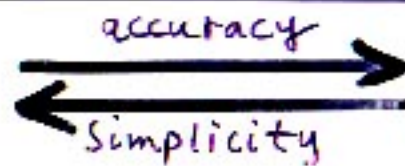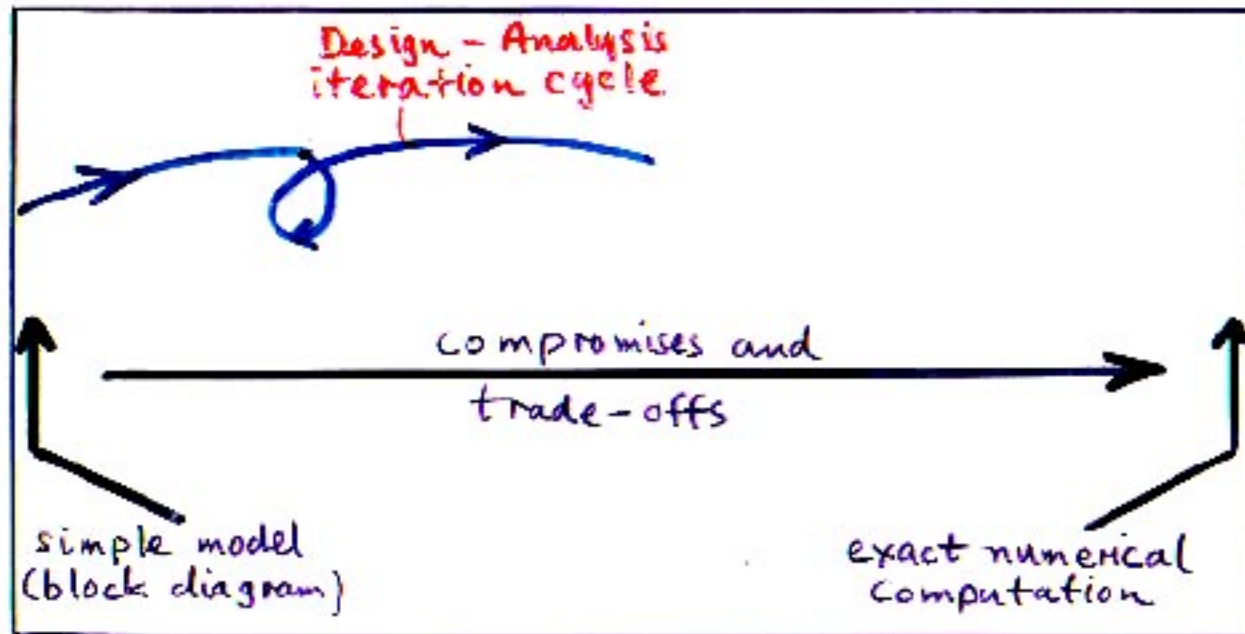

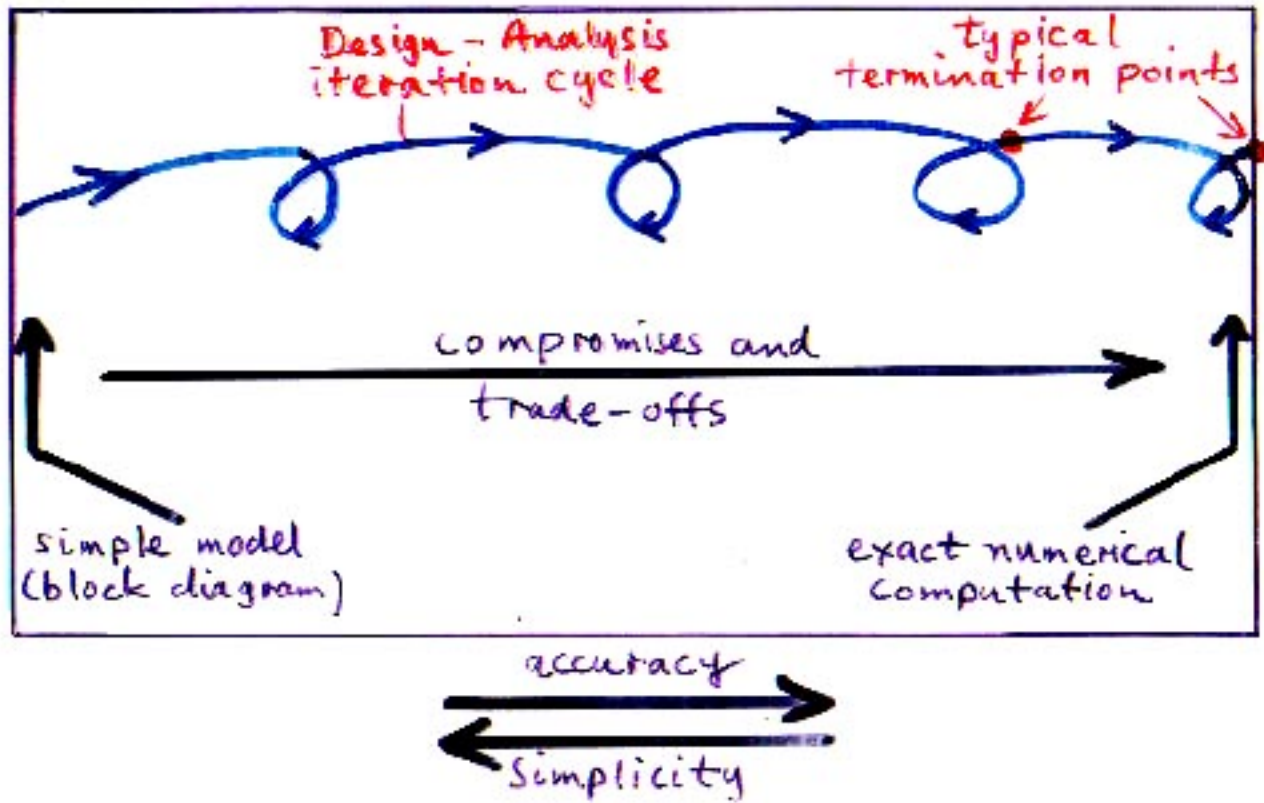

PROJECT  
MANAGER


DESIGN REVIEW  
COMMITTEE

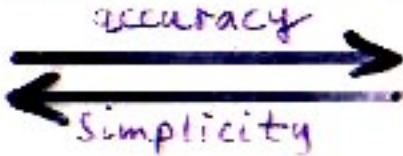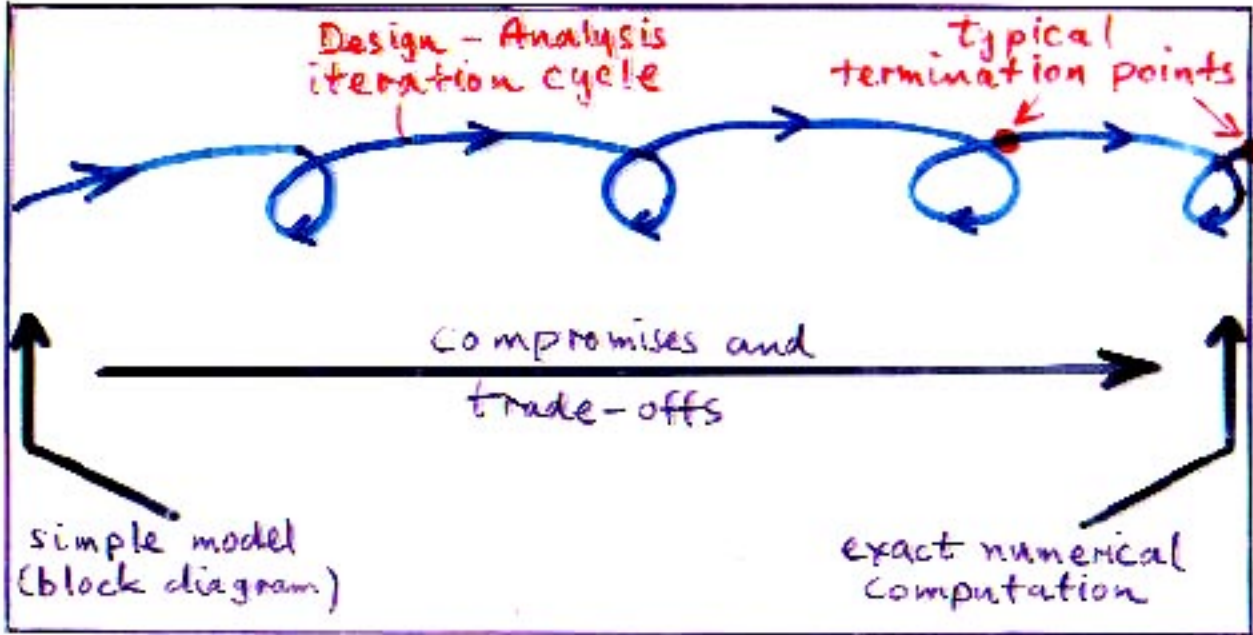

# DESIGN-ORIENTED ANALYSIS



# DESIGN-ORIENTED ANALYSIS

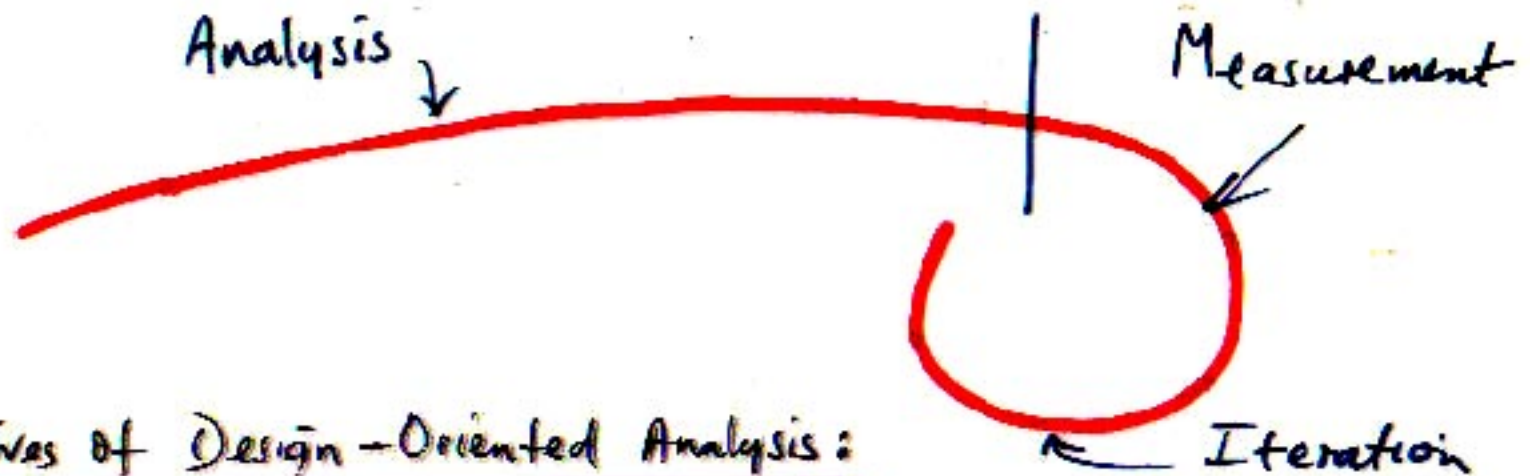

## Objectives of Design-Oriented Analysis:

To get an Analytic Answer in a form useful for Design,  
because:


Design is the Reverse of Analysis

because:


The Starting-Point of the Design Problem (the Specification)  
is the Answer to the Analysis Problem.



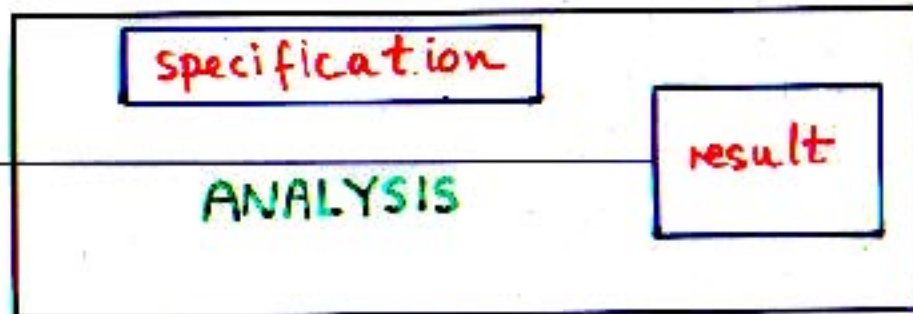⇒ model, with perhaps  
some tentative  
values



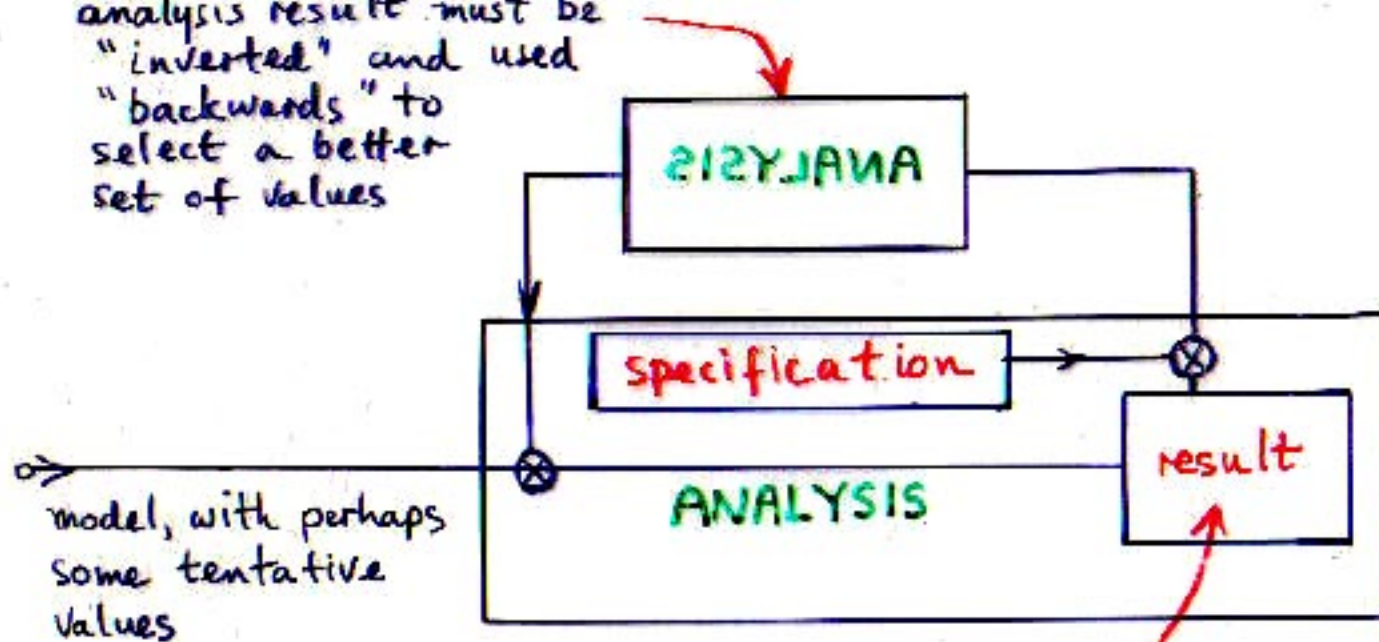analysis result must be  
"inverted" and used  
"backwards" to  
select a better  
set of values



To "invert" the analysis result,  
it must be in "Low Entropy"  
form.

## Techniques of Design-Oriented Analysis

Lowering the Entropy of an expression

Doing the algebra on the circuit diagram.

Doing the algebra on the graph.

Using inverted poles and zeros.

Using numerical values to justify analytic approximations.

Improved formulas for quadratic roots

The Input/Output Impedance Theorem

The Feedback Theorem

Loop gain by injection of a test signal into the closed loop

Measurement of an unstable loop gain

The Extra Element Theorem (EET)

## Lowering the Entropy of an Expression.


Entropy is a measure of Disorder.

A High-Entropy Expression is one in which the arrangement of terms and element symbols conveys no information other than that obtained by substitution of numbers.

An Objective of Design-Oriented Analysis is to lower the Entropy, by ordering and grouping the terms and elements so that their physical origin and relative importance are apparent. Only in this way can one change the values in an informed manner in order to change the analysis answer (that is, to make it meet the Specification).

Solution for gain:

$$A_m \equiv \frac{v_2}{v_1}$$

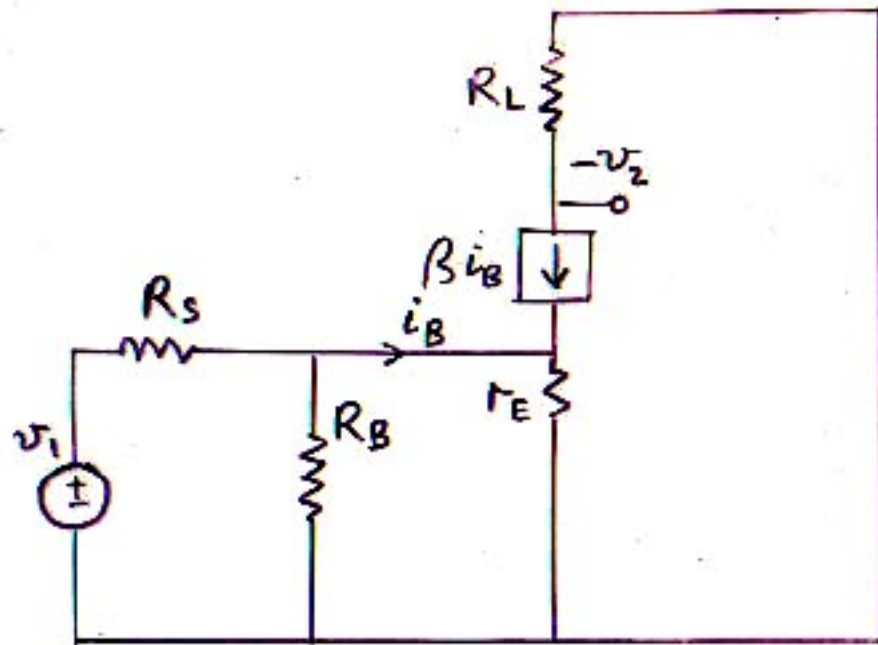


High-entropy form:

$$A_m = \frac{\beta R_B R_L}{(1+\beta)R_E R_s + (1+\beta)R_E R_B + R_s R_B}$$

Low-entropy form:


$$A_m = \frac{R_B}{R_s + R_B} \cdot \frac{\alpha R_L}{\underbrace{R_E}_{(1)} + \underbrace{(R_s \parallel R_B) / (1+\beta)}_{(2)}}$$
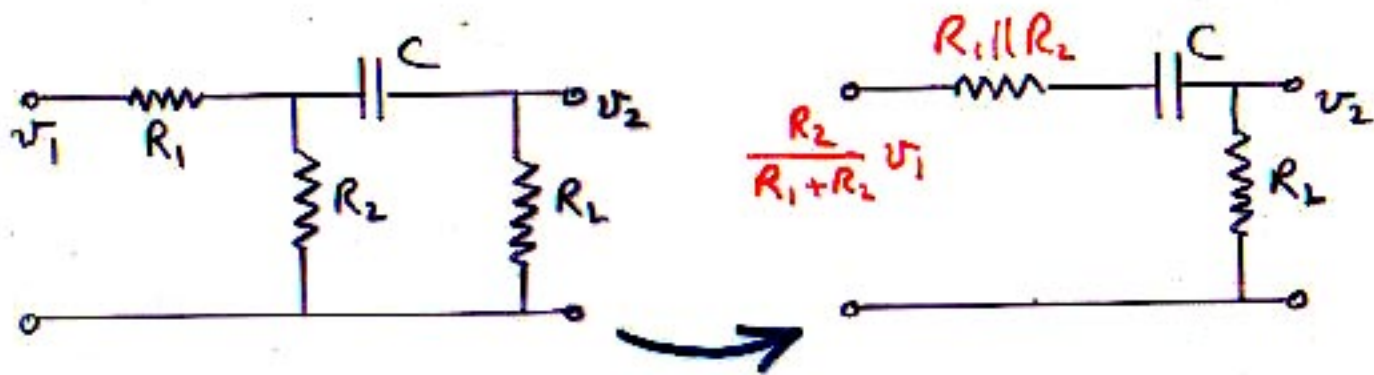
## Doing the Algebra on the Circuit Diagram




This is how (low-entropy) element groupings arise naturally, through successive loop and node reduction by Thevenin's and Norton's theorems.

Doing the algebra on the graph

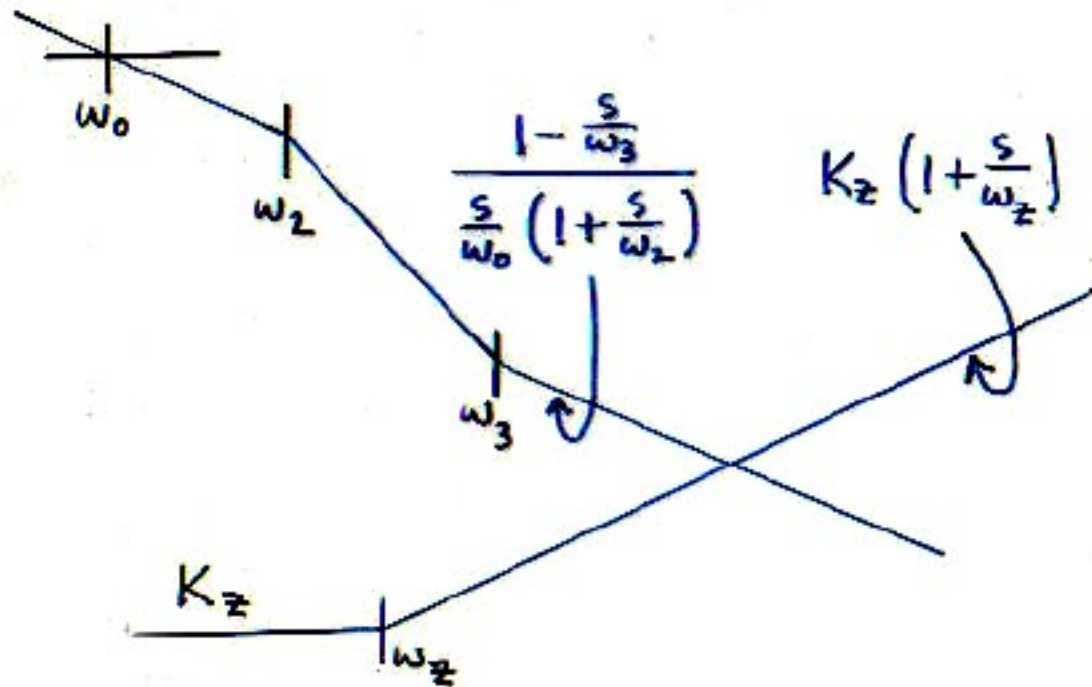


Doing the algebra on the graph

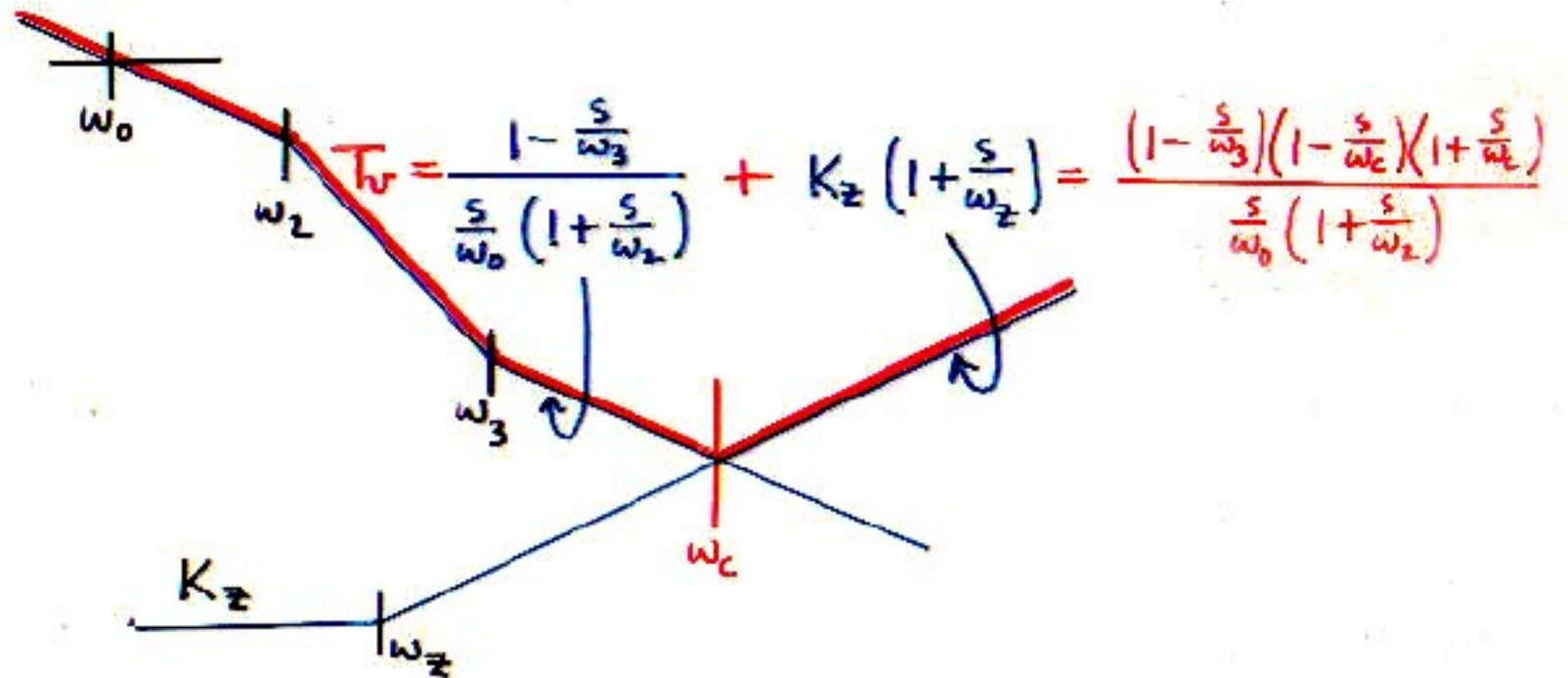



Normal and inverted poles and zeros:

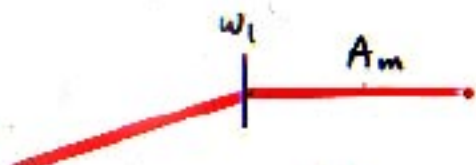

$$A = A_m \frac{1}{\left(1 + \frac{\omega_1}{s}\right)}$$

inverted pole



$$A = A_m \left(1 + \frac{\omega_1}{s}\right)$$

inverted zero

$|A|$  dB  
 $\uparrow$   
 $\omega$  (log)  
 $\rightarrow$



$$A = A_m \frac{1}{\left(1 + \frac{s}{\omega_1}\right)}$$





normal pole



$$A = A_m \left(1 + \frac{s}{\omega_1}\right)$$

normal zero

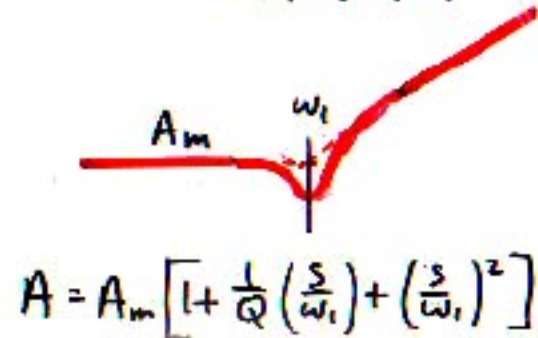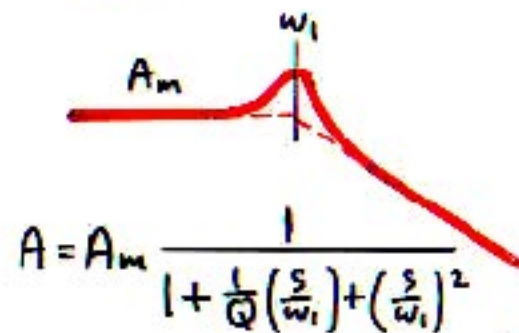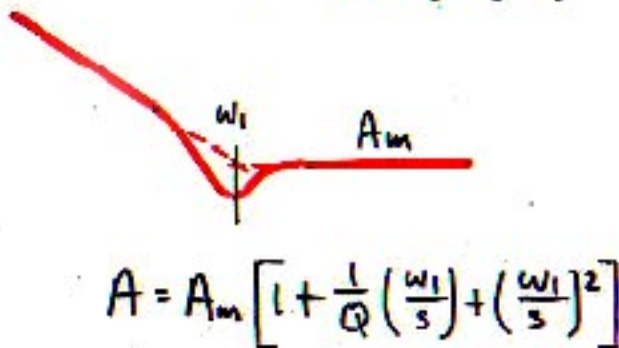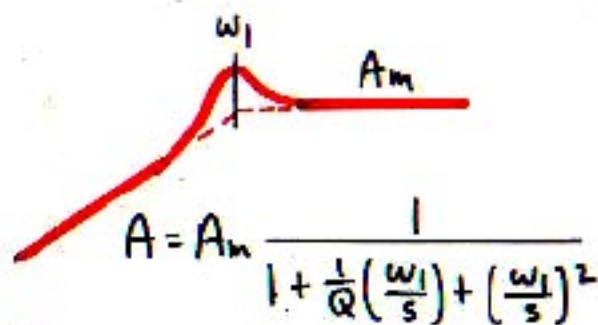
Quadratic normal and inverted poles and zeros:



Use of numerical values to justify analytic approximations

$$A = \frac{R_L}{R_1 + R_L} \frac{1 + C_1 R_2 s}{1 + [C_1(R_2 + R_1 || R_L) + C_2(R_1 || R_L)]s + [C_1 C_2 R_2 (R_1 || R_L)]s^2}$$

Improved formulas for quadratic roots:

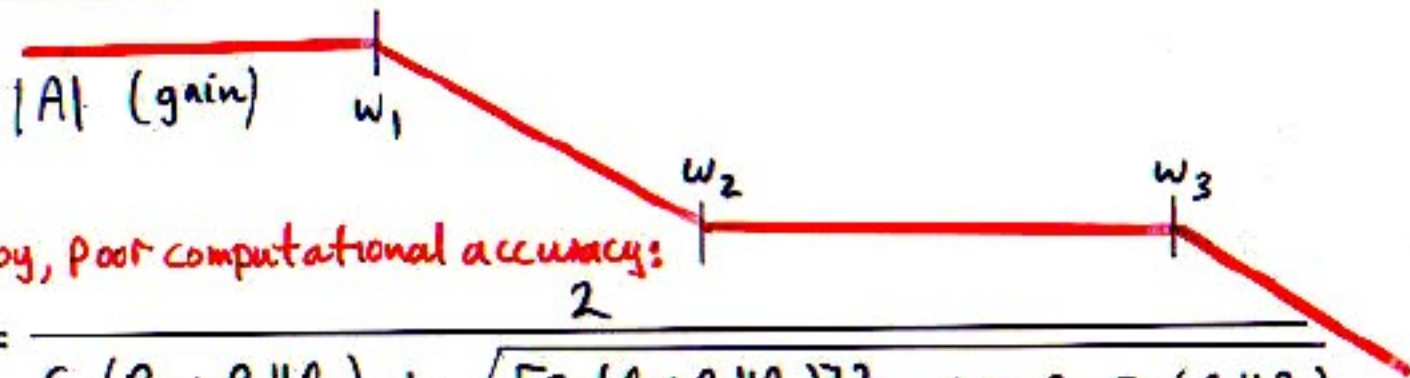

High entropy, poor computational accuracy: 2

$$\omega_{1,3} = \frac{C_1(R_2 + R_1 \parallel R_L) \pm \sqrt{[C_1(R_2 + R_1 \parallel R_L)]^2 - 4C_1C_2R_2(R_1 \parallel R_L)}}{2}$$

Low entropy, superior computational accuracy:

$$\omega_1 = \frac{1}{C_1(R_2 + R_1 \parallel R_L)}$$

$$\omega_3 = \frac{1}{C_2(R_1 \parallel R_2 \parallel R_L)}$$

## Techniques of Design-Oriented Analysis

Lowering the Entropy of an expression

Doing the algebra on the circuit diagram.

Doing the algebra on the graph.

Using inverted poles and zeros.

Using numerical values to justify analytic approximations.

Improved formulas for quadratic roots

The Input/Output Impedance Theorem

The Feedback Theorem

Loop gain by injection of a test signal into the closed loop

Measurement of an unstable loop gain

The Extra Element Theorem (EET)

## Input/Output Impedance Theorem

$$Z_i = \frac{Z_s A |_{Z_s \rightarrow \infty}}{A |_{Z_s \rightarrow 0}}$$

$$Z_o = \frac{A |_{Z_L \rightarrow \infty}}{\frac{A}{Z_L} |_{Z_L \rightarrow 0}}$$

## Feedback Theorem

$$G = \frac{A}{1+AK} = \frac{1}{K} \frac{AK}{1+AK} = G_{\infty} \frac{T}{1+T}$$

design specification  $\swarrow$   
discrepancy factor  $\swarrow$

Avoids having to find  $A$  by opening the loop.

# DESIGN-ORIENTED ANALYSIS

Analysis ↓

Measurement

## Techniques of Design-Oriented Analysis

Lowering the Entropy of an expression

Doing the algebra on the circuit diagram.

Doing the algebra on the graph.

Using inverted poles and zeros.

Using numerical values to justify analytic approximations.

Improved formulas for quadratic roots

The Input/Output Impedance Theorem

The Feedback Theorem

Loop gain by injection of a test signal into the closed loop

Measurement of an unstable loop gain

The Extra Element Theorem (EET)

Iteration

## Techniques of Design-Oriented Analysis

Lowering the Entropy of an expression

Doing the algebra on the circuit diagram.

Doing the algebra on the graph.

Using inverted poles and zeros.

Using numerical values to justify analytic approximations.

Improved formulas for quadratic roots

The Input/Output Impedance Theorem

The Feedback Theorem

Loop gain by injection of a test signal into the closed loop

Measurement of an unstable loop gain

The Extra Element Theorem (EET)



# DESIGN-ORIENTED ANALYSIS



Iteration

Null Double Injection leads to:

Extra Element Theorem (EET)

$$A|_z = A|_{z=\infty} \frac{1 + \frac{z_n}{z}}{1 + \frac{z_d}{z}}$$

Also useful for breaking the analysis of a complicated circuit into sequential easier pieces, as is the:

Two Extra Element Theorem (2EET)