

**11**


**HOW TO MEASURE T**

## Measurement of Loop Gain

As for the calculation of loop gain, an injection point for the test signal must be found that satisfies two conditions:

1. Must be inside the feedback loop
2. Injected signal must add to the forward signal without affecting the impedance loading.


## Example

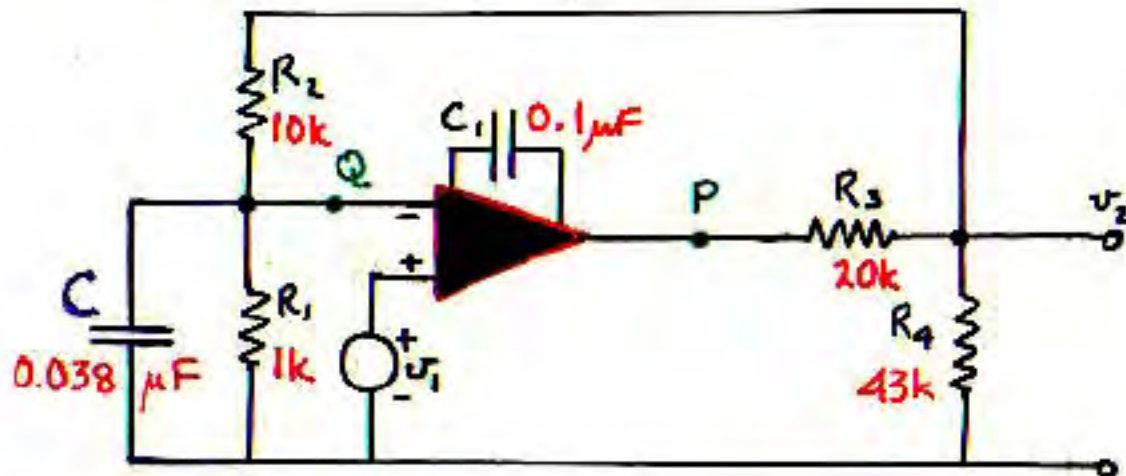

Either point P or point Q could be used for series voltage injection; there is no suitable point for current injection.

Experimentally, P is preferable because the signal levels are higher.

## Example

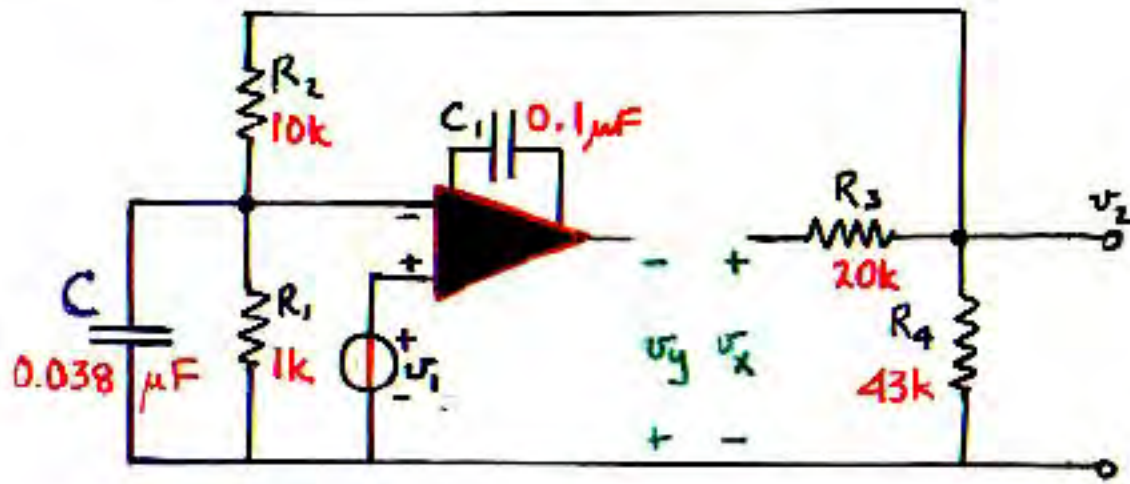


The loop gain  $T = \frac{v_y}{v_x} \Big|_{v_i=0}$  can then be

measured in magnitude and phase by

standard instrumentation.



## Example

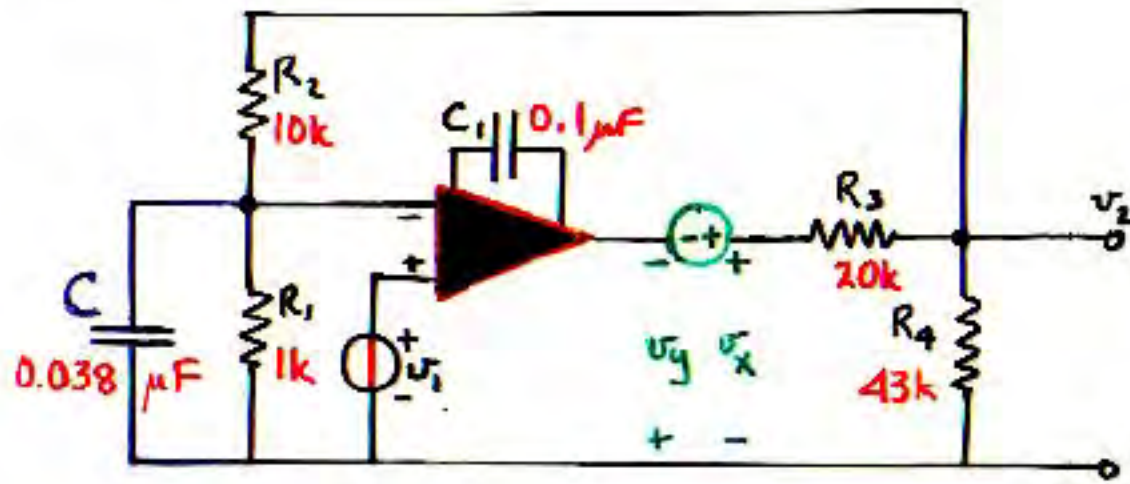

The loop gain  $T = \left. \frac{v_y}{v_x} \right|_{v_i=0}$  can then be measured in magnitude and phase by standard instrumentation.





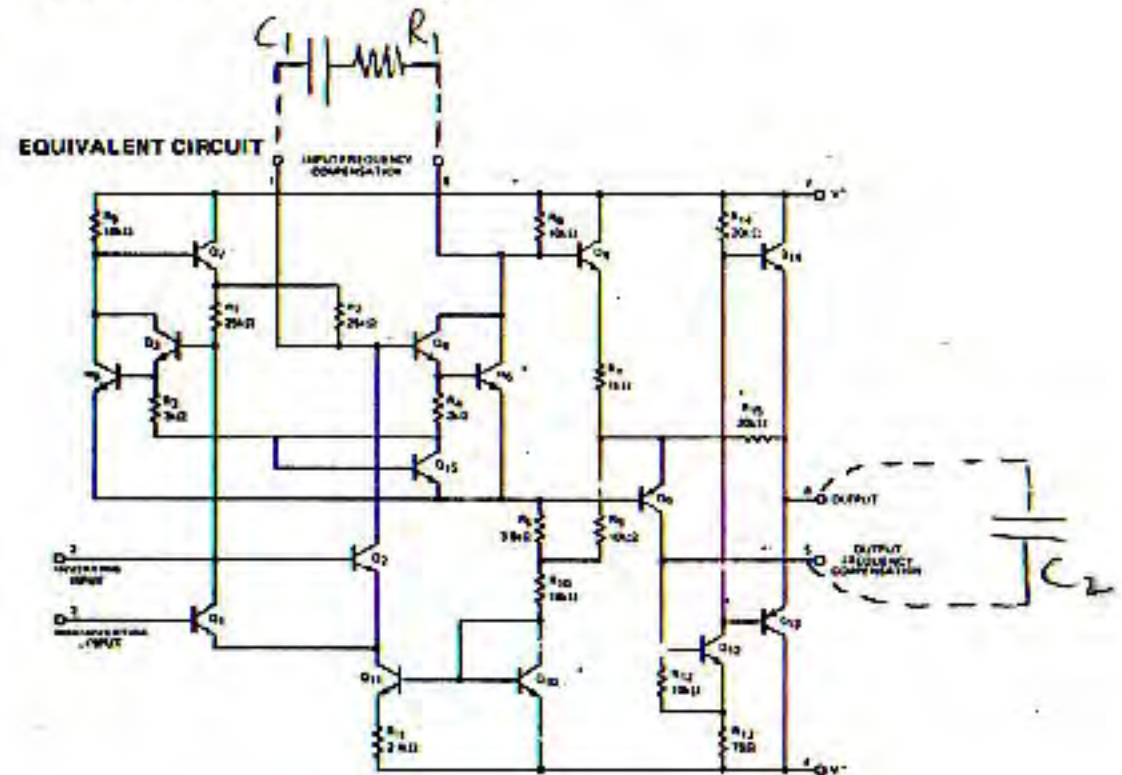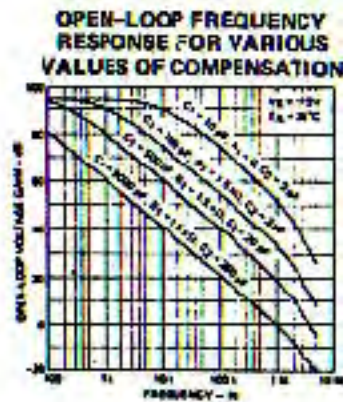In the normal design-analyze-measure sequence, the loop gain  $T$  is first predicted analytically.



With a  $0.005 \mu\text{F}$  compensating capacitor  $C_1$ , the gain-bandwidth product is  $1 \text{ MHz}$

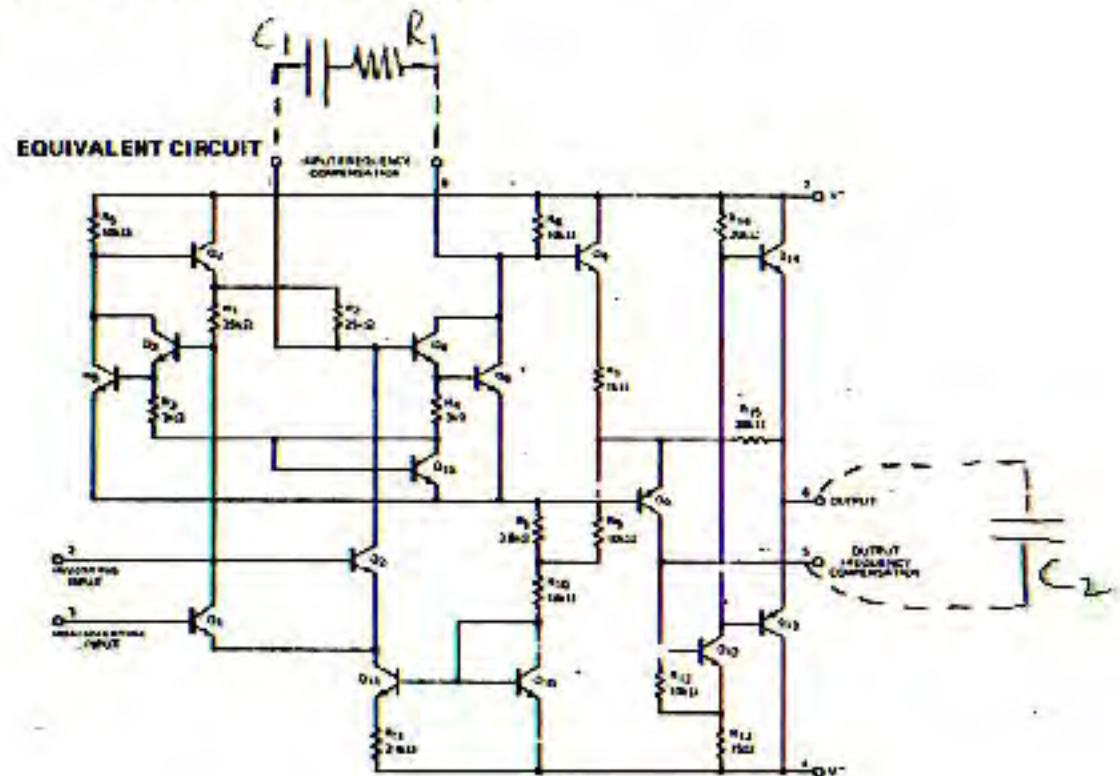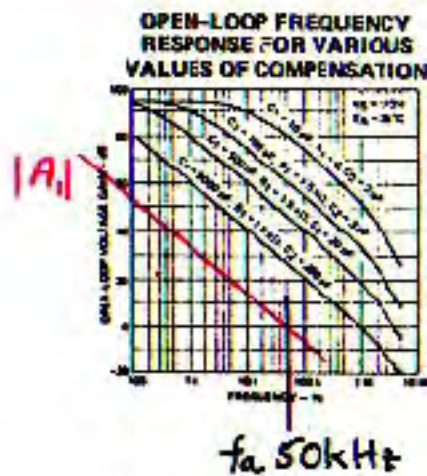In the normal design-analyze-measure sequence, the loop gain  $T$  is first predicted analytically.




With a  $0.005 \mu\text{F}$  compensating capacitor  $C_1$ , the gain-bandwidth product is  $1 \text{ MHz}$ . With  $C_1 = 0.1 \mu\text{F}$ , the gbw product is

$$f_a = \frac{0.005}{0.1} \times 1 = 50 \text{ kHz}$$

So  $A_1 = \frac{\omega_a}{s}$

## Example

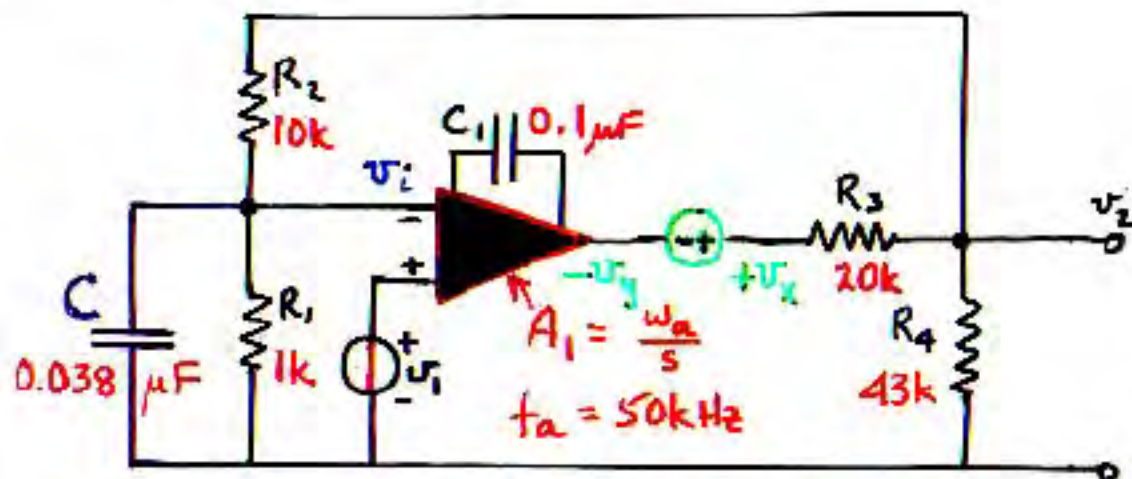

Without  $C$ :  $T = \frac{v_y}{v_x} = \frac{v_y}{v_i} \frac{v_2}{v_x} \frac{v_i}{v_2}$   
 $= A_1 A_2 K$

$$A_1 = \frac{\omega_a}{s}$$

$$A_2 = \frac{R_4 \parallel (R_1 + R_2)}{R_3 + R_4 \parallel (R_1 + R_2)}$$

$$= 0.31$$


$$K = \frac{R_1}{R_1 + R_2}$$

$$= 0.091$$

$C$  introduces a pole at:  $\omega_2 = \frac{1}{C [R_1 \parallel (R_2 + R_3 \parallel R_4)]}$   $f_2 = 4.4 kHz$



## Example

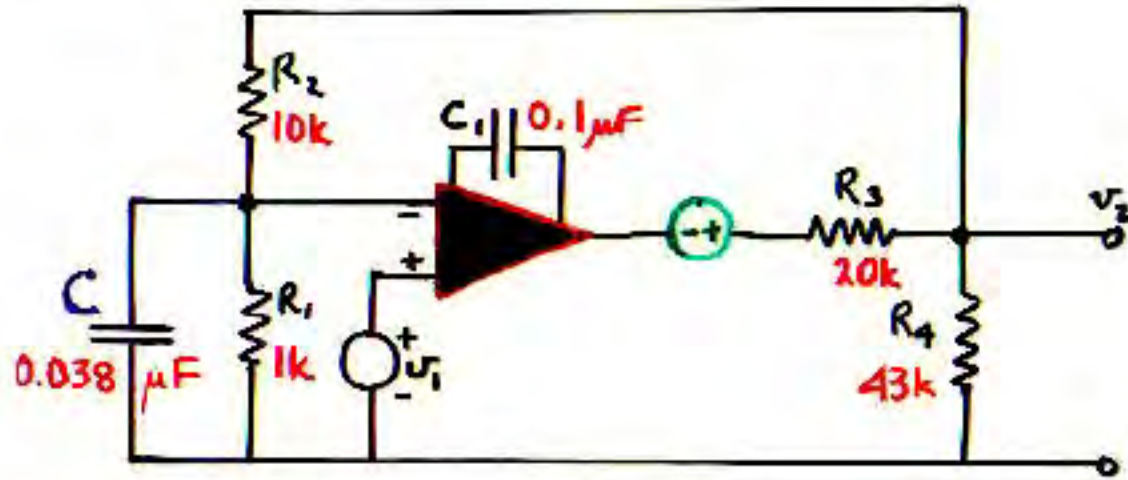

Hence

$$T = \frac{\omega_a}{s} A_2 K \frac{1}{1 + \frac{s}{\omega_2}}$$



$$= \frac{1}{\frac{s}{\omega_0} \left(1 + \frac{s}{\omega_2}\right)} \quad \text{where } \omega_0 \equiv A_2 K \omega_a$$

$$f_0 = 1.4 \text{ kHz}$$



The  $Q$  of the closed-loop quadratic  $D = T/(1+T)$  is

$$Q = \sqrt{\omega_0/\omega_2} = 0.56 \Rightarrow -5 \text{ dB}$$

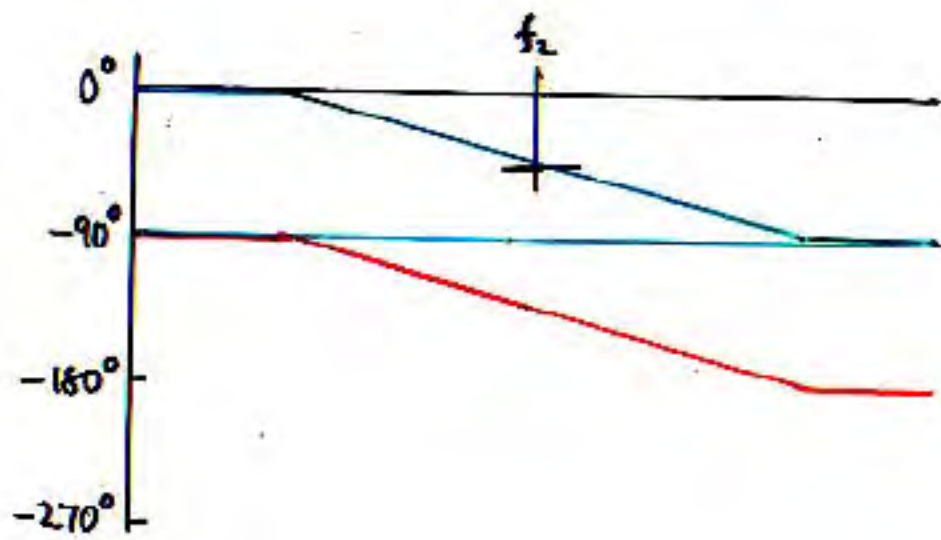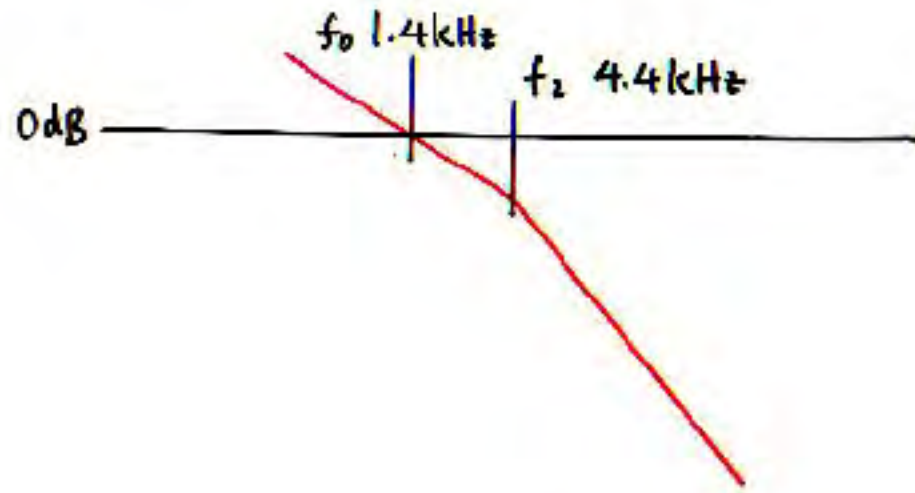and the phase margin is  $\phi_M = 73^\circ$




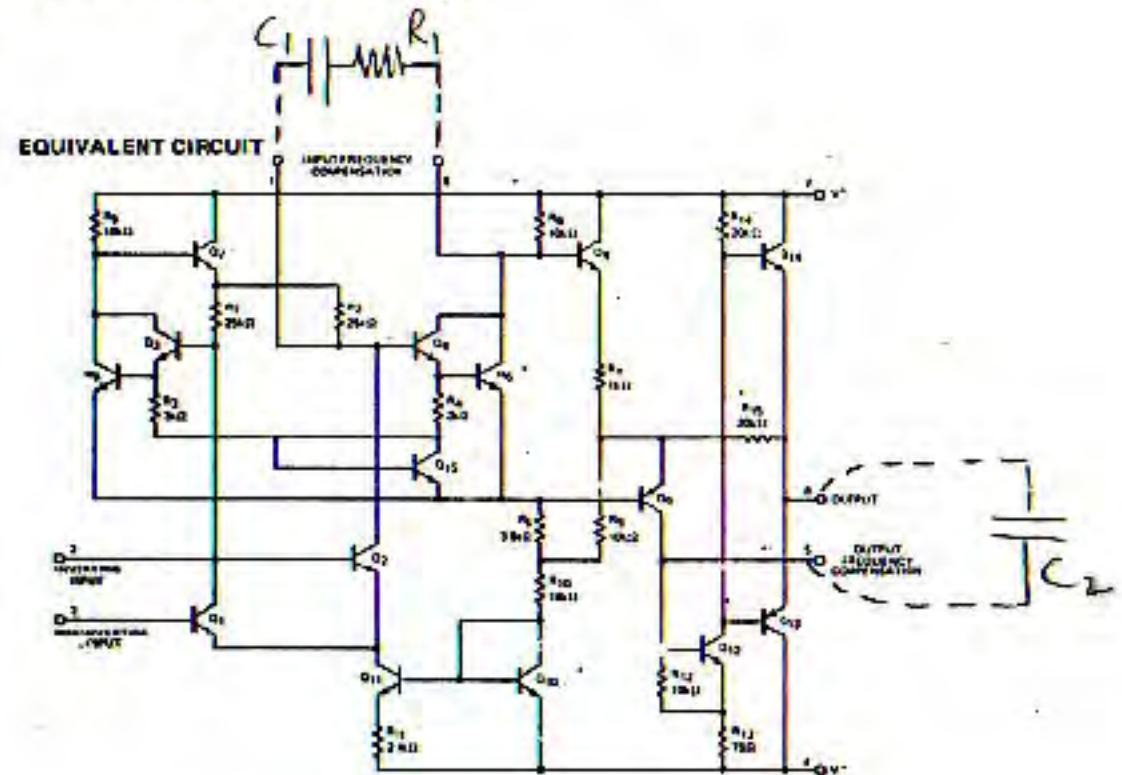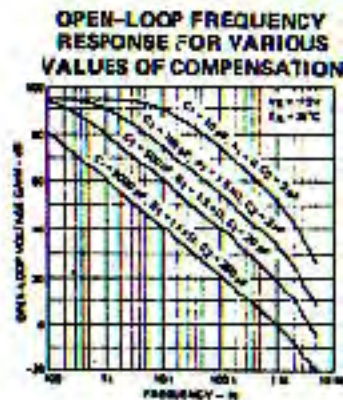In the normal design-analyze-measure sequence, the loop gain  $T$  is first predicted analytically.




With a  $0.005\mu\text{F}$  compensating capacitor  $C_1$ , the gain-bandwidth product is  $1\text{MHz}$

Example

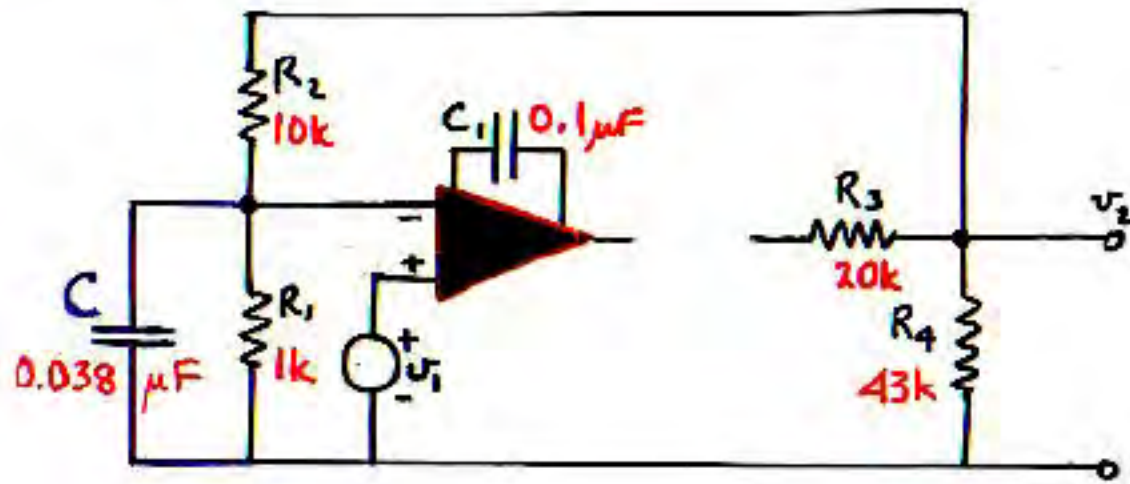





Example

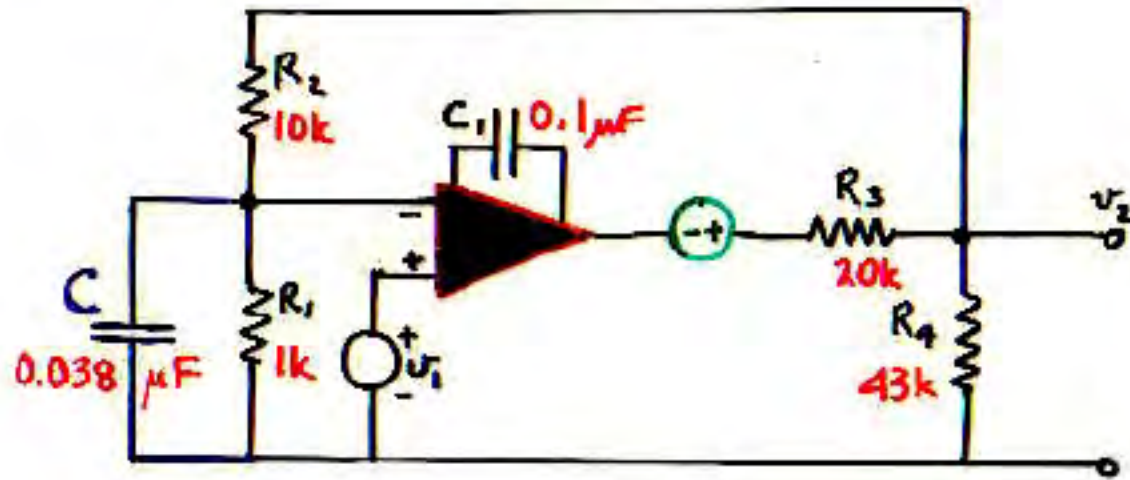


Example Measurement instrumentation:

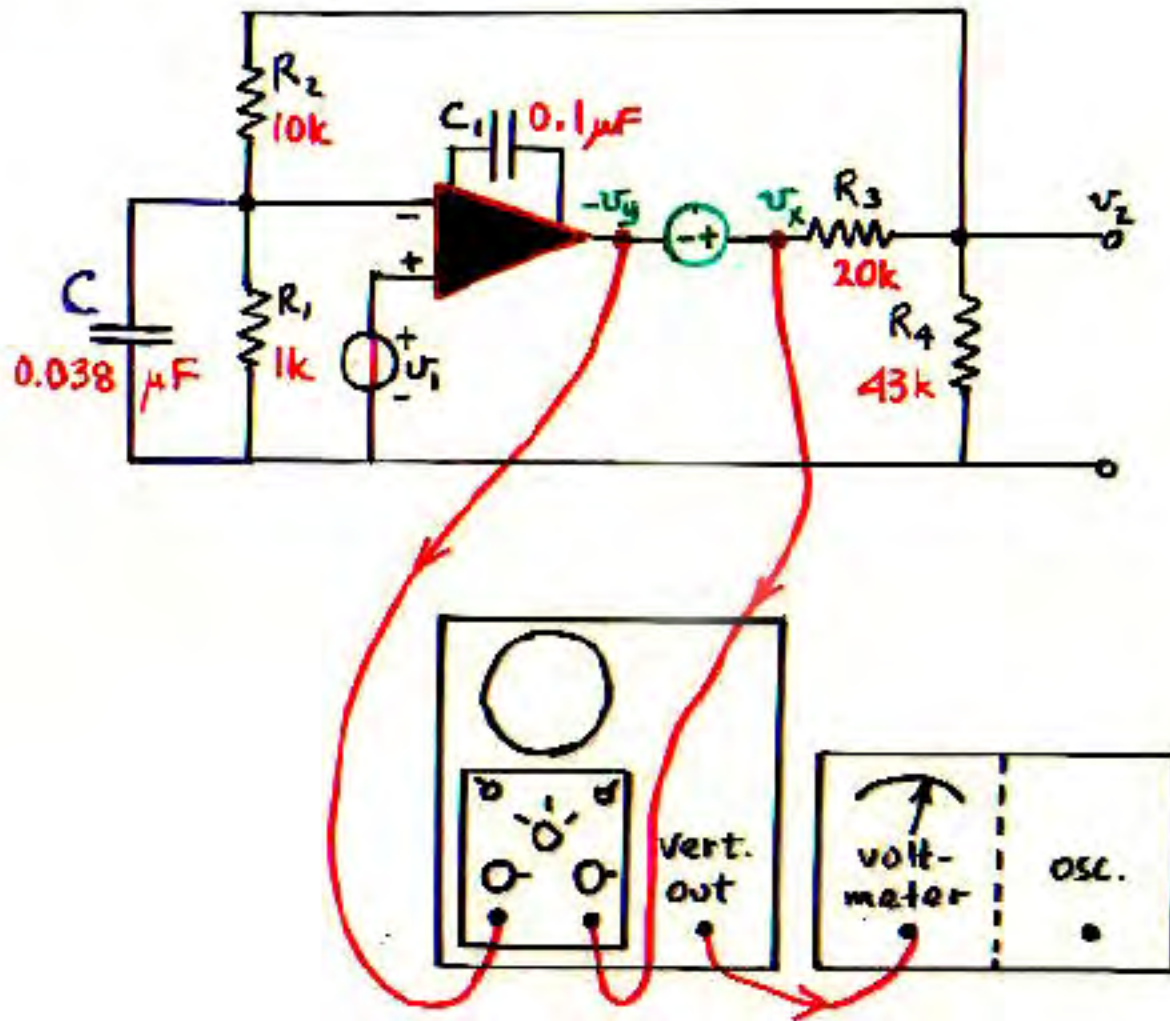

# Example

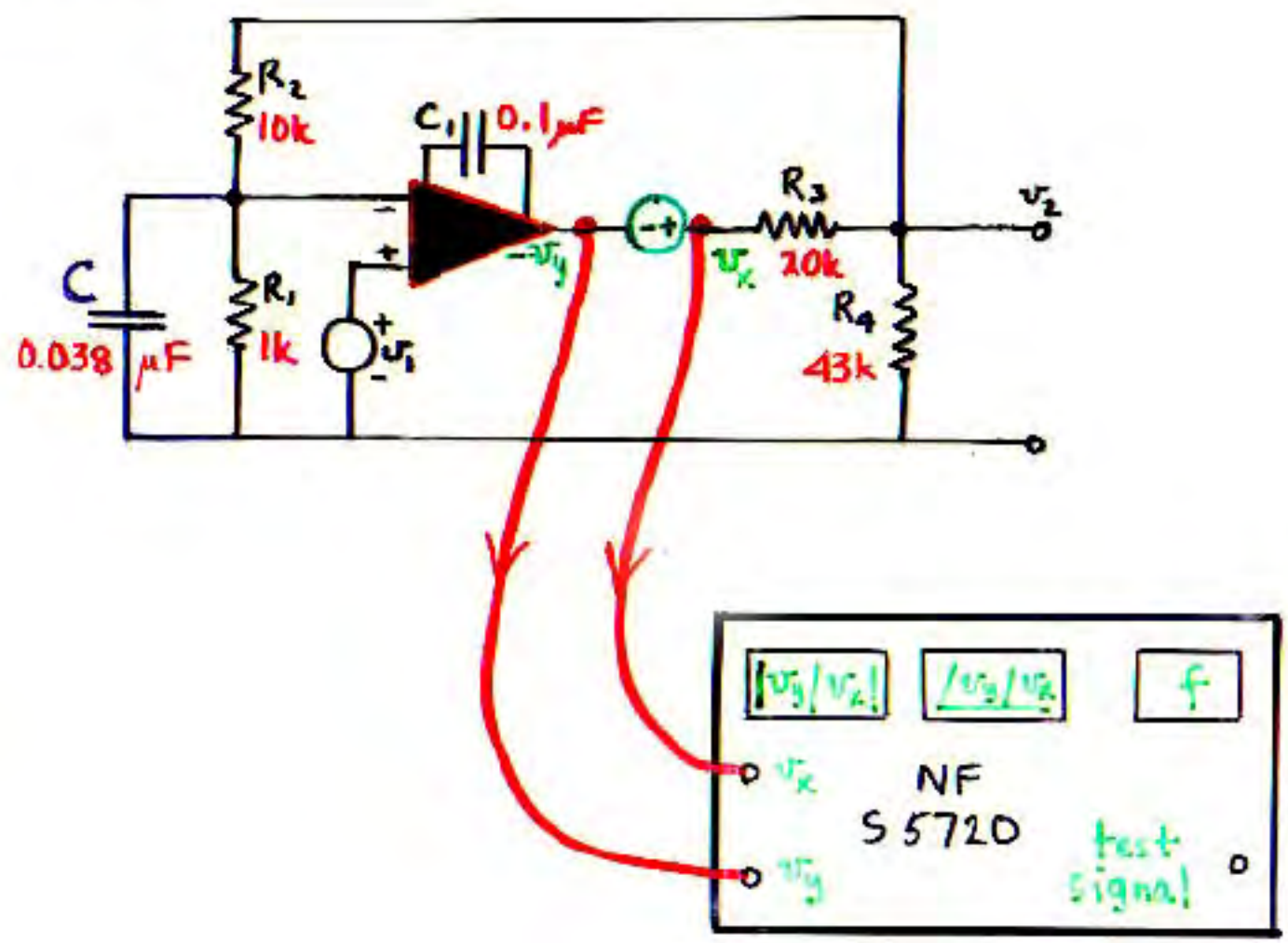


# Example

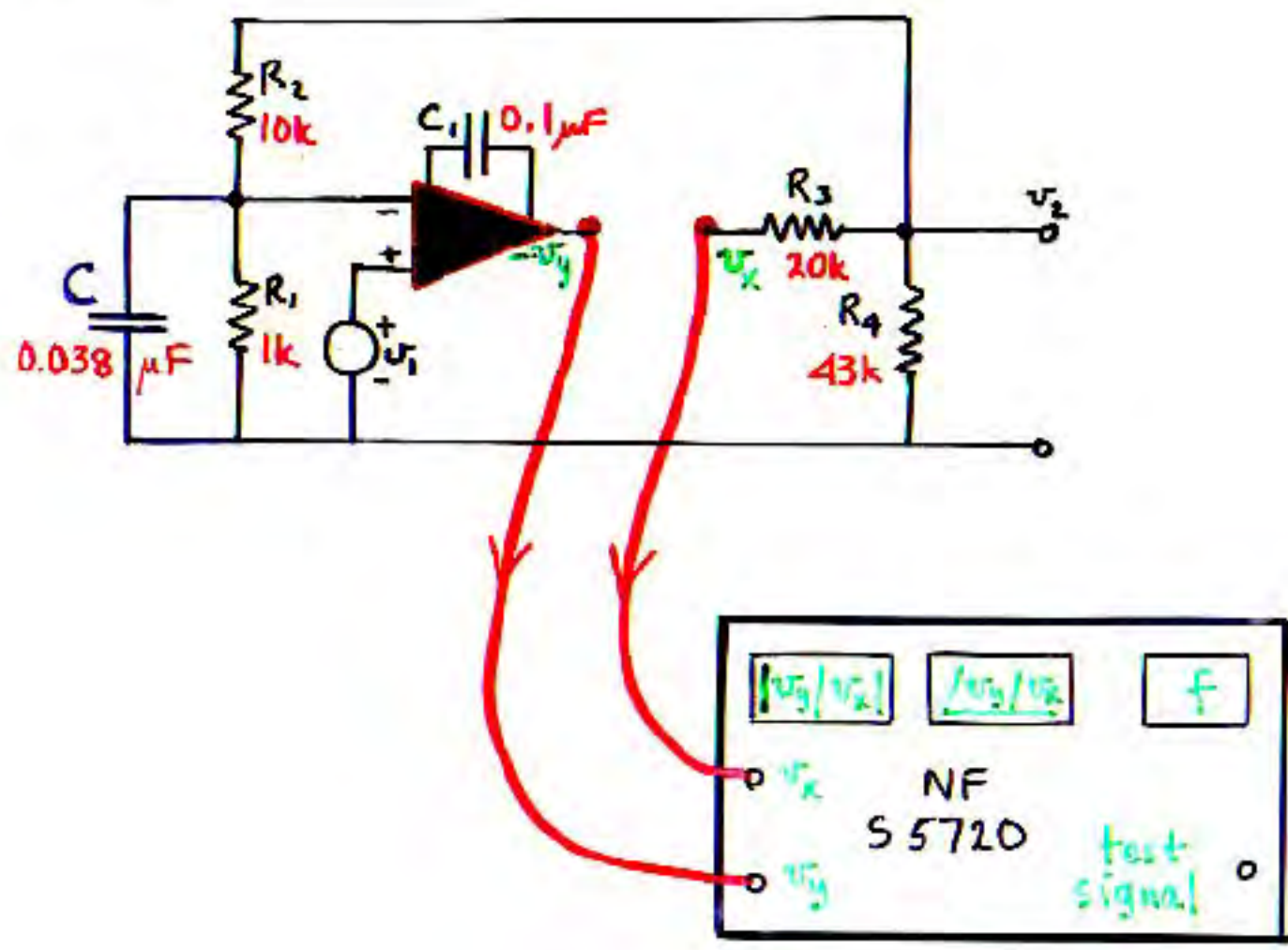





# Example

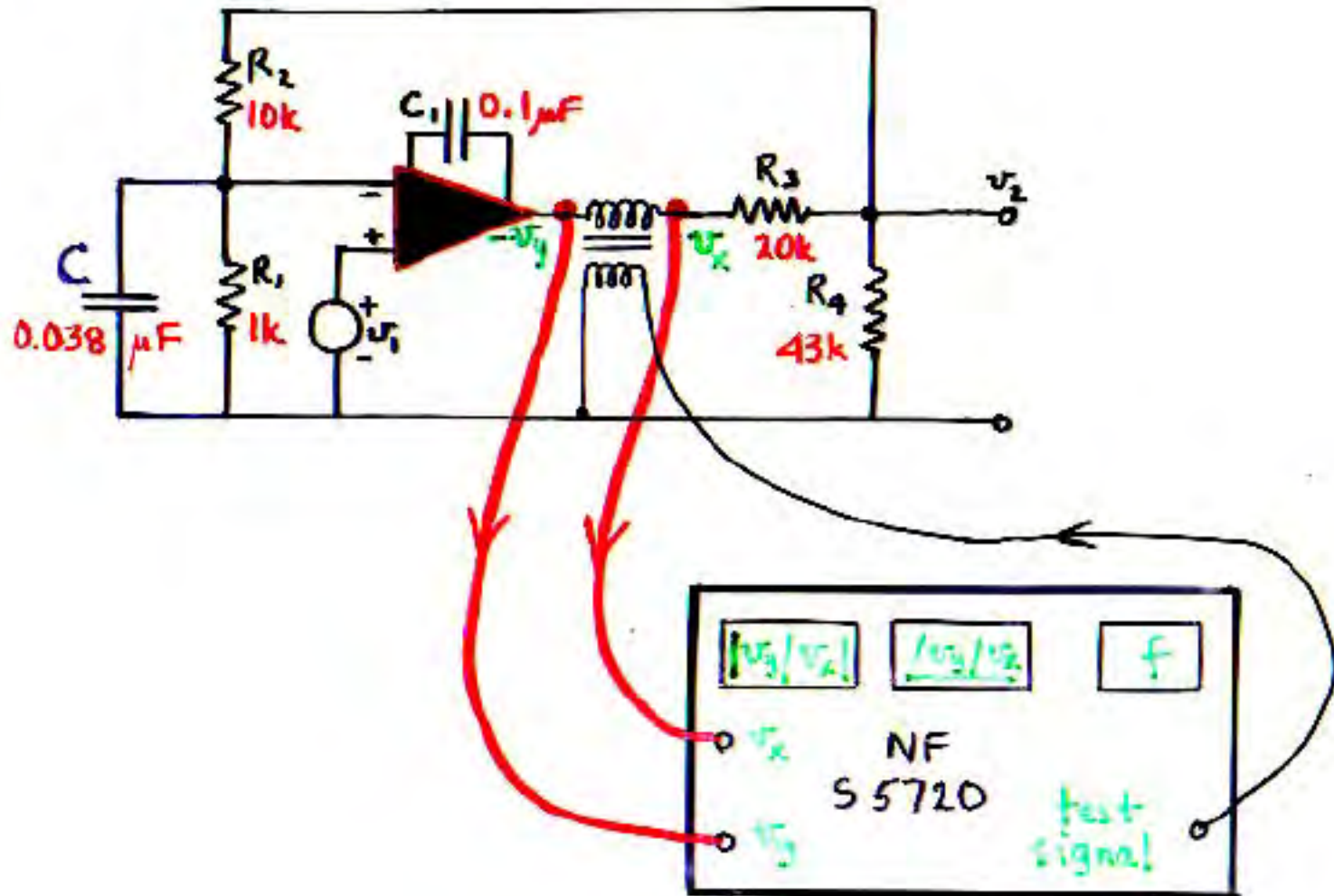


An isolation transformer is needed to couple in the injected signal.


# Example

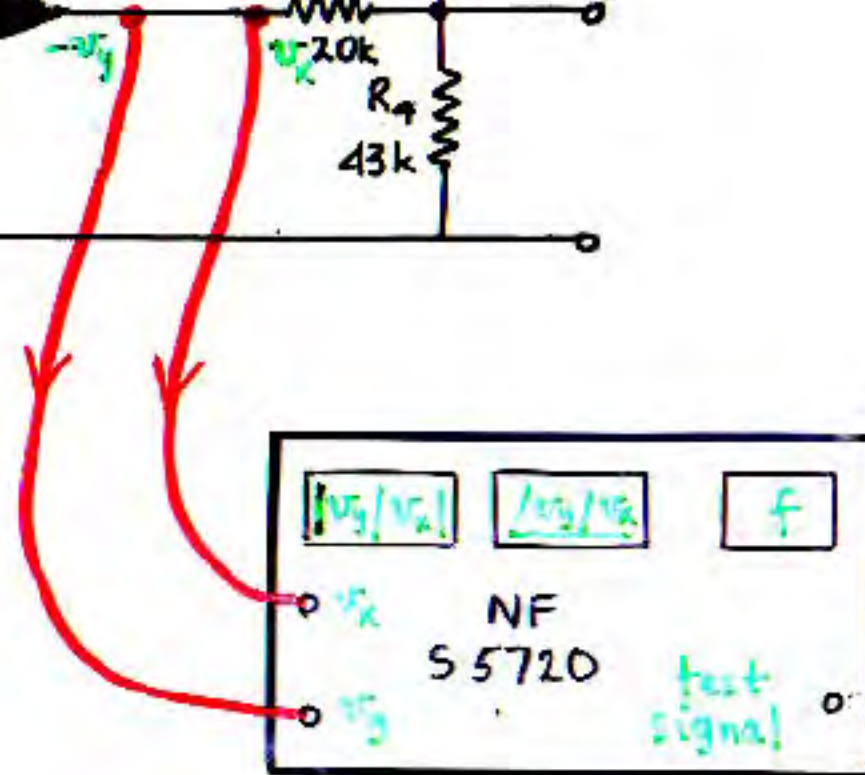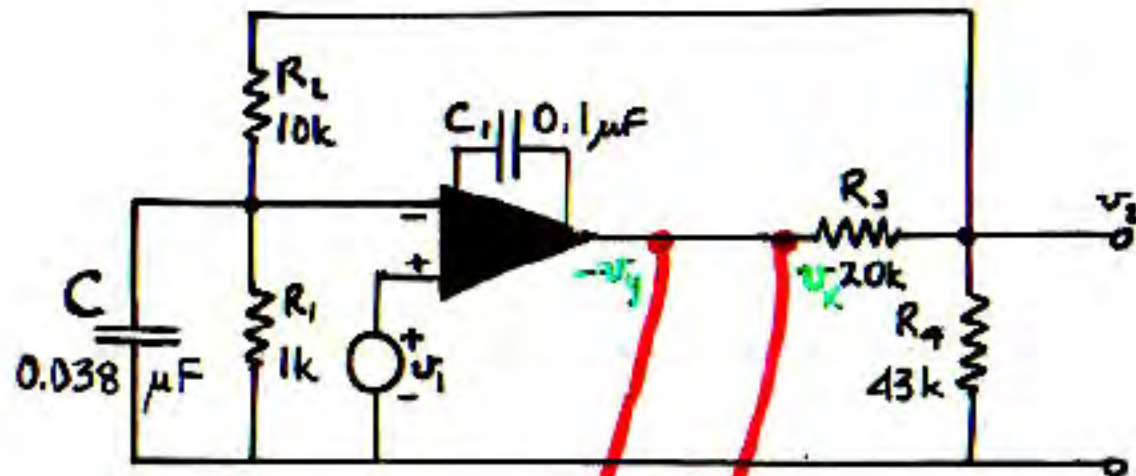



# Example


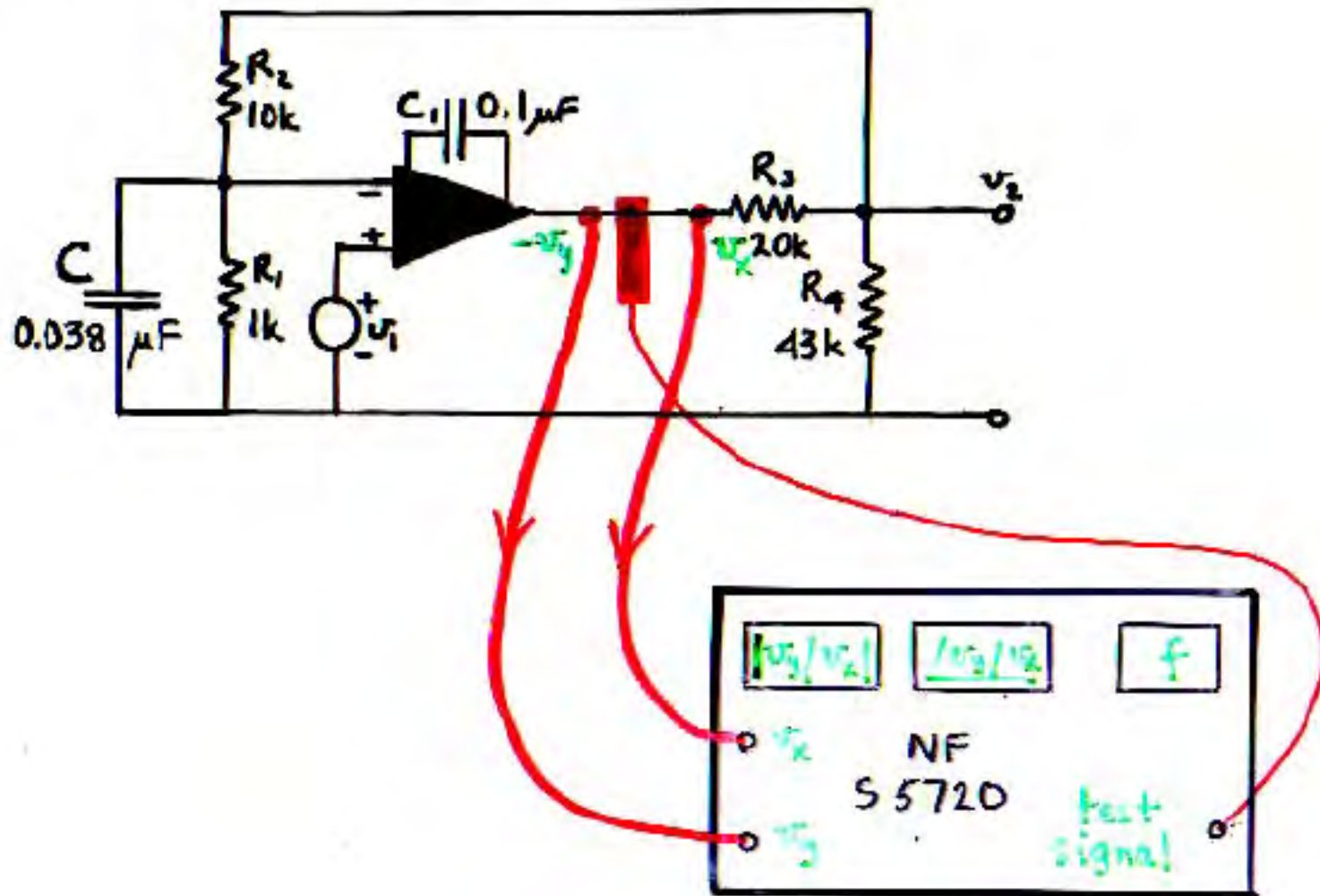



Example

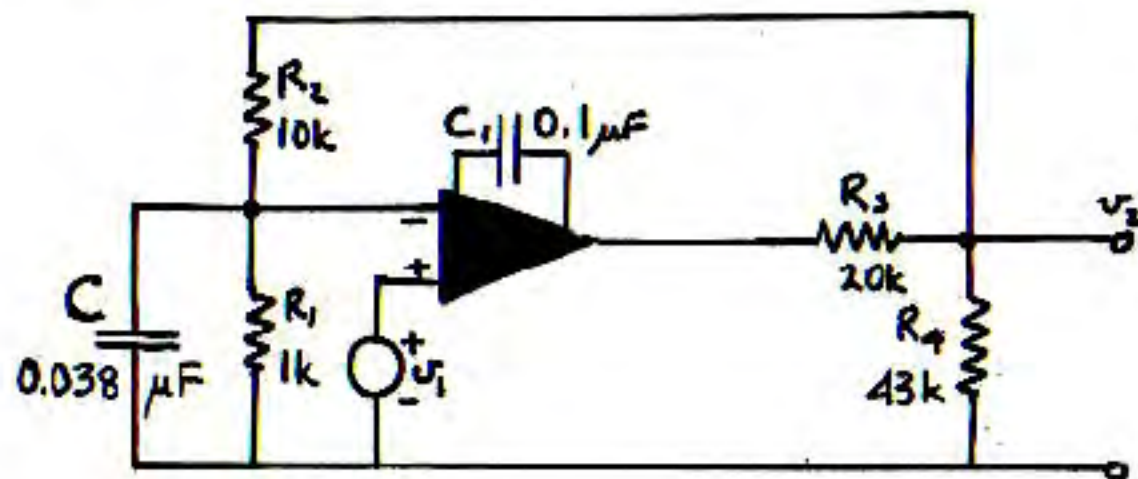



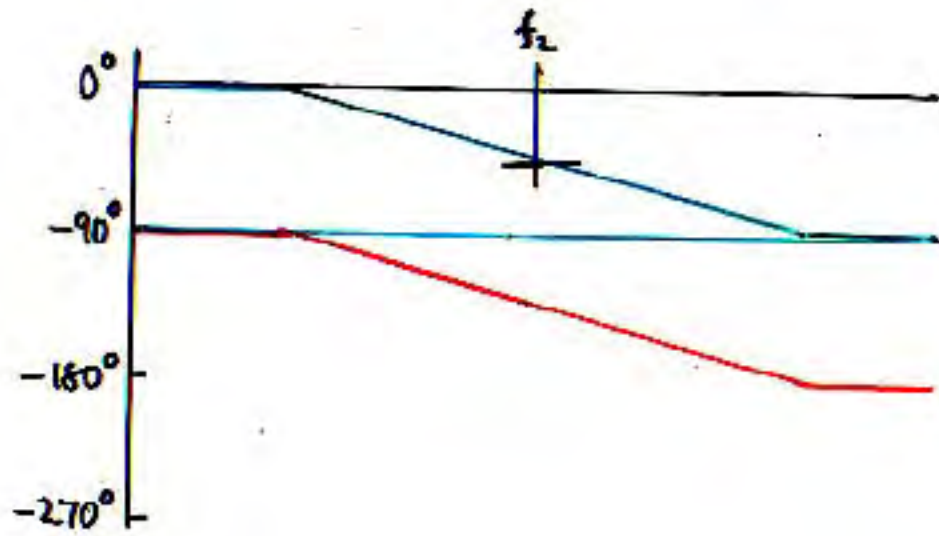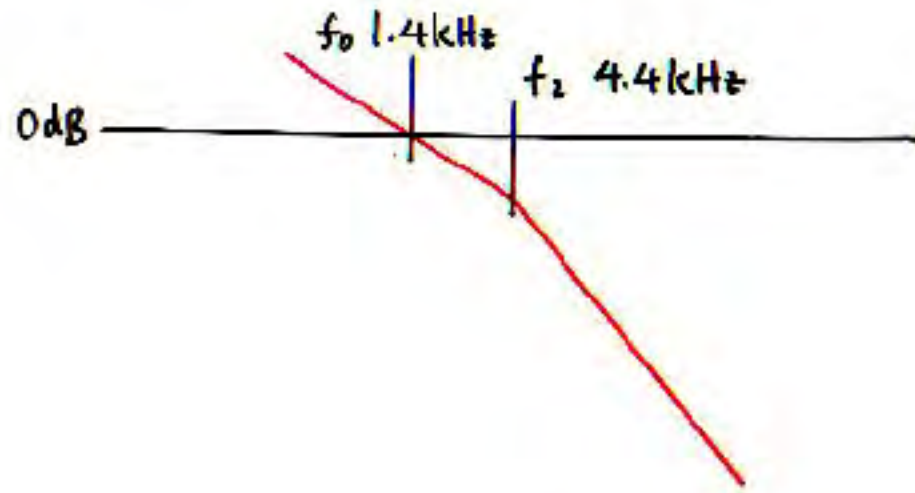

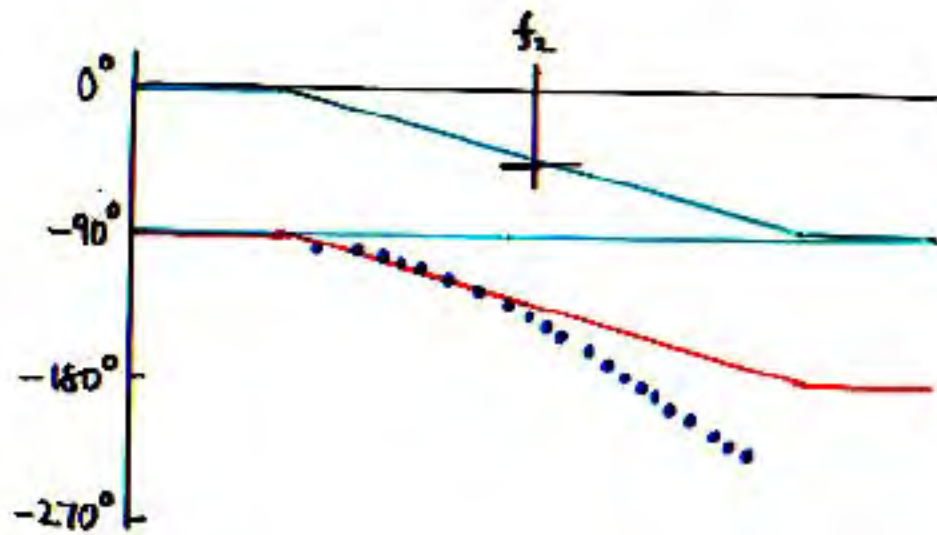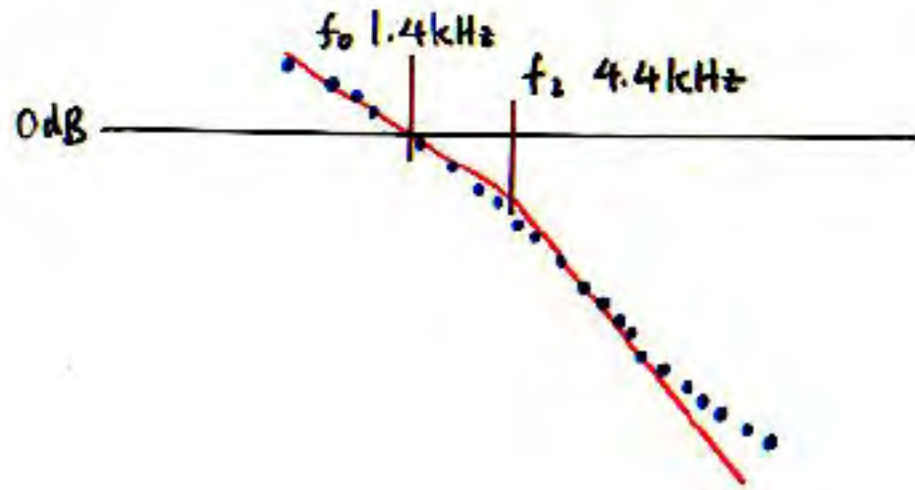

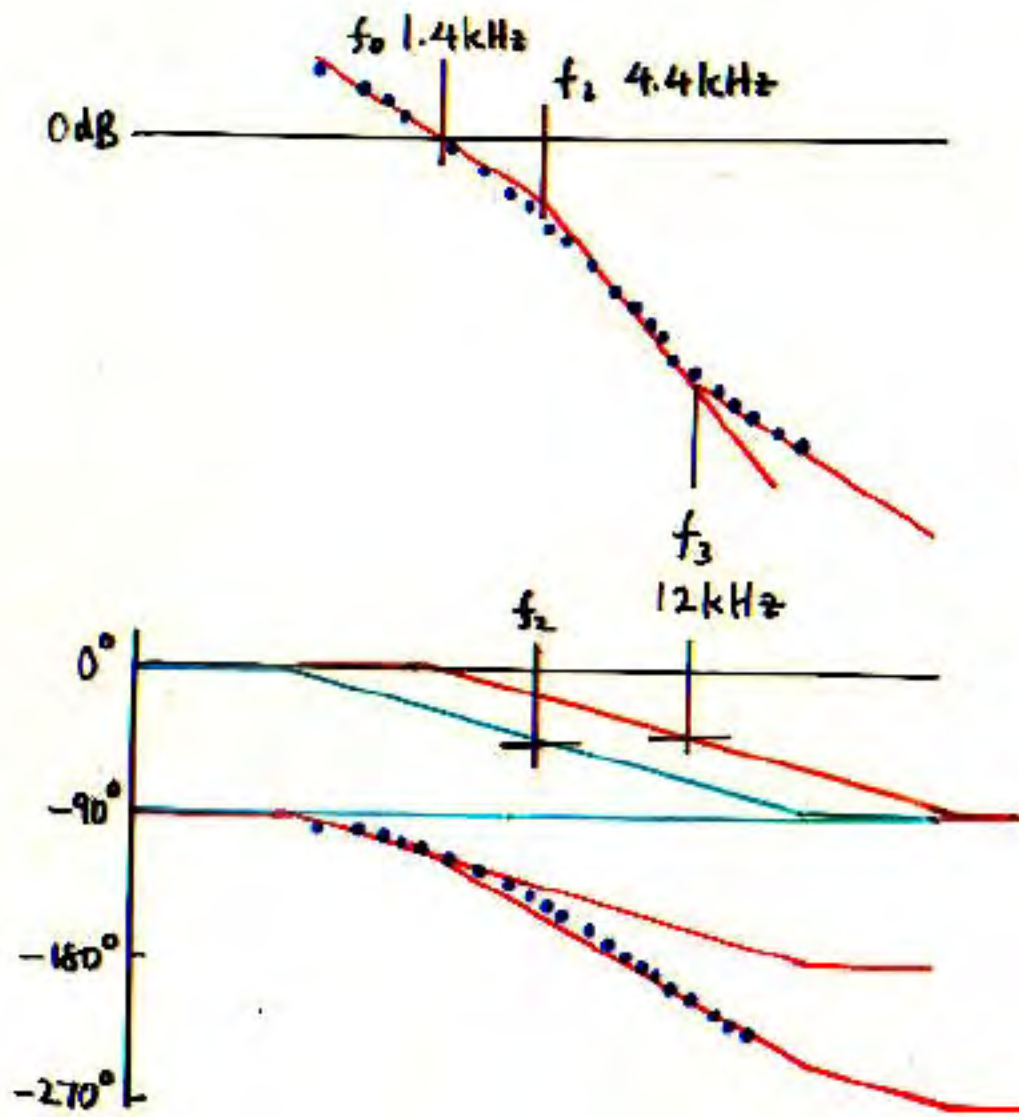

Measurements indicate a right half-plane zero at  $f_3 = 12 \text{ kHz}$ .



Hence the actual loop gain is

$$T = \frac{1 - \frac{s}{\omega_3}}{\frac{s}{\omega_0} \left(1 + \frac{s}{\omega_2}\right)}$$

and the actual phase margin is

$$\phi_M = 73^\circ - \tan^{-1} \frac{\omega_0}{\omega_3} = 73^\circ - 7^\circ = 66^\circ$$

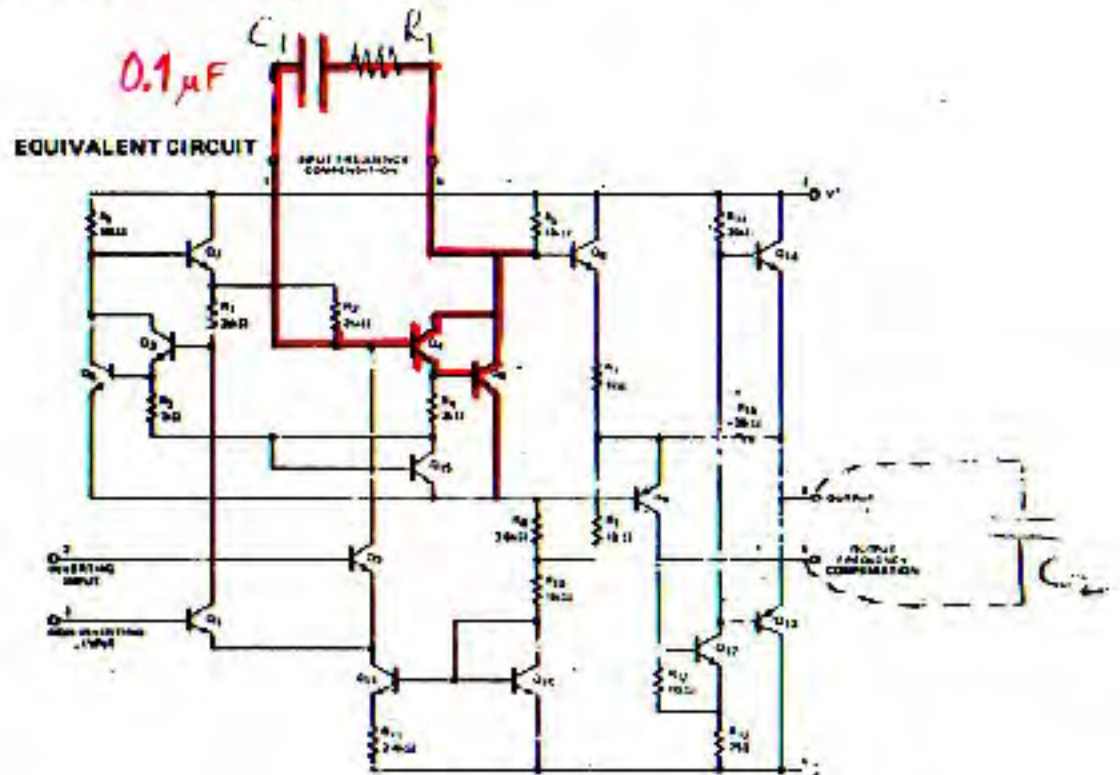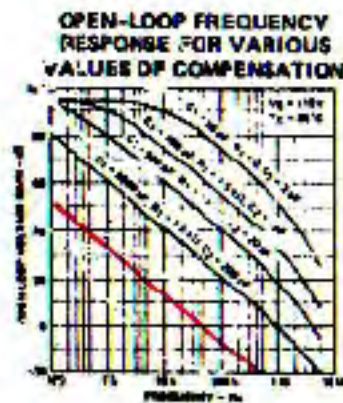In the normal design-analyze-measure sequence, the loop gain  $T$  is first predicted analytically.



With a  $0.005 \mu F$  compensating capacitor  $C_1$ , the gain-bandwidth product is 1 MHz




## Generalization: Implementation of Series Voltage Injection of Loop Gain Test Signal


The necessary floating injection signal can be obtained from a grounded source by "backwards" use of an ac current probe as a "one-turn secondary isolation transformer."

Higher signal injection can be obtained by wrapping more than one secondary turn around the probe.

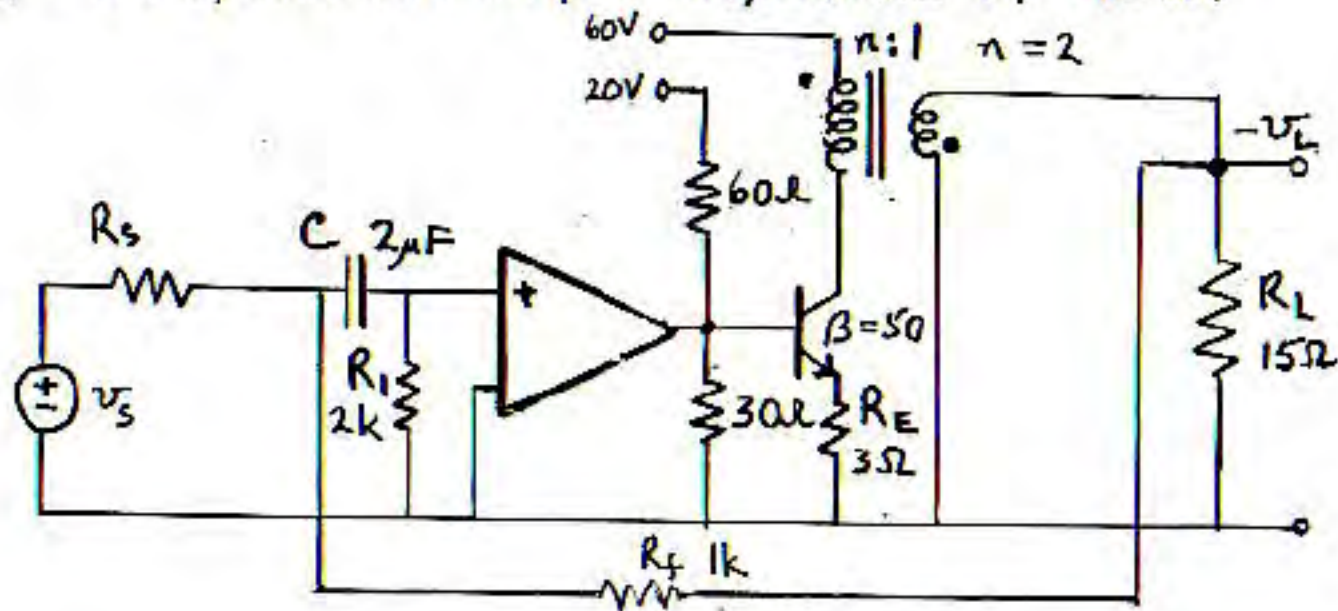Single-ended Class A audio feedback power amplifier, based on the same power stage previously discussed. The driver opamp has a gain  $A_1 = A_{10}/(1+s/\omega_A)$ , where  $A_{10} = 8\text{dB}$  and  $f_A = 2\text{kHz}$ , and an output impedance of  $4.5\Omega$ .



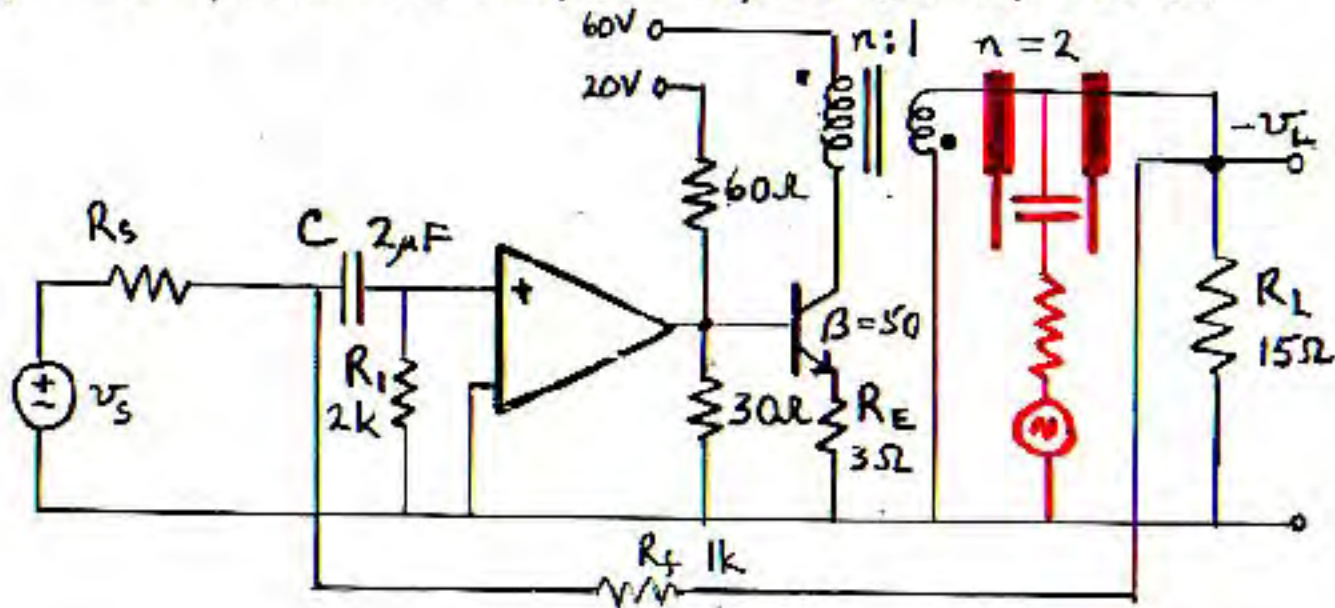Single-ended Class A audio feedback power amplifier, based on the same power stage previously discussed. The driver opamp has a gain  $A_1 = A_{10}/(1+s/\omega_A)$ , where  $A_{10} = 8\text{dB}$  and  $f_A = 2\text{kHz}$ , and an output impedance of  $4.5\Omega$ .



Injection at a non-ideal point:

There are two conditions upon the choice of injection point:

1. Must be inside the feedback loop
2. Injected signal must add to the forward signal without affecting the impedance loading.

What happens if #2 is not satisfied?



Single-ended Class A audio feedback power amplifier, based on the same power stage previously discussed. The driver opamp has a gain  $A_1 = A_{10}/(1+s/\omega_A)$ , where  $A_{10} = 8\text{dB}$  and  $f_A = 2\text{kHz}$ , and an output impedance of  $4.5\Omega$ .

