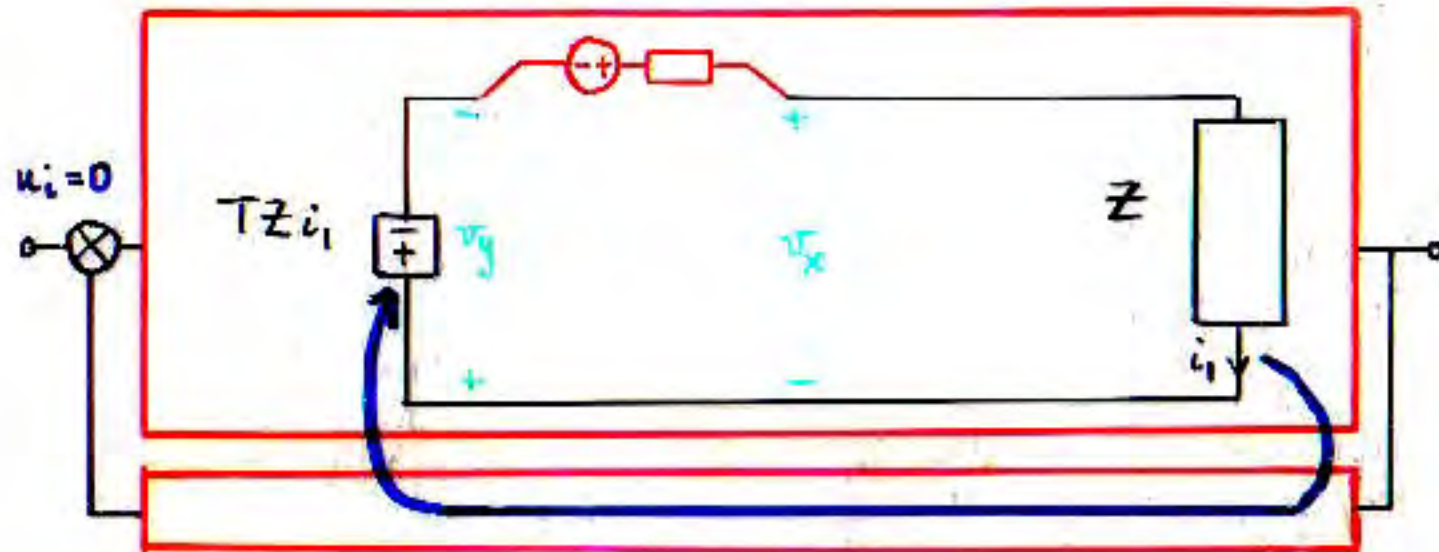


The voltage injection point P is not accessible.

The nearest accessible point is P' .

Consider, in general, voltage injection at a nonideal point. Also, take into account nonzero impedance of the injecting source.






Loop gain by injection of a test signal at an "ideal" point:


$$T_U \equiv \frac{v_y}{v_x} = T$$
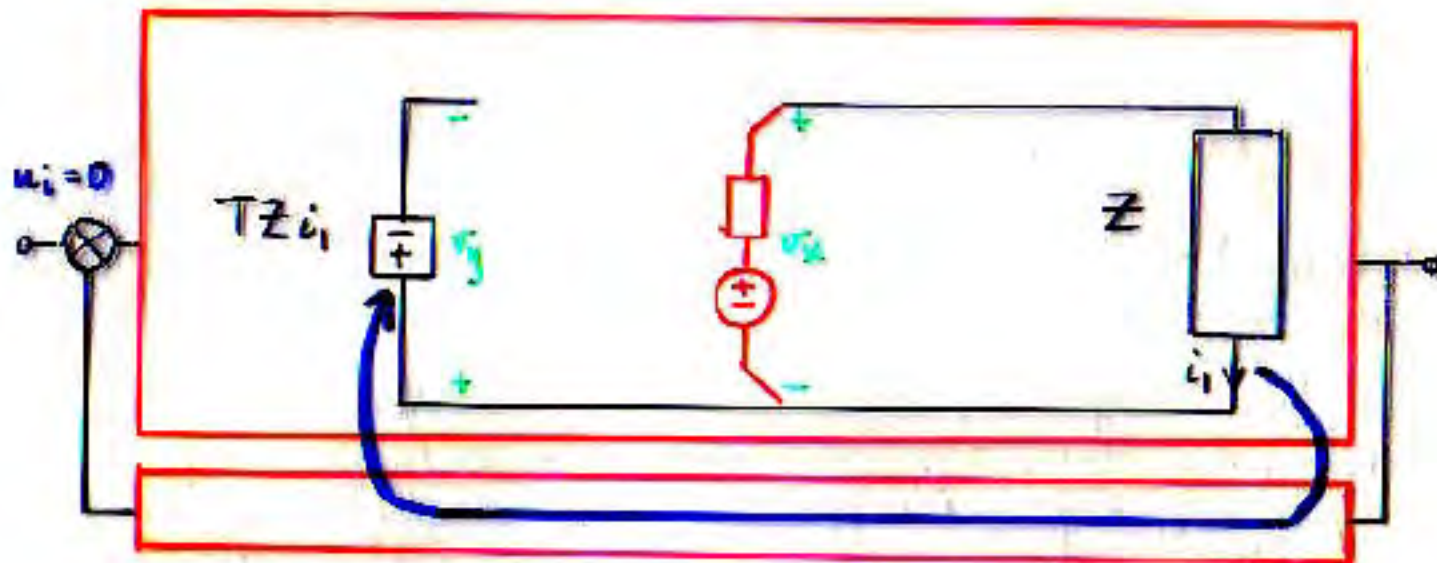
$$\left\{ \begin{array}{l} v_y = Tz i_1 \\ i_1 = \frac{v_x}{Z} \end{array} \right.$$



Loop gain by application of a test signal to the loop broken at an "ideal" point:

$$T_v \equiv \frac{u_y}{u_x} = T$$

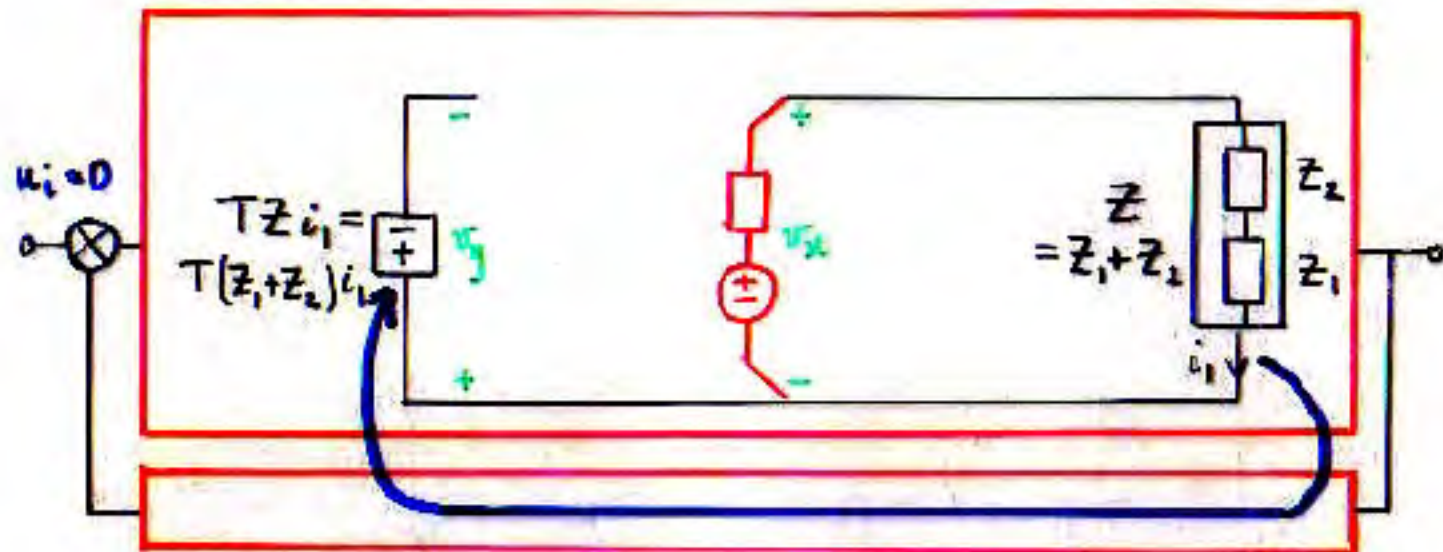


Same results


Loop gain by application of a test signal to the loop broken at an "ideal" point:

$$T_r \equiv \frac{v_y}{v_x} = T$$

Redraw the model:

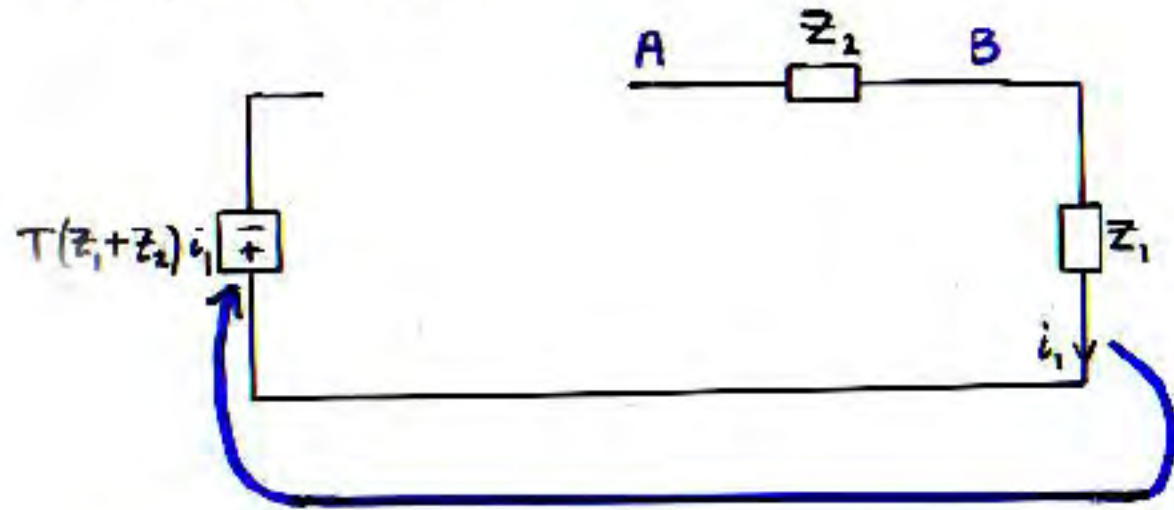


Redraw the model:

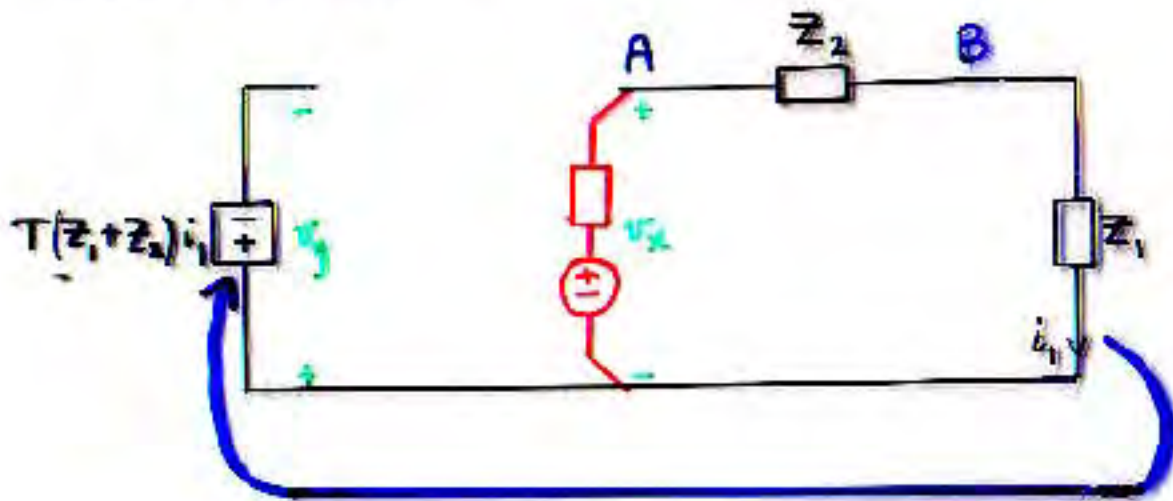

Loop gain by application of a test signal to the loop broken at an "ideal" point:

$$T_v = \frac{v_o}{v_x} = T$$

Redraw the model:

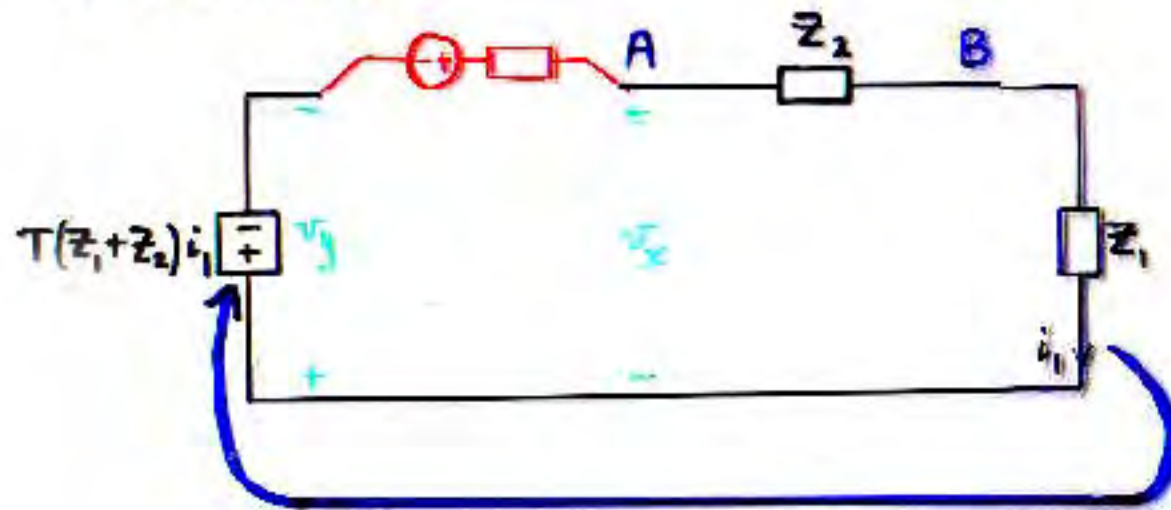


Loop gain by injection of a test signal at an "ideal" point:

$$T_L \equiv \frac{v_1}{v_2} = T$$

$$\left\{ \begin{array}{l} v_1 = T z_2 i_1 \\ i_1 = \frac{v_2}{z_1} \end{array} \right.$$

Redraw the model:

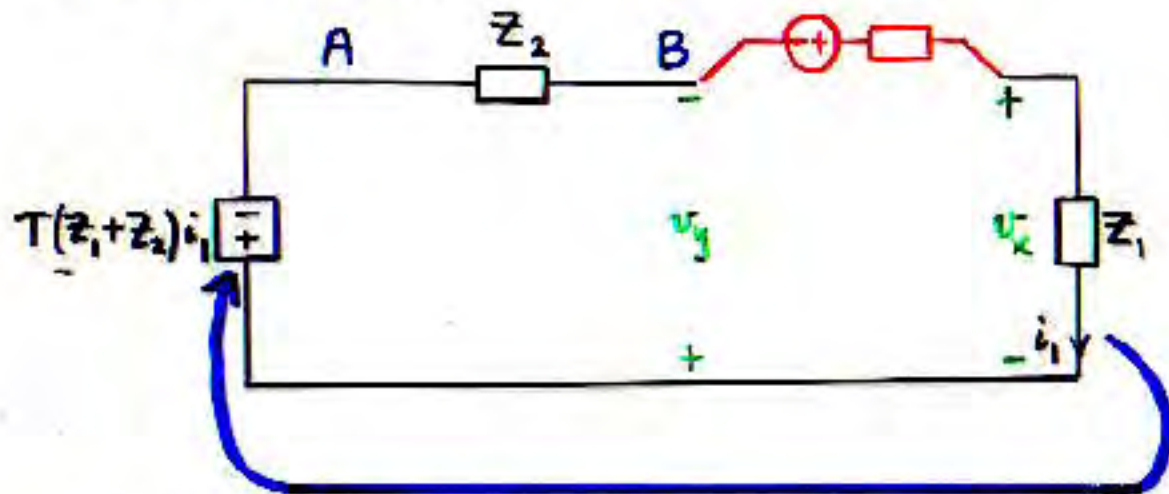


However, results are different if test signal is injected at "nonideal" point B:

$$T_v \equiv \frac{v_y}{v_x} = \left(1 + \frac{z_2}{z_1}\right)T + \frac{z_2}{z_1}$$

$$\left\{ \begin{array}{l} v_y = T(z_1 + z_2)i_1 + z_2 i_1 \\ i_1 = \frac{v_x}{z_1} \end{array} \right.$$

Redraw the model:

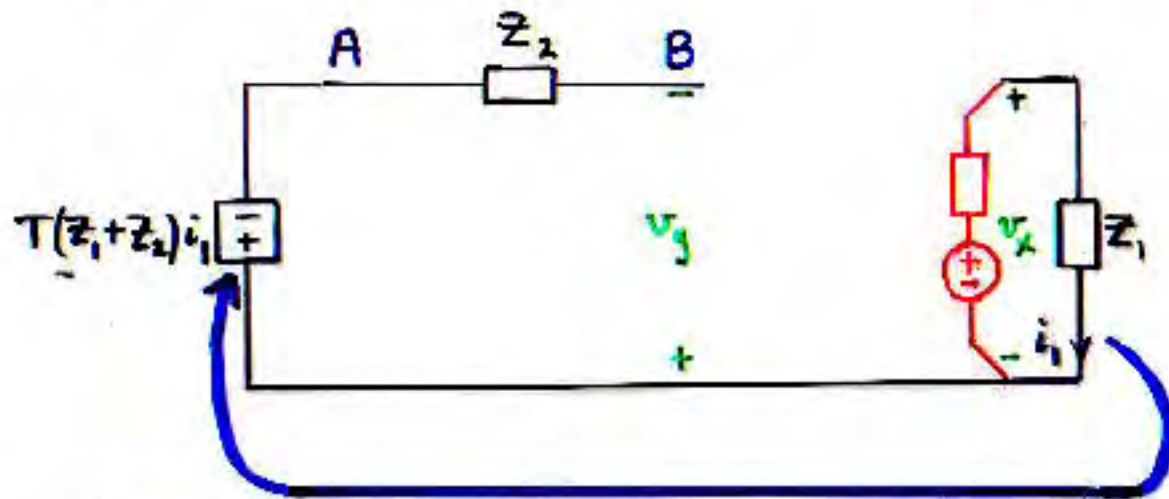


Results are different again if test signal is applied to loop broken at "non ideal" point B:

$$T_v \equiv \frac{v_y}{v_x} = \left(1 + \frac{z_2}{z_1}\right) T$$

$$\left\{ \begin{array}{l} v_y = T(z_1 + z_2)i_1 \\ i_1 = \frac{v_x}{z_1} \end{array} \right.$$

Redraw the model:

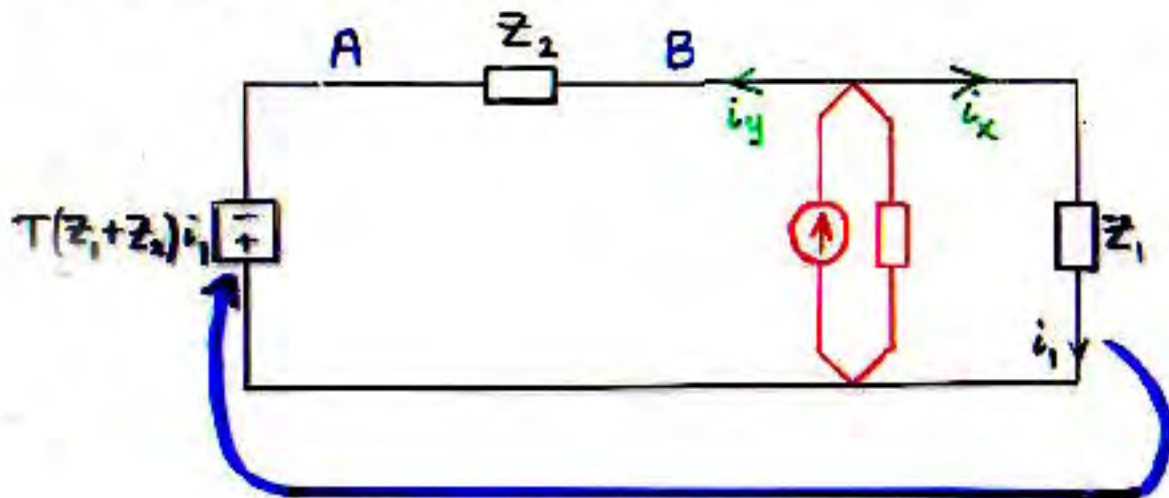


If current test signal is injected at the "nonideal" point B:

$$T_i \equiv \frac{i_y}{i_x} = \left(1 + \frac{z_1}{z_2}\right) T + \frac{z_1}{z_2}$$

$$\left\{ \begin{array}{l} i_y = \frac{T(z_1+z_2)i_1 + z_1 i_1}{z_2} \\ i_1 = i_x \end{array} \right.$$

Redraw the model:

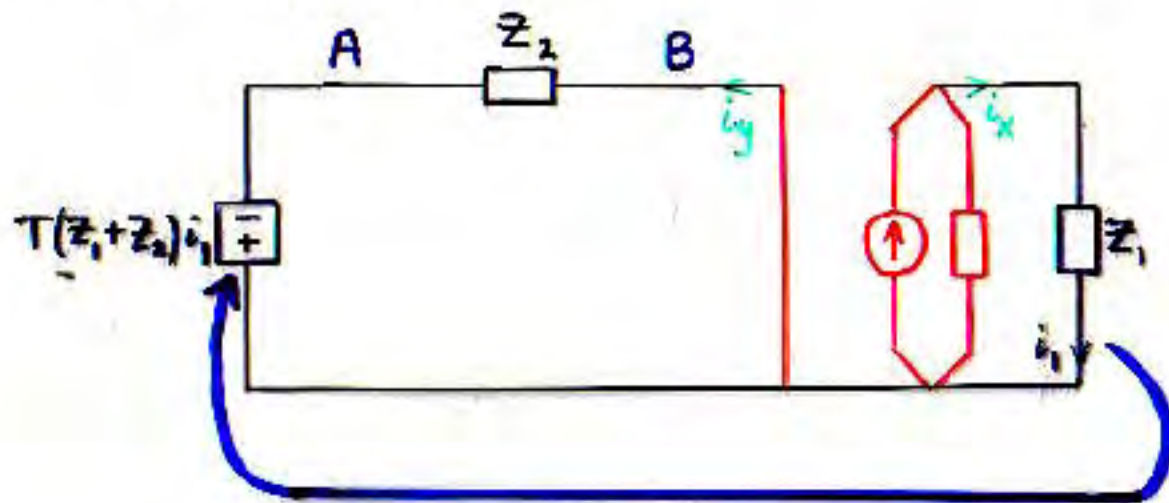

If a current test signal is applied to loop broken (shorted) at the "nonideal" point B:

$$T_i \equiv \frac{i_y}{i_x} = \left(1 + \frac{z_1}{z_2}\right) T \quad \leftarrow \begin{cases} i_y = \frac{T(z_1 + z_2)}{z_2} \\ i_1 = i_x \end{cases}$$

Loop gain T can be calculated or measured by



1. Test signal applied to broken loop
2. Test signal injected into the closed loop.


Method 2 is preferable for measurement, since the loop remains closed and the dc operating points remain undisturbed. If method 1 is used for measurement, a dc bias must be applied to re-establish the proper operating point before the ac test signal can be applied.

In either method, certain inequalities must be satisfied by the impedance ratio Z_2/Z_1 , where

$$\frac{Z_2}{Z_1} = \frac{\text{impedance looking back}}{\text{impedance looking forward}} \left. \vphantom{\frac{Z_2}{Z_1}} \right\} \text{ into the loop from the injection point}$$

$u_i = 0$

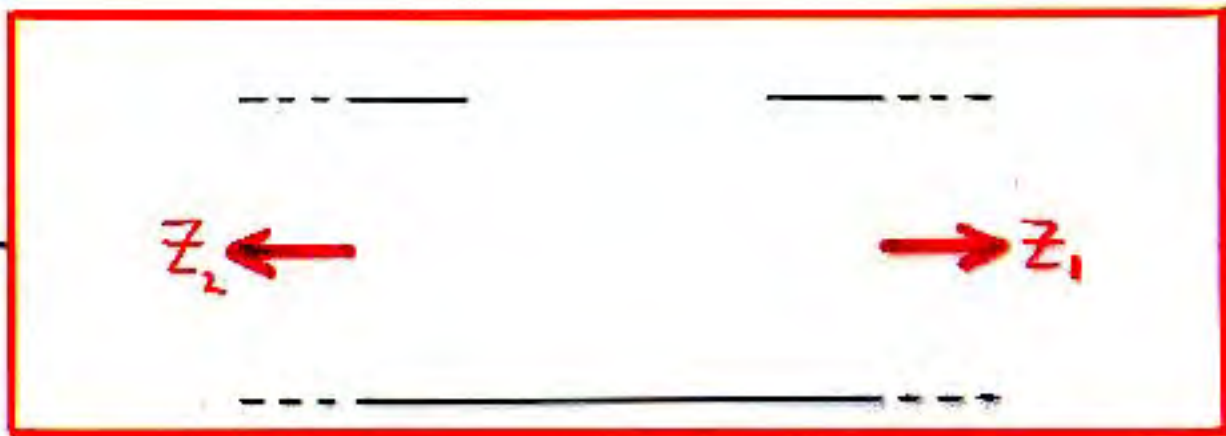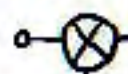


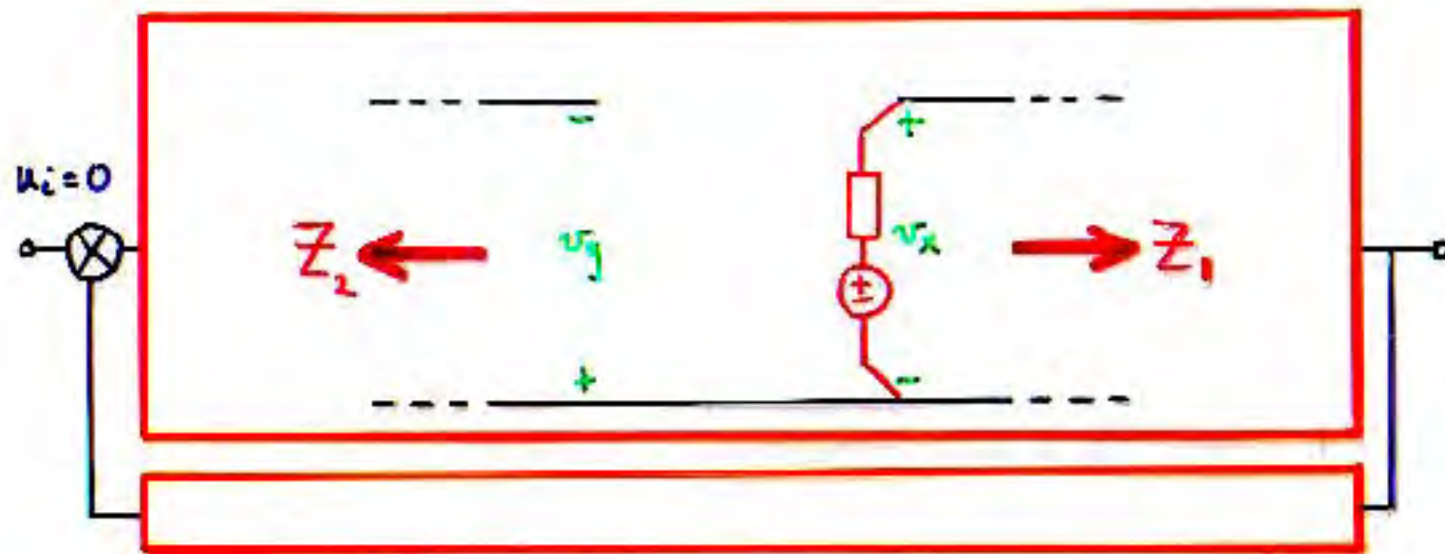

Voltage test signal applied to broken loop:

$$T_v = \frac{V_y}{V_x} = \left(1 + \frac{Z_2}{Z_1}\right) T$$

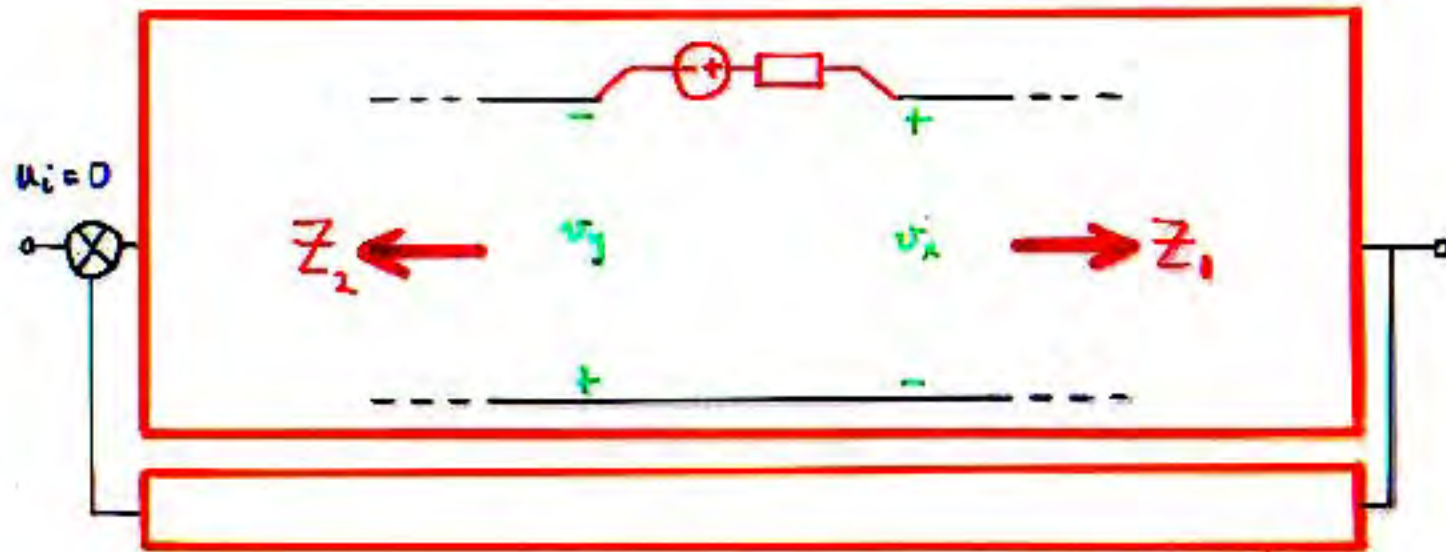
$$\rightarrow T \quad \text{if} \quad \frac{Z_2}{Z_1} \ll 1$$



Voltage test signal injected into closed loop:

$$T_v \equiv \frac{v_y}{v_x} = \left(1 + \frac{Z_2}{Z_1}\right) T + \frac{Z_2}{Z_1}$$

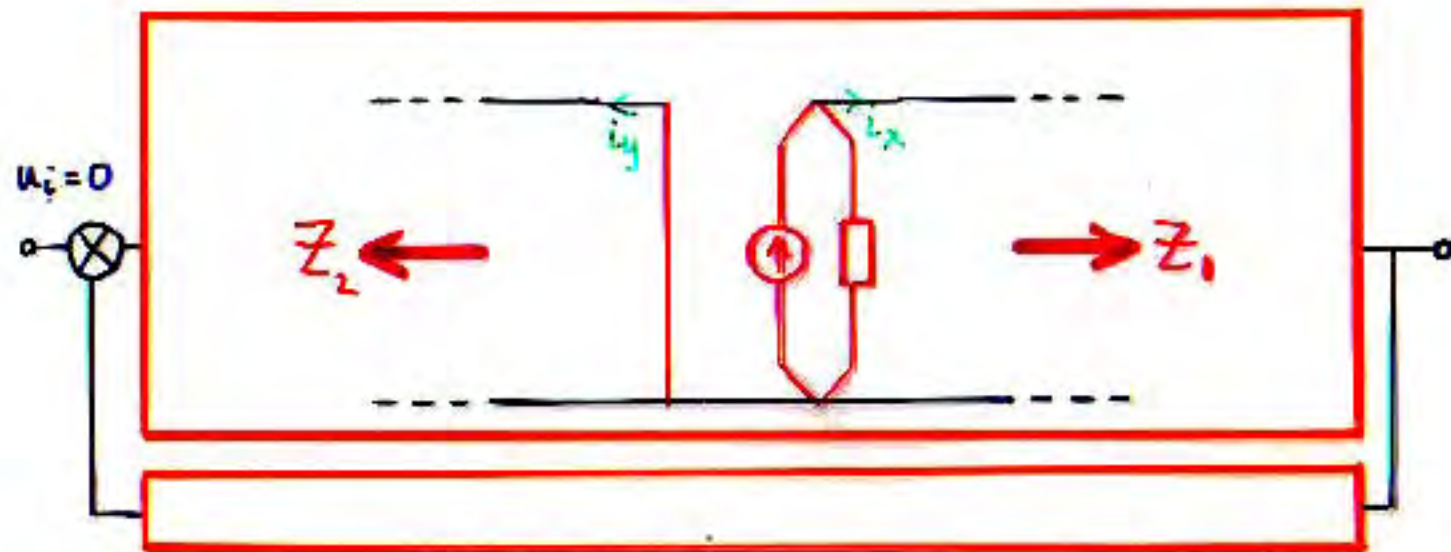
$\rightarrow T$ if $\frac{Z_2}{Z_1} \ll 1$ and $\frac{Z_2}{Z_1} \ll T$



Current test signal applied to broken loop:

$$T_i \equiv \frac{i_y}{i_x} = \left(1 + \frac{Z_1}{Z_2}\right) T$$
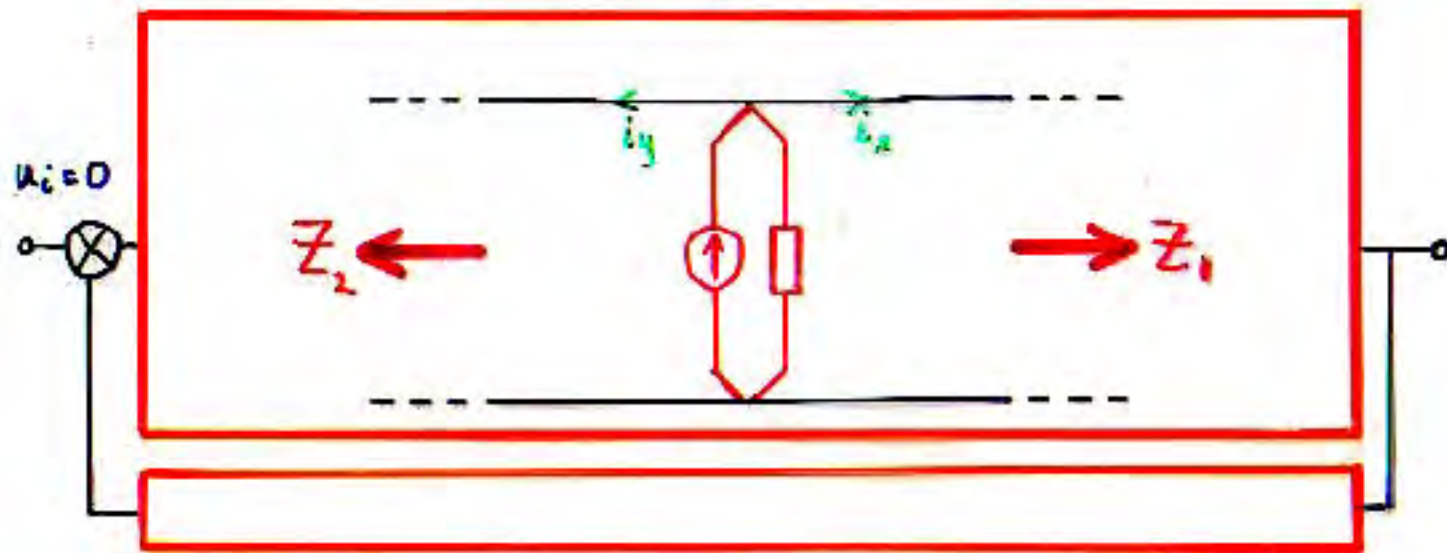
$$\Rightarrow T \quad \text{if} \quad \frac{Z_1}{Z_2} \ll 1$$



Current test signal injected into closed loop:

$$T_i \equiv \frac{i_y}{i_x} = \left(1 + \frac{Z_1}{Z_2}\right) T + \frac{Z_1}{Z_2}$$

$$\rightarrow T \quad \text{if} \quad \frac{Z_1}{Z_2} \ll 1 \quad \text{and} \quad \frac{Z_1}{Z_2} \ll T$$

Generalization: Determination of loop gain by voltage/current application/injection at an ideal/nonideal point

$$Z\text{-ratio} \equiv \begin{cases} \frac{Z_2}{Z_1} & \text{for voltage application/injection} \\ \frac{Z_1}{Z_2} & \text{for current application/injection} \end{cases}$$

where $Z_1 \equiv$ impedance looking forward from application/injection point
 $Z_2 \equiv$ " " backward " " " " " "


To determine loop gain, both by signal application to a broken loop and by signal injection into a closed loop, the Z-ratio must be sufficiently small; the necessary inequalities are different:

For signal application to a broken loop: Z-ratio $\ll 1$


For signal injection into a closed loop: Z-ratio $\ll 1$ and $\ll T$

The impedance of the signal source is irrelevant in all cases.


Example

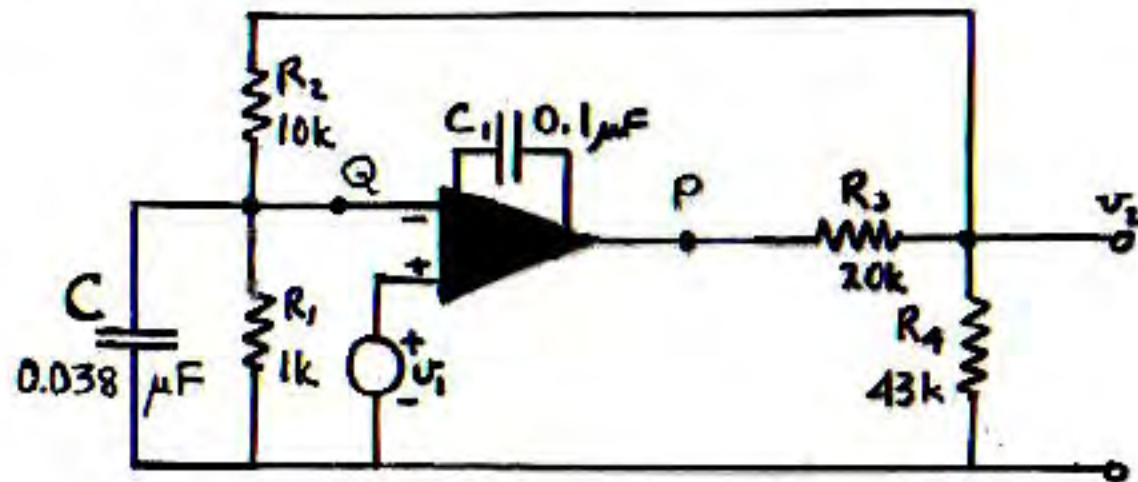

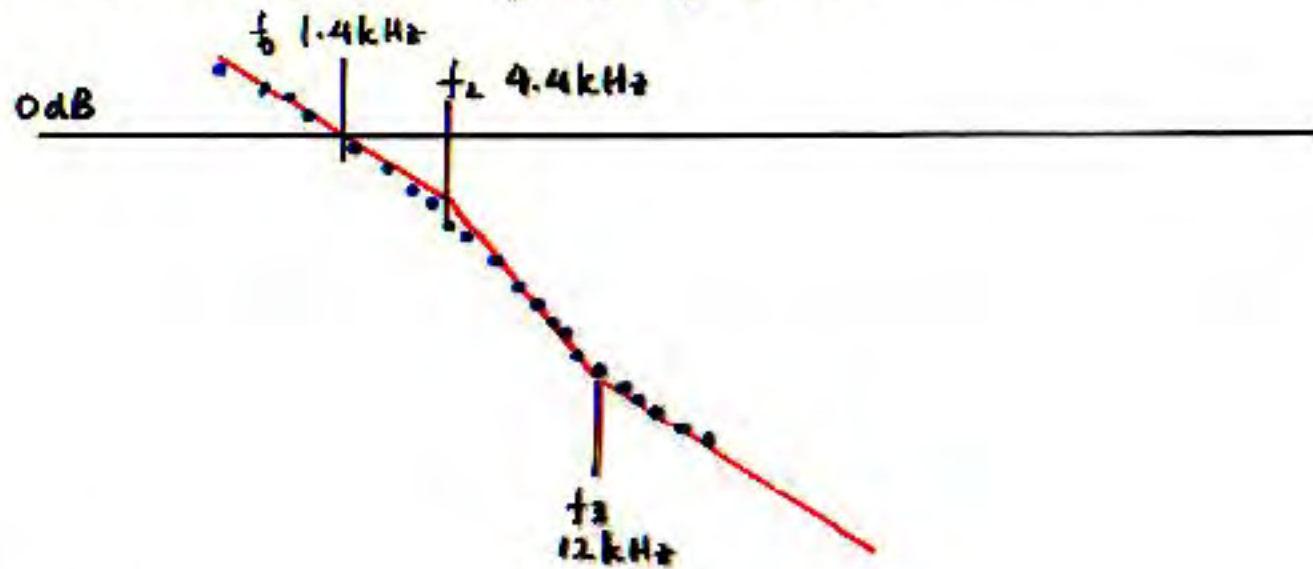
Example of T_v not being equal to T : the previous opamp circuit at high frequencies.




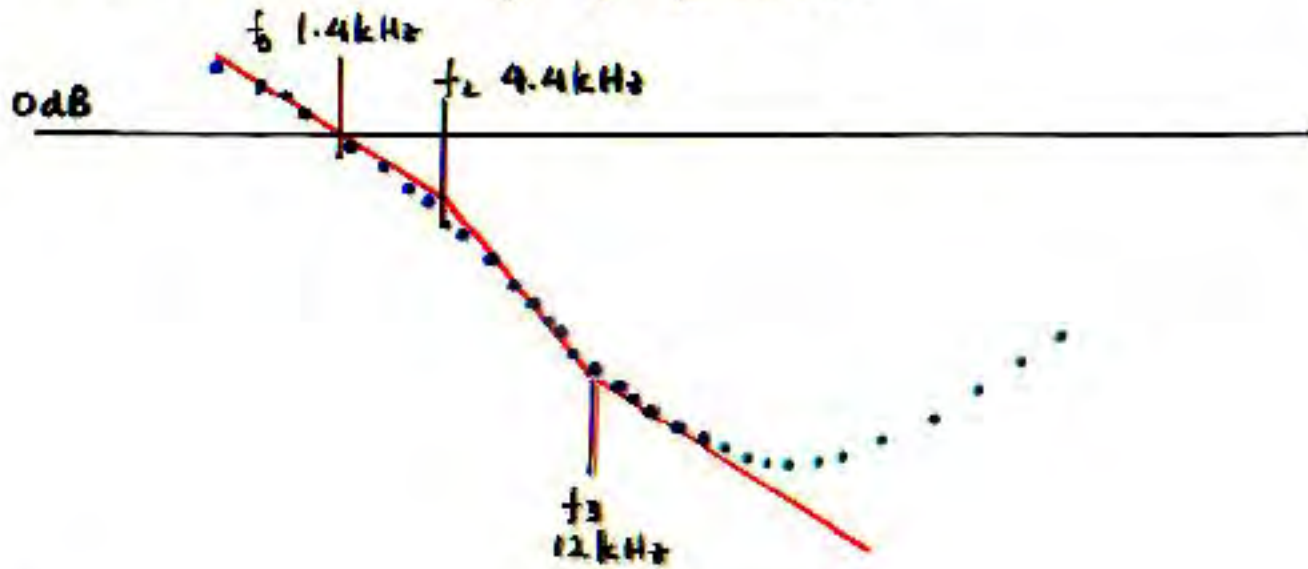Example of T_v not being equal to T : the previous opamp circuit at high frequencies.



Example

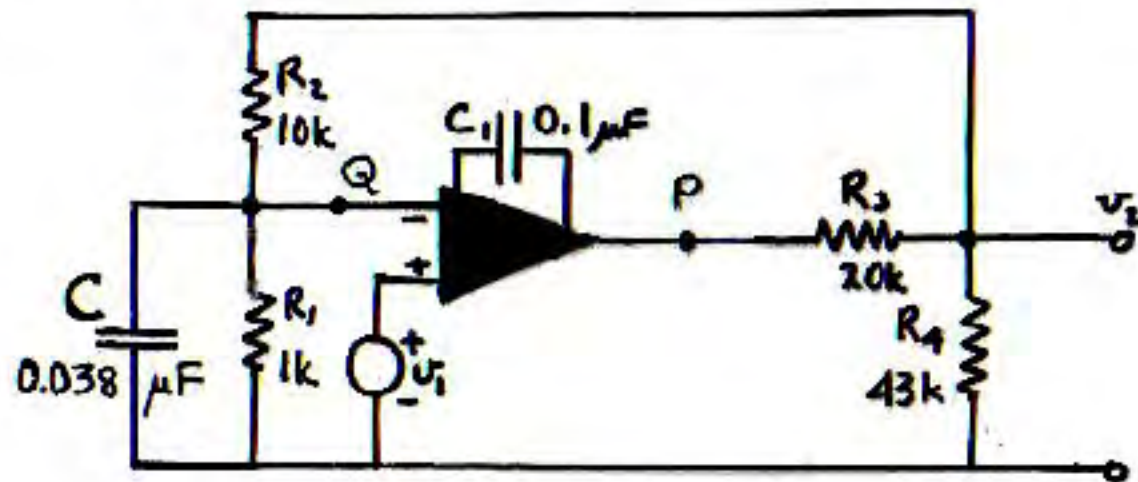

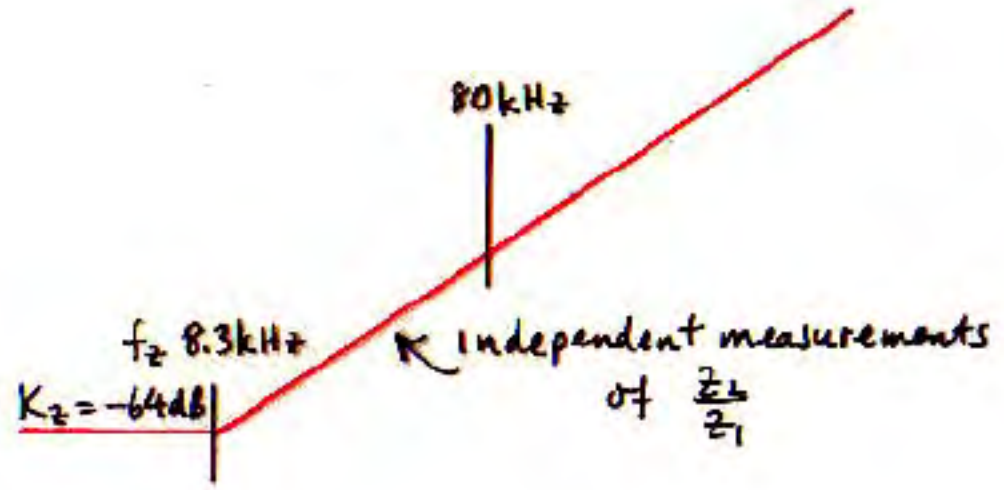

Analytically:


$$\begin{aligned}T_v &= \left(1 + \frac{z_2}{z_1}\right)T + \frac{z_2}{z_1} \approx T + \frac{z_2}{z_1} \\ &= \frac{1 - \frac{s}{\omega_3}}{\frac{s}{\omega_0} \left(1 + \frac{s}{\omega_2}\right)} + K_z \left(1 + \frac{s}{\omega_z}\right)\end{aligned}$$

In the neighborhood of the crossover:

$$\begin{aligned}T_v &= \frac{-\frac{s}{\omega_3}}{\frac{s}{\omega_0} \cdot \frac{s}{\omega_2}} + K_z \frac{s}{\omega_z} \\ &= \frac{-\frac{s}{\omega_3} \left[1 - \left(\frac{s}{\omega_c}\right)^2\right]}{\frac{s}{\omega_0} \cdot \frac{s}{\omega_2}}\end{aligned}$$

where
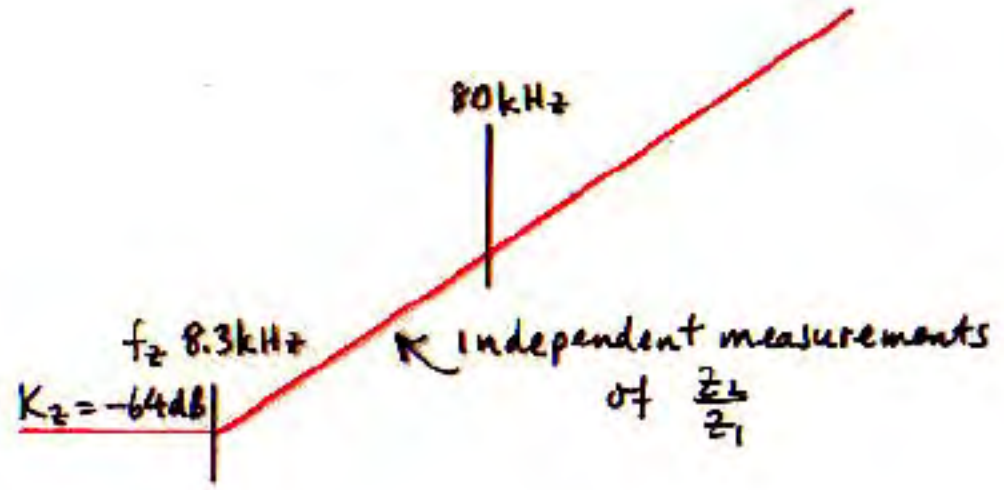
$$\omega_c \equiv \sqrt{\frac{\omega_0 \omega_2 \omega_z}{K_z \omega_3}} \quad f_c = 81 \text{ kHz}$$



Analytically:

$$\begin{aligned}T_v &= \left(1 + \frac{z_2}{z_1}\right)T + \frac{z_2}{z_1} \approx T + \frac{z_2}{z_1} \\ &= \frac{1 - \frac{s}{\omega_3}}{\frac{s}{\omega_0} \left(1 + \frac{s}{\omega_2}\right)} + K_z \left(1 + \frac{s}{\omega_2}\right)\end{aligned}$$

In the neighborhood of the crossover:

$$\begin{aligned}T_v &= \frac{-\frac{s}{\omega_3}}{\frac{s}{\omega_0} \cdot \frac{s}{\omega_2}} + K_z \frac{s}{\omega_2} \\ &= \frac{-\frac{s}{\omega_3} \left[1 - \left(\frac{s}{\omega_c}\right)^2\right]}{\frac{s}{\omega_0} \cdot \frac{s}{\omega_2}}\end{aligned}$$

where

$$\omega_c \equiv \sqrt{\frac{\omega_0 \omega_2 \omega_z}{K_z \omega_3}} \quad f_c = 81 \text{ kHz}$$

Example of T_v not being equal to T : the previous opamp circuit at high frequencies.

