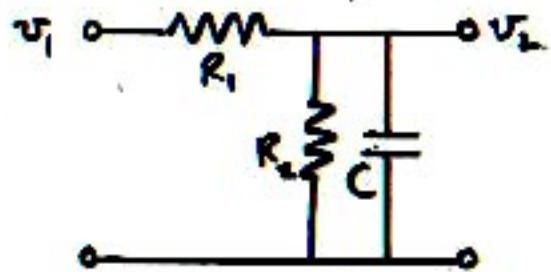


# 3

## **NORMAL AND INVERTED POLES AND ZEROS**


"Flat gain"




The hard way:

$$\frac{v_o}{v_i} = \frac{R_2 \parallel \frac{1}{sC}}{R_1 + R_2 \parallel \frac{1}{sC}} = \frac{\frac{R_2}{1+sCR_2}}{R_1 + \frac{R_2}{1+sCR_2}}$$
$$= \frac{R_2}{R_1 + R_2 + sCR_1R_2}$$
$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}$$

"Flat gain"

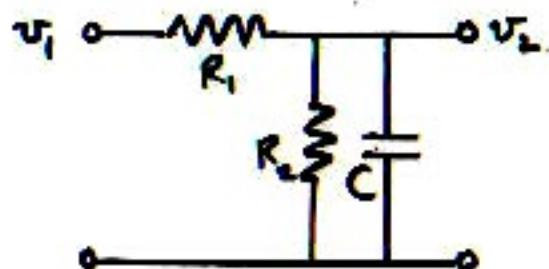

The easy way:

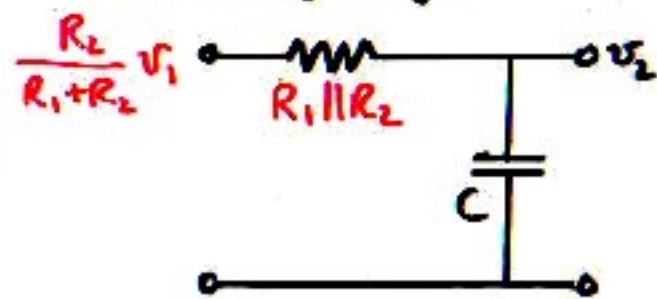

The hard way:


$$\frac{v_2}{v_1} = \frac{R_2 \parallel \frac{1}{sC}}{R_1 + R_2 \parallel \frac{1}{sC}} = \frac{\frac{R_2}{1+sCR_2}}{R_1 + \frac{R_2}{1+sCR_2}}$$

$$= \frac{R_2}{R_1 + R_2 + sCR_1R_2}$$


$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}$$

$$\frac{v_2}{v_1} = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}$$

"Flat gain"

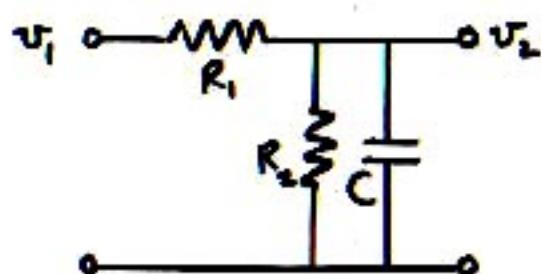

The easy way:

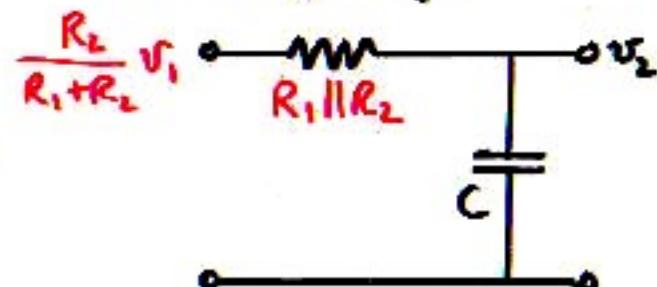

The hard way:

$$\frac{v_2}{v_1} = \frac{R_2 \parallel \frac{1}{sC}}{R_1 + R_2 \parallel \frac{1}{sC}} = \frac{\frac{R_2}{1+sCR_2}}{R_1 + \frac{R_2}{1+sCR_2}}$$

$$= \frac{R_2}{R_1 + R_2 + sCR_1R_2}$$

$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}$$

$$\frac{v_2}{v_1} = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}$$


Result:

$$\frac{v_2}{v_1} \equiv A = A_1 \frac{1}{1 + \frac{s}{\omega_1}} \quad \text{where} \quad A_1 \equiv \frac{R_2}{R_1 + R_2} \quad \omega_1 \equiv \frac{1}{C(R_1 \parallel R_2)}$$

Single-pole response:

$$A = A_1 \frac{1}{1 + \frac{s}{\omega_1}}$$


flat gain  $\nearrow$  normal pole

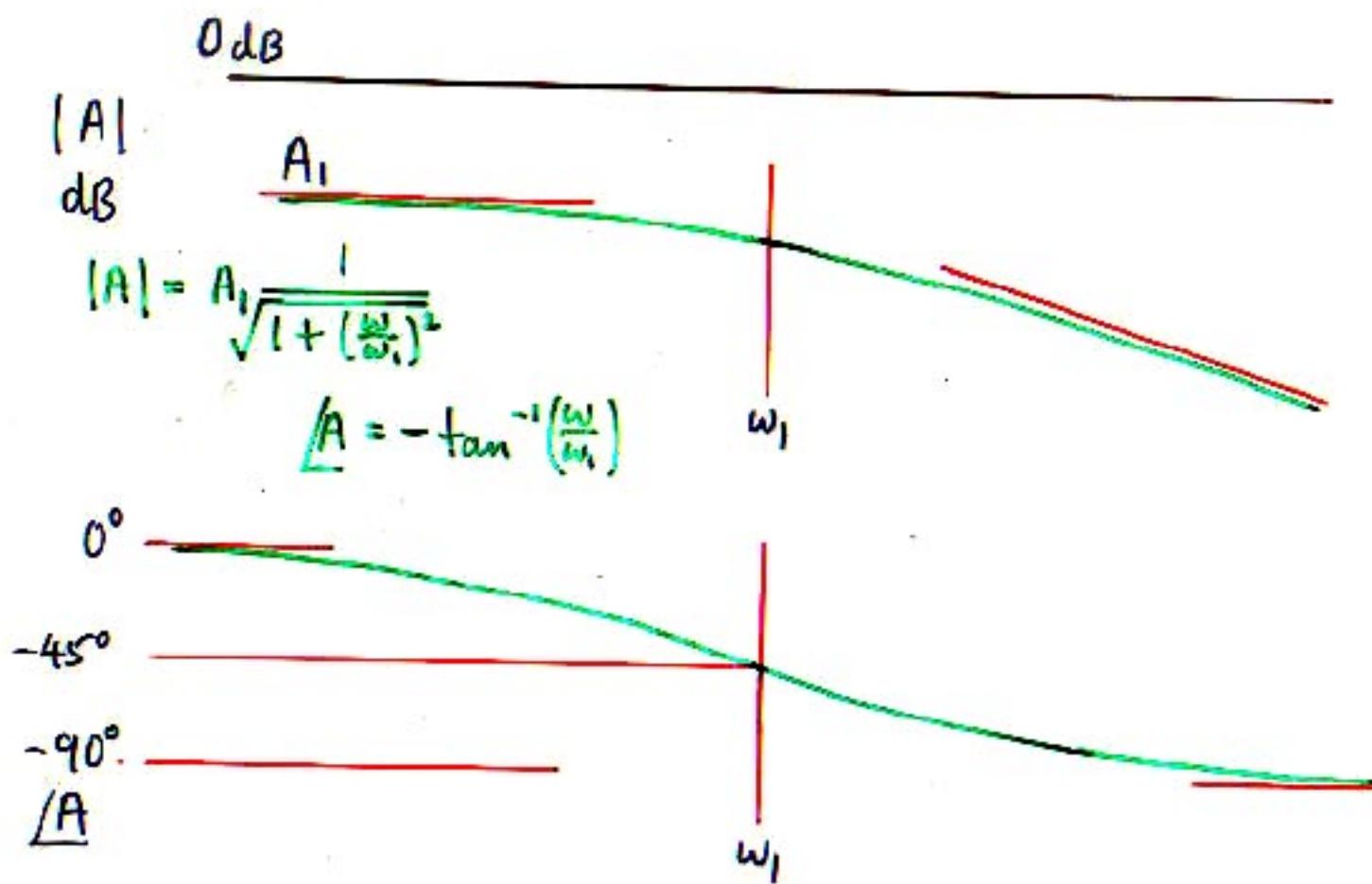

Single-pole response:

$$A = A_1 \frac{1}{1 + \frac{s}{\omega_1}}$$


flat gain  $\nearrow$  normal pole

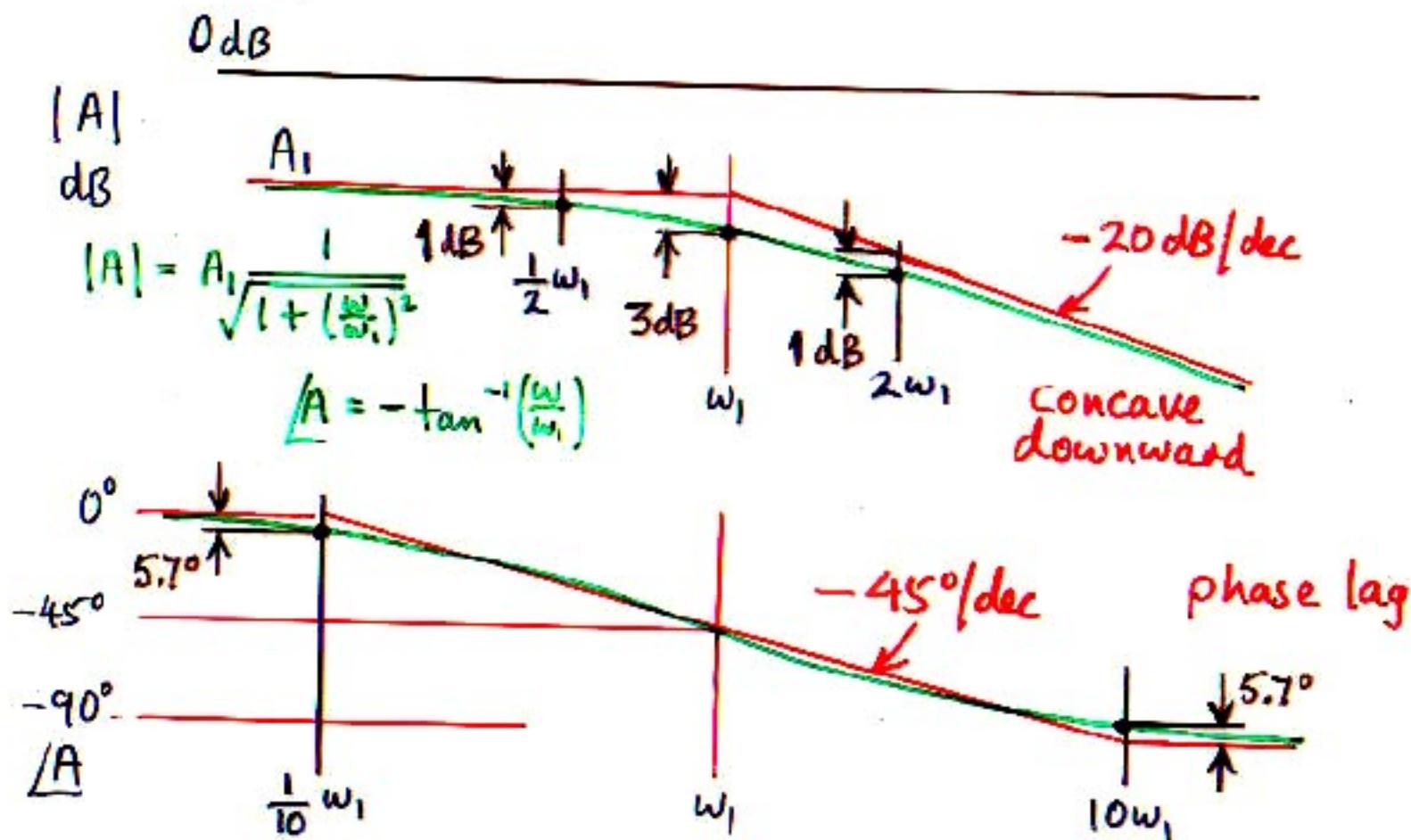

Single-pole response:

$$A = A_1 \frac{1}{1 + \frac{s}{\omega_1}}$$


flat gain  $\nearrow$  normal pole

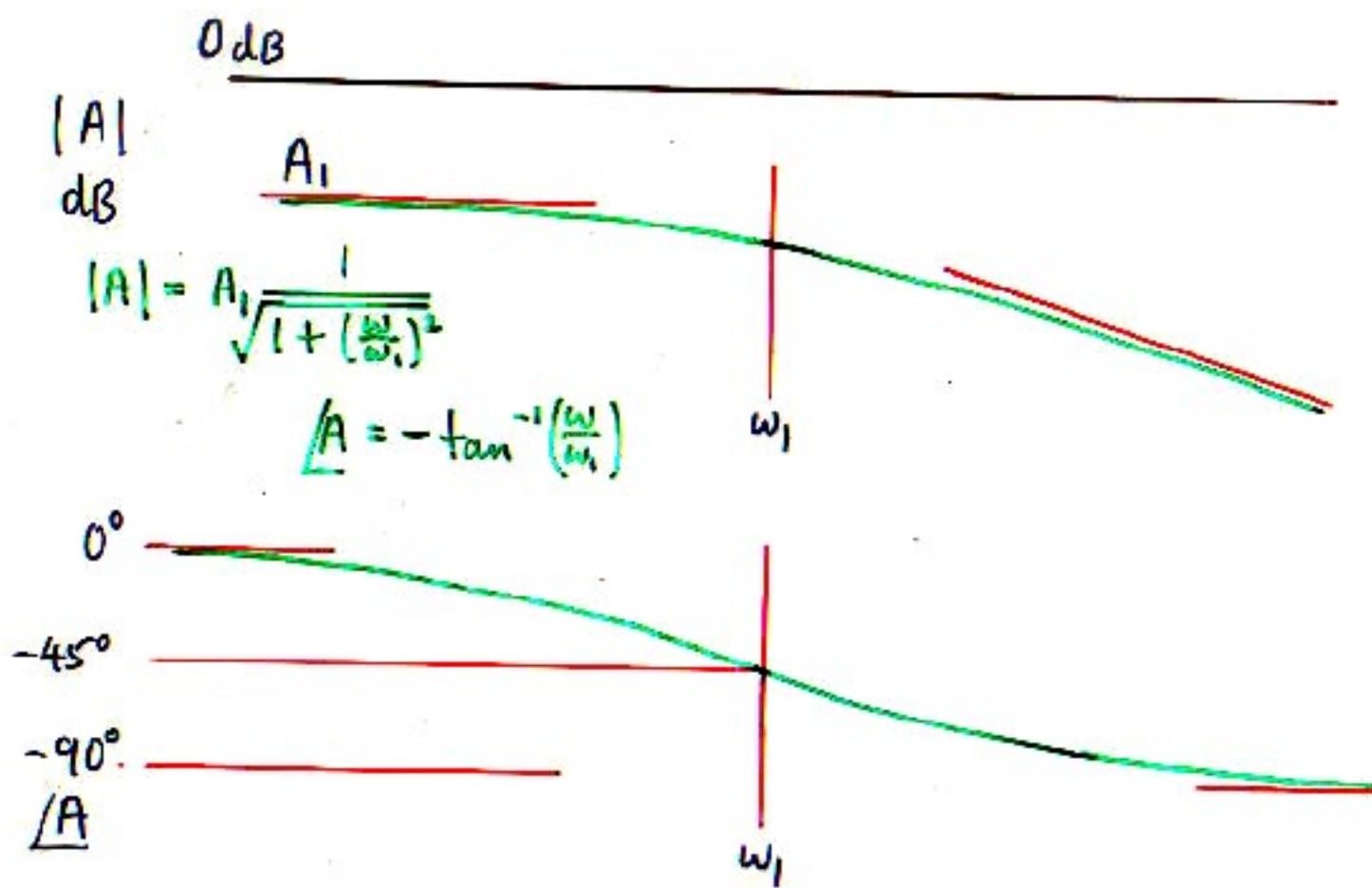

Single-pole response:

$$A = A_1 \frac{1}{1 + \frac{s}{\omega_1}}$$

flat gain  $\nearrow$  normal pole


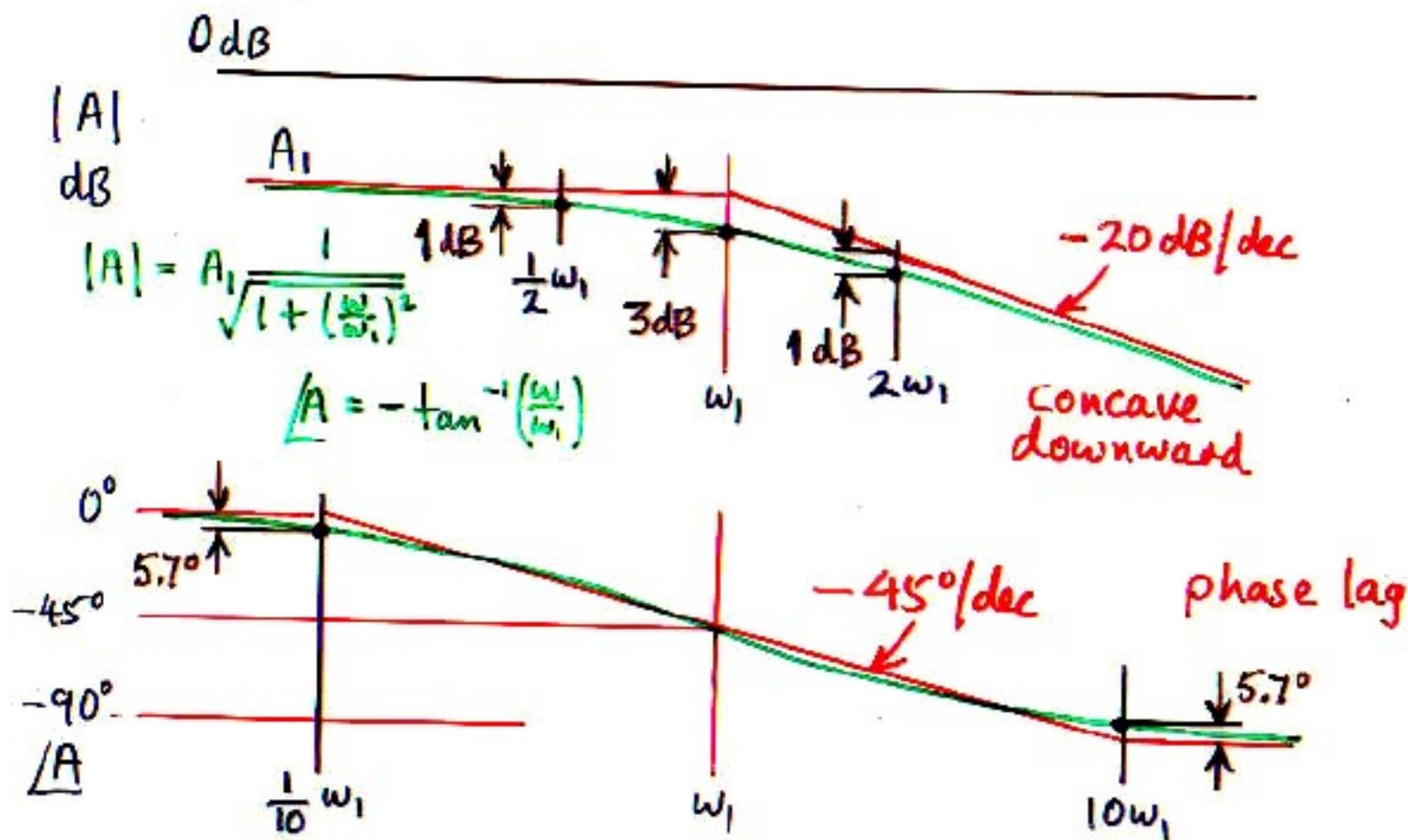


Single-zero response:

$$A = A_1 \left( 1 + \frac{\omega}{\omega_1} \right)$$

*flat gain* ↑      ↙ *normal zero*

$$|A| = A_1 \sqrt{1 + \left( \frac{\omega}{\omega_1} \right)^2}$$

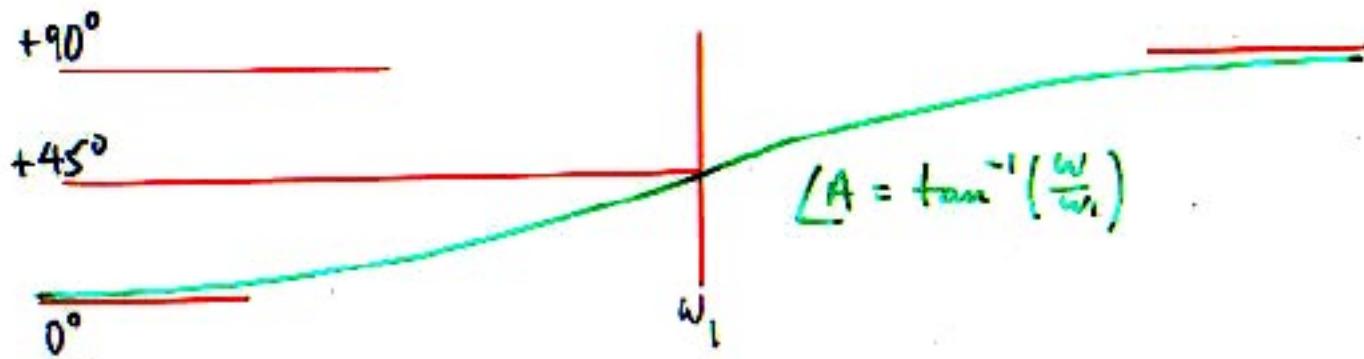
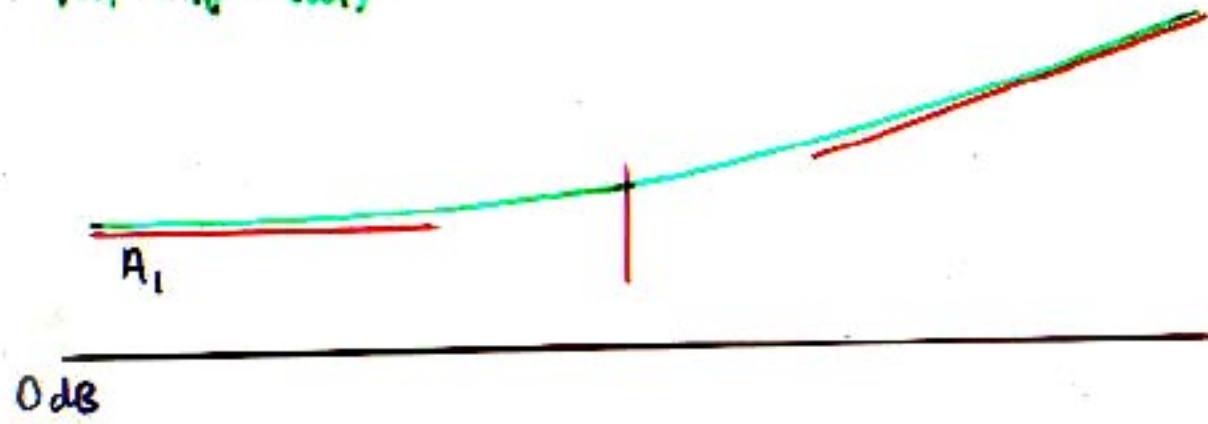


Single-zero response:

$$A = A_1 \left(1 + \frac{\omega}{\omega_1}\right)$$

flat gain ↑                              ↙ normal zero

$$|A| = A_1 \sqrt{1 + \left(\frac{\omega}{\omega_1}\right)^2}$$

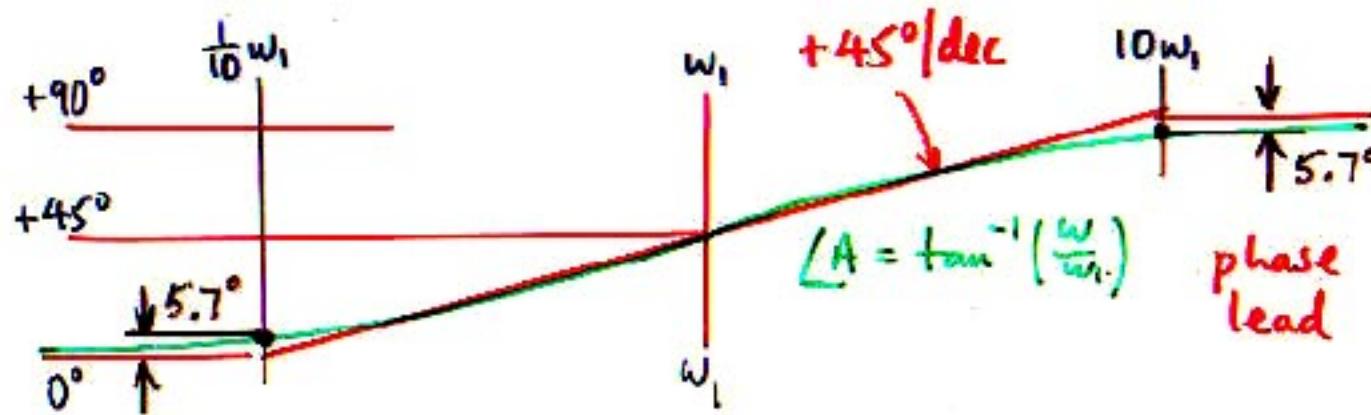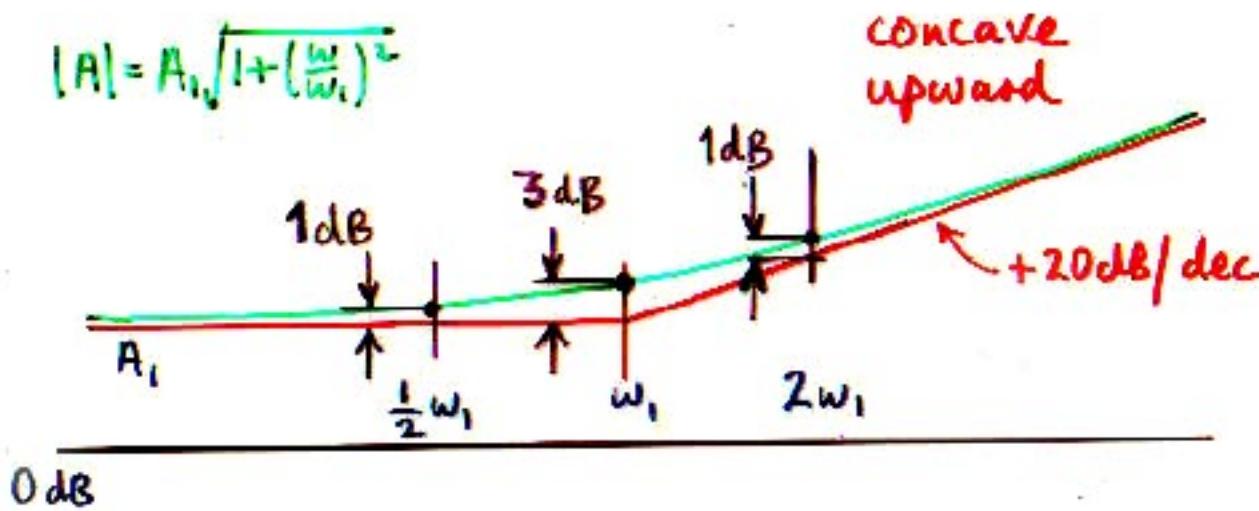

### Generalization: Property of Magnitude and Phase Graphs

A corner can be "seen" from further away on the phase graph than on the magnitude graph.

OR:



The phase gives a more accurate value of a nearby corner frequency than does the magnitude.

Single-zero response:


$$A = A_1 \left(1 + \frac{\omega}{\omega_1}\right)$$

flat gain ↑                              ↙ normal zero

$$|A| = A_1 \sqrt{1 + \left(\frac{\omega}{\omega_1}\right)^2}$$

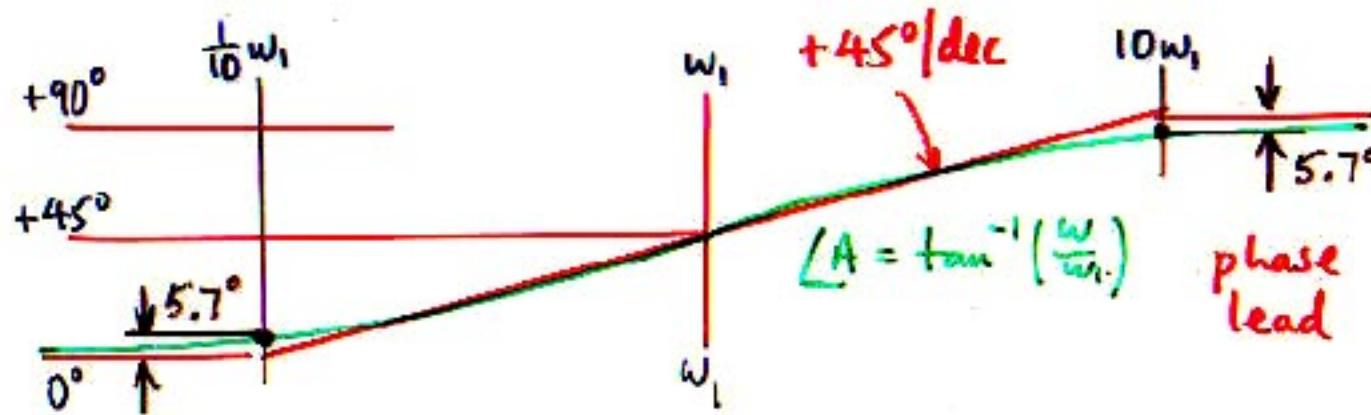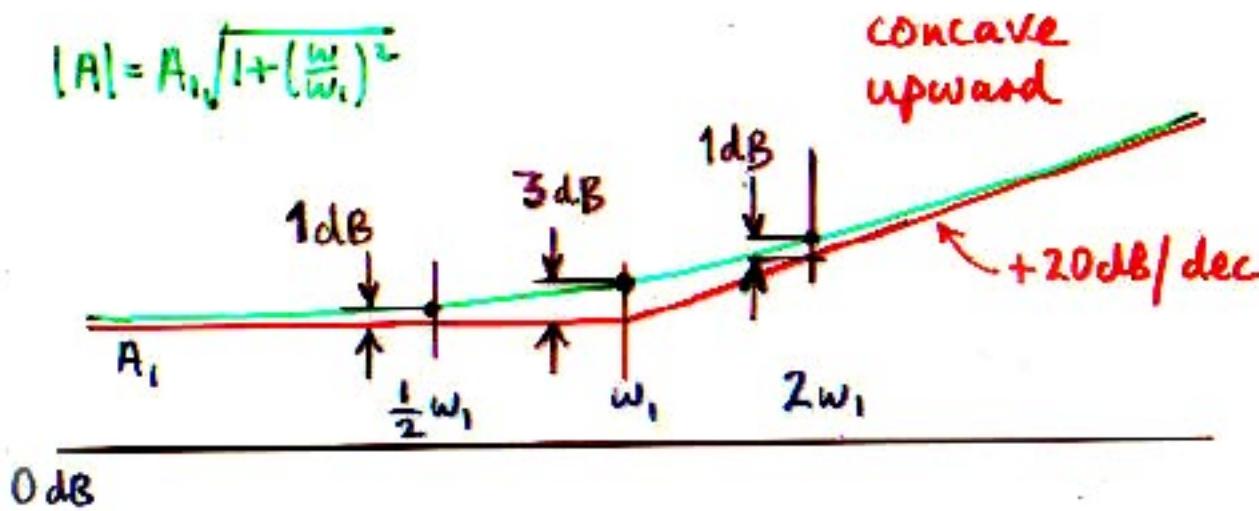

## Double-pole low-pass RC filters

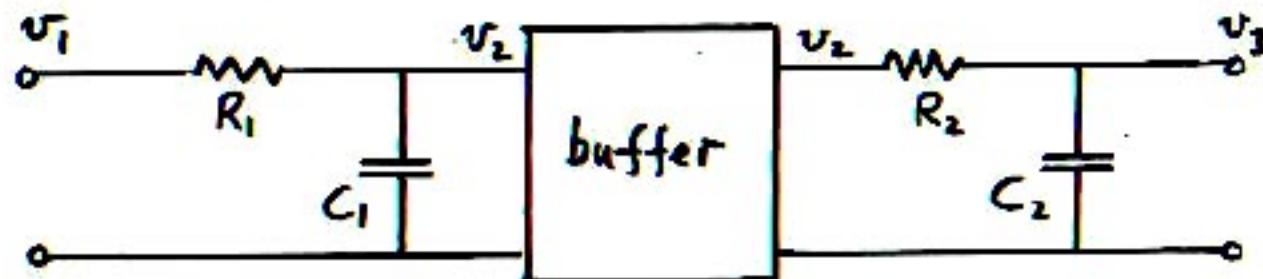



$$\frac{v_3}{v_1} = \frac{1}{(1 + \frac{s}{\omega_1})(1 + \frac{s}{\omega_2})} \quad \text{where } \omega_1 \equiv \frac{1}{C_1 R_1} \quad \omega_2 \equiv \frac{1}{C_2 R_2}$$


$$\left| \frac{v_3}{v_1} \right|_{dB} = -20 \log \sqrt{1 + \left(\frac{\omega}{\omega_1}\right)^2} - 20 \log \sqrt{1 + \left(\frac{\omega}{\omega_2}\right)^2}$$


superposition
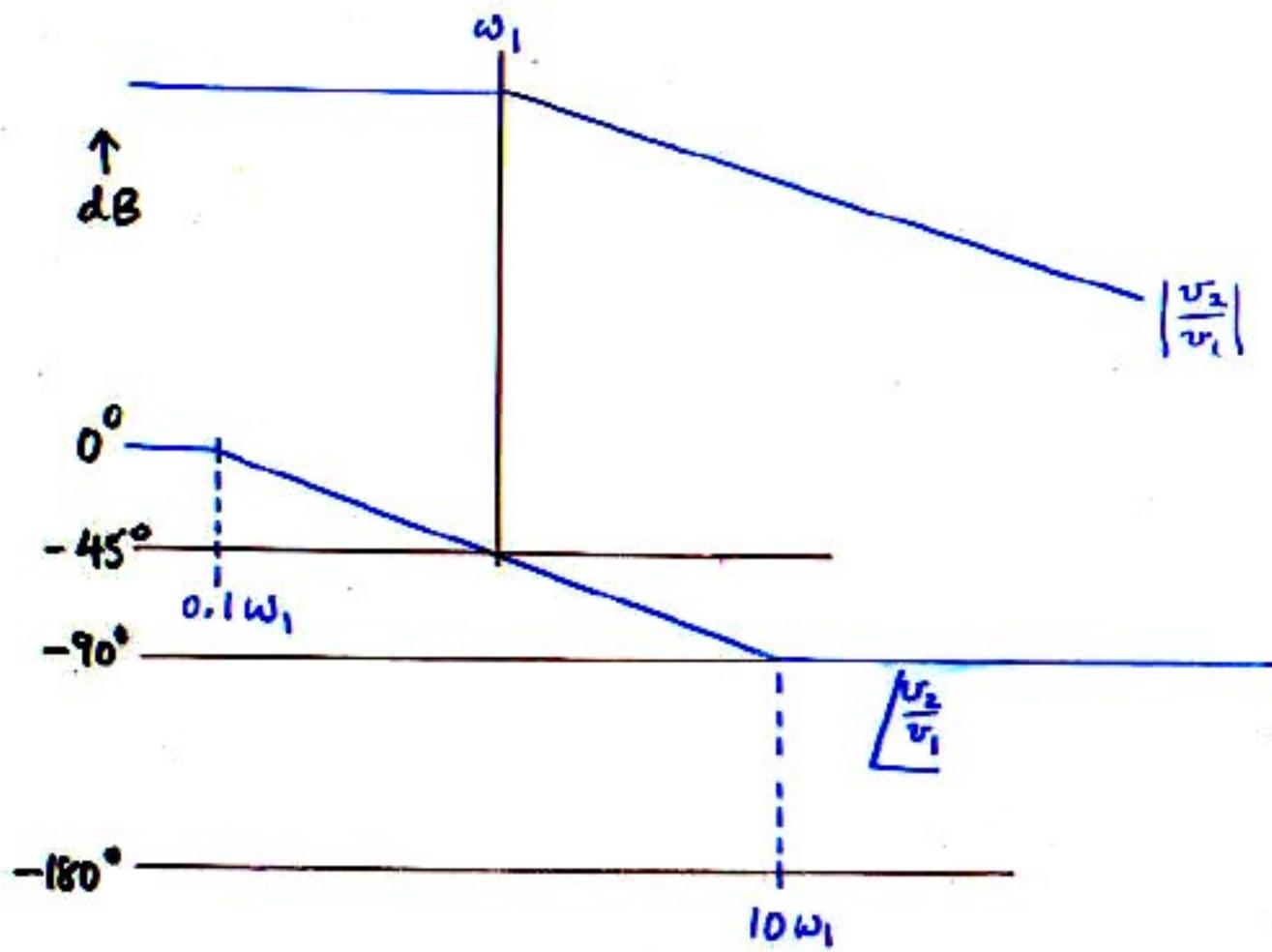
$$\angle \frac{v_3}{v_1} = -\tan^{-1} \left( \frac{\omega}{\omega_1} \right) - \tan^{-1} \left( \frac{\omega}{\omega_2} \right)$$




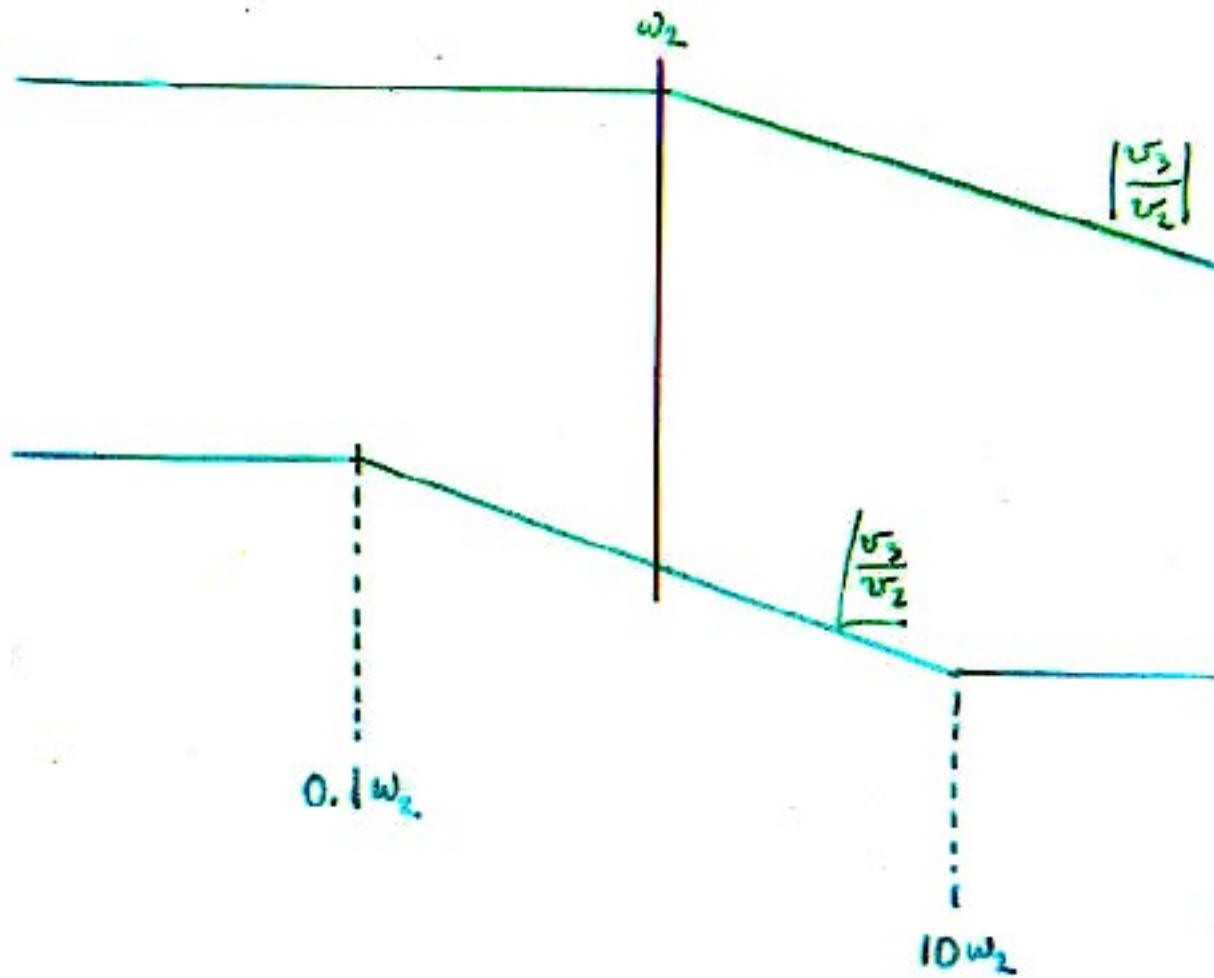

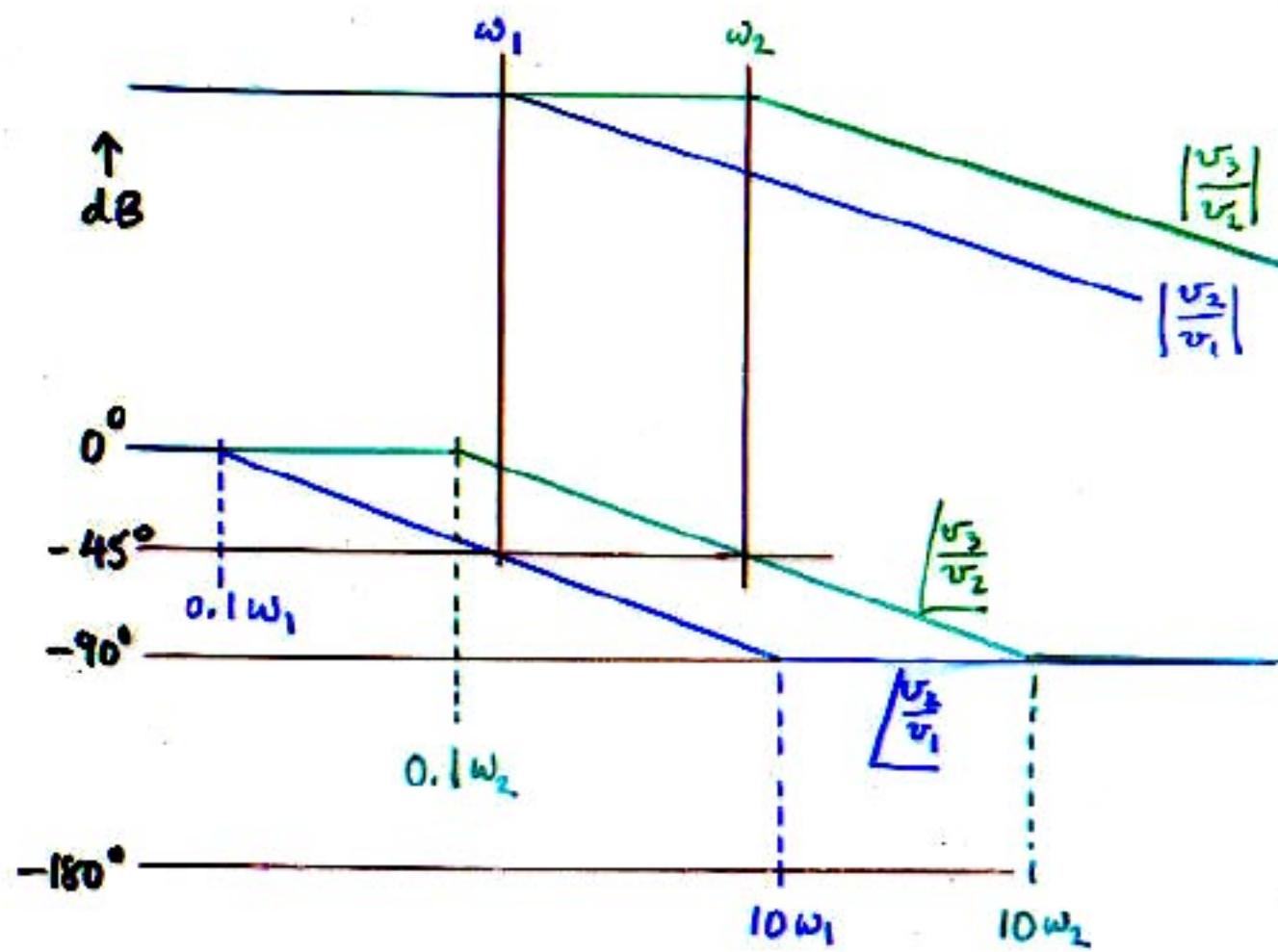

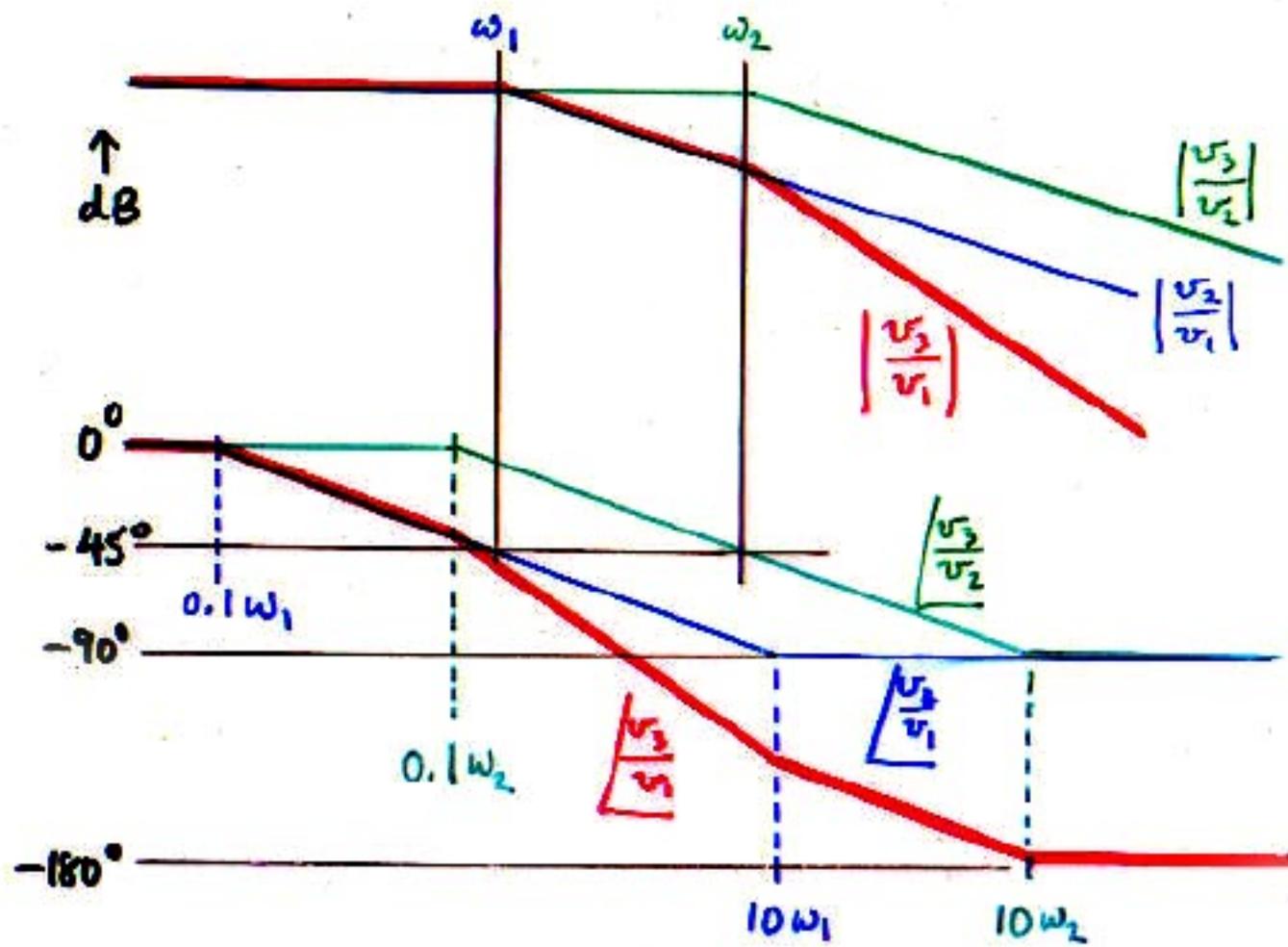


Normal and Inverted poles and zeros

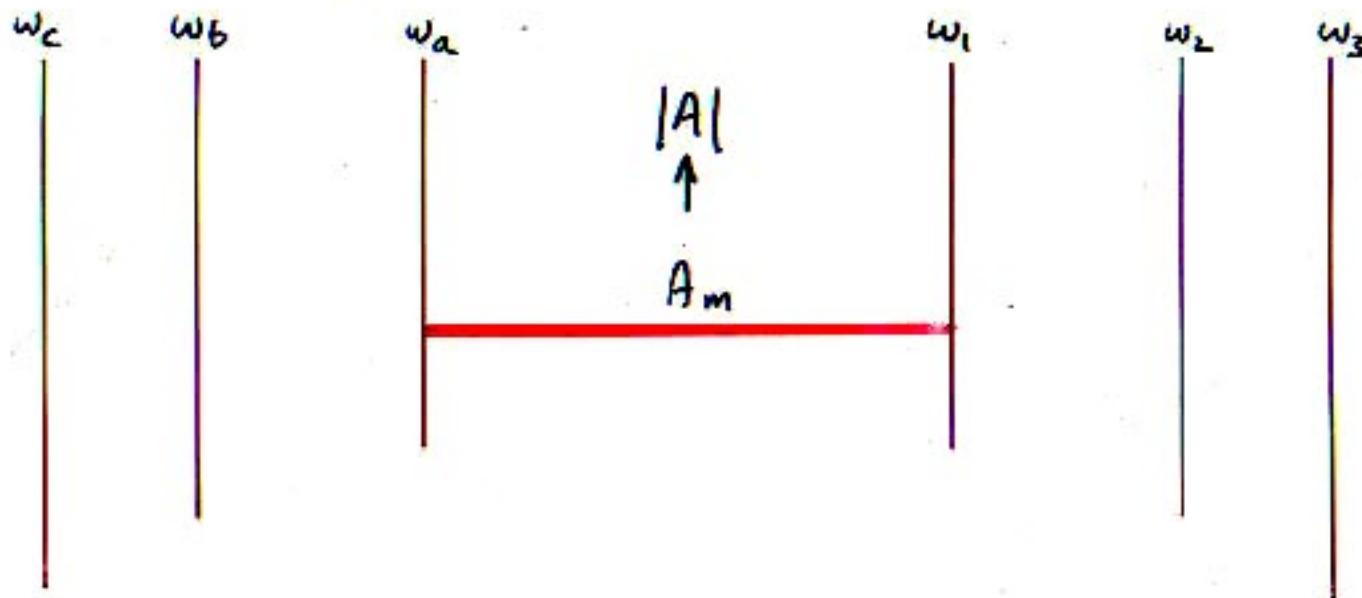


$$A = A_m$$

Normal and Inverted poles and zeros

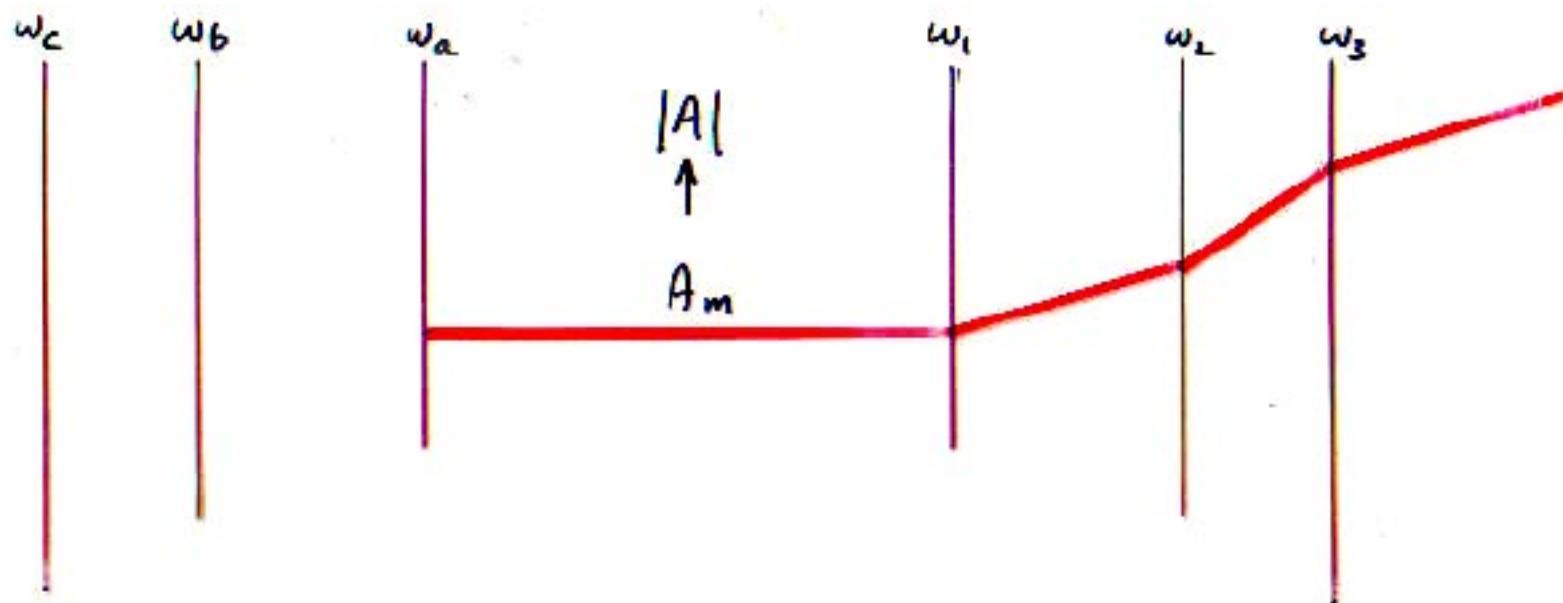

$$A = A_m$$


Normal and Inverted poles and zeros

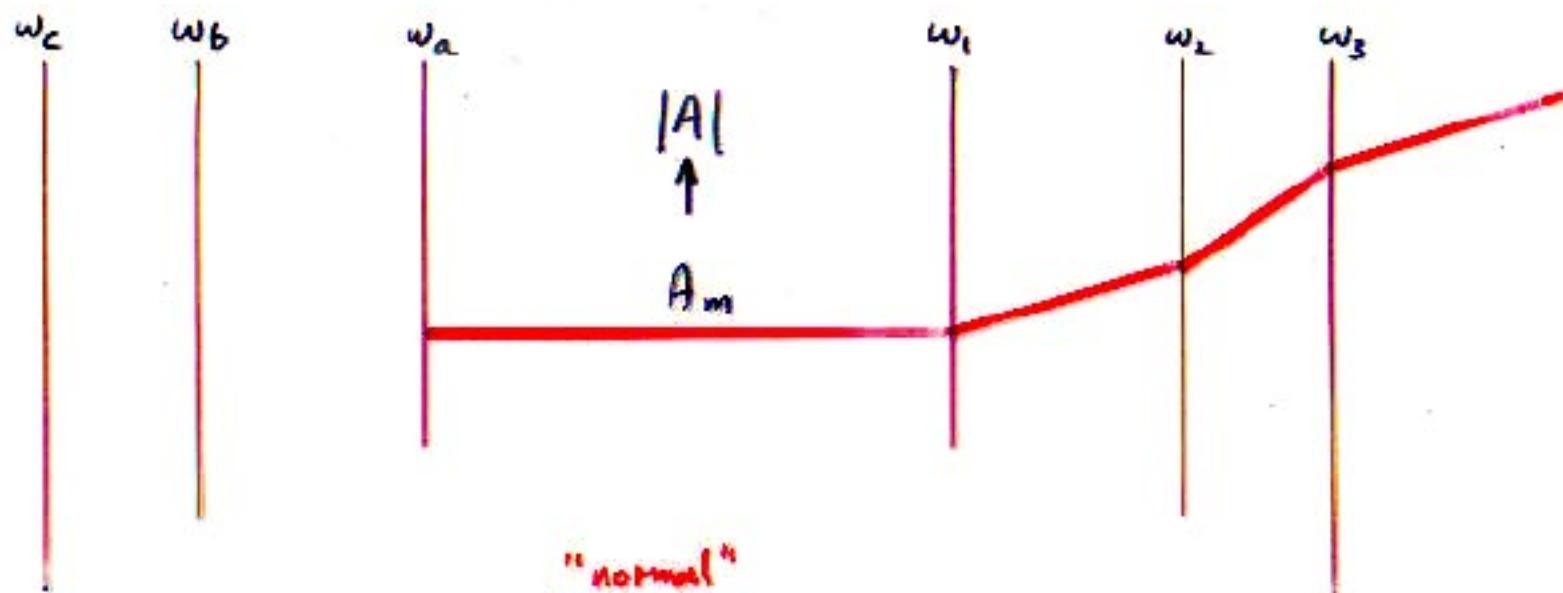

"normal"  
poles and zeros


$$A = A_m \frac{(1 + \frac{s}{\omega_1})(1 + \frac{s}{\omega_2})}{(1 + \frac{s}{\omega_3})}$$

Normal and Inverted poles and zeros

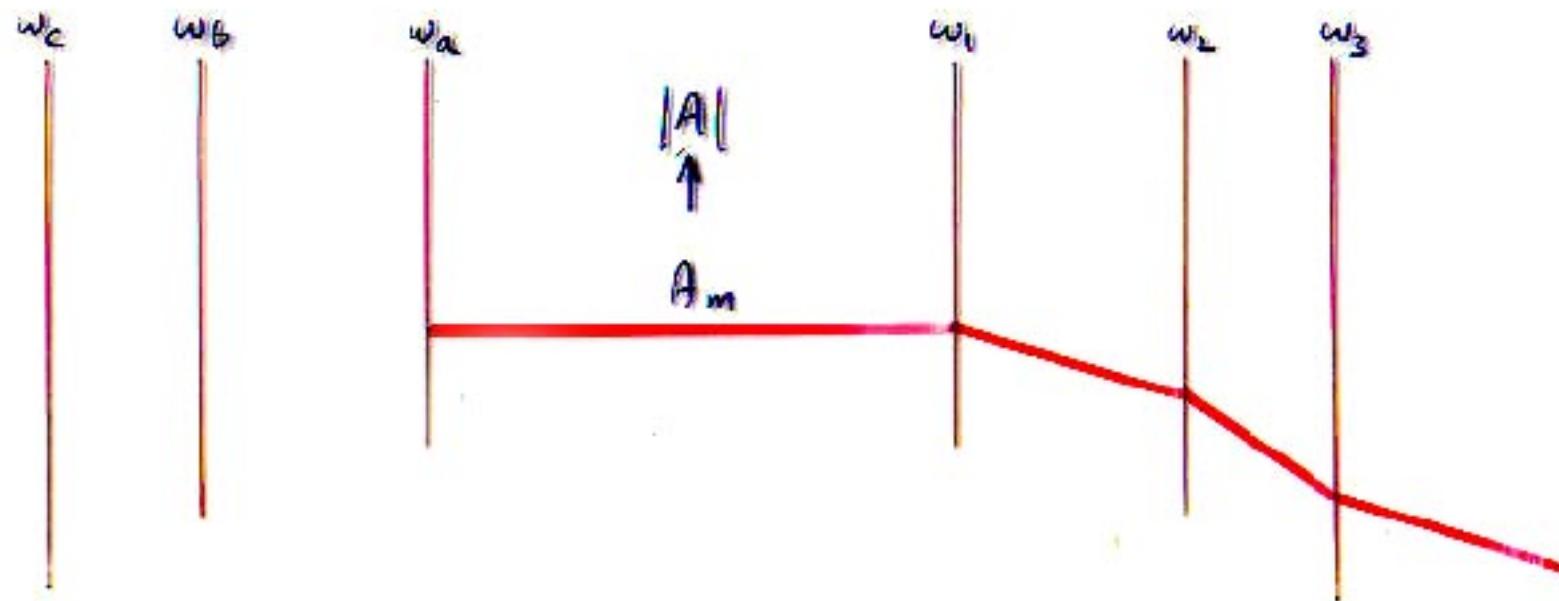

$$A = A_m$$


Normal and Inverted poles and zeros

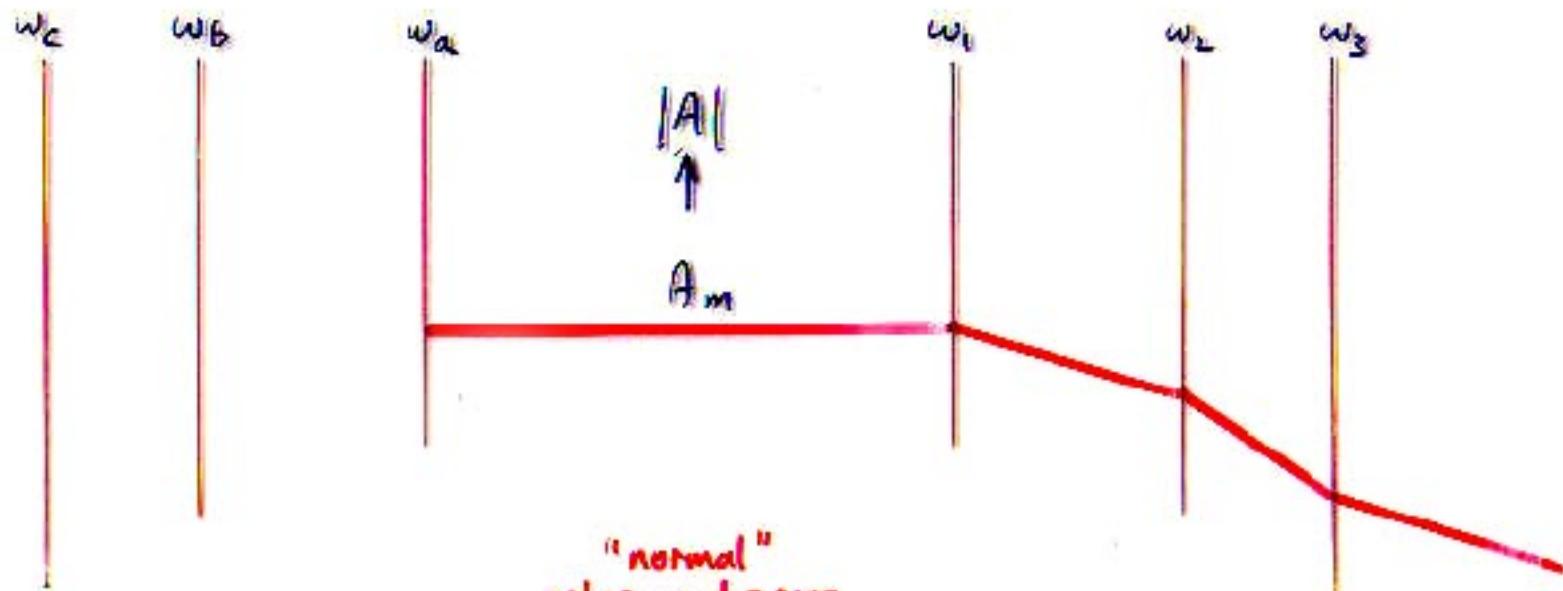

$$A = A_m \frac{(1 + \frac{s}{\omega_3})}{(1 + \frac{s}{\omega_1})(1 + \frac{s}{\omega_2})}$$


Inversion of pole-zero factors  $\Leftrightarrow$  vertical inversion of magnitude graph

Normal and Inverted poles and zeros

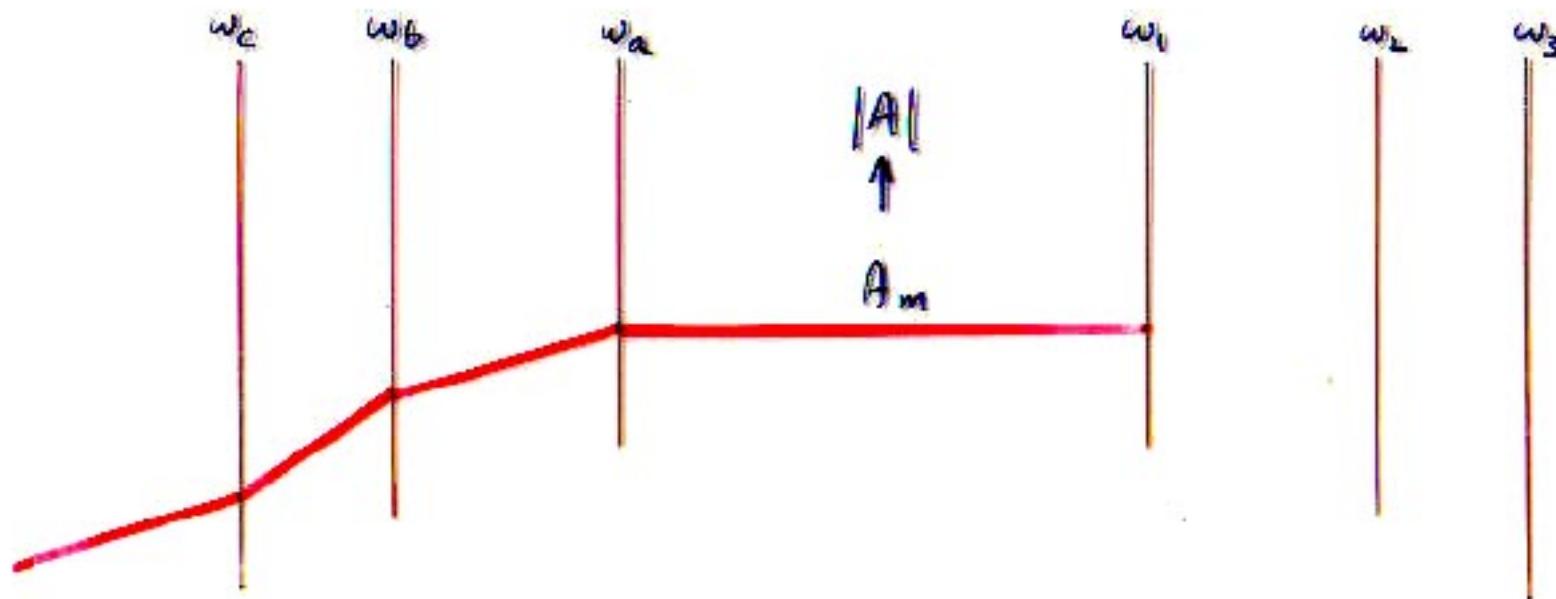

$$A = A_m$$


Normal and Inverted poles and zeros

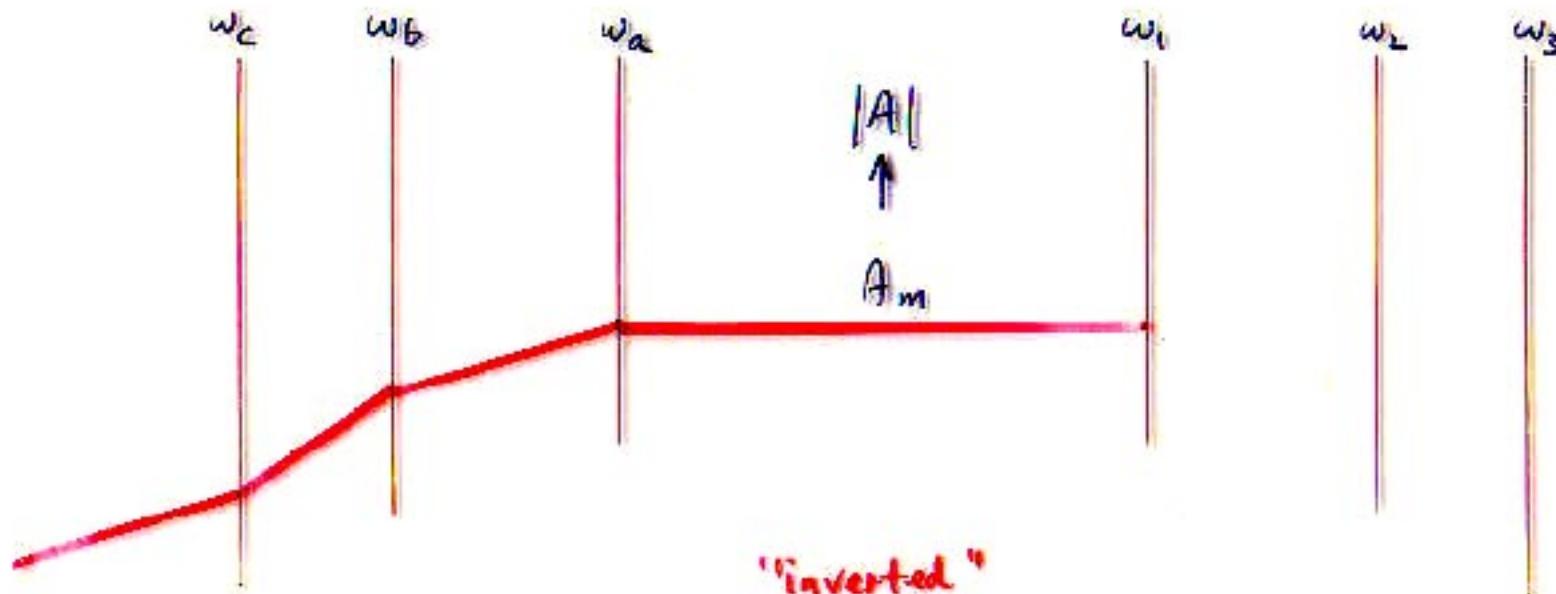

$$A = A_m \frac{\left(1 + \frac{w_c}{s}\right)}{\left(1 + \frac{w_a}{s}\right)\left(1 + \frac{w_b}{s}\right)}$$


Inversion of frequency terms  $\Leftrightarrow$  horizontal reversal of magnitude graph

Normal and Inverted poles and zeros

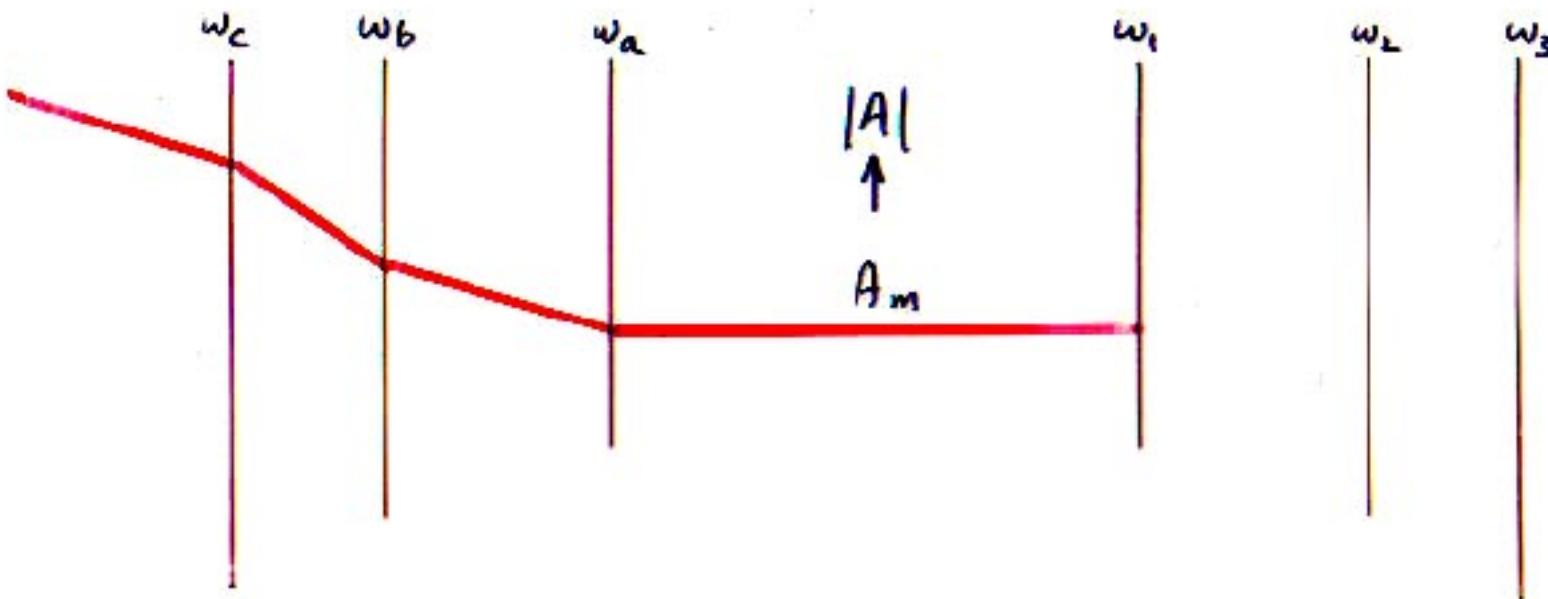


$$A = A_m$$

Normal and Inverted poles and zeros

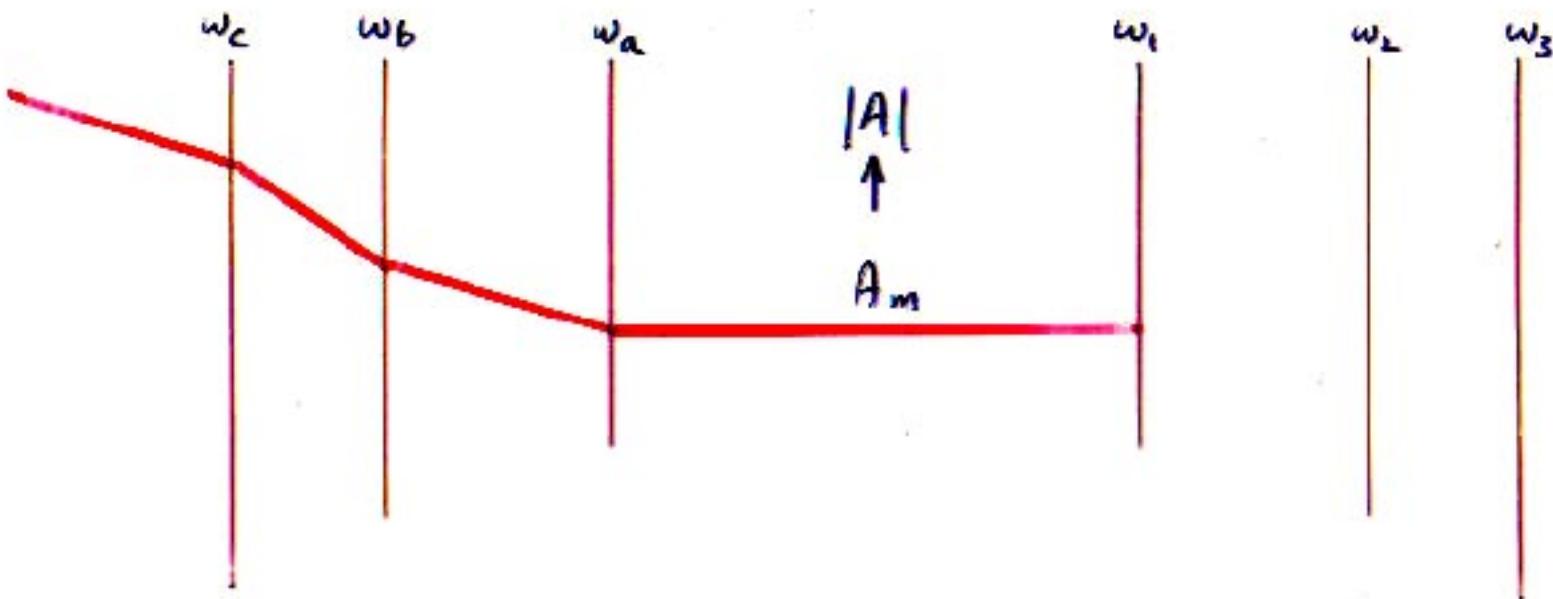

$$A = A_m \frac{(1 + \frac{w_a}{s})(1 + \frac{w_b}{s})}{1 + \frac{w_c}{s}}$$


Normal and Inverted poles and zeros

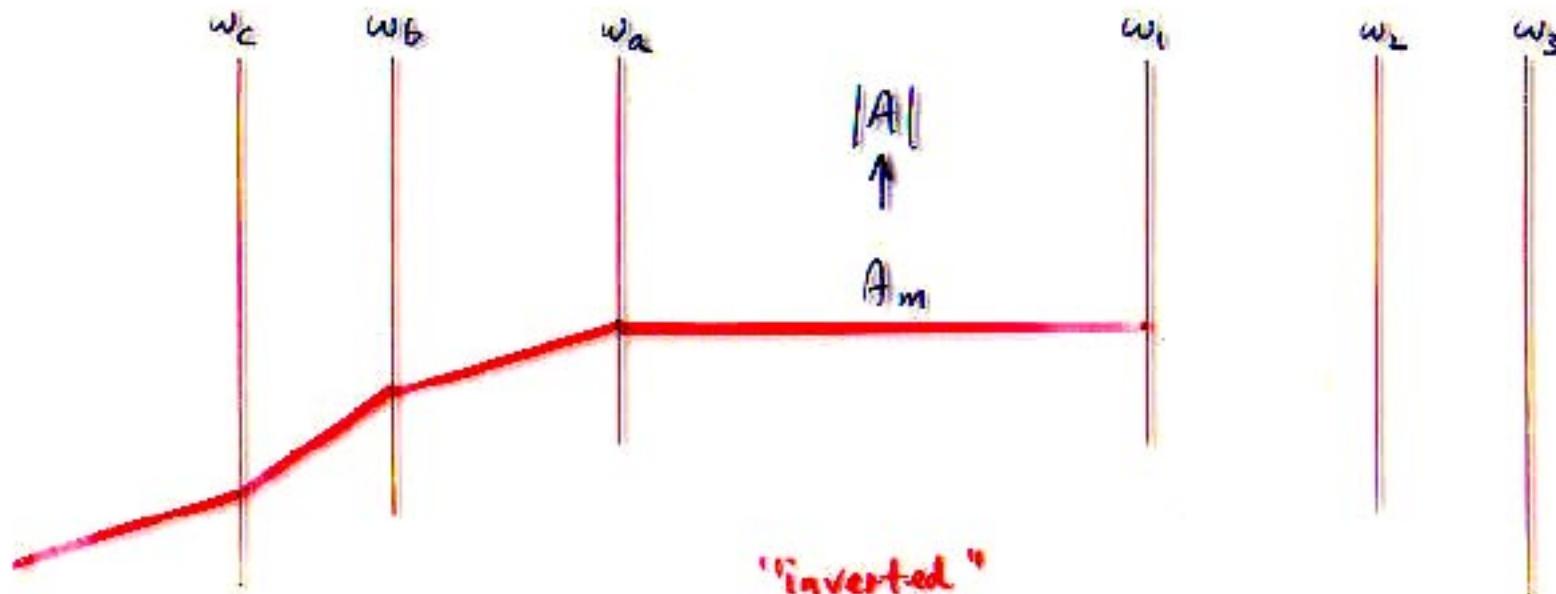

$$A = A_m \frac{\left(1 + \frac{w_c}{s}\right)}{\left(1 + \frac{w_a}{s}\right)\left(1 + \frac{w_b}{s}\right)}$$

Inversion of frequency terms  $\Leftrightarrow$  horizontal reversal of magnitude graph


## Normal and Inverted poles and zeros

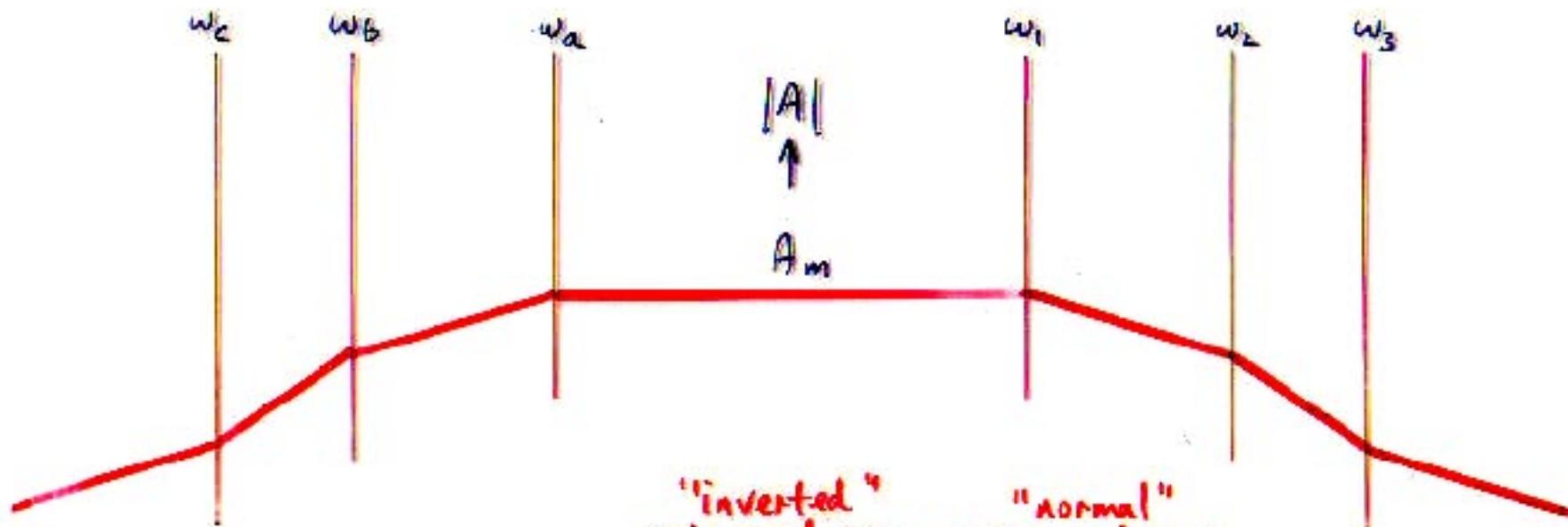


$$A = A_m \cdot \frac{\left(1 + \frac{w_c}{s}\right)}{\left(1 + \frac{w_a}{s}\right)\left(1 + \frac{w_b}{s}\right)} \cdot \frac{\left(1 + \frac{s}{w_3}\right)}{\left(1 + \frac{s}{w_1}\right)\left(1 + \frac{s}{w_2}\right)}$$

Inversion of frequency terms  $\Leftrightarrow$  horizontal reversal of magnitude graph

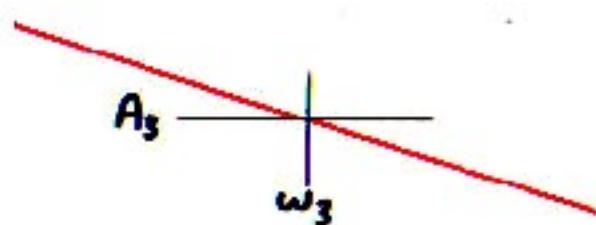If there is no "flat gain", use a reference value:



$|A|$

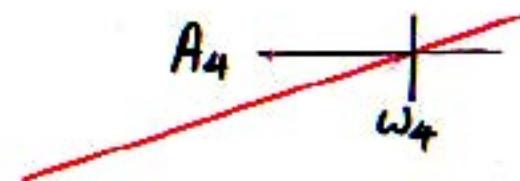

$$A = A_3 \frac{1}{\frac{s}{\omega_3}} = A_3 \frac{\omega_3}{s}$$

$$A = A_4 \frac{s}{\omega_4}$$



$\angle A$


$90^\circ$  \_\_\_\_\_

$45^\circ$  \_\_\_\_\_

$0^\circ$  \_\_\_\_\_

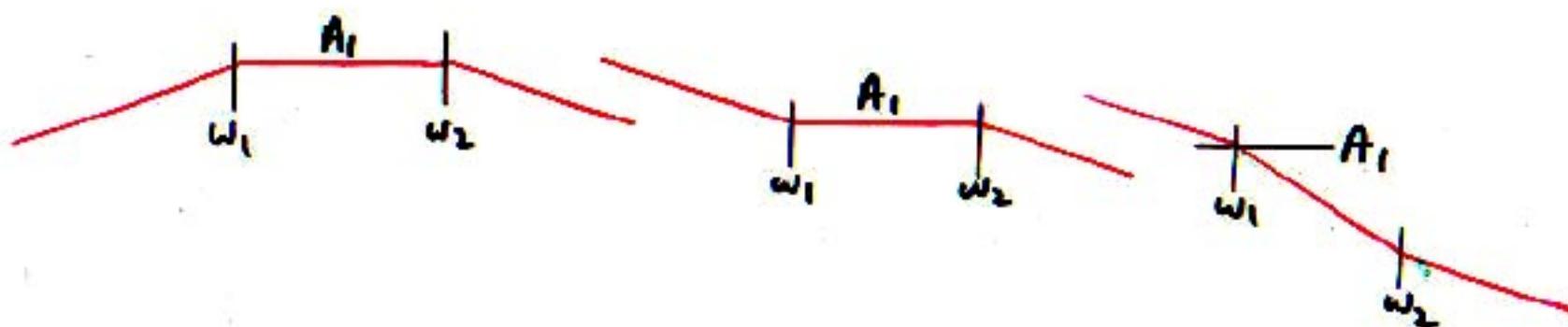
## Exercises

Express the gains in factored pole-zero form


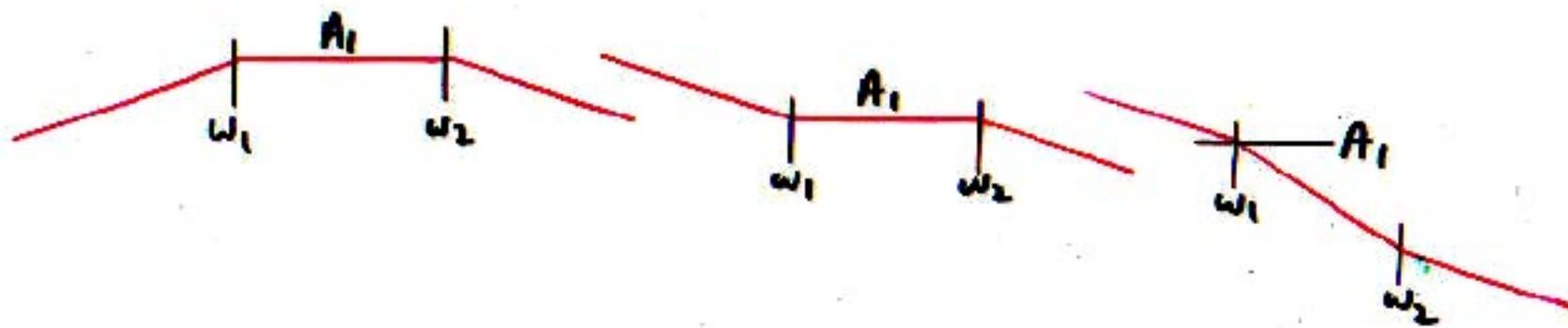
## Exercises


Express the gains in factored pole-zero form



$$A = A_1 \frac{1}{\left(1 + \frac{\omega_1}{s}\right) \left(1 + \frac{s}{\omega_2}\right)}$$
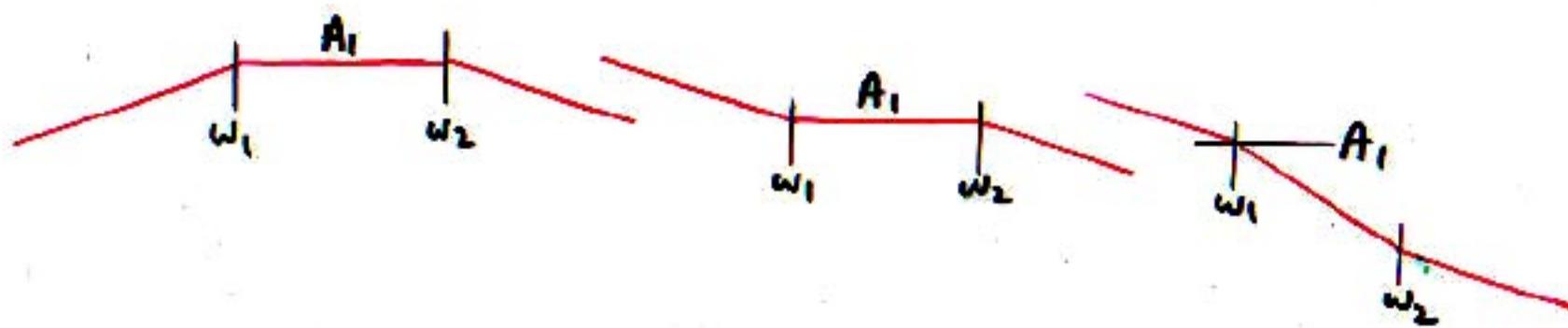
## Exercises

Express the gains in factored pole-zero form




$$A = A_1 \frac{1}{(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_2})}$$

$$A = A_1 \frac{1 + \frac{\omega_1}{s}}{1 + \frac{s}{\omega_2}}$$
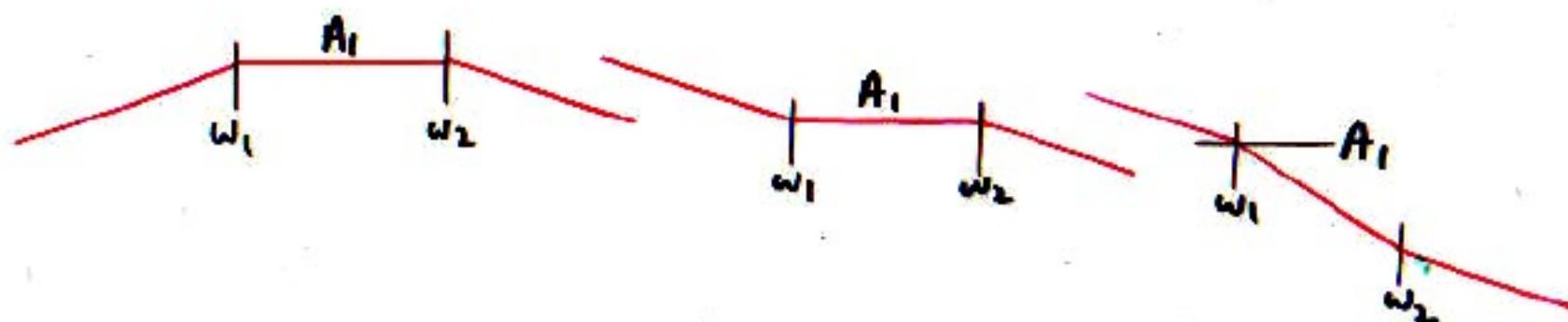
## Exercises

Express the gains in factored pole-zero form





$$A = A_1 \frac{1}{(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_2})}$$

$$A = A_1 \frac{1 + \frac{\omega_1}{s}}{1 + \frac{s}{\omega_2}}$$

$$A = A_1 \left(\frac{\omega_1}{s}\right) \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}}$$
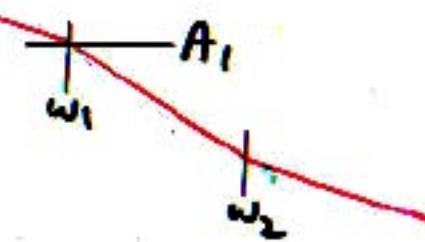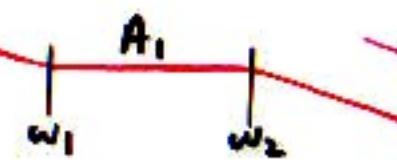
### Exercises

Express the gains in factored pole-zero form




$$A = A_1 \frac{1}{(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_2})}$$

$$A = A_1 \frac{1 + \frac{\omega_1}{s}}{1 + \frac{s}{\omega_2}}$$

$$A = A_1 \left(\frac{\omega_1}{s}\right) \frac{1 + \frac{s}{\omega_2}}{1 + \frac{\omega_1}{s}}$$

$$A = A_1 \left(\frac{\omega_1}{s}\right)^2 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{\omega_1}{s}}$$

## DESIGN-ORIENTED ANALYSIS

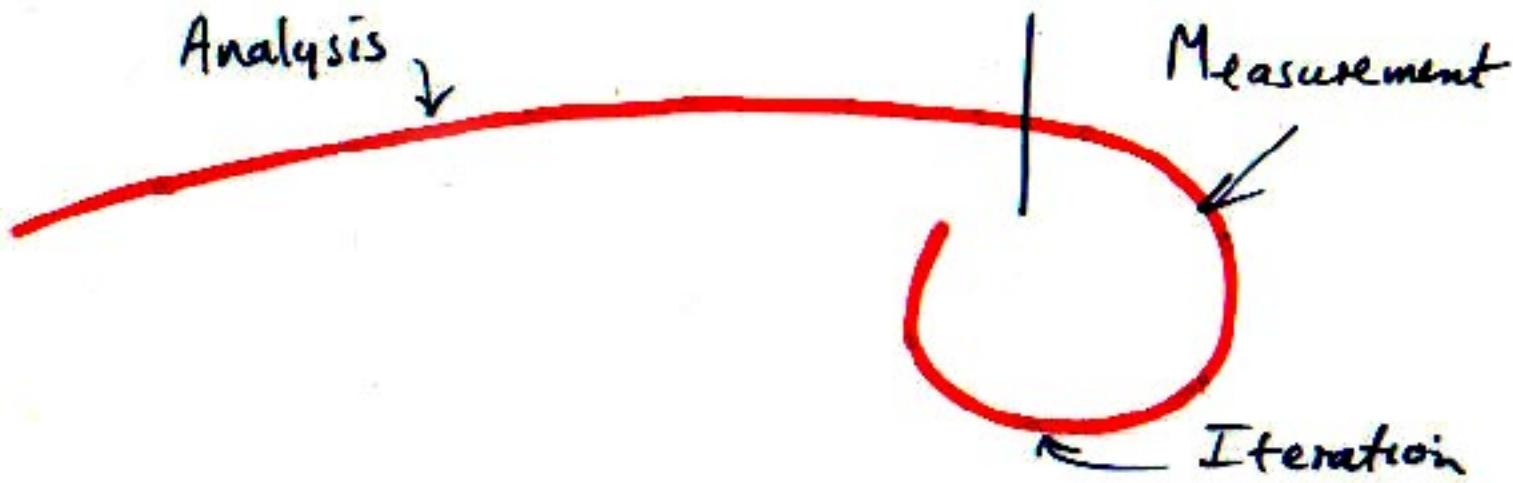

## Techniques of Design-Oriented Analysis

Lowering the Entropy of an expression

Doing the algebra on the circuit diagram.

Doing the algebra on the graph.

Using inverted poles and zeros.

Using numerical values to justify analytic approximations.

Improved formulas for quadratic roots

The Input/Output Impedance Theorem


The Feedback Theorem

Loop gain by injection of a test signal into the closed loop

Measurement of an unstable loop gain


The Extra Element Theorem (EET)

## Lag-lead network

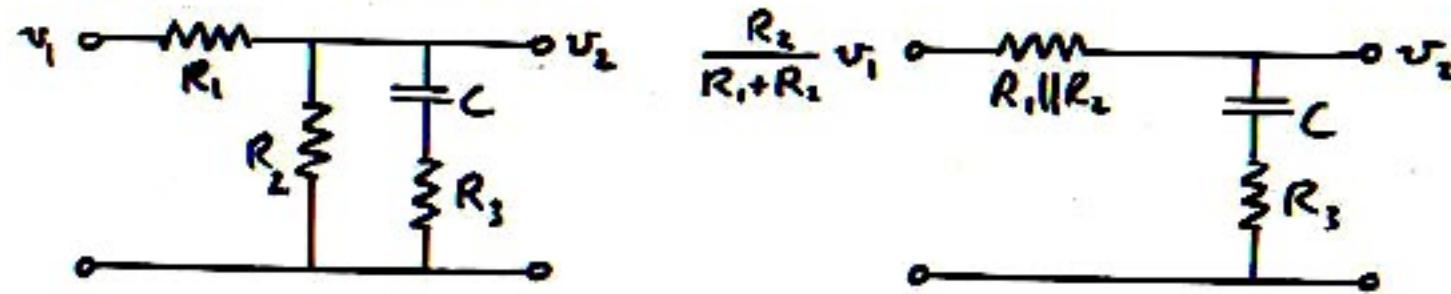

$$\frac{v_2}{v_1} = A = \frac{R_2}{R_1 + R_2} \cdot \frac{\frac{1}{sC} + R_3}{\frac{1}{sC} + R_3 + R_1 || R_2}$$

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} \quad \text{where} \quad A_1 \equiv \frac{R_2}{R_1 + R_2} \quad \omega_1 \equiv \frac{1}{C(R_3 + R_1 || R_2)} \quad \omega_2 \equiv \frac{1}{CR_3}$$

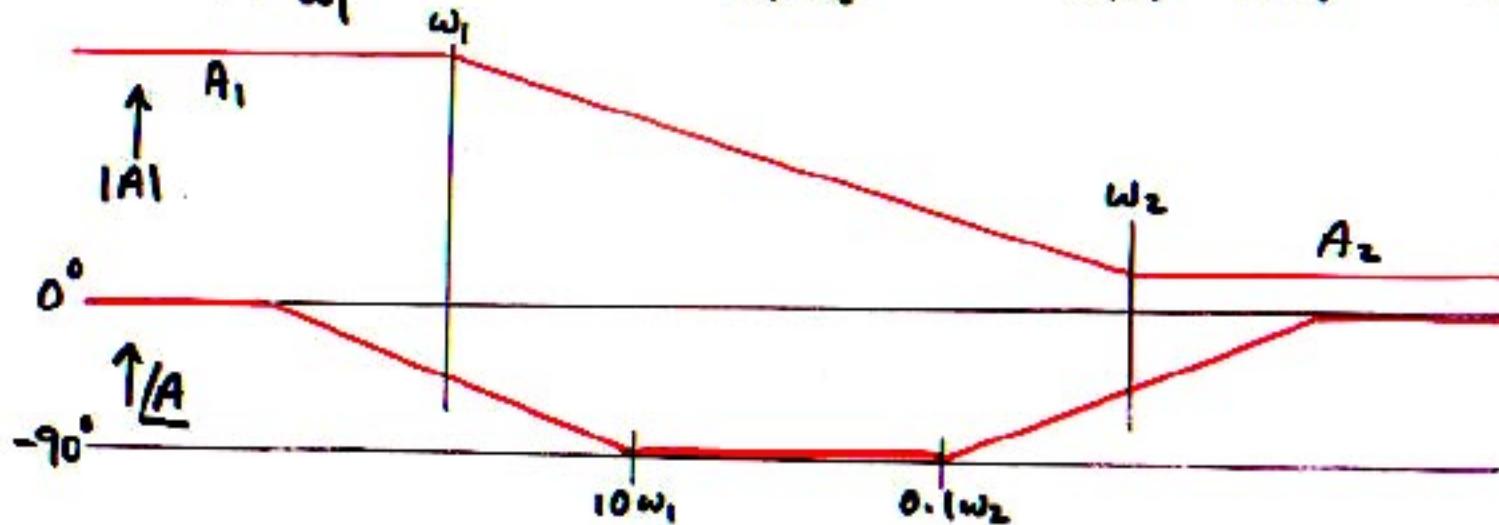

In this case, there are two flat gains. As derived, the low-frequency flat gain  $A_1$  appears as coefficient, together with normal pole and zero:

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}}$$

Equally well, directly from the  $|A|$  asymptotes, the result could be written with the high-frequency flat gain  $A_2$  as coefficient, together with inverted zero and pole:

$$A = A_2 \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

What is the relation between  $A_1$  and  $A_2$ ? One form of the result can be derived from the other algebraically:

$$A = \left( A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} \right) = A_1 \frac{\frac{s}{\omega_2}}{\frac{s}{\omega_1}} \frac{\frac{\omega_2}{s} + 1}{\frac{\omega_1}{s} + 1} = A_1 \frac{\omega_1}{\omega_2} \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

$\uparrow$   
This is  $A_1|_{s \rightarrow 0}$

In this case, there are two flat gains. As derived, the low-frequency flat gain  $A_1$  appears as coefficient, together with normal pole and zero:

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}}$$

Equally well, directly from the  $|A|$  asymptotes, the result could be written with the high-frequency flat gain  $A_2$  as coefficient, together with inverted zero and pole:

$$A = A_2 \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

What is the relation between  $A_1$  and  $A_2$ ? One form of the result can be derived from the other algebraically:

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} = A_1 \frac{s}{\omega_2} \frac{\frac{\omega_2}{s} + 1}{\frac{\omega_1}{s} + 1} = A_1 \frac{\omega_1}{\omega_2} \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

This is  $A|_{s \rightarrow 0}$

This is  $A|_{s \rightarrow \infty}$ , so must be  $A_2$ .

Result:

$$\frac{A_2}{A_1} = \frac{\omega_1}{\omega_2}$$

For the lag-lead network:

$$A_2 = A_1 \frac{\omega_1}{\omega_2} = \frac{R_2}{R_1 + R_2} \frac{CR_3}{C(R_3 + R_1 || R_2)}$$

which is obvious from the reduced model.


Generalization: Gain-Bandwidth Trade-Off

For a single-slope ( $\pm 20\text{dB/dec}$ )

Ratio of flat gains = Ratio of corner frequencies  
that separate them


This is a form of gain-bandwidth trade-off.

## Lag-lead network

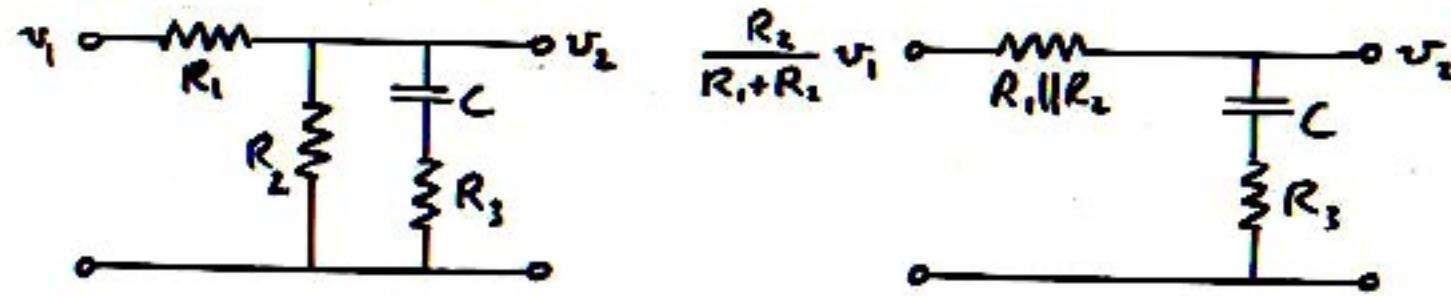

$$\frac{v_2}{v_1} = A = \frac{R_2}{R_1 + R_2} \cdot \frac{\frac{1}{sC} + R_3}{\frac{1}{sC} + R_3 + R_1 || R_2}$$

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} \quad \text{where} \quad A_1 \equiv \frac{R_2}{R_1 + R_2} \quad \omega_1 \equiv \frac{1}{C(R_3 + R_1 || R_2)} \quad \omega_2 \equiv \frac{1}{CR_3}$$

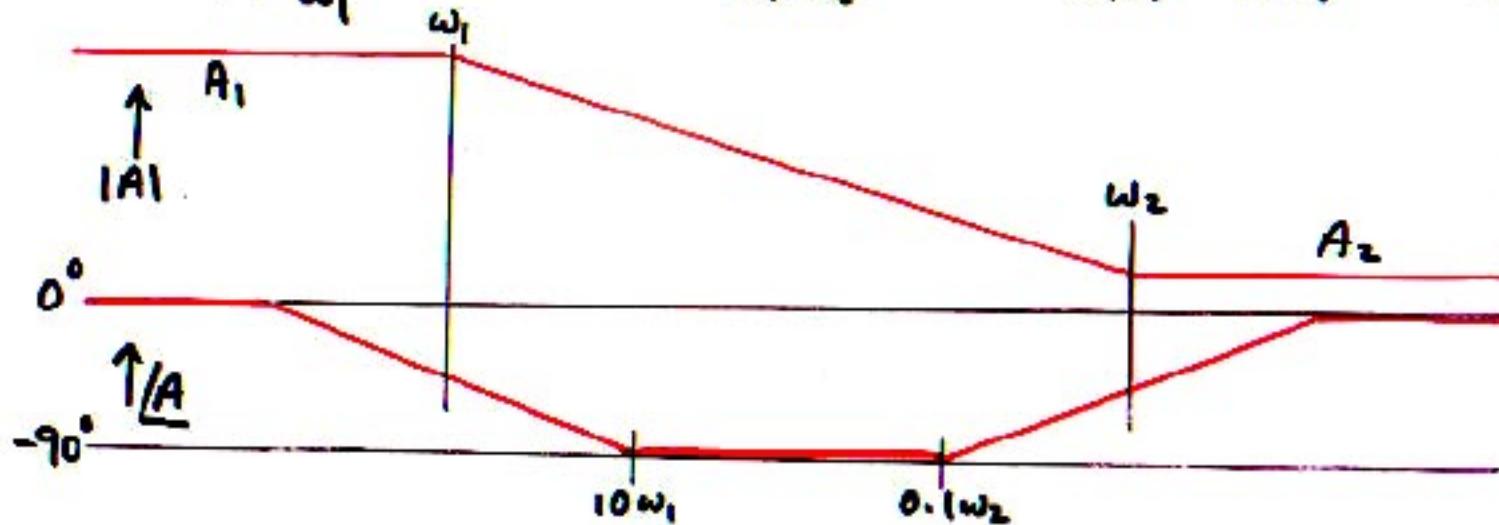

In this case, there are two flat gains. As derived, the low-frequency flat gain  $A_1$  appears as coefficient, together with normal pole and zero:

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}}$$

Equally well, directly from the  $|A|$  asymptotes, the result could be written with the high-frequency flat gain  $A_2$  as coefficient, together with inverted zero and pole:

$$A = A_2 \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

What is the relation between  $A_1$  and  $A_2$ ? One form of the result can be derived from the other algebraically:

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} = A_1 \frac{s}{\omega_2} \frac{\frac{\omega_2}{s} + 1}{\frac{\omega_1}{s} + 1} = A_1 \frac{\omega_1}{\omega_2} \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

This is  $A|_{s \rightarrow 0}$

This is  $A|_{s \rightarrow \infty}$ , so must be  $A_2$ .

Result:

$$\frac{A_2}{A_1} = \frac{\omega_1}{\omega_2}$$

For the lag-lead network:

$$A_2 = A_1 \frac{\omega_1}{\omega_2} = \frac{R_2}{R_1 + R_2} \frac{CR_3}{C(R_3 + R_1 || R_2)}$$

which is obvious from the reduced model.


Generalization: Gain-Bandwidth Trade-Off

For a single-slope ( $\pm 20\text{dB/dec}$ )

Ratio of flat gains = Ratio of corner frequencies  
that separate them


This is a form of gain-bandwidth trade-off.

## Lag-lead network

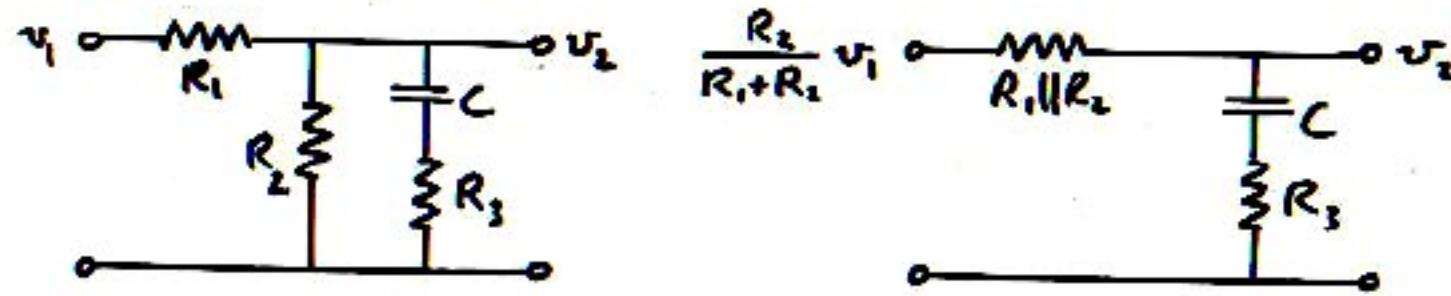

$$\frac{v_2}{v_1} = A = \frac{R_2}{R_1 + R_2} \cdot \frac{\frac{1}{sC} + R_3}{\frac{1}{sC} + R_3 + R_1 || R_2}$$

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} \quad \text{where} \quad A_1 \equiv \frac{R_2}{R_1 + R_2} \quad \omega_1 \equiv \frac{1}{C(R_3 + R_1 || R_2)} \quad \omega_2 \equiv \frac{1}{CR_3}$$

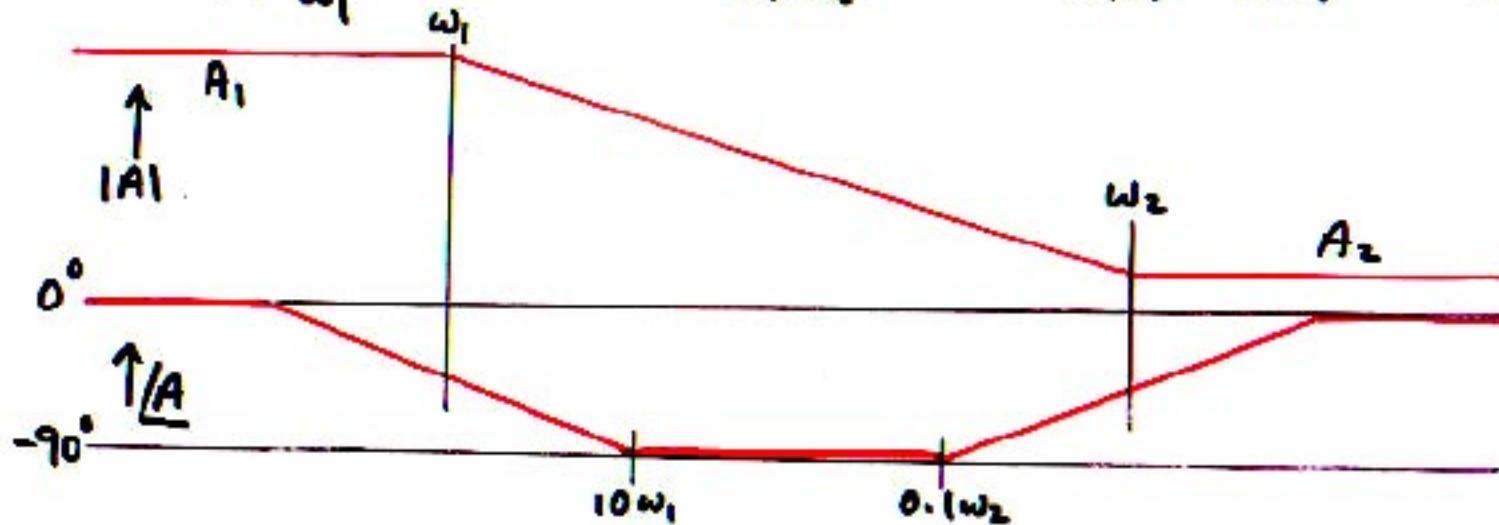

Result:

$$\frac{A_2}{A_1} = \frac{\omega_1}{\omega_2}$$

For the lag-lead network:

$$A_2 = A_1 \frac{\omega_1}{\omega_2} = \frac{R_2}{R_1 + R_2} \frac{CR_3}{C(R_3 + R_1 || R_2)}$$

which is obvious from the reduced model.


Generalization: Gain-Bandwidth Trade-Off

For a single-slope ( $\pm 20\text{dB/dec}$ )

Ratio of flat gains = Ratio of corner frequencies  
that separate them


This is a form of gain-bandwidth trade-off.

## Lag-lead network

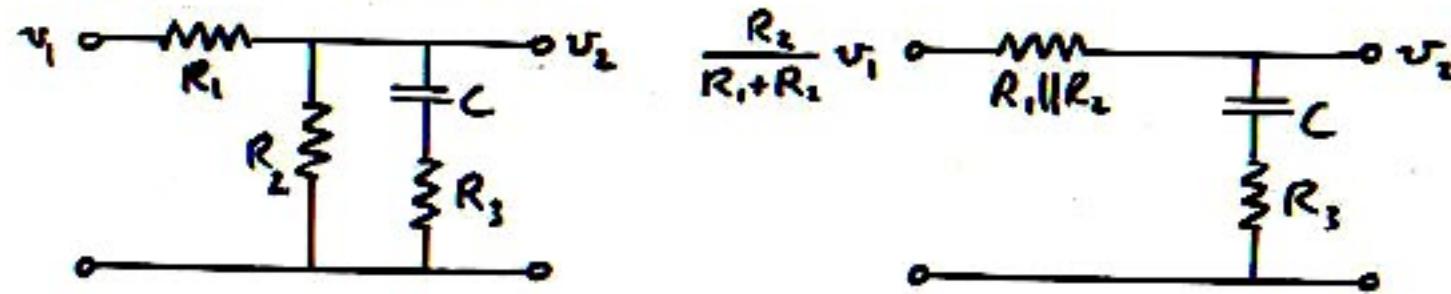

$$\frac{v_2}{v_1} = A = \frac{R_2}{R_1 + R_2} \cdot \frac{\frac{1}{sC} + R_3}{\frac{1}{sC} + R_3 + R_1 \parallel R_2}$$

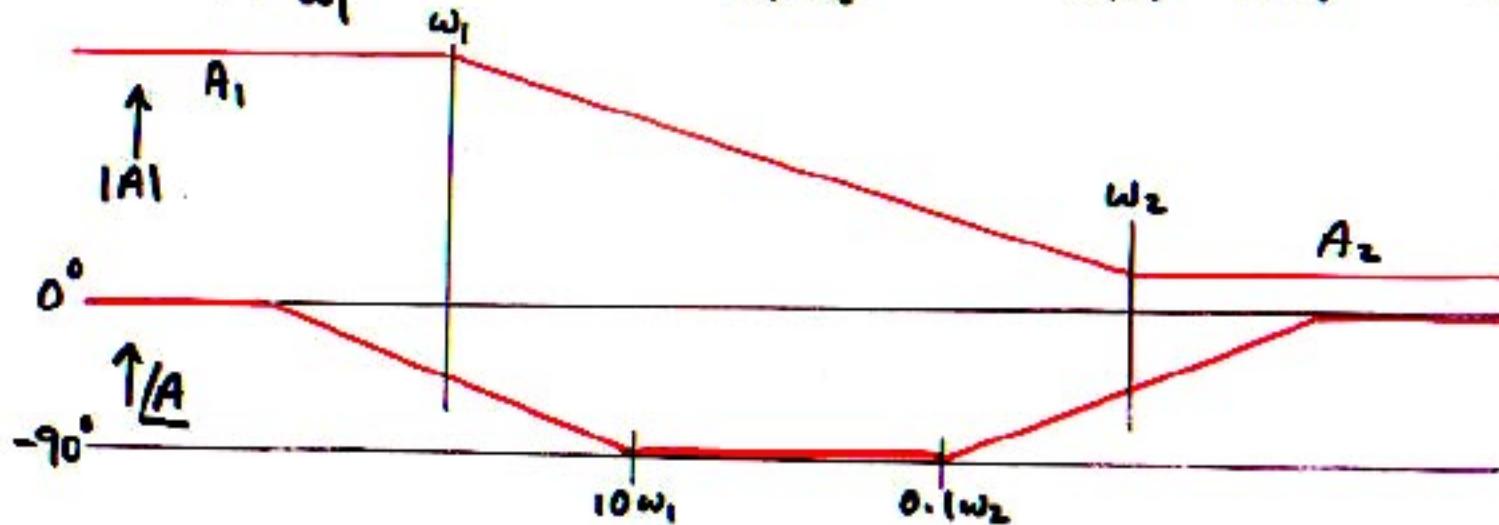
$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} \quad \text{where } A_1 = \frac{R_2}{R_1 + R_2}, \quad \omega_1 = \frac{1}{C(R_3 + R_1 \parallel R_2)}, \quad \omega_2 = \frac{1}{CR_3}$$



If  $\omega_2 > 100\omega_1$ , phase asymptotes do not overlap and the phase lag reaches  $90^\circ$  before returning to zero.


If  $\omega_2 < 100\omega_1$ , the phase asymptotes do overlap, and the phase lag reaches a maximum, less than  $90^\circ$ , which is a function of the ratio of the flat gains.

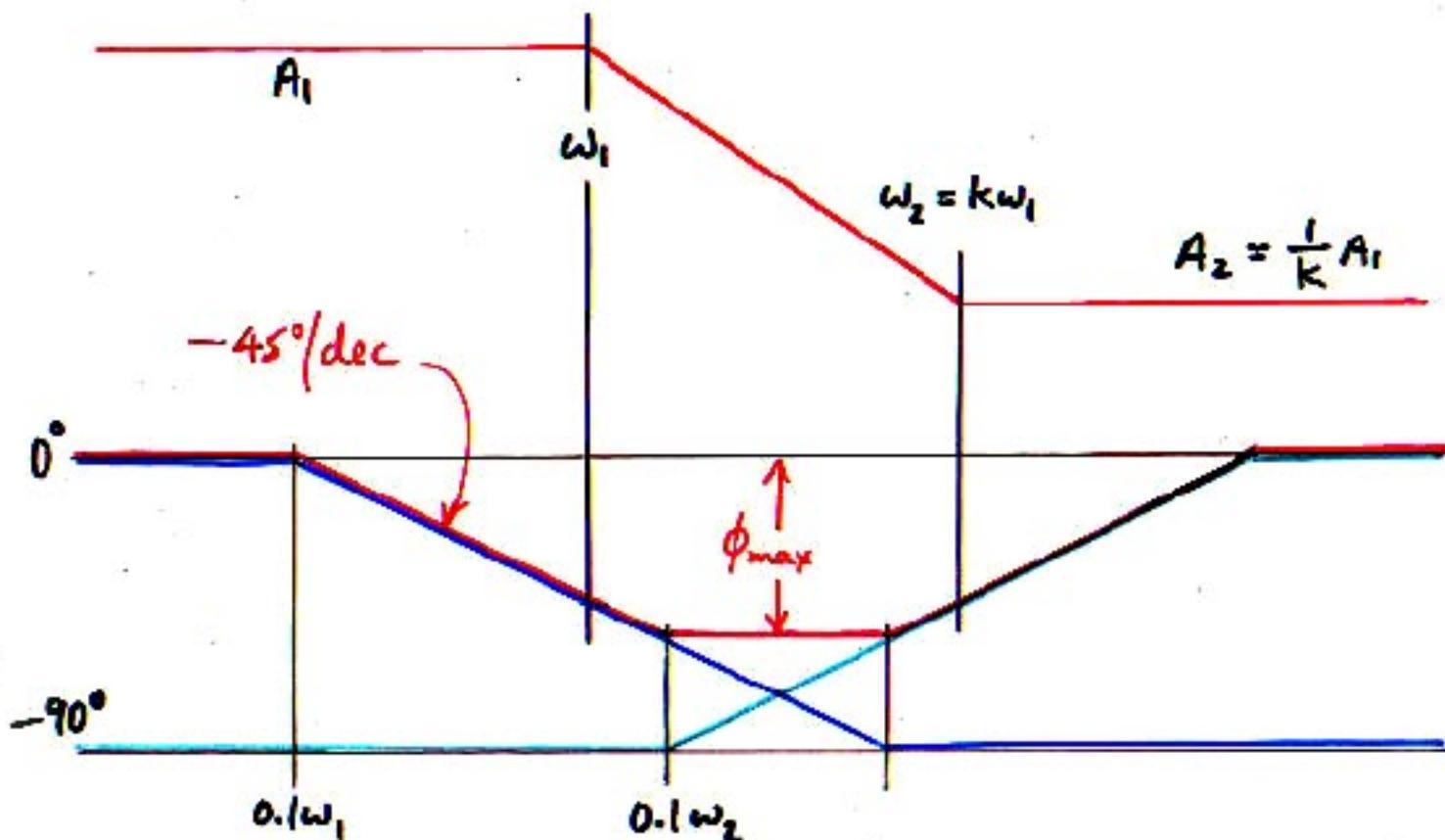Find the maximum phase lag  $\phi_{\max}$  as a function of the gain ratio  $k \equiv A_1/A_2 = \omega_2/\omega_1$



$$\phi_{\max} = -45^\circ \log \frac{0.1\omega_2}{0.1\omega_1} = -45^\circ \log k \quad (k < 100)$$

Relationships to conventional forms:

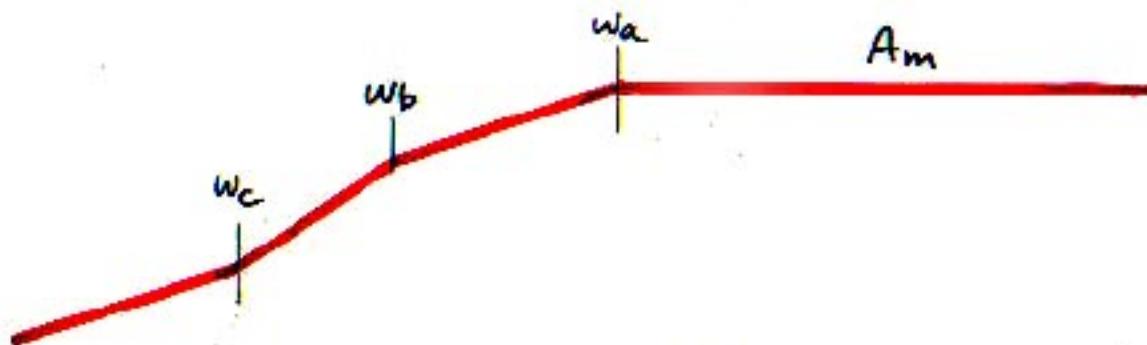


$$\begin{aligned} A &= A_m \frac{\left(1 + \frac{w_c}{s}\right)}{\left(1 + \frac{w_a}{s}\right)\left(1 + \frac{w_b}{s}\right)} = A_m \frac{\frac{w_c}{s}}{\frac{w_a}{s} \frac{w_b}{s}} \frac{\left(\frac{s}{w_c} + 1\right)}{\left(\frac{s}{w_a} + 1\right)\left(\frac{s}{w_b} + 1\right)} \\ &= \frac{A_m w_c s}{w_a w_b} \frac{\left(1 + \frac{s}{w_c}\right)}{\left(1 + \frac{s}{w_a}\right)\left(1 + \frac{s}{w_b}\right)} = \frac{s}{\omega_x} \frac{\left(1 + \frac{s}{\omega_m}\right)}{\left(1 + \frac{s}{\omega_a}\right)\left(1 + \frac{s}{\omega_b}\right)} \end{aligned}$$

conventional  
form  
(normal poles  
and zeros)

Where is  $\omega_x$  on the graph? Where is  $A_m$  in the formula?

$\omega_x$  is not a useful parameter.

Relationships to conventional forms:

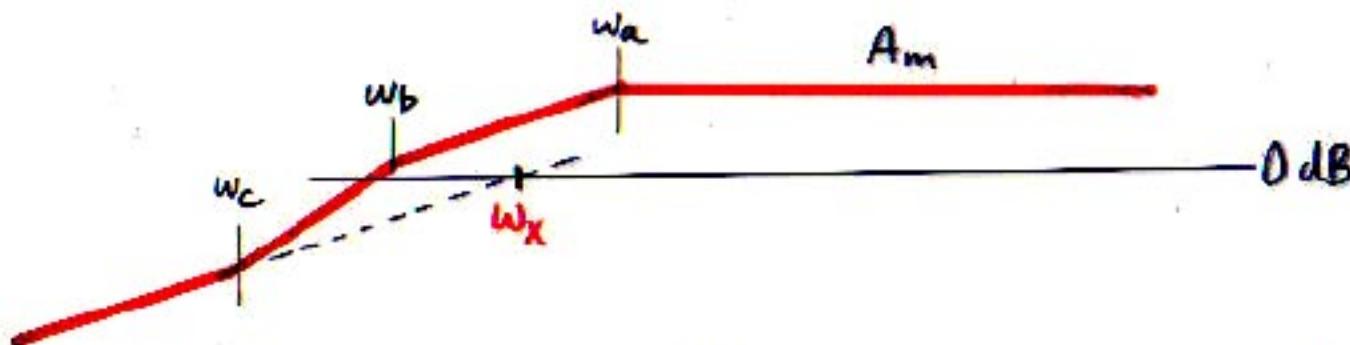


$$\begin{aligned} A &= A_m \frac{\left(1 + \frac{w_c}{s}\right)}{\left(1 + \frac{w_a}{s}\right)\left(1 + \frac{w_b}{s}\right)} = A_m \frac{\frac{w_c}{s}}{\frac{w_a}{s} \frac{w_b}{s}} \frac{\left(\frac{s}{w_c} + 1\right)}{\left(\frac{s}{w_a} + 1\right)\left(\frac{s}{w_b} + 1\right)} \\ &= \frac{A_m w_c s}{w_a w_b} \frac{\left(1 + \frac{s}{w_c}\right)}{\left(1 + \frac{s}{w_a}\right)\left(1 + \frac{s}{w_b}\right)} = \frac{s}{w_x} \frac{\left(1 + \frac{s}{w_c}\right)}{\left(1 + \frac{s}{w_a}\right)\left(1 + \frac{s}{w_b}\right)} \end{aligned}$$

conventional  
form  
(normal poles  
and zeros)

Where is  $w_x$  on the graph? Where is  $A_m$  in the formula?

$w_x$  is not a useful parameter.

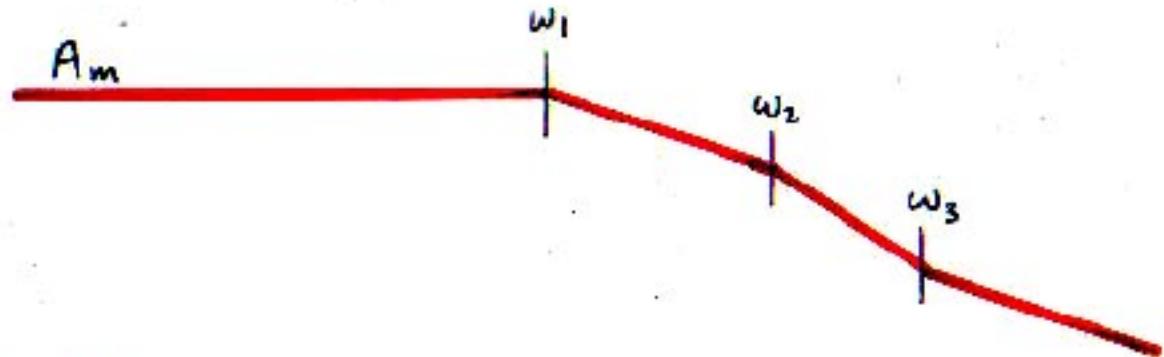


$$\begin{aligned}
 A &= A_m \frac{\left(1 + \frac{s}{\omega_3}\right)}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)} = A_m \frac{\frac{1}{\omega_3}}{\frac{1}{\omega_1} \frac{1}{\omega_2}} \frac{(s + \omega_3)}{(s + \omega_1)(s + \omega_2)} \\
 &= \frac{A_m \omega_1 \omega_2}{\omega_3} \frac{(s + \omega_3)}{(s + \omega_1)(s + \omega_2)} = \omega_y \frac{(s + \omega_3)}{(s + \omega_1)(s + \omega_2)}
 \end{aligned}$$

conventional form

Where is  $\omega_y$  on the graph? Where is  $A_m$  in the formula?

$\omega_y$  is not a useful parameter.

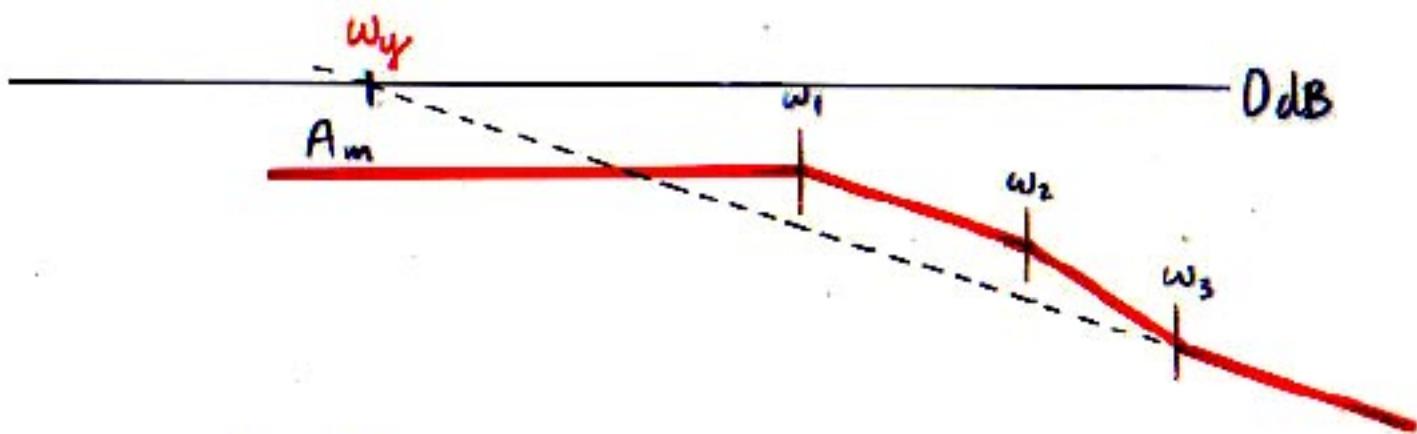

$$\begin{aligned}
 A &= A_m \frac{\left(1 + \frac{s}{\omega_3}\right)}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)} = A_m \frac{\frac{1}{\omega_3}}{\frac{1}{\omega_1} \frac{1}{\omega_2}} \frac{(s + \omega_3)}{(s + \omega_1)(s + \omega_2)} \\
 &= \frac{A_m \omega_1 \omega_2}{\omega_3} \frac{(s + \omega_3)}{(s + \omega_1)(s + \omega_2)} = \omega_y \frac{(s + \omega_3)}{(s + \omega_1)(s + \omega_2)}
 \end{aligned}$$

conventional form

Where is  $\omega_y$  on the graph? Where is  $A_m$  in the formula?

$\omega_y$  is not a useful parameter.

More than one flat gain



$$A = A_1 \frac{1 + \frac{s}{\omega_1}}{1 + \frac{s}{\omega_2}} = A_1 \frac{\omega_2}{\omega_1} \frac{1 + \frac{\omega_1}{s}}{1 + \frac{\omega_2}{s}} = A_2 \frac{1 + \frac{\omega_1}{s}}{1 + \frac{\omega_2}{s}}$$


Hence: "gain-bandwidth tradeoff"

$$\frac{A_2}{A_1} = \frac{\omega_2}{\omega_1}$$

Either flat gain can be used as "reference" gain.

Any flat gain can be used as "reference" gain  $A_{ref}$ .

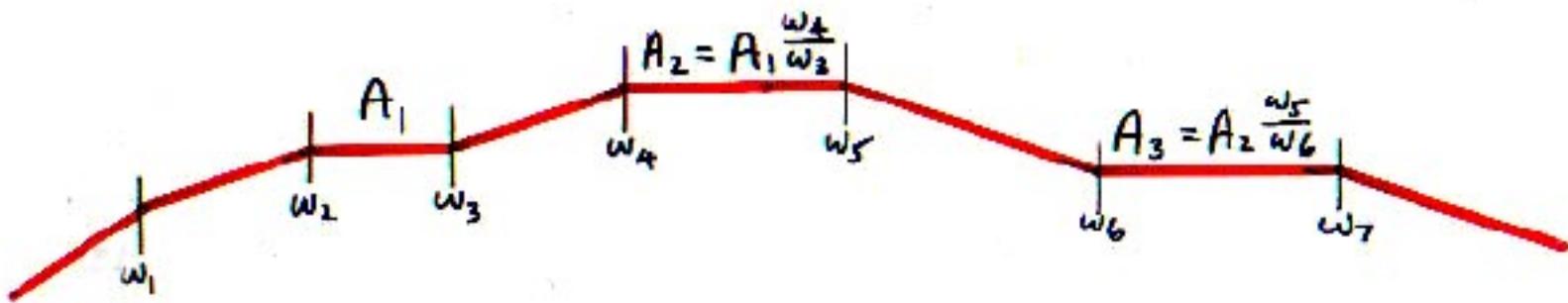With respect to  $A_{ref}$ , poles and zeros above  $A_{ref}$  are normal, those below  $A_{ref}$  are inverted.



$$A = A_1 \frac{(1 + \frac{s}{\omega_3})(1 + \frac{s}{\omega_6})}{(1 + \frac{\omega_2}{s})(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_4})(1 + \frac{s}{\omega_5})(1 + \frac{s}{\omega_7})}$$


$$A = A_2 \frac{(1 + \frac{s}{\omega_3})(1 + \frac{s}{\omega_6})}{(1 + \frac{\omega_4}{s})(1 + \frac{\omega_5}{s})(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_5})(1 + \frac{s}{\omega_7})}$$

$$A = A_3 \frac{(1 + \frac{\omega_6}{s})(1 + \frac{\omega_3}{s})}{(1 + \frac{\omega_7}{s})(1 + \frac{\omega_4}{s})(1 + \frac{\omega_5}{s})(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_7})}$$

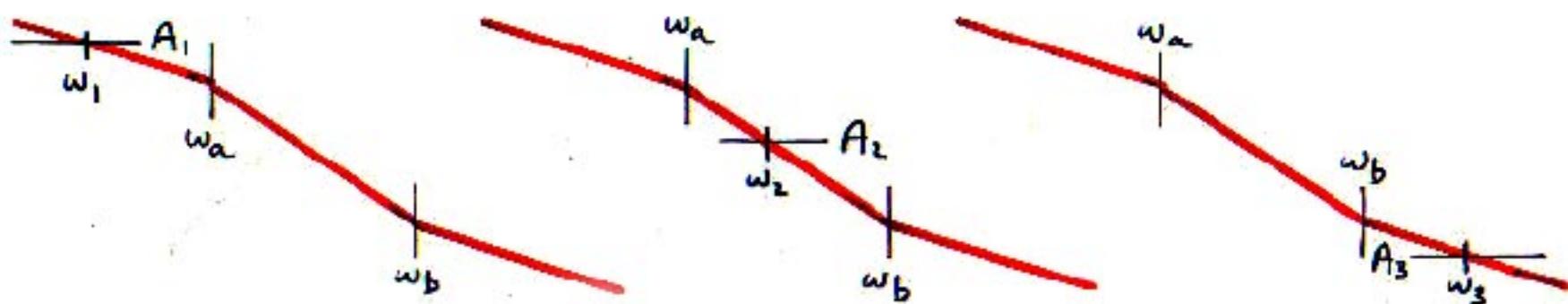Exercise:


No flat gain

Identify the gain at any chosen frequency as "reference" gain



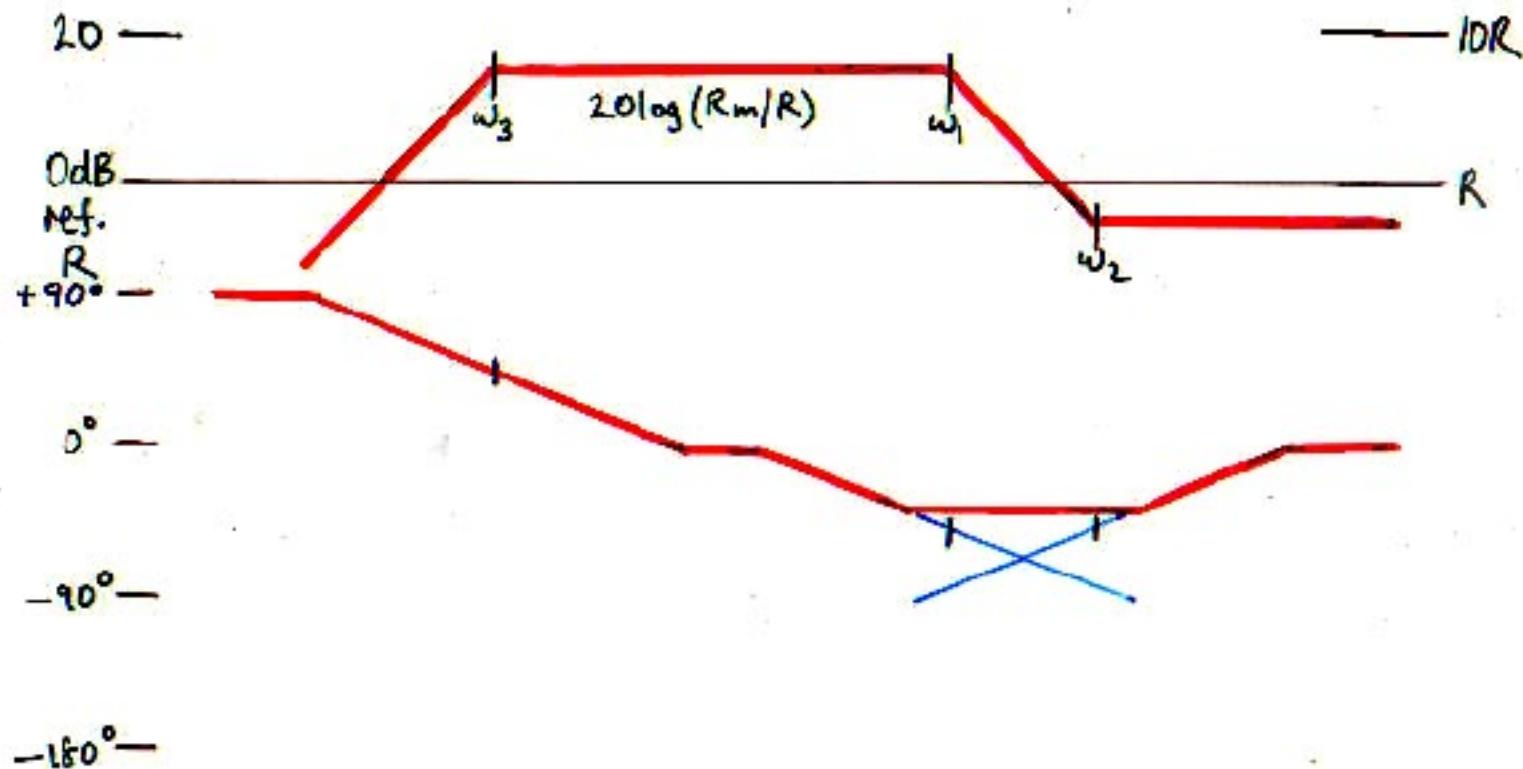
## Impedance asymptotes

$$Z = R_m \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} \frac{1}{1 + \frac{\omega_3}{s}}$$




## Input and output impedances

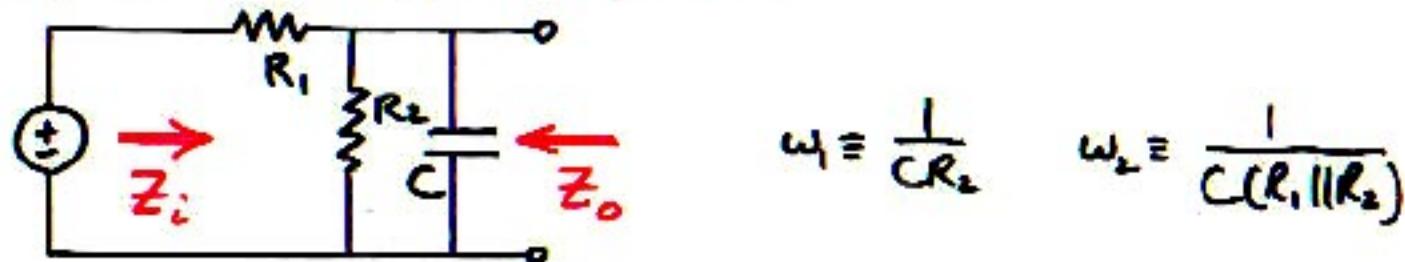

$$\omega_1 = \frac{1}{CR_2} \quad \omega_2 = \frac{1}{C(R_1 \parallel R_2)}$$

$$Z_i = R_1 + \frac{R_2}{1+sCR_2} = (R_1 + R_2) \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} = R_1 \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

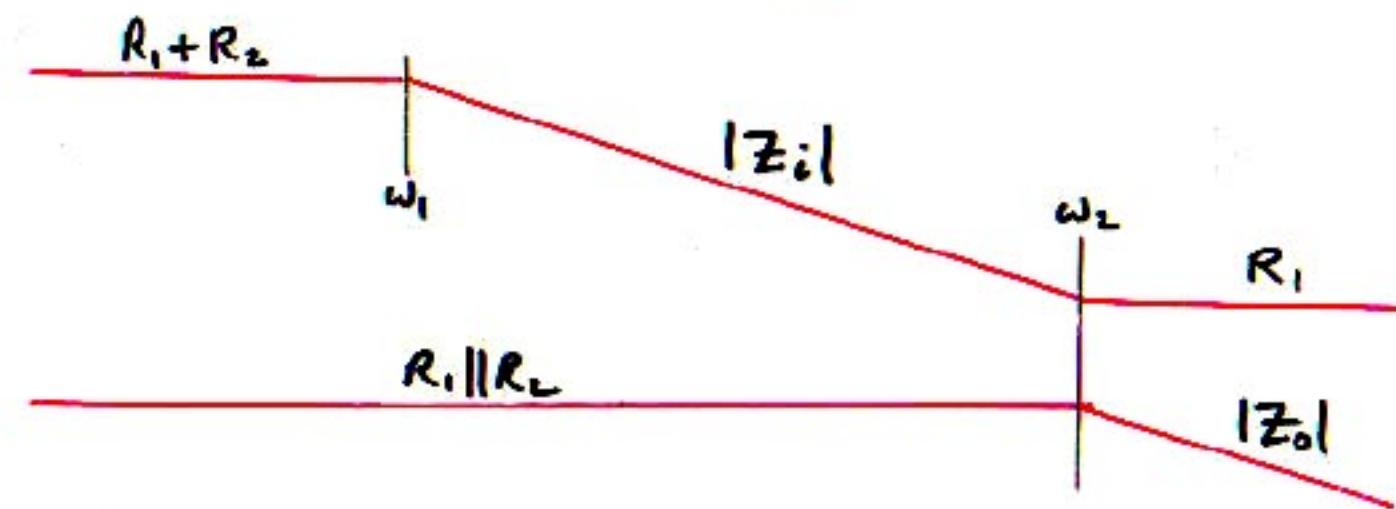
$$Z_o = R_1 \parallel R_2 \parallel \frac{1}{sC} = R_1 \parallel R_2 \frac{1}{1 + \frac{s}{\omega_2}}$$




### Exercise

Find the input and output impedances  $Z_i$  and  $Z_o$  in factored pole-zero form, and sketch the magnitude and phase asymptotes, for each of the two networks:

(a)

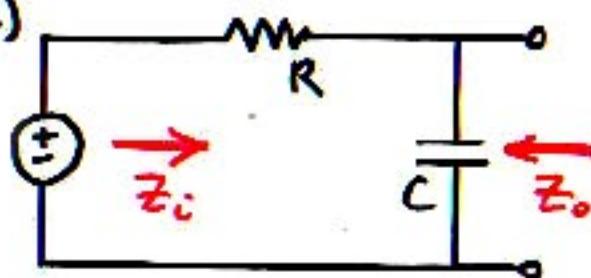


(b)

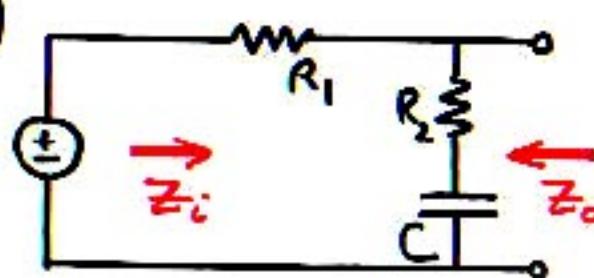
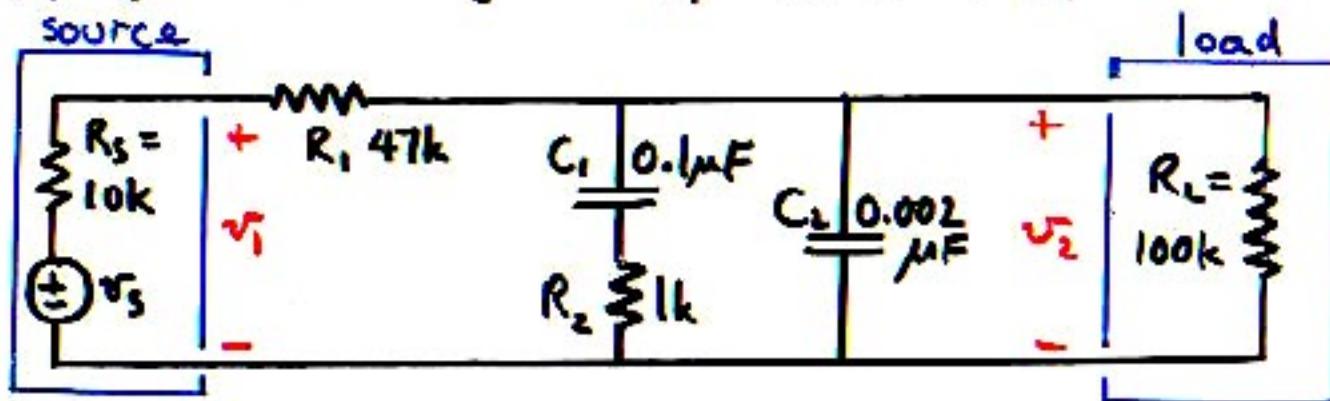
## Example

Analyze the following circuit for the gain response  $v_2/v_1$ , using the given values to justify appropriate analytic approximations:



Express the result in the factored pole-zero form

$$\frac{v_2}{v_1} = A = A_0 \frac{\prod (1 + s/\omega_x)}{\prod (1 + s/\omega_y)}$$

Sketch  $|A|$  and  $\angle A$  showing the straight-line asymptotes, and label salient features with both analytic expressions and numerical values.

$$A = \frac{\frac{\left(\frac{R_L}{1+sC_2R_L}\right)\left(R_2 + \frac{1}{sC_1}\right)}{\frac{R_L}{1+sC_2R_L} + R_2 + \frac{1}{sC_1}}}{\frac{\left(\frac{R_L}{1+sC_2R_L}\right)\left(R_2 + \frac{1}{sC_1}\right)}{\frac{R_L}{1+sC_2R_L} + R_2 + \frac{1}{sC_1}} + R_1}$$

↓  
a lot of algebra

$$= \frac{R_L + sC_1R_2R_L}{[R_1 + R_L] + s[C_1(R_1R_2 + R_LR_2 + R_1R_L) + C_2R_1R_L] + s^2[C_1C_2R_1R_2R_L]}$$

This is a high-entropy expression. To lower the entropy, write the polynomials in  $s$  with a leading term of unity:

$$A = \frac{R_L}{R_1 + R_L} \frac{1 + sC_1 R_2}{1 + s[C_1 \left( \frac{R_1 R_2 + R_L R_2 + R_1 R_L}{R_1 + R_L} \right) + C_2 \left( \frac{R_1 R_L}{R_1 + R_L} \right)] + s^2 [C_1 C_2 \left( \frac{R_1 R_2 R_L}{R_1 + R_L} \right)]}$$

Now, recognize series/  
parallel resistance  
combinations:

$$(R_2 + R_1 \parallel R_L)$$

$$(R_1 \parallel R_L)$$

$$R_2(R_1 \parallel R_L)$$

$$A = \frac{R_L}{R_1 + R_L} \frac{1 + sC_1 R_2}{1 + s[C_1 \left( \frac{R_1 R_2 + R_L R_2 + R_1 R_L}{R_1 + R_L} \right) + C_2 \left( \frac{R_1 R_L}{R_1 + R_L} \right)] + s^2 [C_1 C_2 \left( \frac{R_1 R_2 R_L}{R_1 + R_L} \right)]}$$

Now, recognize series/  
parallel resistance  
combinations:


$$\left( R_2 + R_1 \parallel R_L \right) \quad \left( R_1 \parallel R_L \right) \quad R_2 (R_1 \parallel R_L)$$

The same result, including the series/parallel resistance grouping, could have been obtained with less algebra by elimination, first, of one of the loops of the original circuit.

Circuit with  $R_1$  and  $R_L$  absorbed into a Thvenin equivalent:
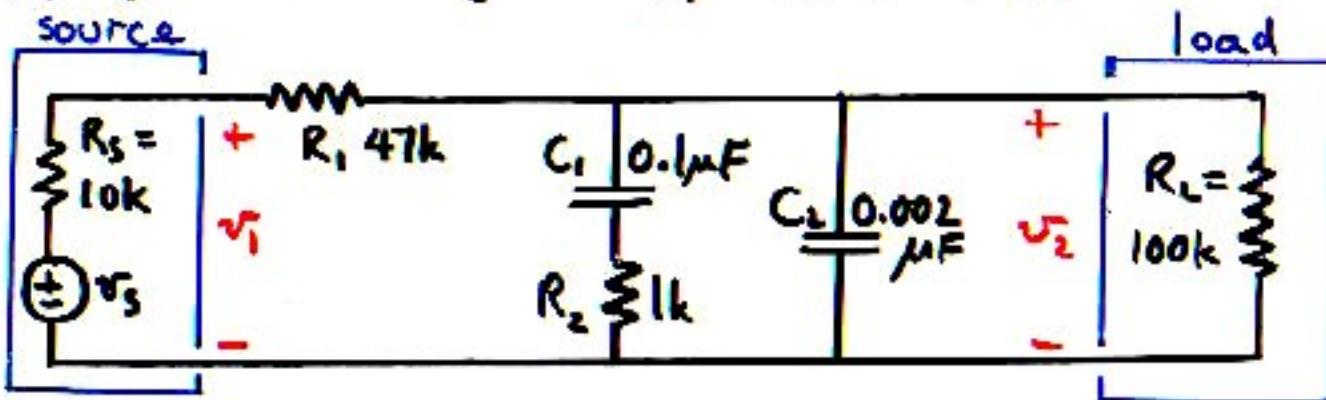
## Example


Analyze the following circuit for the gain response  $v_2/v_1$ , using the given values to justify appropriate analytic approximations:



Express the result in the factored pole-zero form

$$\frac{v_2}{v_1} = A = A_0 \frac{\prod (1 + s/\omega_x)}{\prod (1 + s/\omega_y)}$$

Sketch  $|A|$  and  $\angle A$  showing the straight-line asymptotes, and label salient features with both analytic expressions and numerical values.

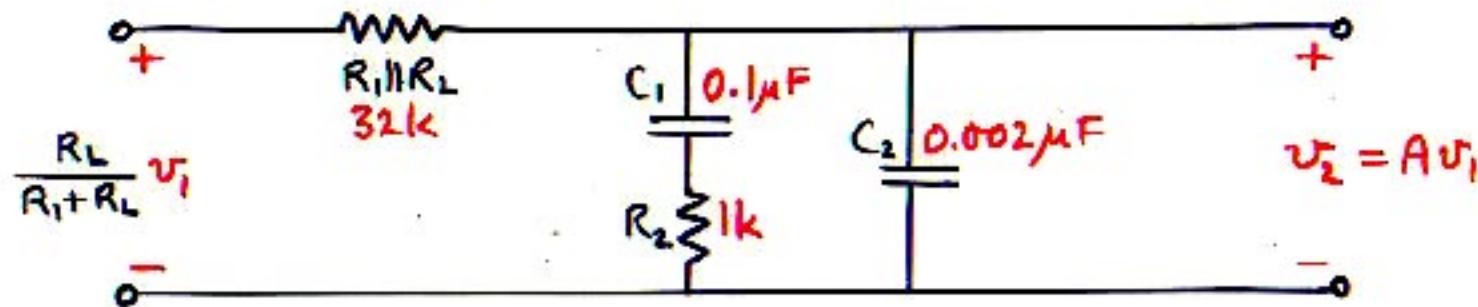


$$A = \frac{\frac{1}{sC_2} \left( R_2 + \frac{1}{sC_1} \right)}{R_2 + \frac{1}{s} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)} \cdot \frac{R_L}{R_1 + R_L}$$

$$\frac{\frac{1}{sC_2} \left( R_2 + \frac{1}{sC_1} \right)}{R_2 + \frac{1}{s} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)} + R_1 \parallel R_L$$

less ↓ algebra
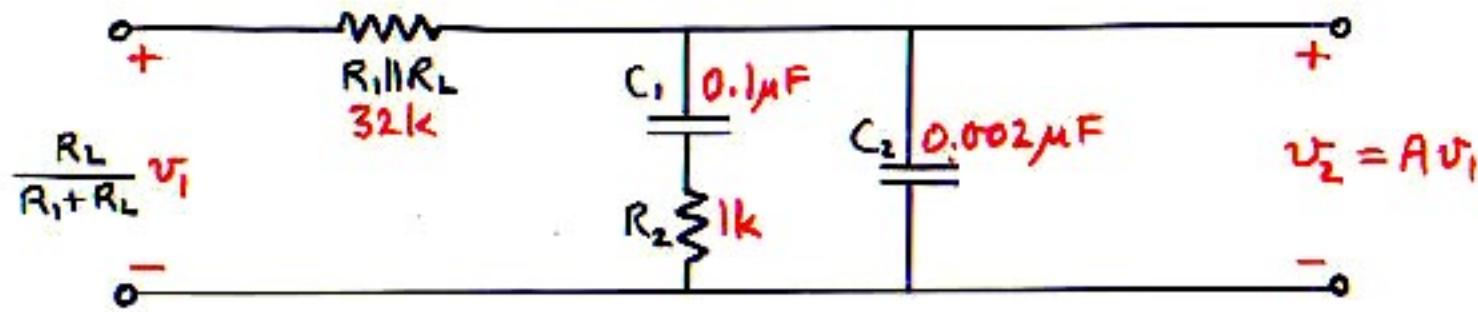
$$= \frac{R_L}{R_1 + R_L} \cdot \frac{1 + sC_1 R_2}{1 + s[C_1(R_2 + R_1 \parallel R_L) + C_2(R_1 \parallel R_L)] + s^2[C_1 C_2 R_2 (R_1 \parallel R_L)]}$$



$$A = \frac{\frac{1}{sC_2} \left( R_2 + \frac{1}{sC_1} \right)}{R_2 + \frac{1}{s} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)} \cdot \frac{R_L}{R_1 + R_L}$$

$$\frac{\frac{1}{sC_2} \left( R_2 + \frac{1}{sC_1} \right)}{R_2 + \frac{1}{s} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)} + R_1 || R_L$$

less ↓ algebra

$$= \frac{R_L}{R_1 + R_L} \cdot \frac{1 + sC_1 R_2}{1 + s[C_1(R_2 + R_1 || R_L) + \cancel{C_2(R_1 || R_L)}] + s^2 [C_1 C_2 R_2 (R_1 || R_L)]}$$

Use of numerical values to justify analytic approximation ↑

$$= A_0 \frac{(1 + \frac{s}{\omega_2})}{(1 + \frac{s}{\omega_1})(1 + \frac{s}{\omega_3})}$$

where

$$\frac{1}{\omega_{1,3}} = \frac{C_1(R_2 + R_1//R_L) \pm \sqrt{C_1^2(R_2 + R_1//R_L)^2 - 4C_1C_2R_2(R_1//R_L)}}{2}$$

This is useless for design, and in any case  
is inaccurate numerically.

## Generalization: Use of Numerical Values to Justify Analytic Approximations

Use numbers to justify leaving out a term, but continue the analysis with the symbols.

This way, the analysis result can be used for design, because the numbers can be changed so that the answer has the desired value.  
(The approximation must be checked to ensure that it is not invalidated by the new numbers.)

## Improved formulas for quadratic roots

$$ax^2 + bx + c = a \left( x^2 + \frac{b}{a}x + \frac{c}{a} \right)$$

$$= a(x - x_1)(x - x_2)$$

$$x_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

Disadvantages of the conventional form

1. Complicated algebraic expressions in terms of element values:

$$\frac{1}{w_{1,3}} = \frac{C_1(R_2 + R_1 || R_L) \pm \sqrt{C_1^2(R_2 + R_1 || R_L)^2 - 4C_1 C_2 R_2(R_1 || R_L)}}{2}$$

2. Computationally inaccurate when  $4ac \ll b^2$ :

$$\frac{1}{w_{1,3}} = 10^{-3} \frac{3.3 \pm \sqrt{3.3^2 - 0.026}}{2}$$

↑  
small difference of large numbers, for one root

Disadvantages of the conventional form:

2. Small difference of large numbers, in some cases:

$$z^2 + bz + 1 = 0; \quad b = 45,000$$

$$z_1 = \frac{-b + \sqrt{b^2 - 4}}{2} \quad z_2 = \frac{-b - \sqrt{b^2 - 4}}{2}$$

1

二

Disadvantages of the conventional form:

2. Small difference of large numbers, in some cases:

$$z^2 + bz + 1 = 0; \quad b = 45,000$$

$$z_{1a} = \frac{-b + \sqrt{b^2 - 4}}{2} \qquad z_2 = \frac{-b - \sqrt{b^2 - 4}}{2}$$

=

=

$$z_{1b} = -\frac{b}{2} \left[ 1 - \sqrt{1 - 4/b^2} \right]$$

=

Disadvantages of the conventional form:

2. Small difference of large numbers, in some cases:

$$z^2 + bz + l = 0; \quad b = 45,000$$

$$z_{1,2} = \frac{-b + \sqrt{b^2 - 4}}{2}$$

$$= -2,000,000,000 \times 10^{-5} \quad = -44,999,999,98$$

$$z_{1b} = -\frac{b}{2} [1 - \sqrt{1 - 4/b^2}]$$

=

HP15C: works with 10 digits, last one rounded.

Disadvantages of the conventional form:

2. Small difference of large numbers, in some cases:

$$z^2 + bz + 1 = 0; \quad b = 45,000$$

$$z_{1a} = \frac{-b + \sqrt{b^2 - 4}}{2}$$

$$= -2,000,000,000 \times 10^{-5} \quad = -44,999.999,98$$

$$z_{1b} = -\frac{b}{2} [1 - \sqrt{1 - 4/b^2}]$$

$$= -2,250,000,000 \times 10^{-5}$$

HPISC: works with 10 digits, last one rounded.

Is  $z_{1a}$  or  $z_{1b}$  the correct answer? Or is neither correct?

Try a third algorithm: successive approximation

$$z^2 + bz + 1 = 0$$

$$bz_1 = -(1+z_1^2)$$

$$z_1 = -\frac{1}{b}(1+z_1^2)$$

Since  $b \gg 1$ , then  $z_1 \ll 1$ , so:

$$z_1 \approx -\frac{1}{b}\left(1+\frac{1}{b^2}\right) = -\frac{1}{b} - \frac{1}{b^3}$$

$$= -2.222,222,222, \times 10^{-5}$$
$$-0.000,000,001,097,393,690 \times 10^{-5}$$

So, the correct answer is

$z_1 = -2.222,222,222 \times 10^{-5}$  correct to 9 significant figures.

Note that:

$$\frac{z_{1a}}{z_1} - 1 = \frac{-2,000,000,000}{-2.222,222,222} - 1 = -10\%$$

$$\frac{z_{1b}}{z_1} - 1 = \frac{-2,250,000,000}{-2.222,222,222} - 1 = +1.25\%$$

$b$	$Z_{1a}$ error	$Z_{1b}$ error
42,000	5.00%	5.84%
43,000	7.50%	1.70%
44,000	10.0%	6.48%
45,000	-10.0%	1.25%
46,000	-8.00%	5.60%
47,000	-6.00%	-5.99%
48,000	-4.00%	3.68%
49,000	-2.00%	8.05%
50,000	0%	0%
51,000	2.00%	4.04%

Conclusions:

- (a) The correct result was obtained with use of an algebraic approximation, whereas the incorrect results were obtained without an algebraic approximation.
- (b) The numerical error introduced depends on the algebraic format. (Small difference of large numbers)

Hence, need a better algebraic format for the roots of a quadratic.

Better method:

$$x_2 = \frac{-b - \sqrt{b^2 - 4ac}}{2a} = -\frac{b}{a} \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2} \right] = -\frac{b}{a} F$$

where

$$F \equiv \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}, \quad Q^2 \equiv \frac{ac}{b^2}$$

$$\begin{aligned} x_1 &= \frac{-b + \sqrt{b^2 - 4ac}}{2a} = -\frac{b}{a} \left[ \frac{1}{2} - \frac{1}{2} \sqrt{1 - 4Q^2} \right] \\ &= -\frac{b}{a} \frac{\left[ \frac{1}{2} - \frac{1}{2} \sqrt{1 - 4Q^2} \right] \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2} \right]}{\left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2} \right]} = -\frac{b}{a} \frac{\frac{1}{4} - \frac{1}{4}(1 - 4Q^2)}{F} \\ &= -\frac{b}{a} \frac{Q^2}{F} = -\frac{c}{b} \frac{1}{F} \end{aligned}$$

Better method:

$$x_2 = \frac{-b - \sqrt{b^2 - 4ac}}{2a} = -\frac{b}{a} \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2} \right] = -\frac{b}{a} F$$

where

$$F \equiv \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}, \quad Q^2 \equiv \frac{ac}{b^2}$$

$$\begin{aligned} x_1 &= \frac{-b + \sqrt{b^2 - 4ac}}{2a} = -\frac{b}{a} \left[ \frac{1}{2} - \frac{1}{2} \sqrt{1 - 4Q^2} \right] \\ &= -\frac{b}{a} \frac{\left[ \frac{1}{2} - \frac{1}{2} \sqrt{1 - 4Q^2} \right] \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2} \right]}{\left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2} \right]} = -\frac{b}{a} \frac{\frac{1}{4} - \frac{1}{4}(1 - 4Q^2)}{F} \\ &= -\frac{b}{a} \frac{Q^2}{F} = -\frac{c}{b} \frac{1}{F} \end{aligned}$$

Crucial step: Large numbers are subtracted exactly, leaving the small difference in analytic form.

Hence, both roots can be computed with equal accuracy:

$$x_1 = -\frac{c}{b} \frac{1}{F} \quad x_2 = -\frac{b}{a} F$$

Rewrite the two roots:

$$x_1 = \frac{-b + \sqrt{b^2 - 4ac}}{2a}$$

$$x_2 = \frac{-b - \sqrt{b^2 - 4ac}}{2a}$$

$x_2$  is acceptable for all values;  $x_1$  is unacceptable for  $4ac < b^2$ .

Rewrite  $x_2$ :

$$x_2 = -\frac{b}{a} \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - \frac{4ac}{b^2}} \right]$$

Now, instead of using the formula for  $x_1$  directly, use the property of the quadratic that  $x_1 x_2 = \frac{c}{a}$ :

$$x_1 = \frac{c}{a} \frac{1}{x_2} = -\frac{c}{a} \frac{a}{b} \frac{1}{\frac{1}{2} + \frac{1}{2} \sqrt{1 - \frac{4ac}{b^2}}}$$

Thus, the improved formulas for the quadratic roots are:

$$x_1 = -\frac{c}{b} \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - \frac{4ac}{b^2}} \right]$$

$$x_2 = -\frac{b}{a} \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - \frac{4ac}{b^2}} \right]$$

## Improved formulas for quadratic roots

$$\begin{aligned} ax^2 + bx + c &= a \left( x^2 + \frac{b}{a}x + \frac{c}{a} \right) \quad \leftarrow \\ &= a(x - x_1)(x - x_2) \quad \rightarrow \\ x_{1,2} &= \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \end{aligned}$$

Rewrite the two roots:

$$x_1 = \frac{-b + \sqrt{b^2 - 4ac}}{2a}$$

$$x_2 = \frac{-b - \sqrt{b^2 - 4ac}}{2a}$$

$x_2$  is acceptable for all values;  $x_1$  is unacceptable for  $4ac < b^2$ .

Rewrite  $x_2$ :

$$x_2 = -\frac{b}{a} \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - \frac{4ac}{b^2}} \right]$$

Now, instead of using the formula for  $x_1$  directly, use the property of the quadratic that  $x_1 x_2 = \frac{c}{a}$ :

$$x_1 = \frac{c}{a} \frac{1}{x_2} = -\frac{c}{a} \frac{a}{b} \frac{1}{\frac{1}{2} + \frac{1}{2} \sqrt{1 - \frac{4ac}{b^2}}}$$

Thus, the improved formulas for the quadratic roots are:

$$x_1 = -\frac{c}{b} \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - \frac{4ac}{b^2}} \right]$$

$$x_2 = -\frac{b}{a} \left[ \frac{1}{2} + \frac{1}{2} \sqrt{1 - \frac{4ac}{b^2}} \right]$$

More elegant form:

$$x_1 = -\frac{c}{b} \frac{1}{F} \quad \frac{x_1}{x_2} = \frac{Q^2}{F^2} \quad x_2 = -\frac{b}{a} F$$

where

$$F \equiv \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2} \quad \text{in which} \quad Q^2 \equiv \frac{ac}{b^2}$$

More elegant form:

$$x_1 = -\frac{c}{b} \frac{1}{F} \quad \frac{x_1}{x_2} = \frac{Q^2}{F^2} \quad x_2 = -\frac{b}{a} F$$

simple ratios of the original quadratic coefficients

where

$$F \equiv \frac{1}{2} + \frac{1}{2}\sqrt{1-4Q^2} \text{ in which } Q^2 \equiv \frac{ac}{b^2}$$

More elegant form:

$$x_1 = -\frac{c}{b} \frac{1}{F} \quad \frac{x_1}{x_2} = \frac{Q^2}{F^2} \quad x_2 = -\frac{b}{a} F$$

simple ratios of the original quadratic coefficients

where

$$F \equiv \frac{1}{2} + \frac{1}{2}\sqrt{1-4Q^2} \text{ in which } Q^2 \equiv \frac{ac}{b^2}$$

This is exact for all values.

If  $Q > 0.5$ ,  $F$  is complex  $\Rightarrow$  complex roots

If  $Q < 0.5$ ,  $F$  is real  $\Rightarrow$  real roots

If  $Q \approx 0.5$ ,  $F \approx 1$

Note how simple the analytic roots, and therefore  
the quadratic factorization, become if  $F \approx 1$ .

More elegant form:


$$x_1 = -\frac{c}{b} \frac{1}{F} \quad \frac{x_1}{x_2} = \frac{Q^2}{F^2} \quad x_2 = -\frac{b}{a} F$$

simple ratios of the original quadratic coefficients

where

$$F \equiv \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2} \text{ in which } Q^2 \equiv \frac{ac}{b^2}$$

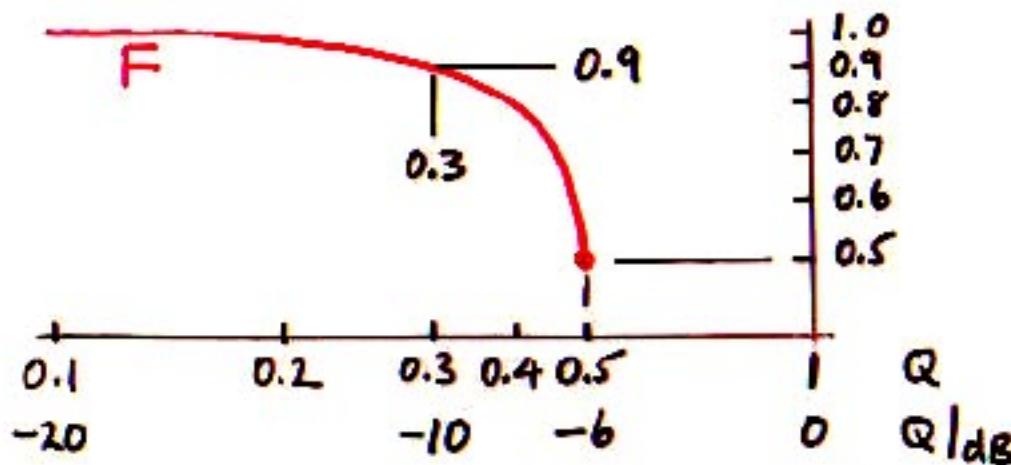$F \rightarrow 1$  very rapidly as  $Q$  drops below 0.5:



$F \approx 1$  with 10% error for  $Q \leq 0.3$

General result:

$$\begin{aligned} ax^2 + bx + c &= a\left(x^2 + \frac{b}{a}x + \frac{c}{a}\right) \\ &= a(x - x_1)(x - x_2) \\ &= a\left(x + \frac{c}{b}F\right)\left(x + \frac{b}{a}F\right) \end{aligned}$$

where

$$F \equiv \frac{1}{2} + \frac{1}{2}\sqrt{1 - \frac{4ac}{b^2}}$$

$$x_1 = -\frac{c}{b}F$$

$$x_2 = -\frac{b}{a}F$$

General result:

$$ax^2 + bx + c = a\left(x^2 + \frac{b}{a}x + \frac{c}{a}\right)$$

$$= a(x - x_1)(x - x_2)$$

$$= a\left(x + \frac{c}{b} - \frac{1}{F}\right)\left(x + \frac{b}{a}F\right)$$

Good approximation  
for real roots,  $Q = \sqrt{\frac{ac}{b^2}} \leq 0.5$ :  
 $F \approx 1$

$$\stackrel{F=1}{\approx} a\left(x + \frac{c}{b}\right)\left(x + \frac{b}{a}\right)$$

where

$$F \equiv \frac{1}{2} + \frac{1}{2}\sqrt{1 - \frac{4ac}{b^2}}$$

$$x_1 = -\frac{c}{b} - \frac{1}{F} \approx -\frac{c}{b}$$

$$x_2 = -\frac{b}{a}F \approx -\frac{b}{a}$$

Alternative format:

$$\begin{aligned} ax^2 + bx + c &= c \left(1 + \frac{b}{c}x + \frac{a}{c}x^2\right) \\ &= c \left(1 - \frac{x}{x_1}\right) \left(1 - \frac{x}{x_2}\right) \\ &= c \left(1 + \frac{b}{c}Fx\right) \left(1 + \frac{a}{b} \frac{1}{F}x\right) \end{aligned}$$

where

$$F = \frac{1}{2} + \frac{1}{2}\sqrt{1 - 4Q^2}$$

$$Q^2 = \frac{ac}{b^2}$$

Alternative format:

$$\begin{aligned} ax^2 + bx + c &= c \left( 1 + \frac{b}{c}x + \frac{a}{c}x^2 \right) \\ &= c \left( 1 - \frac{x}{x_1} \right) \left( 1 - \frac{x}{x_2} \right) \\ &= c \left( 1 + \frac{b}{c}Fx \right) \left( 1 + \frac{a}{b} \frac{1}{F}x \right) \end{aligned}$$

where

$$F \equiv \frac{1}{2} + \frac{1}{2}\sqrt{1-4Q^2}$$

$$Q^2 \equiv \frac{ac}{b^2}$$

Redefine coefficients:

$$\begin{aligned} 1 + a_1 x + a_2 x^2 &= \left( 1 - \frac{x}{x_1} \right) \left( 1 - \frac{x}{x_2} \right) \\ &= \left( 1 + a_1 Fx \right) \left( 1 + \frac{a_2}{a_1} \frac{1}{F}x \right) \end{aligned}$$

where

$$F \equiv \frac{1}{2} + \frac{1}{2}\sqrt{1-4Q^2}$$

$$Q^2 \equiv \frac{a_2}{a_1^2}$$

Alternative format:

$$\begin{aligned} ax^2 + bx + c &= c \left( 1 + \frac{b}{c}x + \frac{a}{c}x^2 \right) \\ &= c \left( 1 - \frac{x}{x_1} \right) \left( 1 - \frac{x}{x_2} \right) \\ &= c \left( 1 + \frac{b}{c}Fx \right) \left( 1 + \frac{a}{b}\frac{1}{F}x \right) \stackrel{F=1}{\approx} c \left( 1 + \frac{b}{c}x \right) \left( 1 + \frac{a}{b}x \right) \end{aligned}$$

Good approximation  
for real roots,  $|Q| \leq 0.5$ :  
 $F \approx 1$

where

$$F = \frac{1}{2} + \frac{1}{2}\sqrt{1-4Q^2}$$

$$Q^2 = \frac{ac}{b^2}$$

Redefine coefficients:

$$\begin{aligned} 1 + a_1x + a_2x^2 &= \left( 1 - \frac{x}{x_1} \right) \left( 1 - \frac{x}{x_2} \right) \\ &= \left( 1 + a_1Fx \right) \left( 1 + \frac{a_2}{a_1} \frac{1}{F}x \right) \stackrel{F=1}{\approx} \left( 1 + a_1x \right) \left( 1 + \frac{a_2}{a_1}x \right) \end{aligned}$$

where

$$F = \frac{1}{2} + \frac{1}{2}\sqrt{1-4Q^2}$$

$$Q^2 = \frac{a_2}{a_1^2}$$

## Generalization: Improved Formulas for Roots of a Quadratic

$$F \equiv \frac{1}{2} + \frac{1}{2}\sqrt{1 - 4Q^2}$$

$$Q^2 \equiv \frac{ac}{b^2}$$

$$Q^2 \equiv \frac{a_2}{a_1^2}$$

$$ax^2 + bx + c = a(x - x_1)(x - x_2)$$

$$x_1 = -\frac{c}{b} \frac{1}{F}$$

$$x_2 = -\frac{b}{a} F$$

$$1 + a_1 x + a_2 x^2 = \left(1 - \frac{x}{x_1}\right) \left(1 - \frac{x}{x_2}\right)$$

$$x_1 = -\frac{1}{a_1 F}$$

$$x_2 = -\frac{a_1}{a_2} F$$

$$ax^2 + bx + c = a\left(x + \frac{c}{b} \frac{1}{F}\right)\left(x + \frac{b}{a} F\right)$$

$$1 + a_1 x + a_2 x^2 = (1 + a_1 F x)(1 + \frac{a_2}{a_1} \frac{1}{F} x)$$

For real roots,  $Q \leq 0.5$  and  $F \approx 1$ :

$$x_1 \approx -\frac{c}{b}$$

$$\frac{x_1}{x_2} \approx Q^2$$

$$x_1 \approx -\frac{1}{a_1}$$

$$x_2 \approx -\frac{b}{a}$$

$$x_2 \approx -\frac{a_1}{a_2}$$

$$ax^2 + bx + c \approx a\left(x + \frac{c}{b}\right)\left(x + \frac{b}{a}\right)$$

①    ②    ③

③/②    ②/①

$$1 + a_1 x + a_2 x^2 \approx (1 + a_1 x)(1 + \frac{a_2}{a_1} x)$$

①    ②    ③    ②/①    ③/②

Advantages over the conventional formulas

1. Both roots can be computed with equal accuracy  
(avoids small difference of large numbers).
2. For real roots, to a very good approximation,  
there is no  $\sqrt{\quad}$  anywhere in the results,  
and each root is a simple ratio of  
coefficients of the original quadratic.

Useful format of quadratic  $1+a_1s+a_2s^2$

Define:  $Q \equiv \frac{\sqrt{a_2}}{a_1}$

If  $Q > 0.5$  ( $F$  complex), roots are complex.

Leave in quadratic form:

$$1+a_1s+a_2s^2 = 1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}s) + (\sqrt{a_2}s)^2$$

$\frac{1}{Q} \nearrow$        $\nwarrow$  normalized frequency

If  $Q < 0.5$  ( $F \approx 1$ ), roots are real.

Factor into two real roots:  $\nearrow$  real corner frequencies

$$\begin{aligned} 1+a_1s+a_2s^2 &\approx (1+a_1s)\left(1+\frac{a_2}{a_1}s\right) \\ &= \left[1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}s)\right] \left[1 + \frac{\sqrt{a_2}}{a_1} (\sqrt{a_2}s)\right] \\ &\quad \frac{1}{Q} \nearrow \quad Q \nearrow \quad \nwarrow \text{normalized frequency} \end{aligned}$$

Exercise:

Find, both analytically and numerically, the Q and hence the roots  $\omega_1$  and  $\omega_3$  of the quadratic:

$$1 + C_1 [R_2 + R_1 \parallel R_L] s + [C_1 C_2 R_2 (R_1 \parallel R_L)] s^2$$

where  $C_1 = 0.1\mu F$ ,  $C_2 = 0.002\mu F$ ,  $R_1 = 47k$ ,  $R_2 = 1k$ ,  $R_L = 100k$ . Express the analytic results in terms of series/parallel element combinations, and express the numerical results in Hz or kHz.

Exercise:

Find, both analytically and numerically, the Q and hence the roots  $\omega_1$  and  $\omega_3$  of the quadratic:

$$1 + \underbrace{C_1 [R_2 + R_1 \parallel R_L]}_{a_1} s + \underbrace{[C_1 C_2 R_2 (R_1 \parallel R_L)]}_{a_2} s^2$$

where  $C_1 = 0.1 \mu F$ ,  $C_2 = 0.002 \mu F$ ,  $R_1 = 47k$ ,  $R_2 = 1k$ ,  $R_L = 100k$ . Express the analytic results in terms of series/parallel element combinations, and express the numerical results in Hz or kHz.

$$Q^2 = \frac{a_2}{a_1^2} = \frac{C_1 C_2 R_2 (R_1 \parallel R_L)}{C_1^2 (R_2 + R_1 \parallel R_L)^2} = \frac{C_2}{C_1} \frac{R_2 \parallel R_1 \parallel R_L}{\cancel{R_2} + \cancel{R_1} \parallel \cancel{R_L}} \approx \frac{C_2}{C_1} \frac{R_2}{R_1 \parallel R_L} = \frac{1}{50} \frac{1}{47 \parallel 100} = \frac{1}{1,600}$$

Hence,  $F = \frac{1}{2} + \frac{1}{2}\sqrt{1 - 4Q^2} \approx 1$ , so the roots are real: ( $F = 0.9994$ )  $Q = \frac{1}{40} \ll 0.5$

$$\omega_1 = \frac{1}{a_1} = \frac{1}{C_1 (R_2 + R_1 \parallel R_L)} \quad f_1 = \frac{159}{0.1 (1 + \frac{47 \parallel 100}{32})} \text{ Hz} = 48 \text{ Hz}$$

$$\begin{aligned} \omega_3 &= \frac{a_1}{a_2} = \frac{C_1 (R_2 + R_1 \parallel R_L)}{C_1 C_2 R_2 (R_1 \parallel R_L)} \\ &= \frac{1}{C_2 (R_2 \parallel R_1 \parallel R_L)} \quad f_3 = \frac{159}{0.002 (\underbrace{1 \parallel 32}_{0.97})} \text{ Hz} = 82 \text{ kHz} \end{aligned}$$

Hence

$$A \approx \frac{R_L}{R_L + R_1} \frac{1 + sC_1R_2}{[1 + C_1(R_2 + R_1 \parallel R_L)s][1 + C_2(R_1 \parallel R_2 \parallel R_L)s]}$$
$$= A_0 \frac{\left(1 + \frac{s}{\omega_3}\right)}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

where

$$A_0 = \frac{R_L}{R_L + R_1}$$

$$\omega_1 = \frac{1}{C_1(R_2 + R_1 \parallel R_L)}$$

$$\omega_2 = \frac{1}{C_1 R_2}$$

$$\omega_3 = \frac{1}{C_2(R_1 \parallel R_2 \parallel R_L)}$$

Hence

$$A \approx \frac{R_L}{R_L + R_1} \frac{1 + sC_1R_2}{[1 + C_1(R_2 + R_1||R_L)s][1 + C_2(R_1||R_2||R_L)s]}$$
$$= A_0 \frac{\left(1 + \frac{s}{\omega_3}\right)}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

where

$$A_0 = \frac{R_L}{R_L + R_1} = \frac{100}{100+47} = 0.68 \Rightarrow -3.4 \text{ dB}$$

$$\omega_1 = \frac{1}{C_1(R_2 + R_1||R_L)} \quad f_1 = \frac{159}{0.1(1 + \frac{47||100}{32})} = 48 \text{ Hz}$$

$$\omega_2 = \frac{1}{C_1R_2} \quad f_2 = \frac{159}{0.1 \times 1} = 1.6 \text{ kHz}$$

$$\omega_3 = \frac{1}{C_2(R_1||R_2||R_L)} \quad f_3 = \frac{159}{0.002(47||1||100)} = 82 \text{ kHz}$$

The conventional quadratic formula for the two poles  $w_1$  and  $w_3$  is much higher entropy (gives much less useful information) than does the modified formula.

Conventional:

$$\frac{1}{w_{1,3}} = \frac{C_1(R_2 + R_1 \parallel R_L) \pm \sqrt{C_1^2(R_2 + R_1 \parallel R_L)^2 - 4C_1C_2R_2(R_1 \parallel R_L)}}{2}$$


Modified:

$$w_1 = \frac{1}{C_1(R_2 + R_1 \parallel R_L)} \quad w_3 = \frac{1}{C_2(R_1 \parallel R_2 \parallel R_L)}$$



Note, in particular, (when the two roots are real and well-separated) that the modified formula is much lower entropy and not only gives both roots with equal numerical accuracy, but also exposes the fact that  $C_1$  affects only  $w_1$  and  $C_2$  affects only  $w_3$  — which is useful information for design purposes.


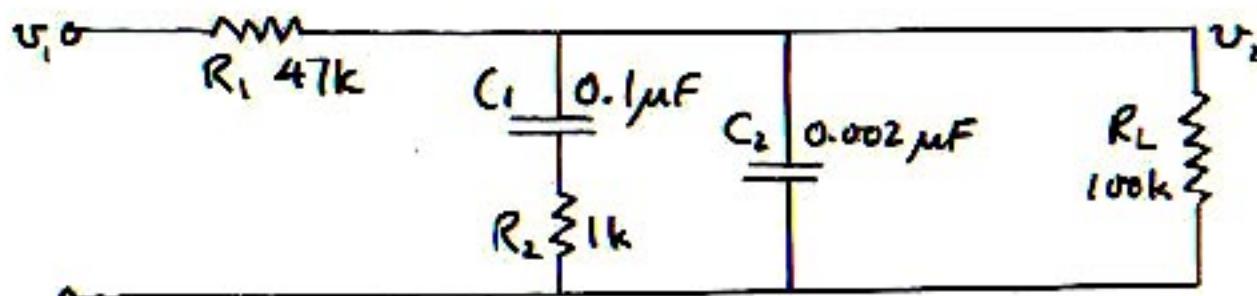
## A still better solution

Look at the original circuit and consider response as frequency increases:




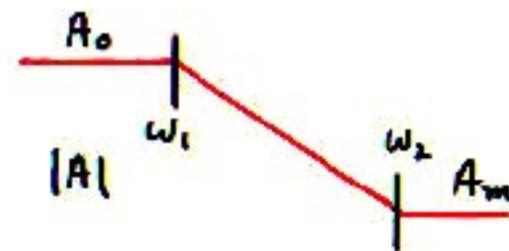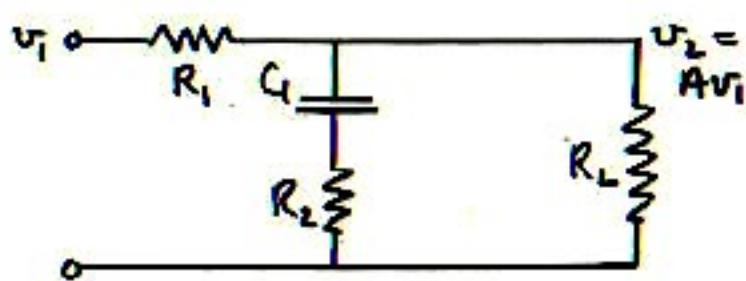At low frequencies, both capacitances are open, so have flat response. As frequency increases, the reactance of  $C_1$ , the larger capacitance, comes down causing a pole. When the reactance of  $C_1$  drops below  $R_2$ , the response flattens causing a zero. However, at this frequency the reactance of  $C_2$  is still 50 times higher than  $R_2$ , so  $C_2$  has negligible effect.




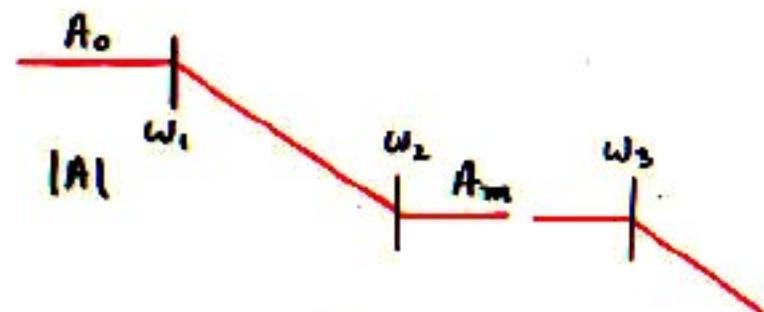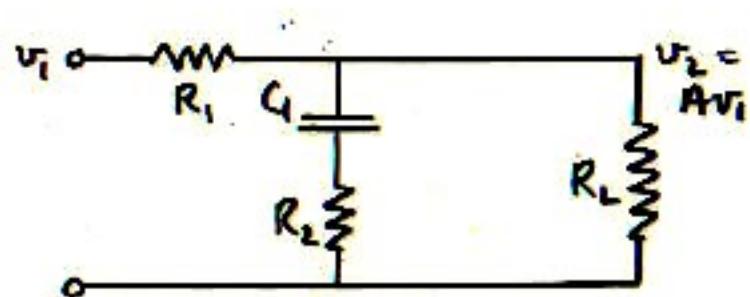

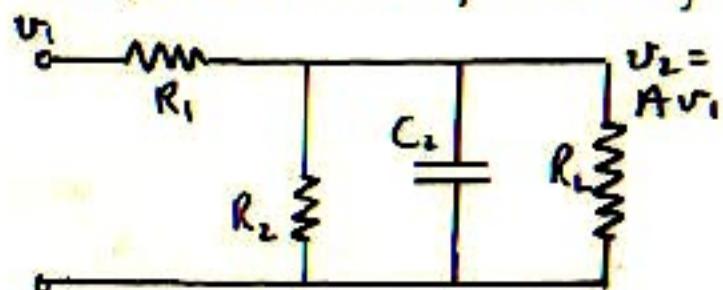At still higher frequencies, the reactance of  $C_2$  drops below  $R_2$ , causing a second pole



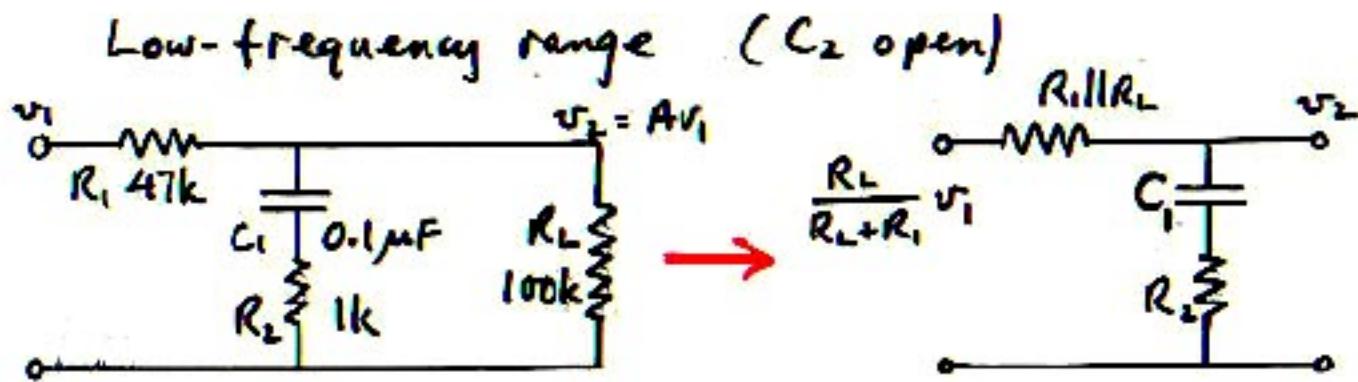Hence, the solution can be obtained in two parts, each containing only one reactance (one pole).



$$A = \frac{R_L}{R_L + R_1} \frac{R_2 + \frac{1}{sC_1}}{R_2 + \frac{1}{sC_1} + R_2 || R_L} = A_0 \frac{1 + \frac{\omega_2}{\omega_1}}{1 + \frac{\omega_2}{\omega_1}} = A_m \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

where


$$A_0 = \frac{R_L}{R_L + R_1} = \frac{100}{100 + 47} = 0.68 \Rightarrow -3.4 \text{ dB}$$

$$\omega_1 = \frac{1}{C_1 (R_2 + R_2 || R_L)} \quad f_1 = \frac{159}{0.1 (1 + \underbrace{47 || 100}_{32})} = 4.8 \text{ Hz}$$

$$\omega_2 = \frac{1}{C_1 R_2} \quad f_2 = \frac{159}{0.1 \times 1} = 1.6 \text{ kHz}$$

$$A_m = A_0 \frac{\omega_1}{\omega_2} = \frac{R_L}{R_L + R_1} \cdot \frac{R_2}{R_2 + R_2 || R_L} = 0.68 \frac{0.048}{1.6} = 0.02 \Rightarrow -34 \text{ dB}$$

High-frequency range ( $C_1$  short)


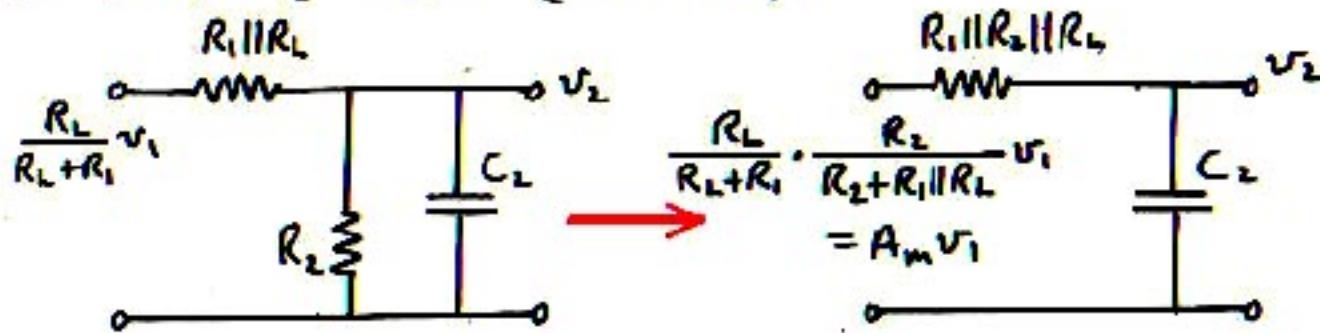


$$A = A_m \frac{1}{1 + \frac{s}{\omega_3}} \quad \text{where} \quad \omega_3 = \frac{1}{C_2 (R_1 || R_L || R_L)}$$

$$f_3 = \frac{159}{0.002(47 || 1 || 100)} = 82 \text{ kHz}$$

Hence, overall response is
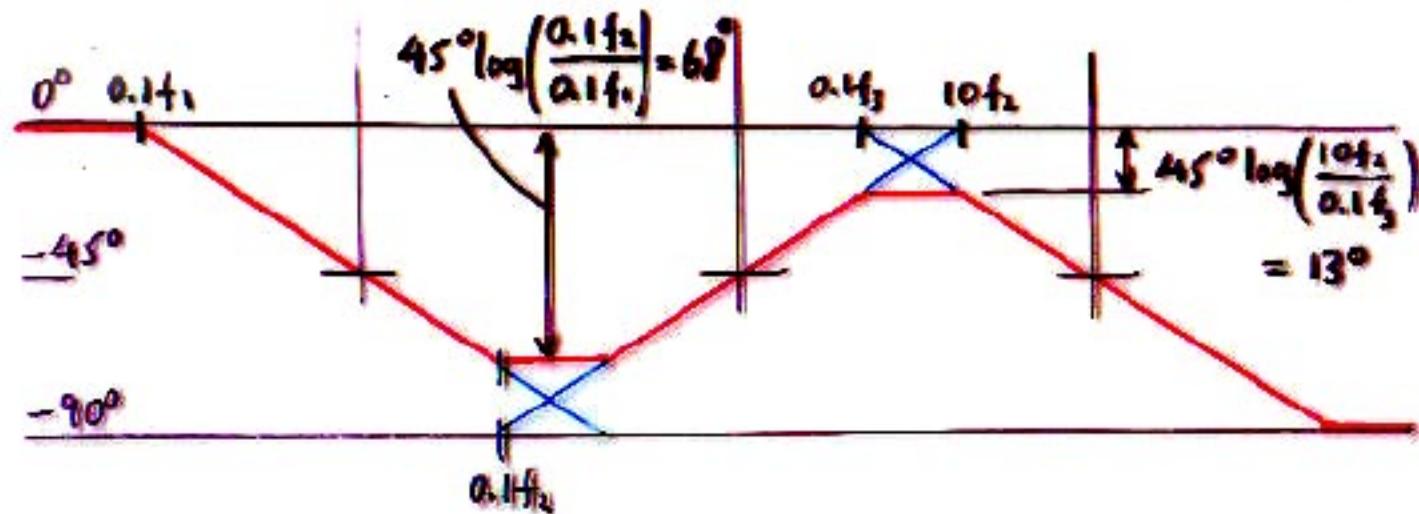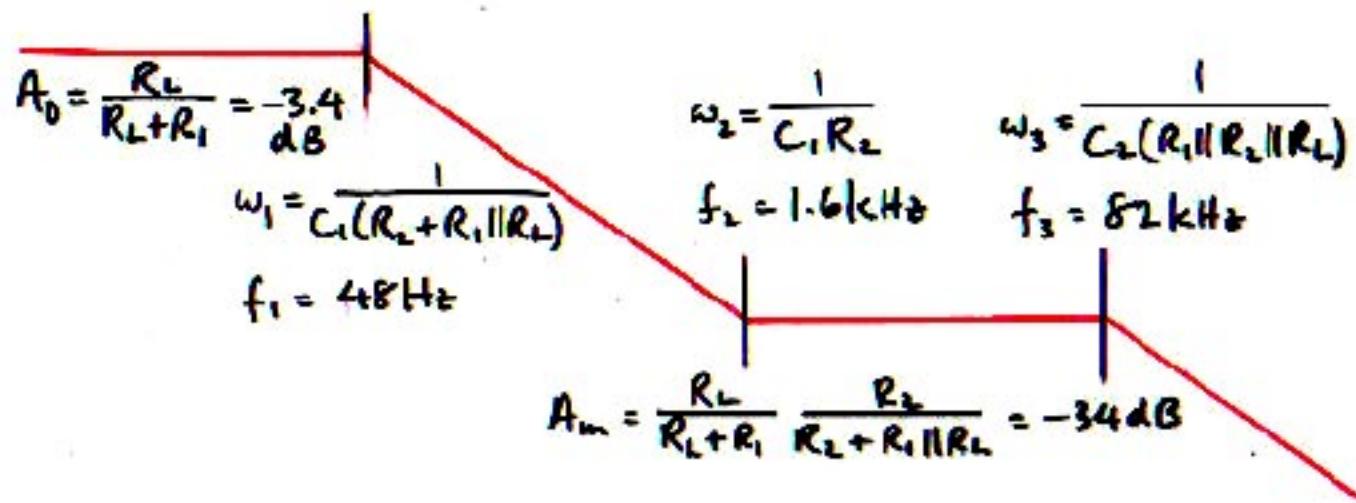
$$A = A_0 \frac{\left(1 + \frac{s}{\omega_2}\right)}{\left(1 + \frac{s}{\omega_1}\right) \left(1 + \frac{s}{\omega_3}\right)} = A_m \frac{\left(1 + \frac{\omega_2}{s}\right)}{\left(1 + \frac{\omega_1}{s}\right) \left(1 + \frac{s}{\omega_3}\right)}$$



$$= A_0 \frac{(1 + \frac{s}{\omega_2})}{(1 + \frac{s}{\omega_1})(1 + \frac{s}{\omega_3})}$$

where

$$\frac{1}{\omega_{1,3}} = \frac{C_1(R_2 + R_1//R_L) \pm \sqrt{C_1^2(R_2 + R_1//R_L)^2 - 4C_1C_2R_2(R_1//R_L)}}{2}$$

This is useless for design, and in any case  
is inaccurate numerically.

## Generalization: Presentation of Results

Sketch magnitude and phase by straight-line asymptotes, and label salient features (flat gains, corner frequencies, Q's, etc.) with both analytic expressions and numerical values.

This is a compact summary so that both the analytic and numerical results can be interpreted at a glance, which is especially useful for reports, design reviews, etc. so that managers can easily and quickly see and understand the results obtained by others.

For design, the element values that must be changed to give different numerical results can easily be seen.