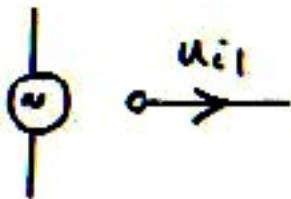


# **6**

**NULL DOUBLE INJECTION (NDI)**  
**AND THE**  
**EXTRA ELEMENT THEOREM (EET)**

## Null Double Injection


Consider a system with a single injected (input) signal  $u_{i1}$ , and two dependent (output) signals  $u_{o1}, u_{o2}$ :



$$u_{o1} = A_1 u_{i1}$$

$$u_{o2} = B_1 u_{i1}$$

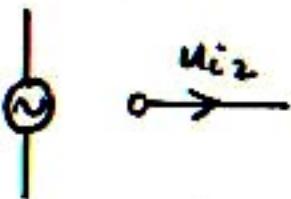Consider a second injected signal  $u_{i2}$  which alone would give:



$$u_{o1} = A_2 u_{i2}$$

$$u_{o2} = B_2 u_{i2}$$

If the system is linear, in general each output is a linear sum of the outputs due to each input:

$$u_{i1}$$
  


$$u_{o1} = A_1 u_{i1} + A_2 u_{i2}$$
  


$$u_{i2}$$
  


$$u_{o2} = B_1 u_{i1} + B_2 u_{i2}$$
  


Note definition of "gains":

$$\frac{u_{o1}}{u_{i1}} \Big|_{u_{i2}=0} = A_1$$

$$\frac{u_{o1}}{u_{i2}} \Big|_{u_{i1}=0} = A_2$$

$$\frac{u_{o2}}{u_{i1}} \Big|_{u_{i2}=0} = B_1$$

$$\frac{u_{o2}}{u_{i2}} \Big|_{u_{i1}=0} = B_2$$

By adjustment of  $u_{i2}$  relative to  $u_{i1}$  (in magnitude and phase), either output can be nullled:

For example, if  $u_{o1}$  is nullled:

$$0 = A_1 u_{i1} + A_2 u_{i2} \Big|_{u_{o1}=0}$$

$$u_{o2} = B_1 u_{i1} + B_2 u_{i2} \Big|_{u_{o1}=0}$$


By elimination of  $u_{i1}$ :

$$\frac{u_{o2}}{u_{i2}} \Big|_{u_{o1}=0} = \frac{A_1 B_2 - A_2 B_1}{A_1}$$

Notice the difference from

$$\frac{u_{o2}}{u_{i2}} \Big|_{u_{i1}=0} = B_2$$

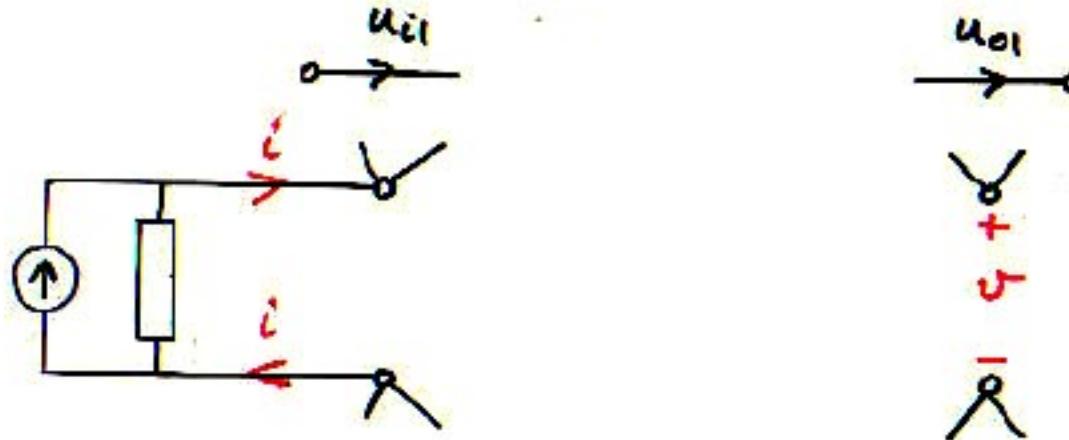Particular example:  $u_{i_2} = i$ ,  $u_{o_2} = v$ :



$$u_{o_1} = A_1 u_{i_1} + A_2 i$$

$$v = B_1 u_{i_1} + B_2 i$$


So

$$\frac{v}{i} \Big|_{u_{i_1}=0} = B_2$$

$$\frac{v}{i} \Big|_{u_{o_1}=0} = \frac{A_1 B_2 - A_2 B_1}{A_1}$$

Special case: the Extra Element Theorem

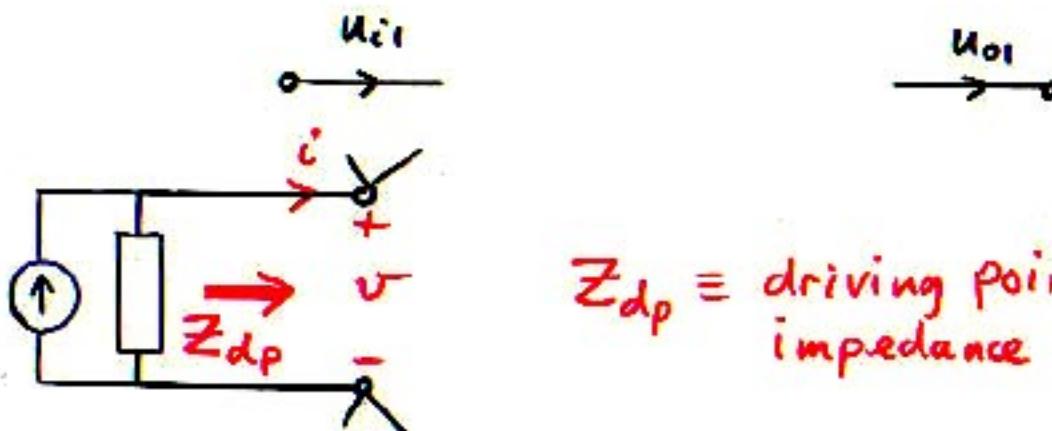The second output  $v$  is across the second input terminals:



$Z_{dp}$  = driving point impedance

Then

$$\frac{v}{i} \Big|_{u_{ii}=0} = Z_{dp} \Big|_{u_{ii}=0} \equiv Z_d = B_2$$

$$\frac{v}{i} \Big|_{u_{oi}=0} = Z_{dp} \Big|_{u_{oi}=0} \equiv Z_n = \frac{A_1 B_2 - A_2 B_1}{A_1}$$

Consider the original circuit without  $u_{cz} = i$ :



$$u_{ci}$$

$$u_{oi}$$



$$\text{Original gain} = A_1 = \frac{u_{oi}}{u_{ci}} \Big|_{u_{cz}=0}$$

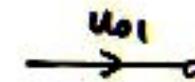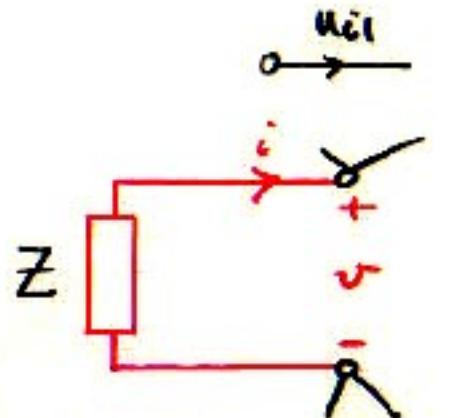Consider the original circuit without  $u_{i2} = i$ :



$$\text{Original gain} = A_1 = \frac{u_{o1}}{u_{i1}} \Big|_{u_{i2}=0}$$

Now consider the circuit with an extra element  $Z$ :

$$i = -\frac{v}{Z}$$

$$\text{So } u_{o1} = A_1 u_{i1} - \frac{A_2}{Z} v$$

$$v = B_1 u_{i1} - \frac{B_2}{Z} v$$

Eliminate  $v$ :

$$u_{o1} = A_1 \frac{1 + \frac{1}{Z} \frac{A_1 B_2 - A_2 B_1}{A_1}}{1 + \frac{1}{Z} B_2} u_{i1}$$

Hence

$$u_{o1} = A_1 \frac{1 + \frac{Z_n}{Z}}{1 + \frac{Z_d}{Z}} u_{i1}$$

or

$$\text{gain}|_Z = \text{gain}|_{Z=\infty} \frac{1 + \frac{Z_n}{Z}}{1 + \frac{Z_d}{Z}}$$

This is the Extra Element Theorem: how to calculate the gain, after an extra element is added, by a correction factor instead of starting from scratch.

Hence

$$u_{o1} = A_1 \frac{1 + \frac{Z_N}{Z}}{1 + \frac{Z_d}{Z}} u_{i1}$$

or

$$\text{gain}|_Z = \text{gain}|_{Z=\infty} \frac{1 + \frac{Z_N}{Z}}{1 + \frac{Z_d}{Z}}$$

This is the Extra Element Theorem: how to calculate the gain, after an extra element is added, by a correction factor instead of starting from scratch.

The Theorem also proves that any transfer function (e.g. gain) of a linear system is a bilinear function of any single element (e.g.  $Z$ ).

forming  $\Delta_{11}$  the terms by which  $z$  is multiplied must be the minor  $\Delta_{11,jj}$  obtained by omitting both the first and  $j$ th rows and columns. If we let  $\Delta^0$  and  $\Delta_{11}^0$  represent, respectively,  $\Delta$  and  $\Delta_{11}$  when  $z = 0$ , therefore, we have

$$Z = \frac{\Delta^0 + z\Delta_{jj}}{\Delta_{11}^0 + z\Delta_{11,jj}}. \quad (I-11)$$

Since  $\Delta_{jj}$  and  $\Delta_{11,jj}$  are evidently independent of  $z$  they can equally well be written as  $\Delta_{jj}^0$  and  $\Delta_{11,jj}^0$ . This will occasionally be done in later analysis in order to facilitate further transformations.

The relation between  $Z_T$  and  $z$  can be found in similar fashion. It is given by

$$Z_T = \frac{\Delta^0 + z\Delta_{jj}}{\Delta_{12}^0 + z\Delta_{12,jj}}. \quad (I-12)$$

If  $z$  represents a unilateral coupling term, instead of a bilateral element, the expansion is essentially the same. Thus, if we suppose that  $z$  is a part of  $Z_{ij}$  in the original determinant, we readily find

$$Z = \frac{\Delta^0 + z\Delta_{ij}}{\Delta_{11}^0 + z\Delta_{11,ij}} \quad (I-13)$$

and

$$Z_T = \frac{\Delta^0 + z\Delta_{ij}}{\Delta_{12}^0 + z\Delta_{12,ij}}. \quad (I-14)$$

The "brute-force" method: loop analysis


$$(R_s + R_B) i_1 - R_B \cdot i_B = v_1$$

$$-R_B i_1 + [R_B + (1+\beta)r_E] i_B = 0$$

$$i_B = \frac{\begin{vmatrix} R_s + R_B & v_1 \\ -R_B & 0 \end{vmatrix}}{\begin{vmatrix} R_s + R_B & -R_B \\ -R_B & R_B + (1+\beta)r_E \end{vmatrix}} \frac{R_B v_1}{}$$

$$= \frac{(R_s + R_B)[R_B + (1+\beta)r_E] - R_B^2}{R_B v_1}$$
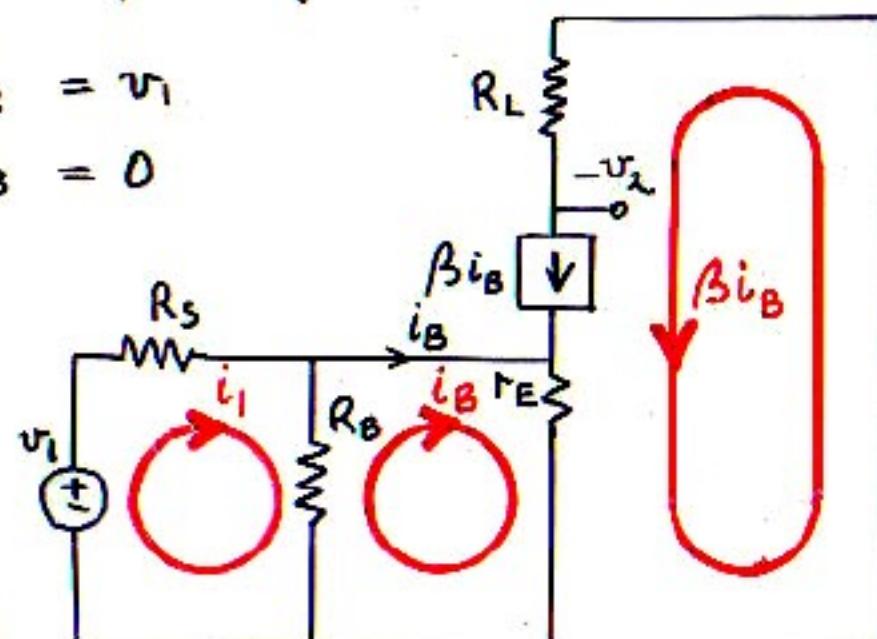
$$= \frac{R_s R_B + (1+\beta)r_E R_s + R_B^2 + (1+\beta)r_E R_B - R_B^2}{R_s R_B + (1+\beta)r_E R_s + R_B^2 + (1+\beta)r_E R_B - R_B^2}$$



Finally,  $v_2 = R_L \beta i_B$

which leads to:

$$A_m = \frac{v_2}{v_1} = \frac{\beta R_B R_L}{(1+\beta)r_E R_s + (1+\beta)r_E R_B + R_s R_B}$$

Implementation:


All that is needed is to calculate the driving point impedance across the terminals to which the extra element is to be added, under two conditions:

$$Z_d = Z_{dp} \Big|_{u_{i1}=0} \quad (\text{original input zero})$$

$$Z_n = Z_{dp} \Big|_{u_{o1}=0} \quad (\text{original output nulled})$$

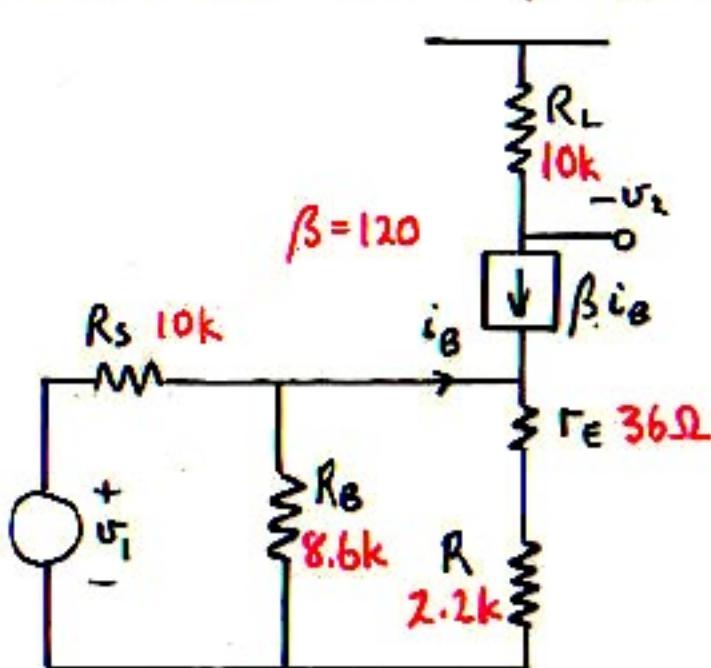
Example: The previously designed CE amplifier

Suppose the gain has been calculated without the emitter bypass capacitance, and the correction factor resulting from addition of the extra element  $Z \rightarrow 1/sC_2$  is desired.




Original gain :

$$A_o = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_e + (R_s || R_B)/(1+\beta)}$$
$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$
$$= 2.0 \Rightarrow 6\text{dB}$$

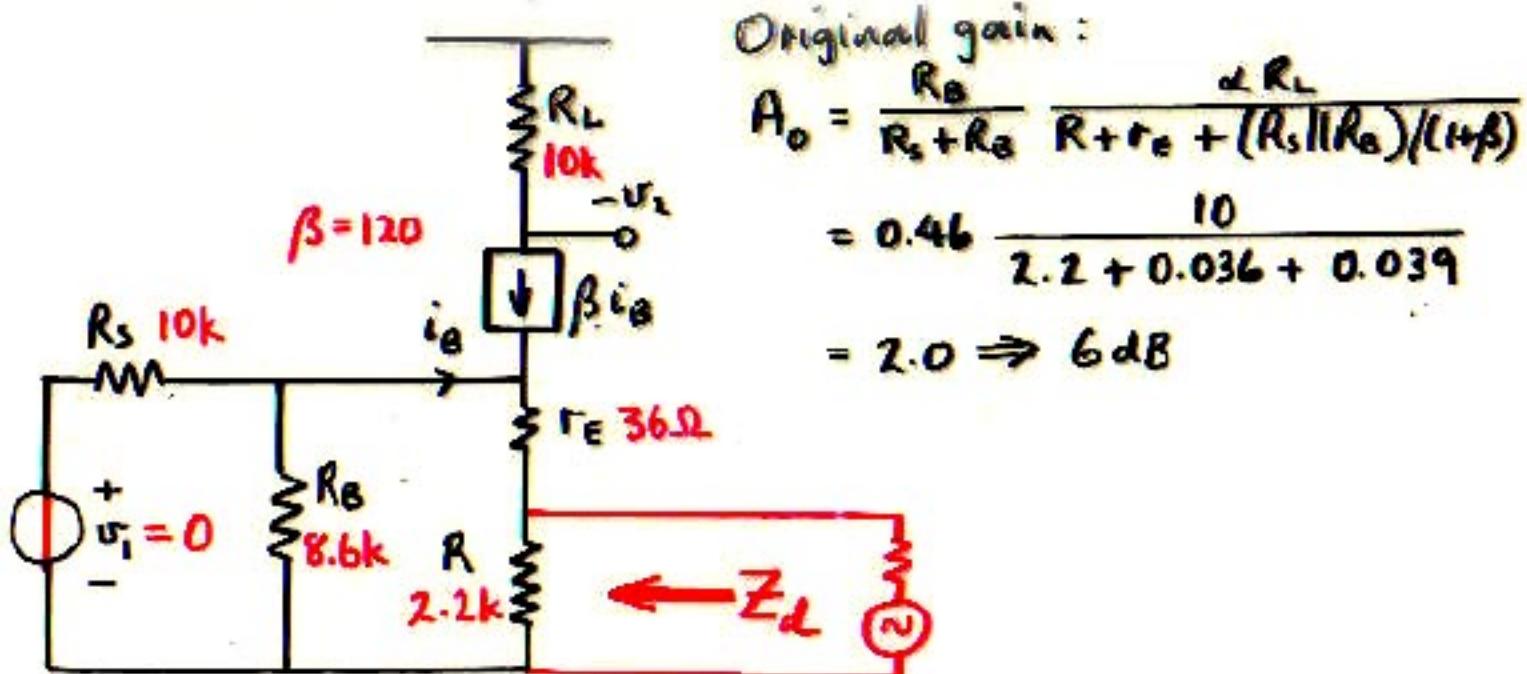


Step 1. Calculate  $Z_d$  by shorting  $u_{c1} = u_i$ , and applying a second injected signal across  $R$ :


$$\begin{aligned} Z_d &= R_d = R \parallel [r_E + (R_s || R_B)/(1+\beta)] \\ &= 2.2 \parallel [0.036 + \underbrace{(10 \parallel 8.6)/120}_{0.039}] \\ &= 75.52 \end{aligned}$$

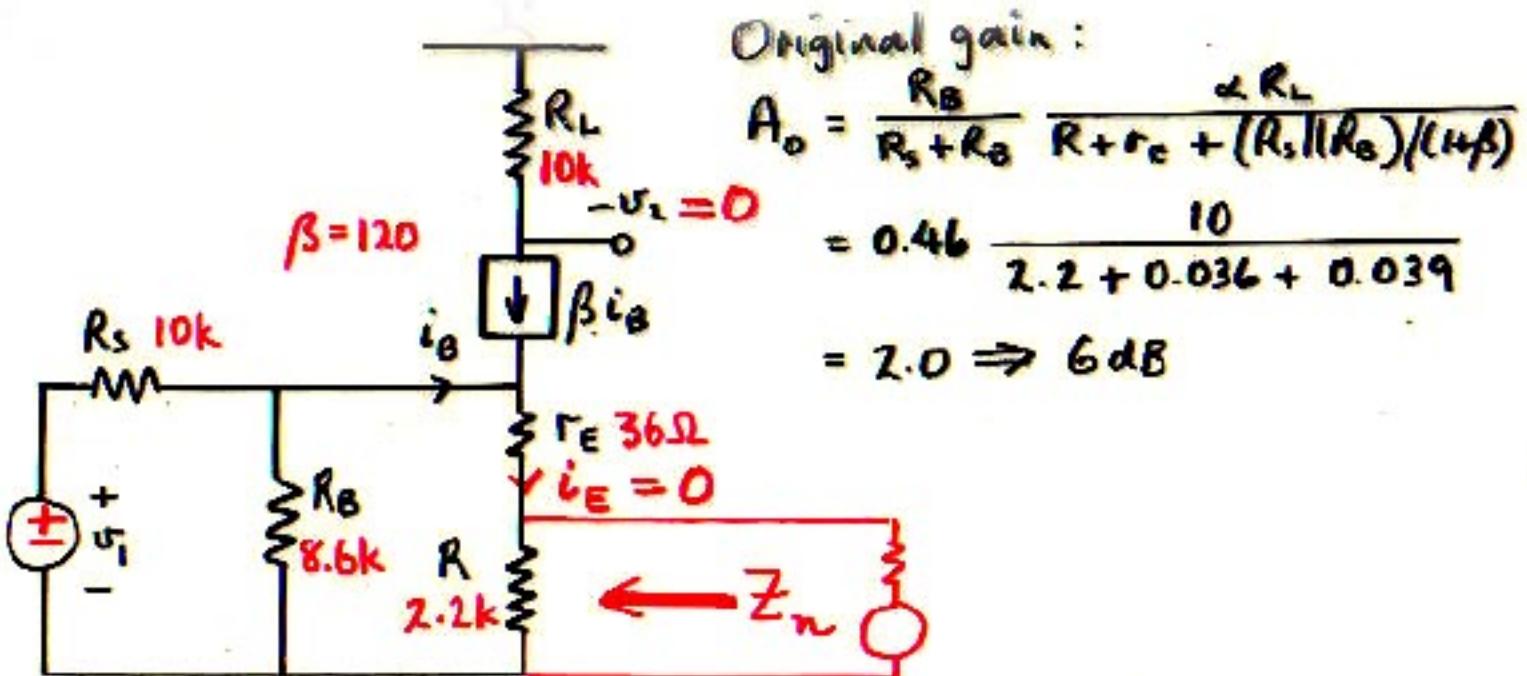


Step 2. Calculate  $Z_n$  by applying a second injected signal across  $R$ , and adjusting it with respect to  $v_i$  to null  $v_{o1} = v_2 = 0$ . Then, since  $v_2 = 0$ ,  $i_E = 0$ , hence:

$$Z_n = R_n = R = 2.2\text{k}$$

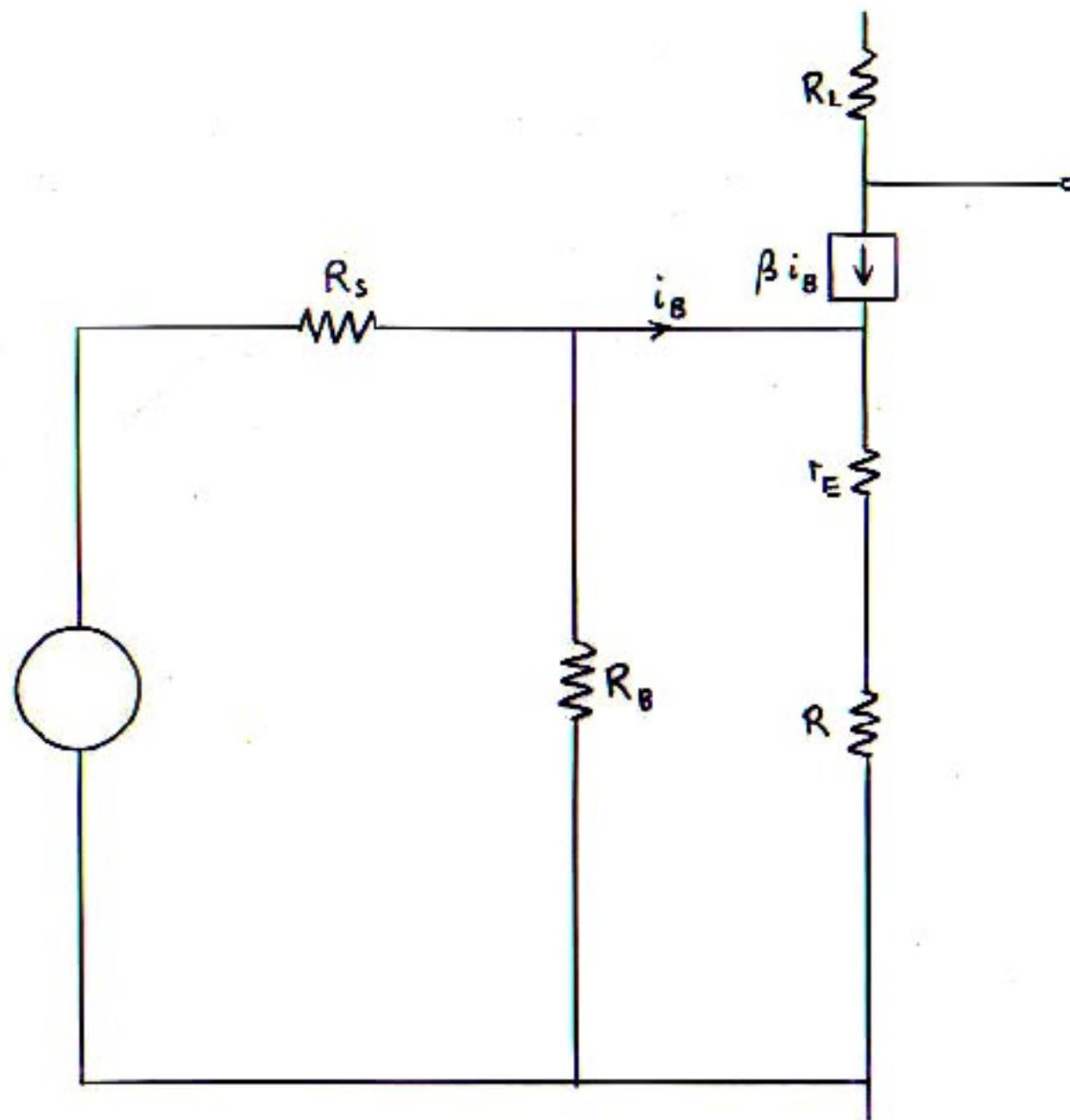


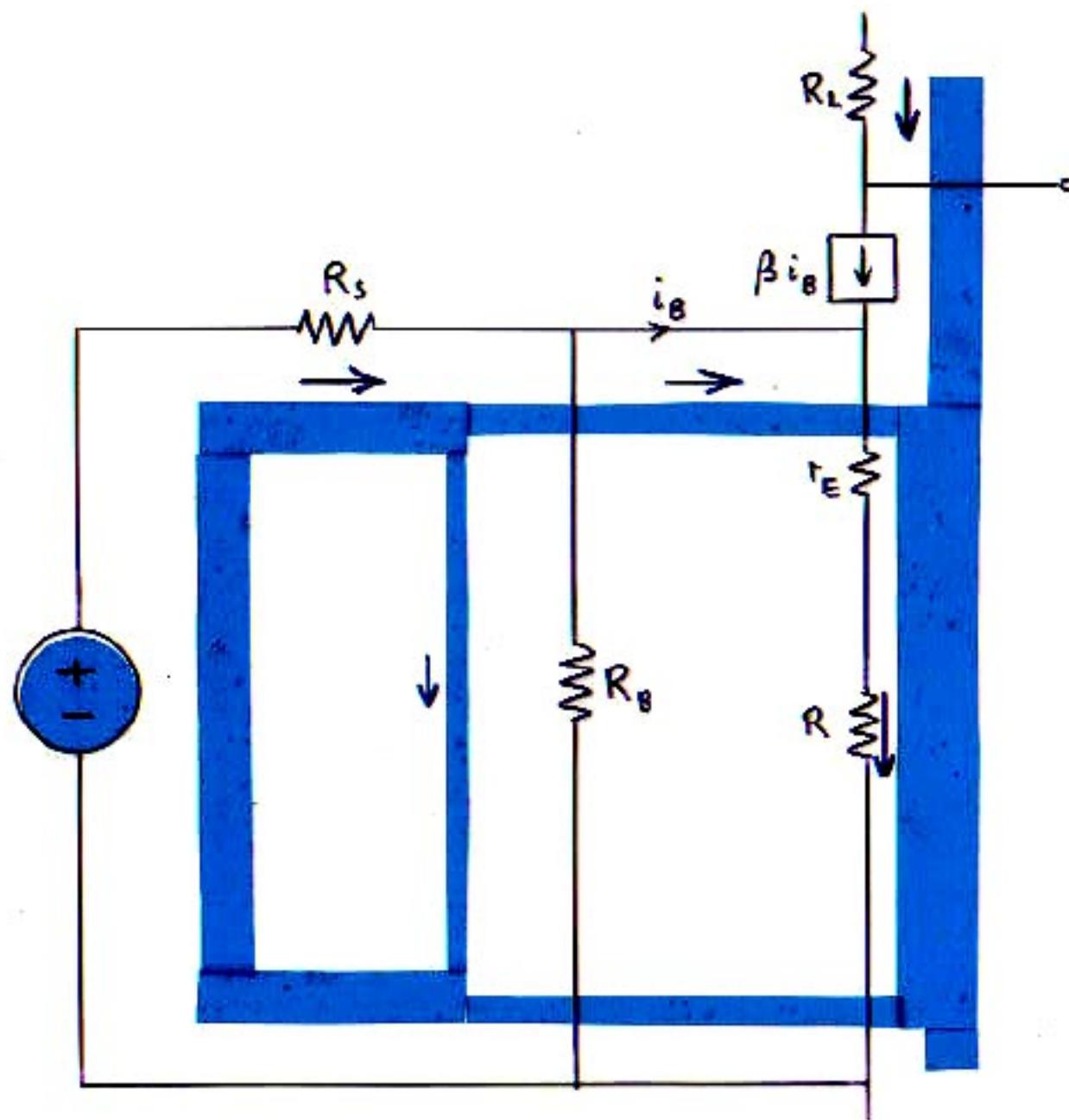


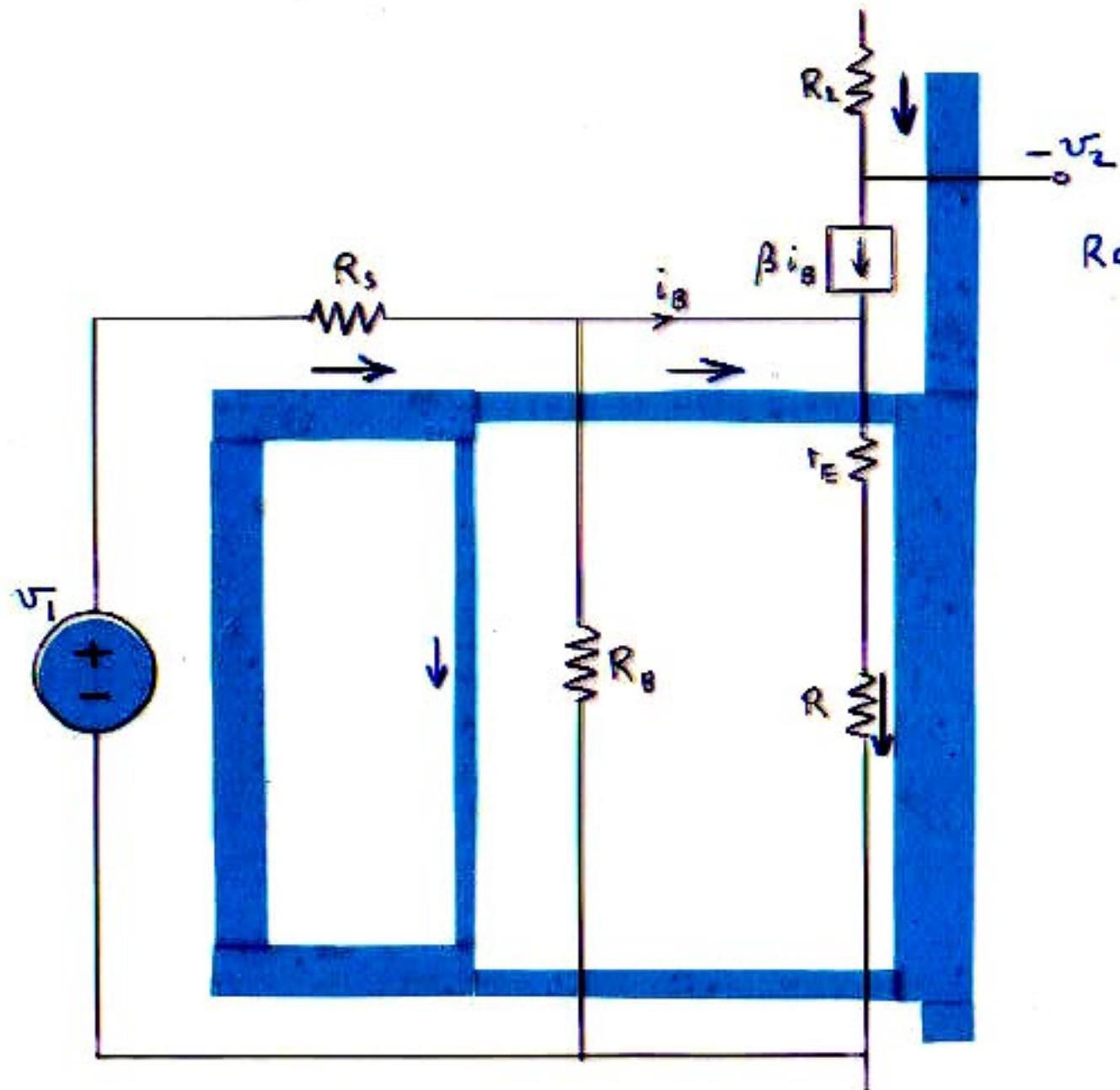



Reference gain:


$$A_o = \frac{v_2}{v_1}$$

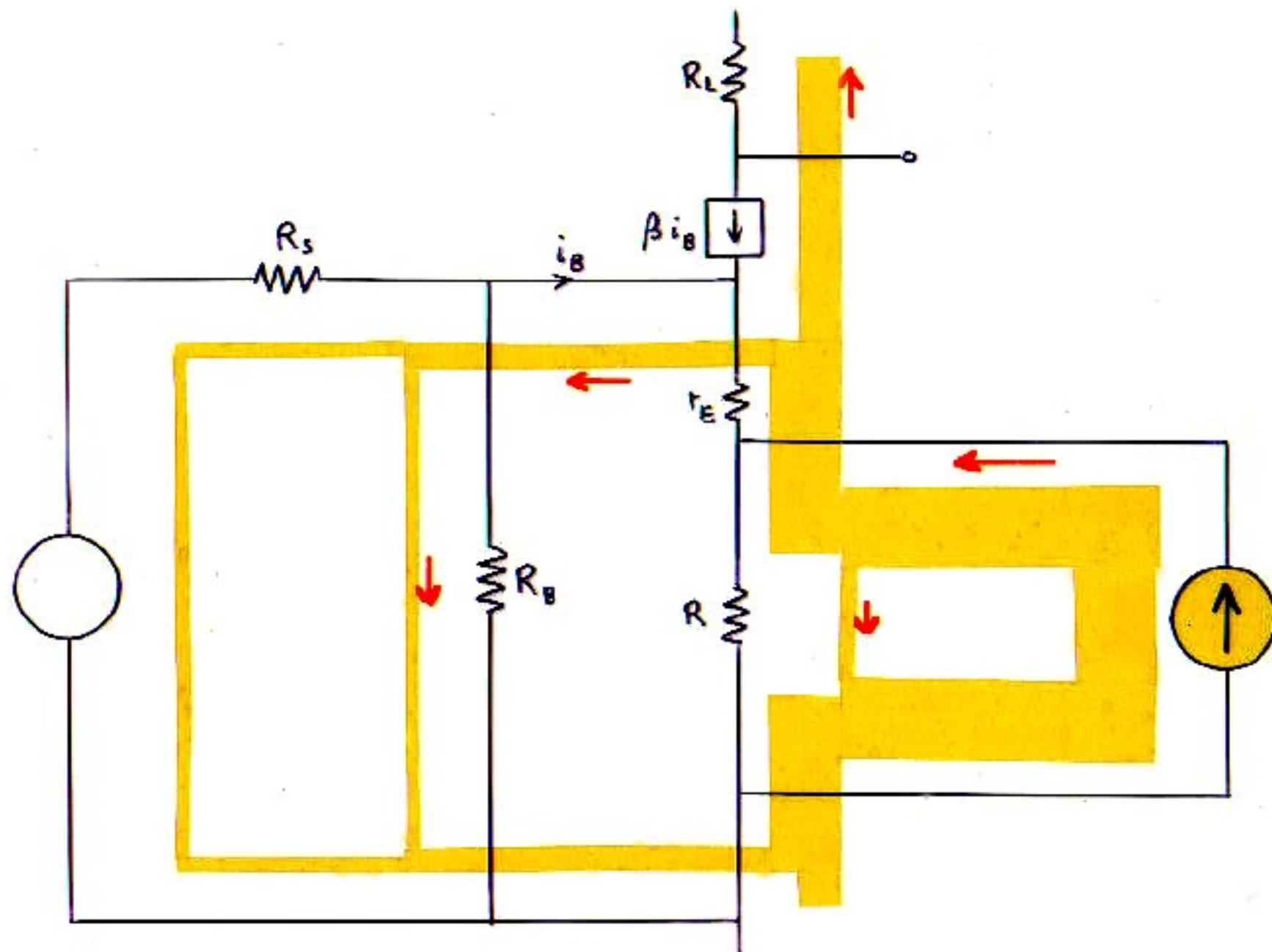

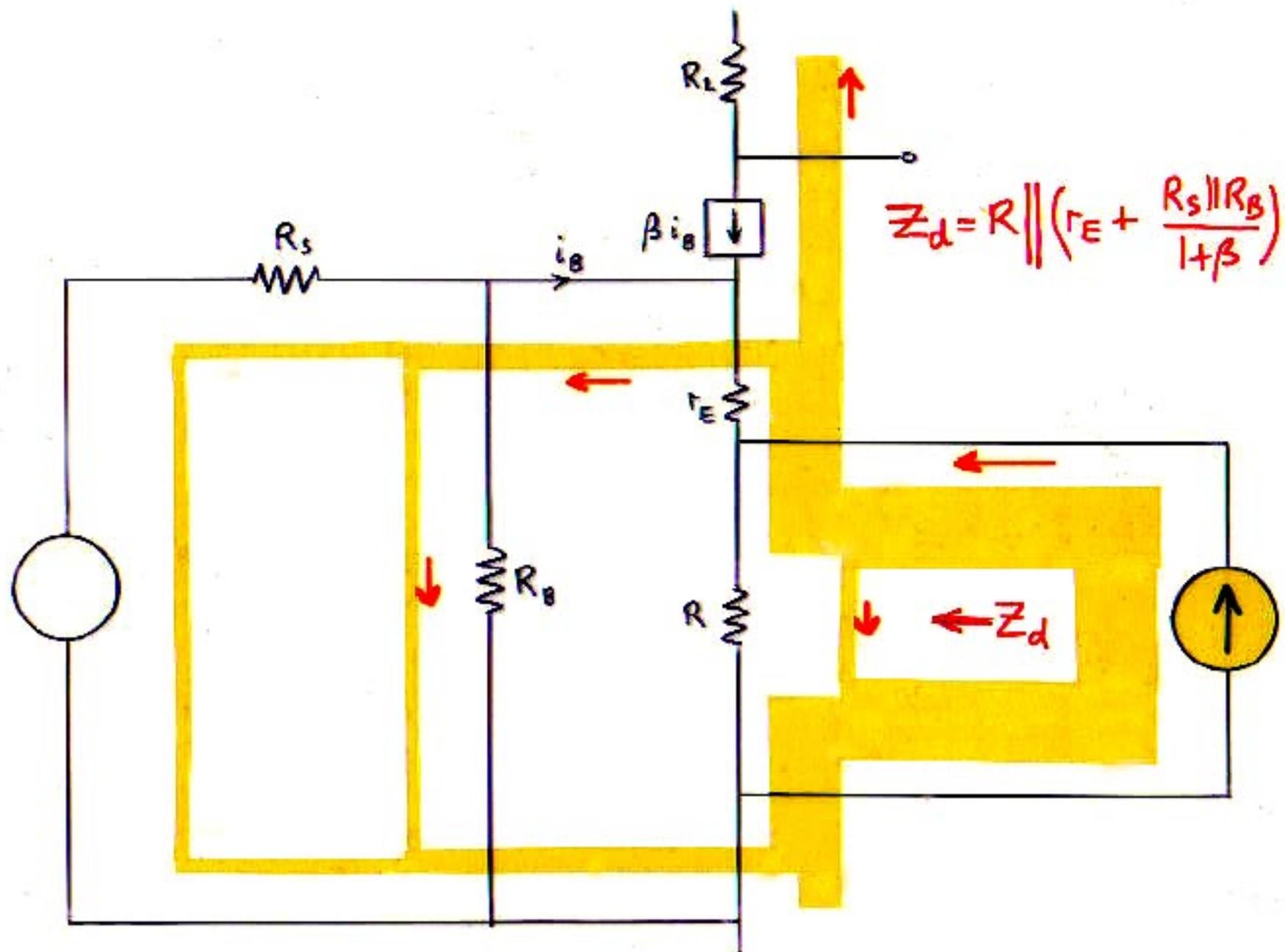

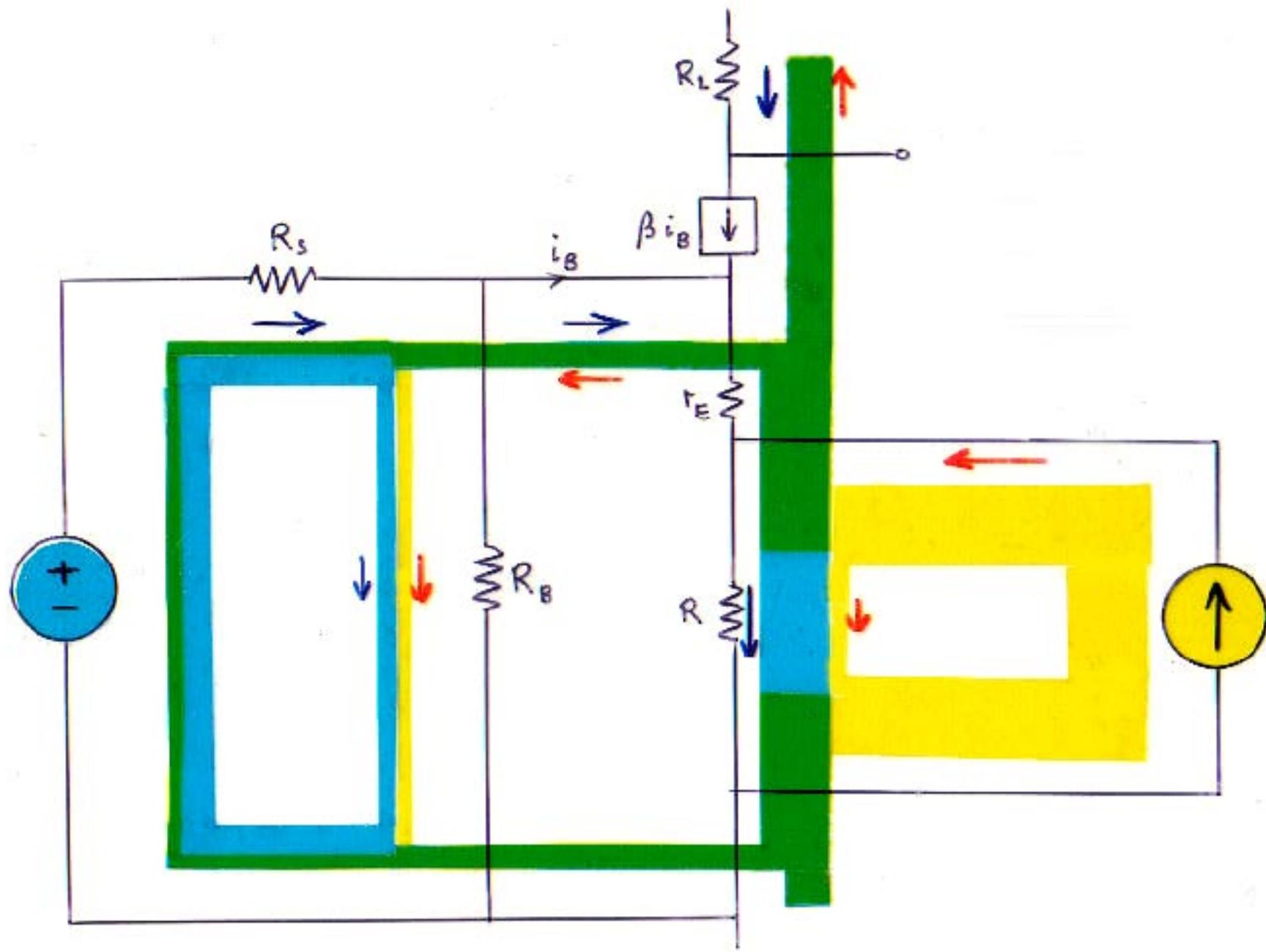


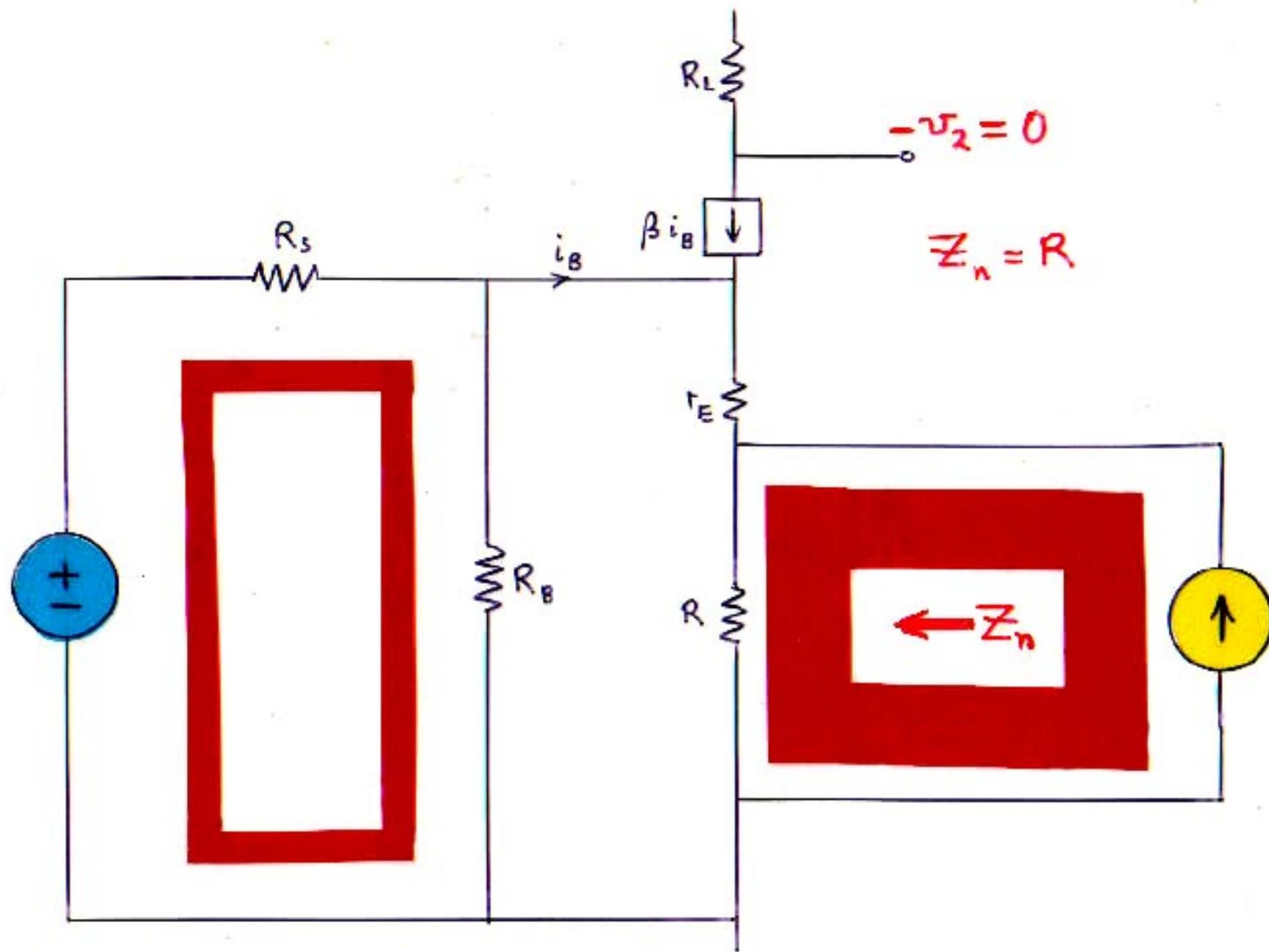

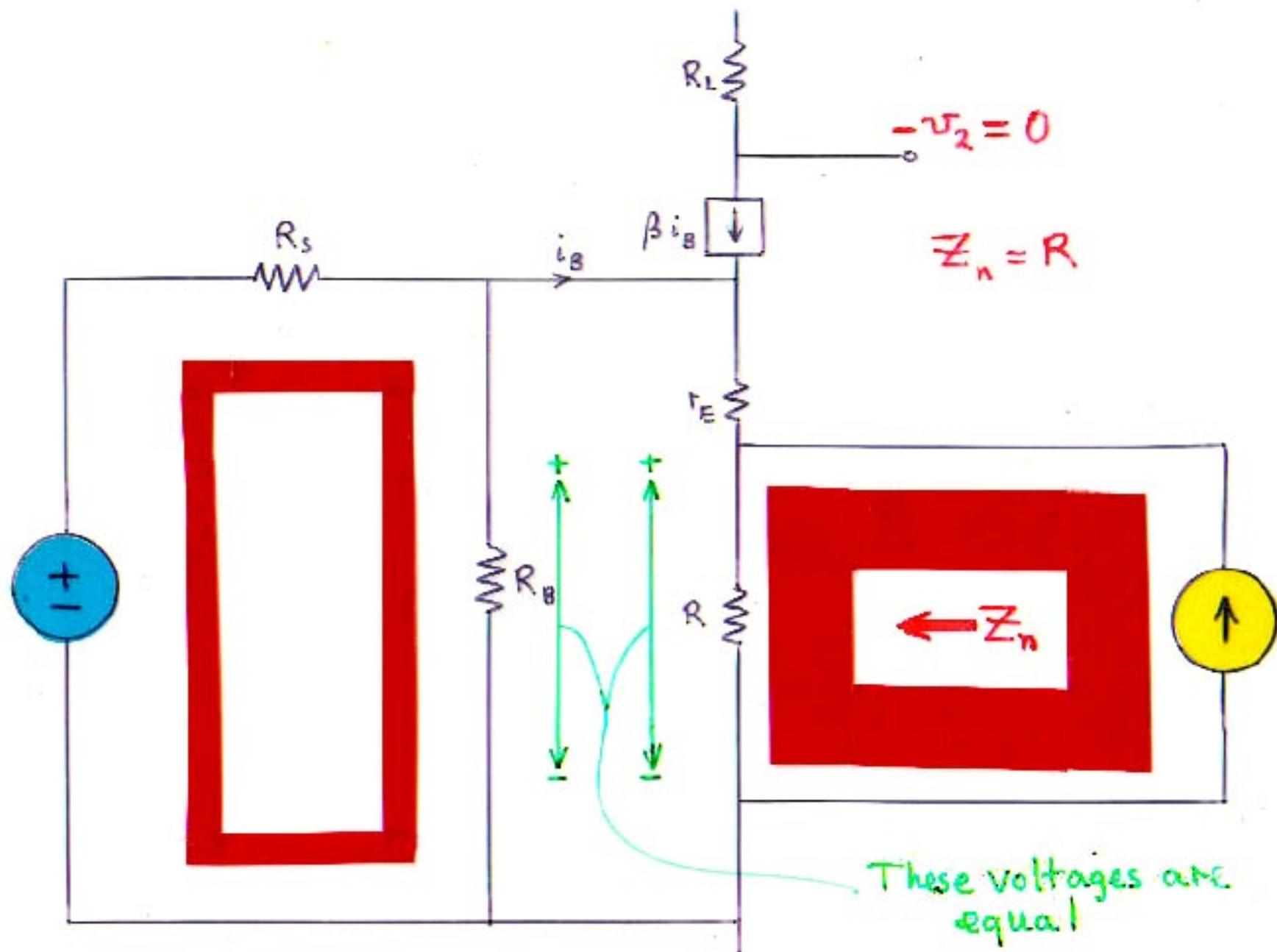

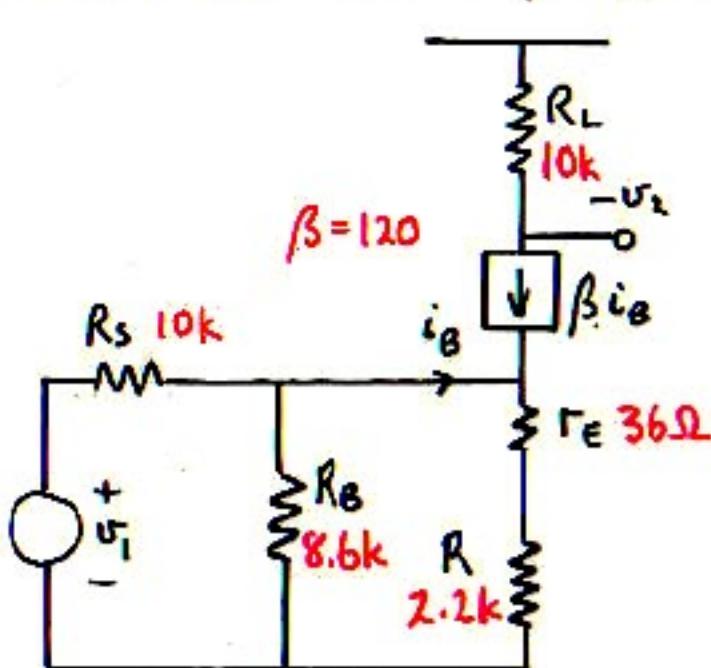
Example: The previously designed CE amplifier

Suppose the gain has been calculated without the emitter bypass capacitance, and the correction factor resulting from addition of the extra element  $Z \rightarrow 1/sC_2$  is desired.



Original gain :

$$A_o = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_e + (R_s || R_B)/(1+\beta)}$$
$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$
$$= 2.0 \Rightarrow 6\text{dB}$$

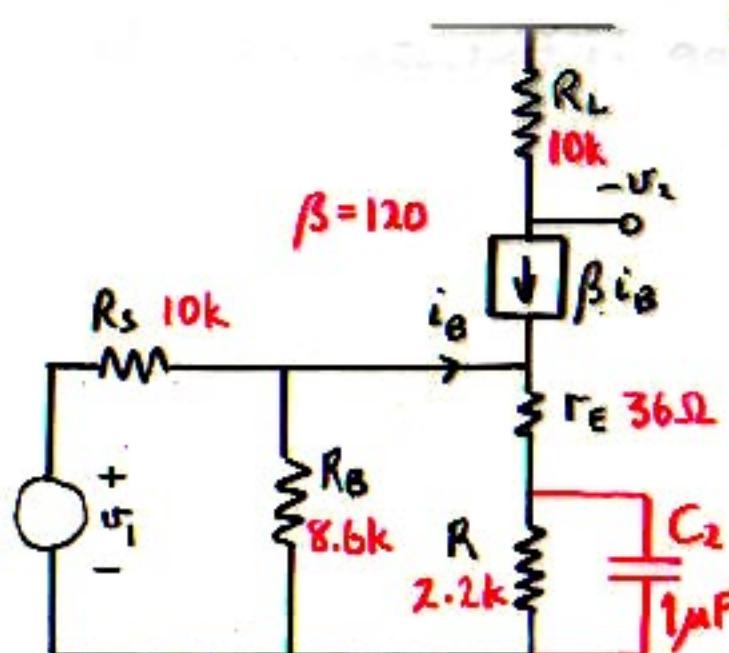

Original gain :

$$A_0 = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)}$$

$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$

$$= 2.0 \Rightarrow 6\text{dB}$$

Hence, corrected gain in presence of  $C_2 = 1\mu\text{F}$  bypass capacitance is :

$$A = A_0 \frac{1 + \frac{R_n}{Z}}{1 + \frac{R_d}{Z}} = A_0 \frac{1 + sC_2 R_n}{1 + sC_2 R_d} = A_0 \frac{1 + \frac{s}{\omega_1}}{1 + \frac{s}{\omega_2}} = A_m \frac{1 + \frac{\omega_1}{s}}{1 + \frac{\omega_2}{s}}$$

where

$$\omega_1 \equiv \frac{1}{C_2 R_n} \quad f_1 = \frac{159}{1 \times 2.2} = 72\text{Hz} \quad \omega_2 \equiv \frac{1}{C_2 R_d} = \frac{159}{1 \times 0.075} = 2.1\text{kHz}$$


$$A_m = A_0 \frac{\omega_2}{\omega_1} = A_0 \frac{R_n}{R_d}$$


$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)} \frac{R[R + r_E + (R_s || R_B)/(1+\beta)]}{R[r_E + (R_s || R_B)/(1+\beta)]}$$

$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)} = 62 \Rightarrow 36\text{dB}$$

NOTE: Nulling a voltage is not the same as  
shorting it!

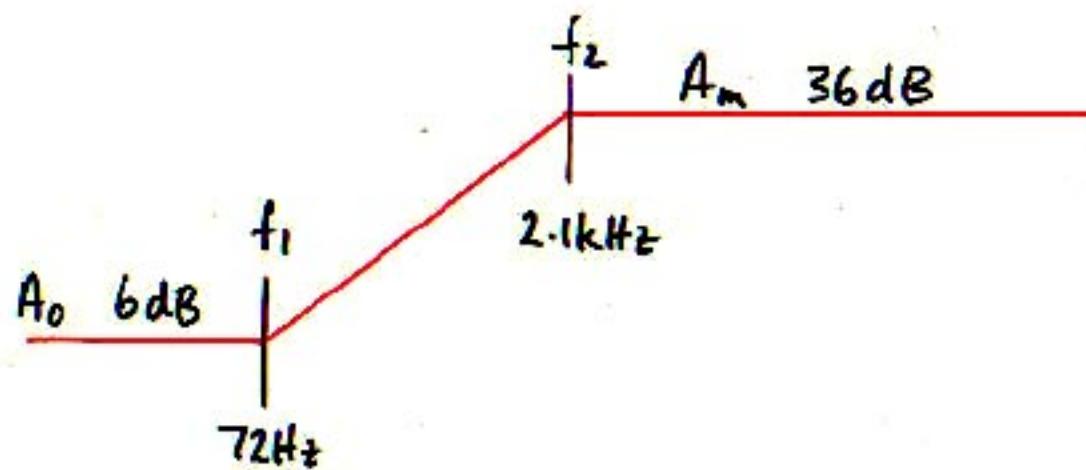NOTE: the null double injection calculation is  
easier than the single injection calculation!



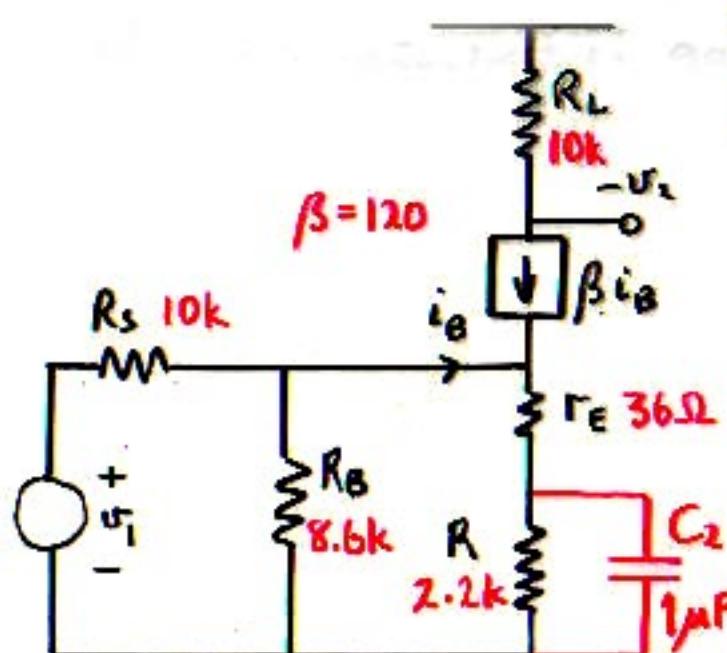

Original gain :

$$A_0 = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)}$$

$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$

$$= 2.0 \Rightarrow 6\text{dB}$$

Hence, corrected gain in presence of  $C_2 = 1\mu\text{F}$  bypass capacitance is :

$$A = A_0 \frac{1 + \frac{R_n}{Z}}{1 + \frac{R_d}{Z}} = A_0 \frac{1 + sC_2 R_n}{1 + sC_2 R_d} = A_0 \frac{1 + \frac{s}{\omega_1}}{1 + \frac{s}{\omega_2}} = A_m \frac{1 + \frac{\omega_1}{s}}{1 + \frac{\omega_2}{s}}$$


where


$$\omega_1 \equiv \frac{1}{C_2 R_n} \quad f_1 = \frac{159}{1 \times 2.2} = 72\text{Hz} \quad \omega_2 \equiv \frac{1}{C_2 R_d} = \frac{159}{1 \times 0.075} = 2.1\text{kHz}$$

$$A_m = A_0 \frac{\omega_2}{\omega_1} = A_0 \frac{R_n}{R_d}$$

$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)} \frac{R[R + r_E + (R_s || R_B)/(1+\beta)]}{R[r_E + (R_s || R_B)/(1+\beta)]}$$

$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)} = 62 \Rightarrow 36\text{dB}$$

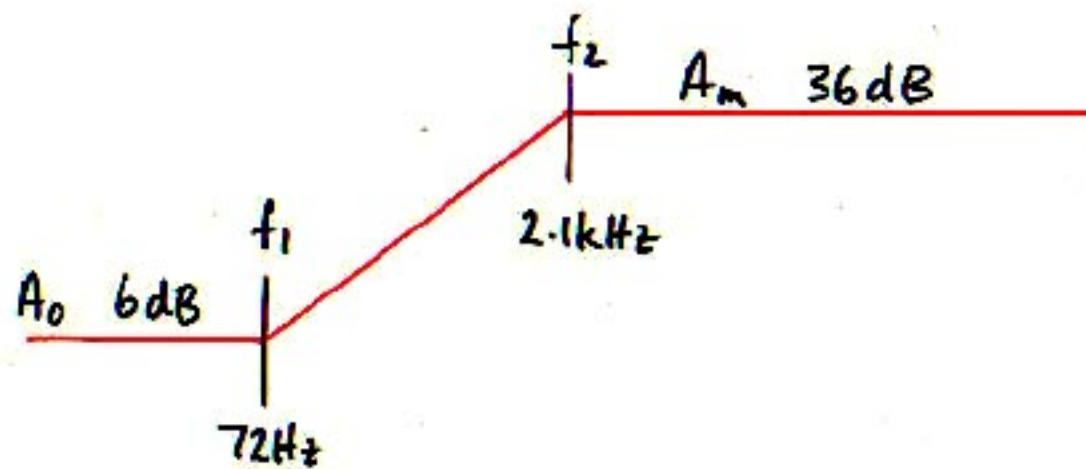

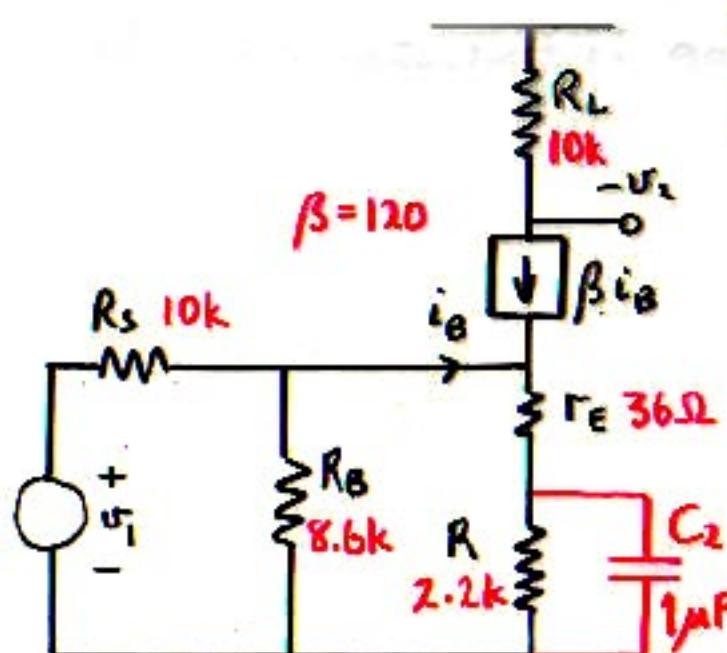

Original gain :

$$A_0 = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)}$$

$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$

$$= 2.0 \Rightarrow 6\text{dB}$$

Hence, corrected gain in presence of  $C_2 = 1\mu\text{F}$  bypass capacitance is :

$$A = A_0 \frac{1 + \frac{R_n}{Z}}{1 + \frac{R_d}{Z}} = A_0 \frac{1 + sC_2 R_n}{1 + sC_2 R_d} = A_0 \frac{1 + \frac{s}{\omega_1}}{1 + \frac{s}{\omega_2}} = A_m \frac{1 + \frac{\omega_1}{s}}{1 + \frac{\omega_2}{s}}$$


where

$$\omega_1 \equiv \frac{1}{C_2 R_n} \quad f_1 = \frac{159}{1 \times 2.2} = 72\text{Hz} \quad \omega_2 \equiv \frac{1}{C_2 R_d} = \frac{159}{1 \times 0.075} = 2.1\text{kHz}$$

$$A_m = A_0 \frac{\omega_2}{\omega_1} = A_0 \frac{R_n}{R_d}$$


$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)} \frac{R[R + r_E + (R_s || R_B)/(1+\beta)]}{R[r_E + (R_s || R_B)/(1+\beta)]}$$


$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)} = 62 \Rightarrow 36\text{dB}$$

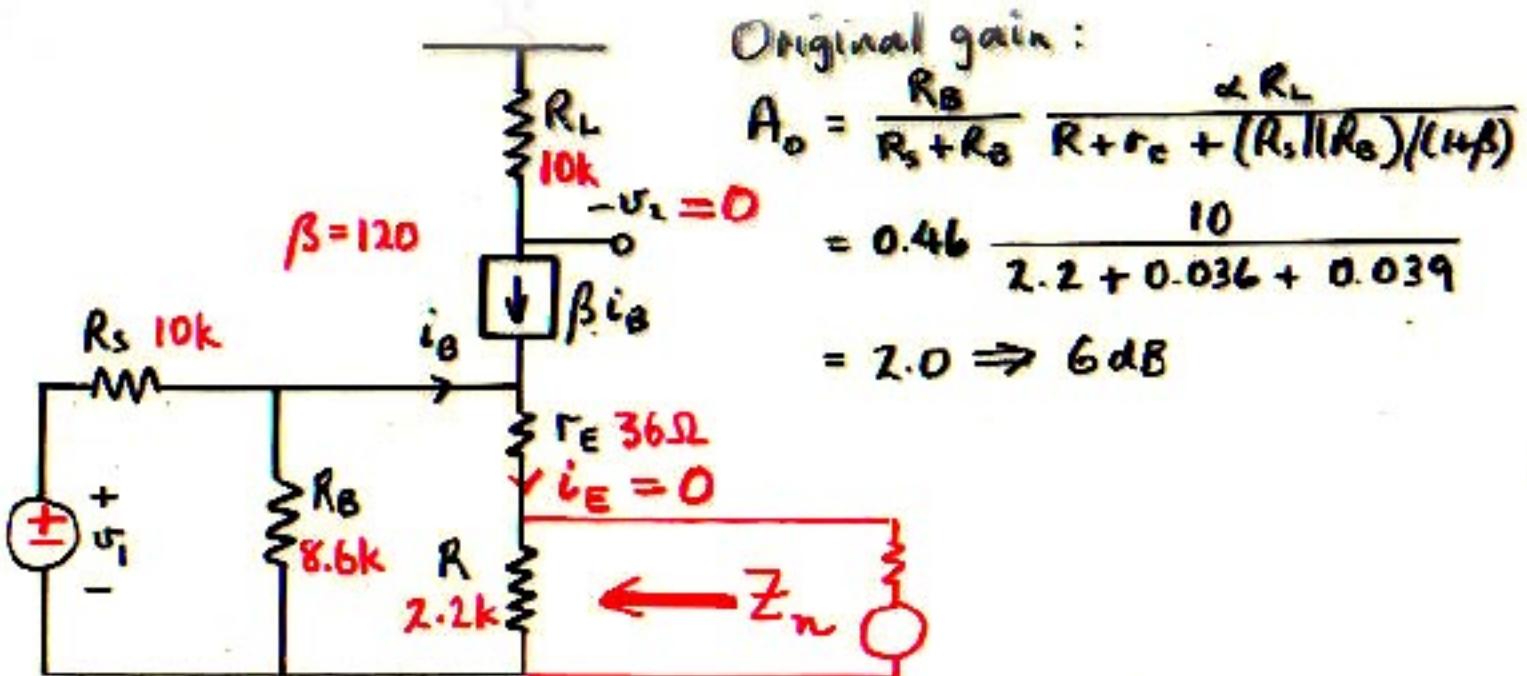


Step 2. Calculate  $Z_n$  by applying a second injected signal across  $R$ , and adjusting it with respect to  $v_i$  to null  $v_{o1} = v_2 = 0$ . Then, since  $v_2 = 0$ ,  $i_E = 0$ , hence:

$$Z_n = R_n = R = 2.2\text{k}$$

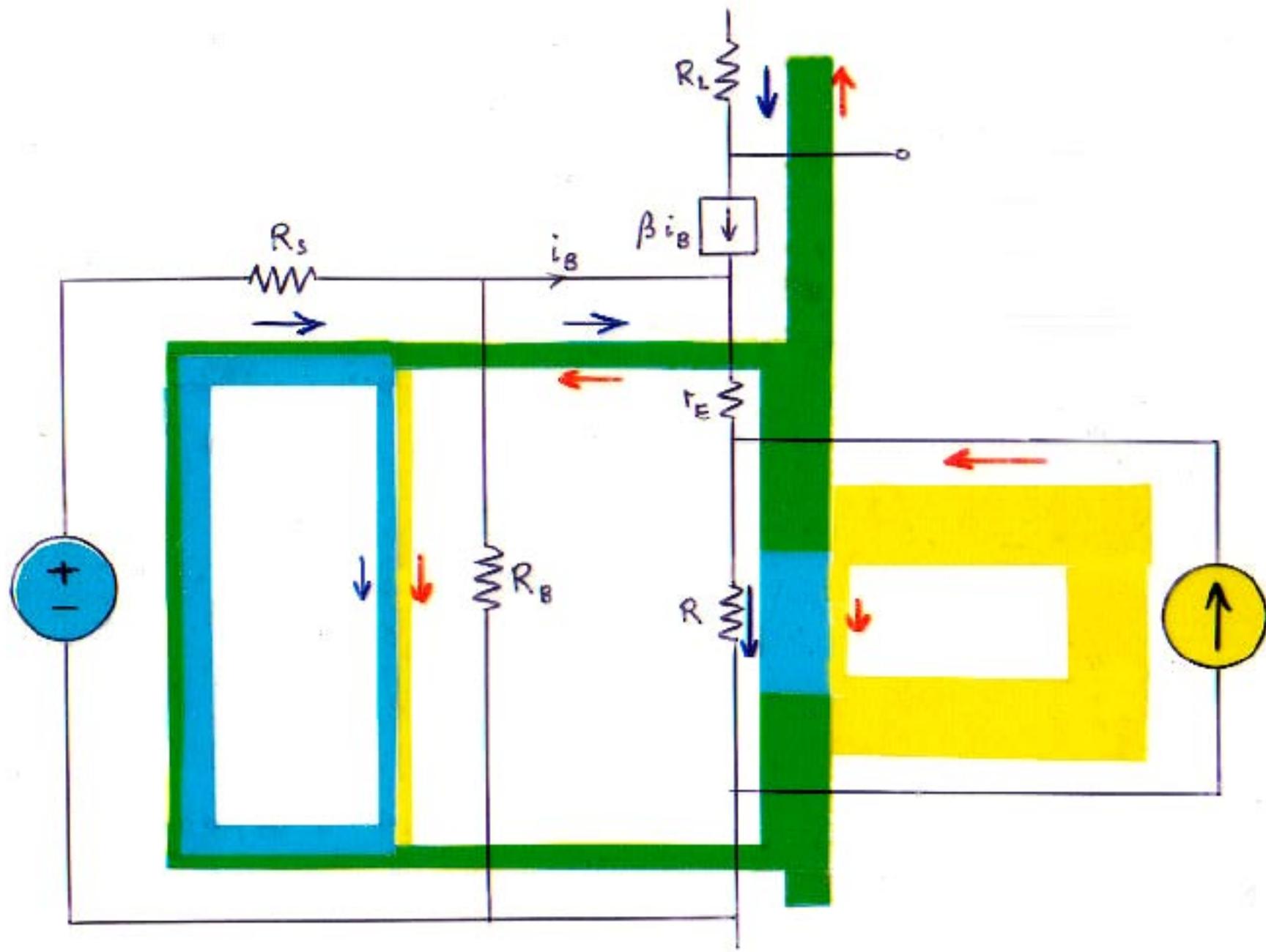

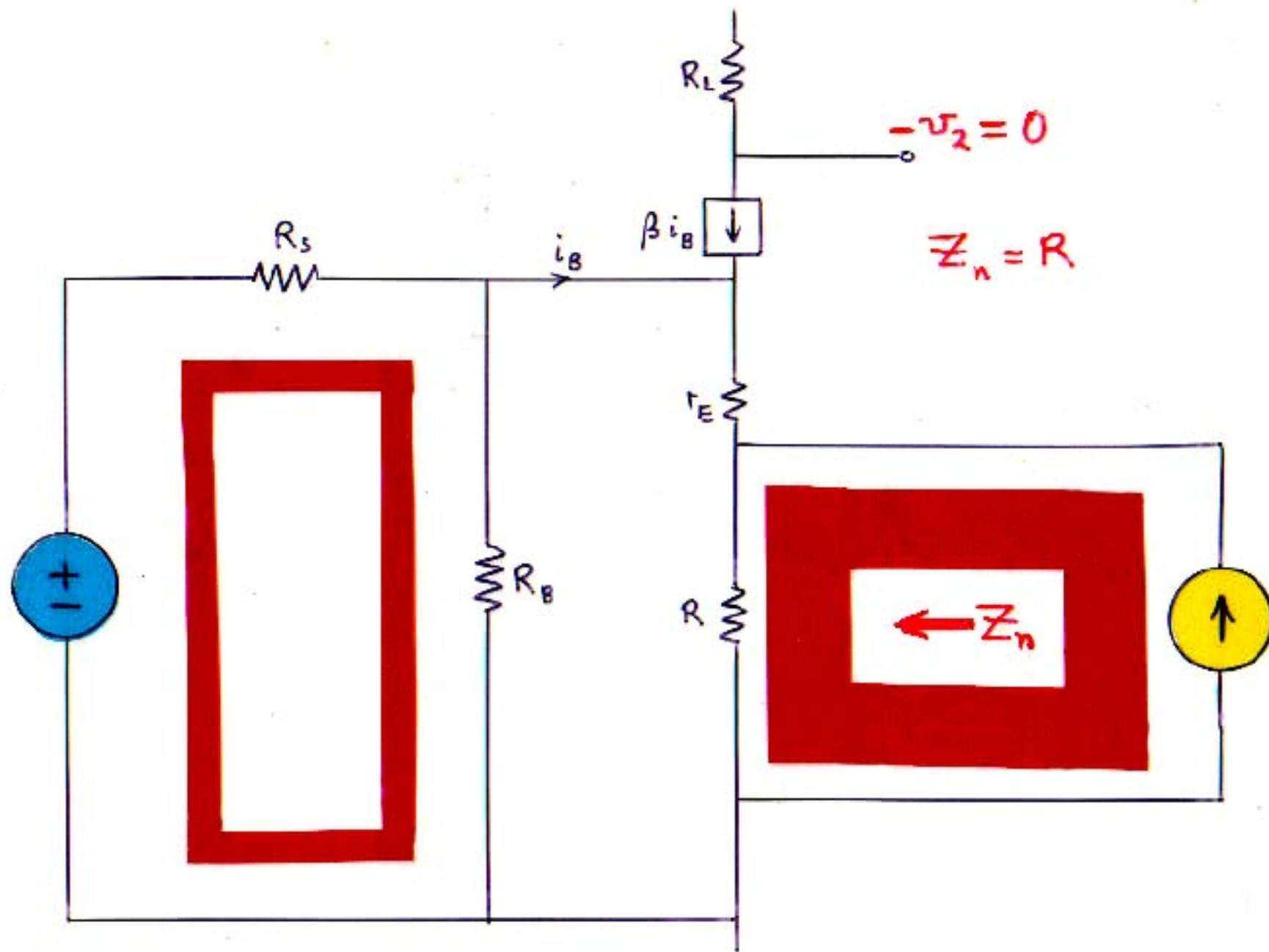

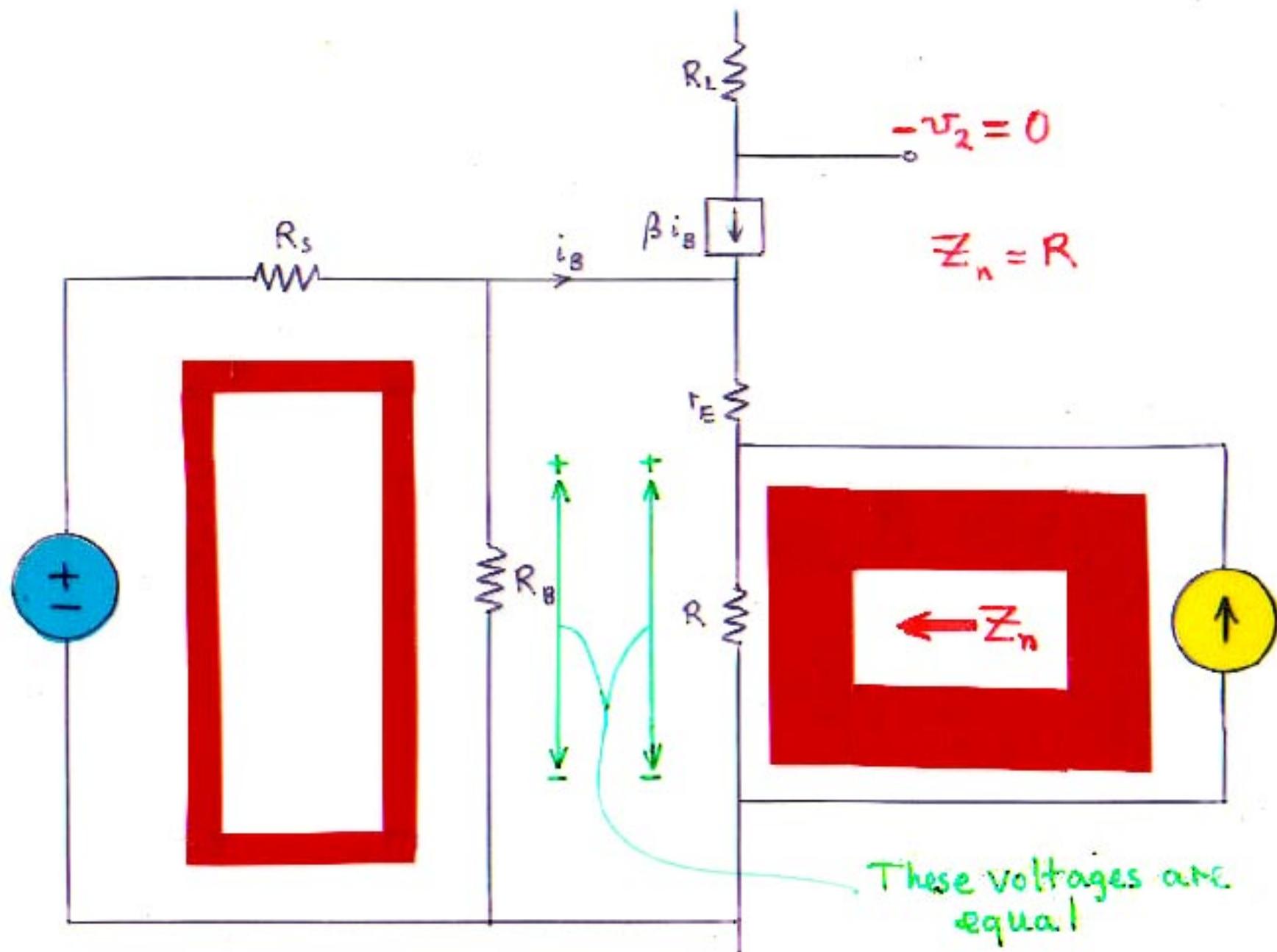

The Extra Element Theorem as derived applies to  
the correction factor resulting from an extra shunt element.

There is a corresponding form to find the correction factor  
resulting from an extra series element:

$$\text{reference gain} \downarrow$$

$$\text{gain } |z| = \text{gain} |_{z=\infty} \frac{1 + \frac{z_n}{z}}{1 + \frac{z_d}{z}}$$

$$= \text{gain} |_{z=\infty} \frac{\frac{z_n}{z}}{\frac{z_d}{z}} \frac{\frac{z}{z_n} + 1}{\frac{z}{z_d} + 1}$$

$$= \frac{z_n}{z_d} \text{gain} |_{z=\infty} \frac{1 + \frac{z}{z_n}}{1 + \frac{z}{z_d}}$$

The Extra Element Theorem as derived applies to the correction factor resulting from an extra shunt element.

There is a corresponding form to find the correction factor resulting from an extra series element:

$$\text{reference gain} \downarrow$$

$$\text{gain } |_{Z} = \text{gain } |_{Z=\infty} \frac{1 + \frac{z_n}{Z}}{1 + \frac{z_d}{Z}}$$

$$= \text{gain } |_{Z=\infty} \frac{\frac{z_n}{Z}}{\frac{z_d}{Z}} \frac{\frac{Z}{z_n} + 1}{\frac{Z}{z_d} + 1}$$


$$\text{reference gain} \downarrow$$

$$= \text{gain } |_{Z=0} \frac{1 + \frac{Z}{z_n}}{1 + \frac{Z}{z_d}}$$

$$= \left( \frac{z_n}{z_d} \cdot \text{gain } |_{Z=\infty} \right) \frac{1 + \frac{Z}{z_n}}{1 + \frac{Z}{z_d}}$$

This must be  
the gain when  $Z=0$

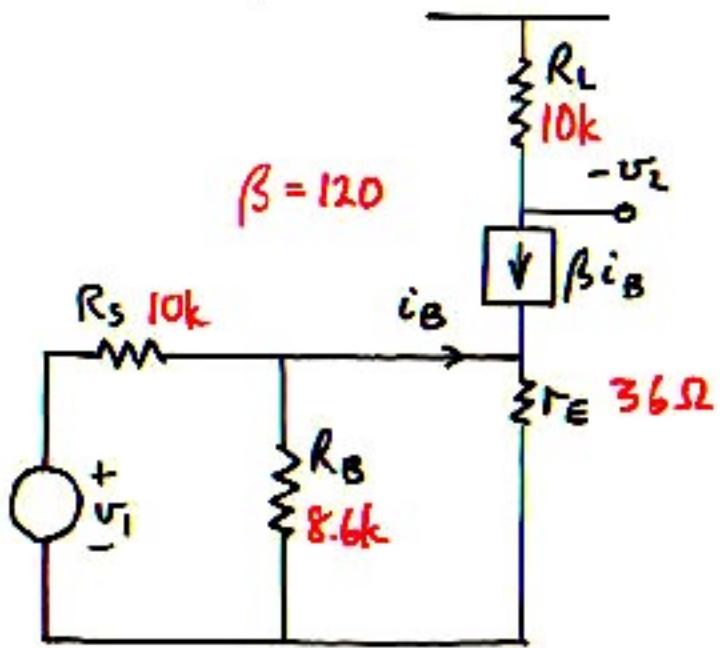
Example: An alternative to the method of the previous example is to find the correction factor to the midband gain  $A_m$  resulting from addition of the series "extra element"  $Z \rightarrow R \parallel 1/\text{SC}$ .



Original gain:


$$A_m = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)}$$

$$= 62 \Rightarrow 36 \text{ dB}$$

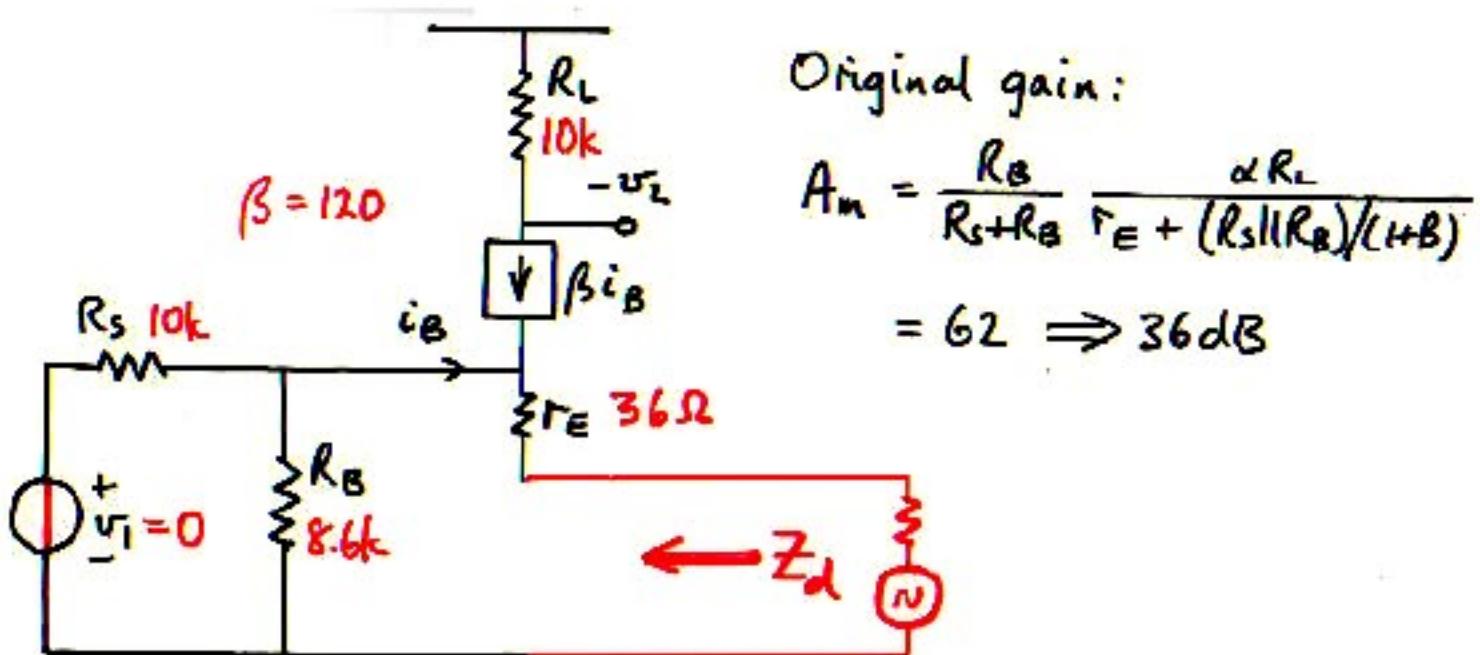

Step 1. Calculate  $Z_d$  by shorting  $v_{i1} = v_i$  and applying a second injected signal in series with  $r_E$ :

$$Z_d = R_d' = r_E + (R_s || R_B)/(1+\beta)$$

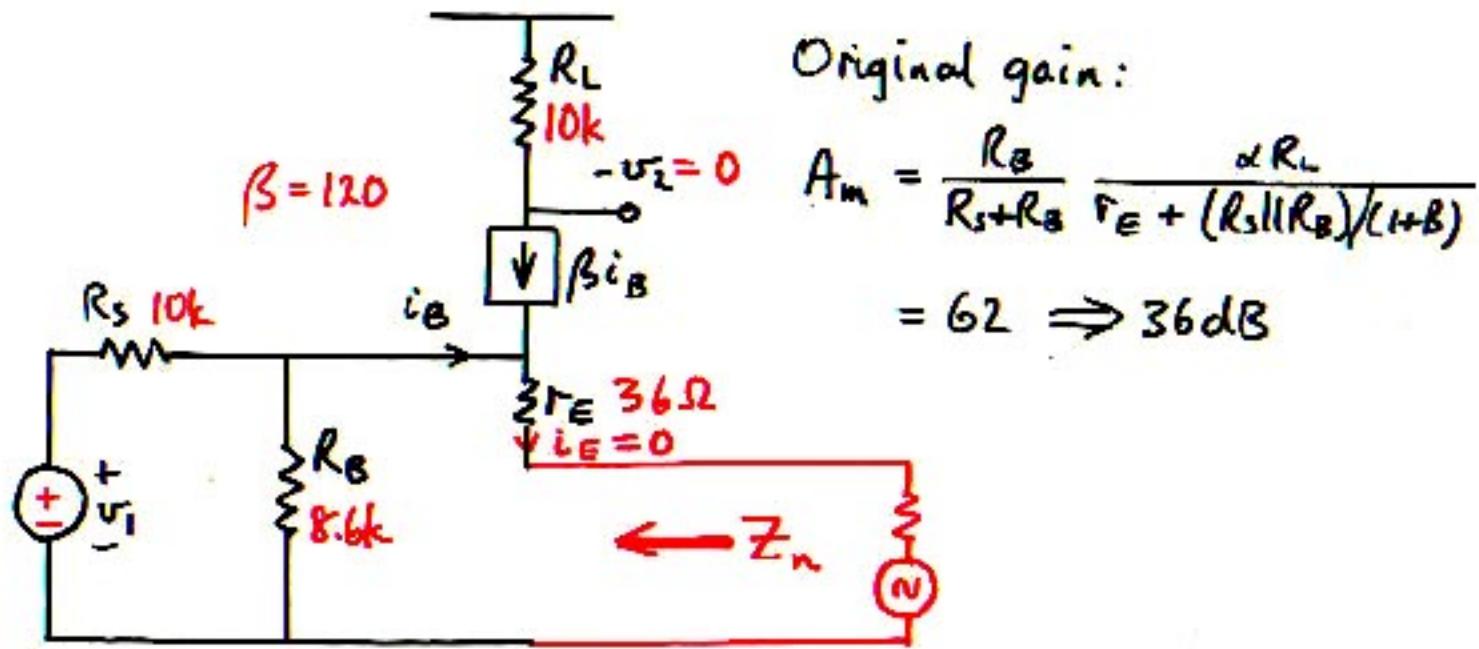

Original gain:


$$A_m = \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)}$$

$$= 62 \Rightarrow 36 \text{ dB}$$

Step 2. Calculate  $Z_n$  by applying a second injected signal in series with  $r_E$ , and adjusting it with respect to  $v_i$  to null  $v_{o1} = v_2 = 0$ .

Then, since  $v_2 = 0$ ,  $i_E = 0$ , hence

$$Z_n = R_n' = \infty$$

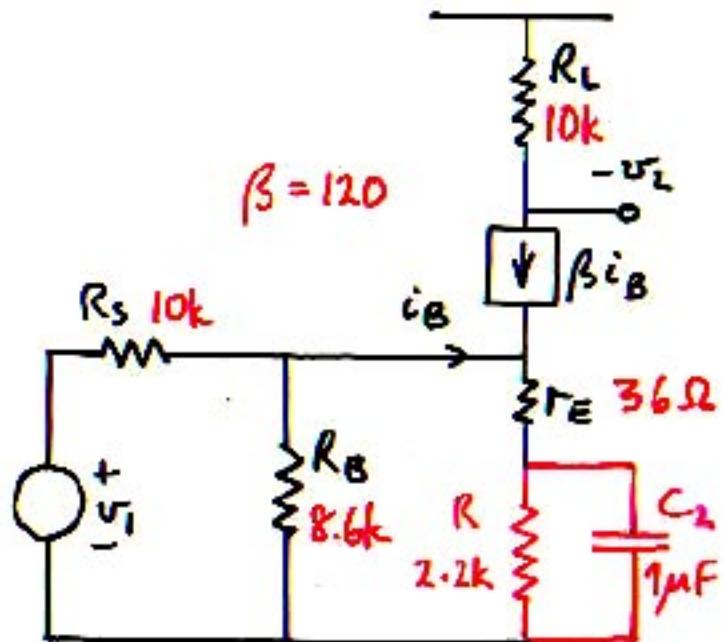

Original gain:

$$A_m = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)}$$

$$= 62 \Rightarrow 36 \text{ dB}$$

Hence, corrected gain in presence of  $R || 1/sC_2$  is:

$$A = A_m \frac{1 + \frac{R}{R_d'}}{1 + \frac{R}{R_d'}} = A_m \frac{1}{1 + \frac{R}{R_d'} \frac{1}{1 + sC_2 R}} = A_m \frac{1 + 1/sC_2 R}{1 + 1/sC_2 (R || R_d')}$$

However,  $R || R_d' = R_d$ , so

$$A = A_m \frac{1 + 1/sC_2 R}{1 + 1/sC_2 R_d} \longrightarrow \text{same result as before}$$

## Generalization: Extra Element Theorem - #1

There are two forms of Extra Element Theorem:

1.

$$\text{gain}|_z = \text{gain}|_{z=\infty} \frac{1 + \frac{z_n}{z}}{1 + \frac{z_d}{z}}$$

Provides a correction factor for an extra element added in shunt across a node pair.

2.

$$\text{gain}|_z = \text{gain}|_{z=0} \frac{1 + \frac{z}{z_n}}{1 + \frac{z}{z_d}}$$

Provides a correction factor for an extra element added in series with a branch.

The "extra element"  $z$  can be any two-terminal combination of impedances.

Note that in all cases the null double injection calculation is easier than the single injection calculation.


This results from use of the null condition  
(which makes several other quantities zero);

and


because the relation between  $u_{i_1}$  and  $u_{i_2}$  to produce the null is never needed — only the null itself is used.
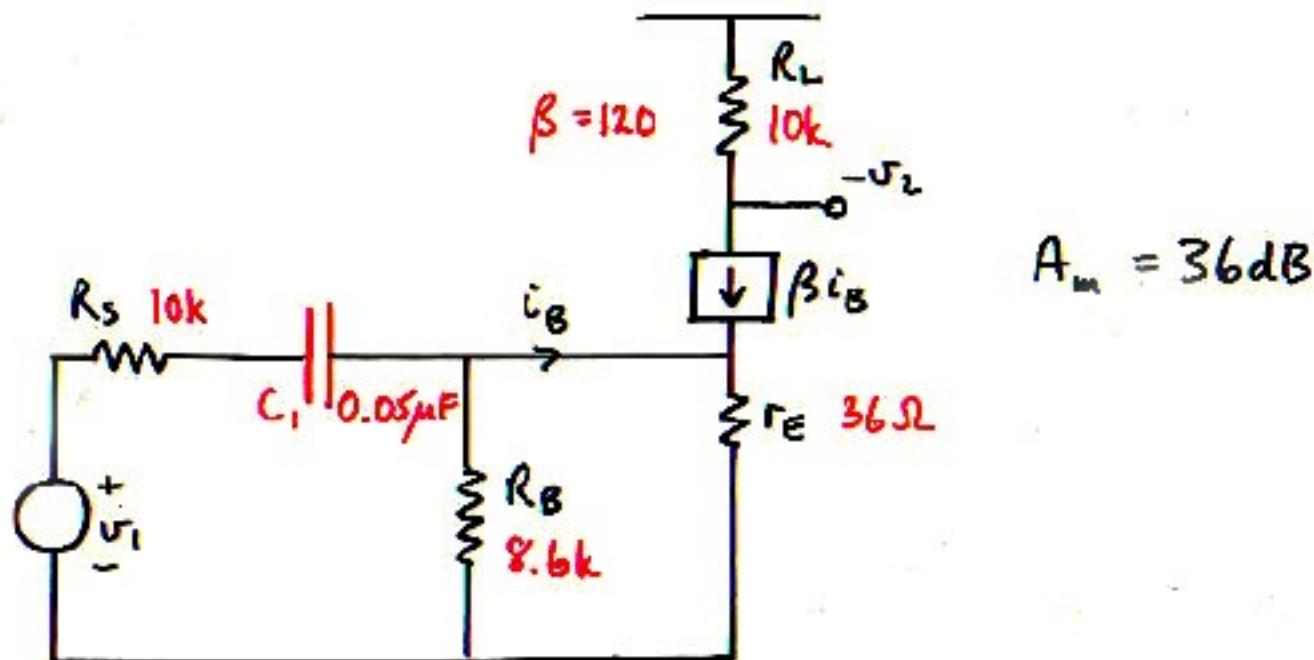
### Exercise


In the CE amplifier stage, find the correction factor to the midband gain  $A_m$  resulting from inclusion of the coupling capacitance  $C_1 = 0.05\mu F$ :



## Exercise Solution

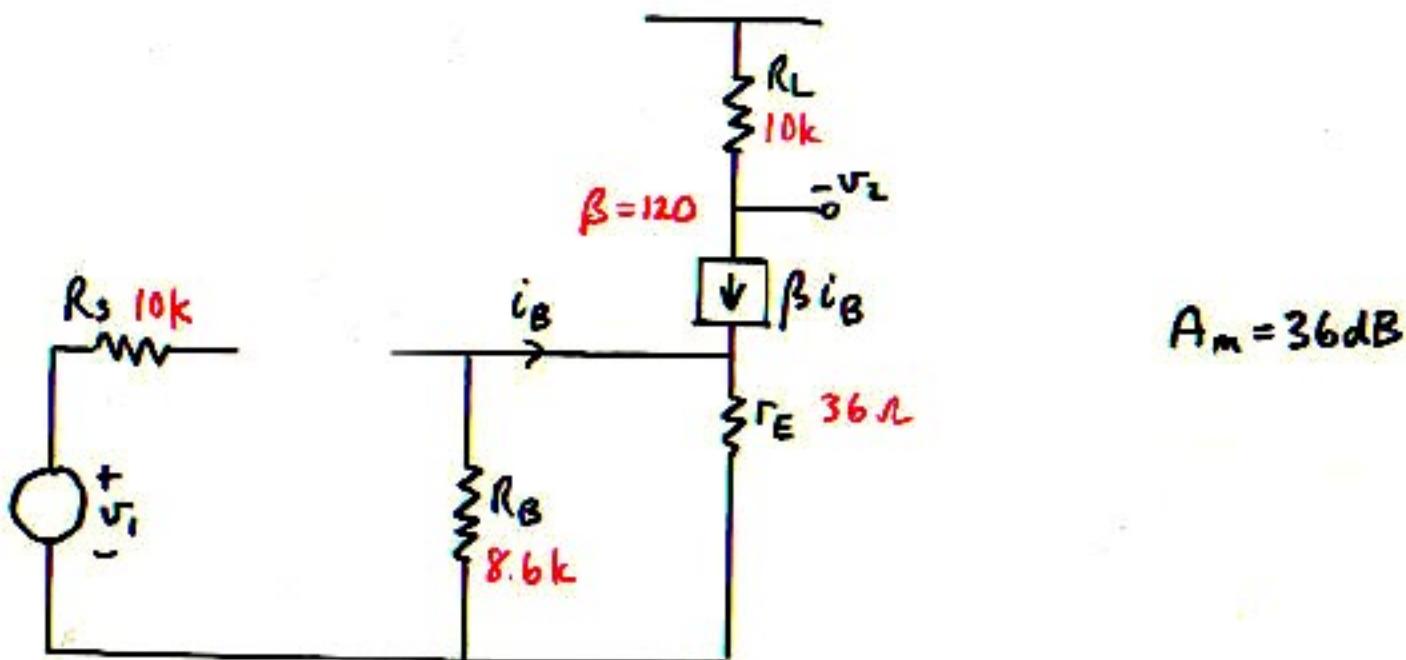


## Exercise Solution

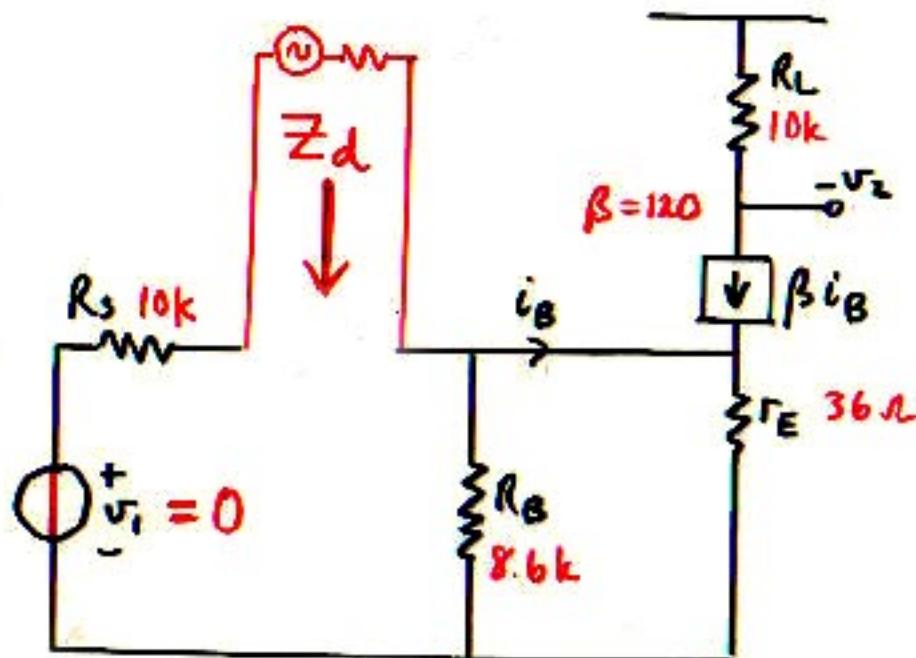

$$A_m = 36 \text{ dB}$$

## Exercise Solution

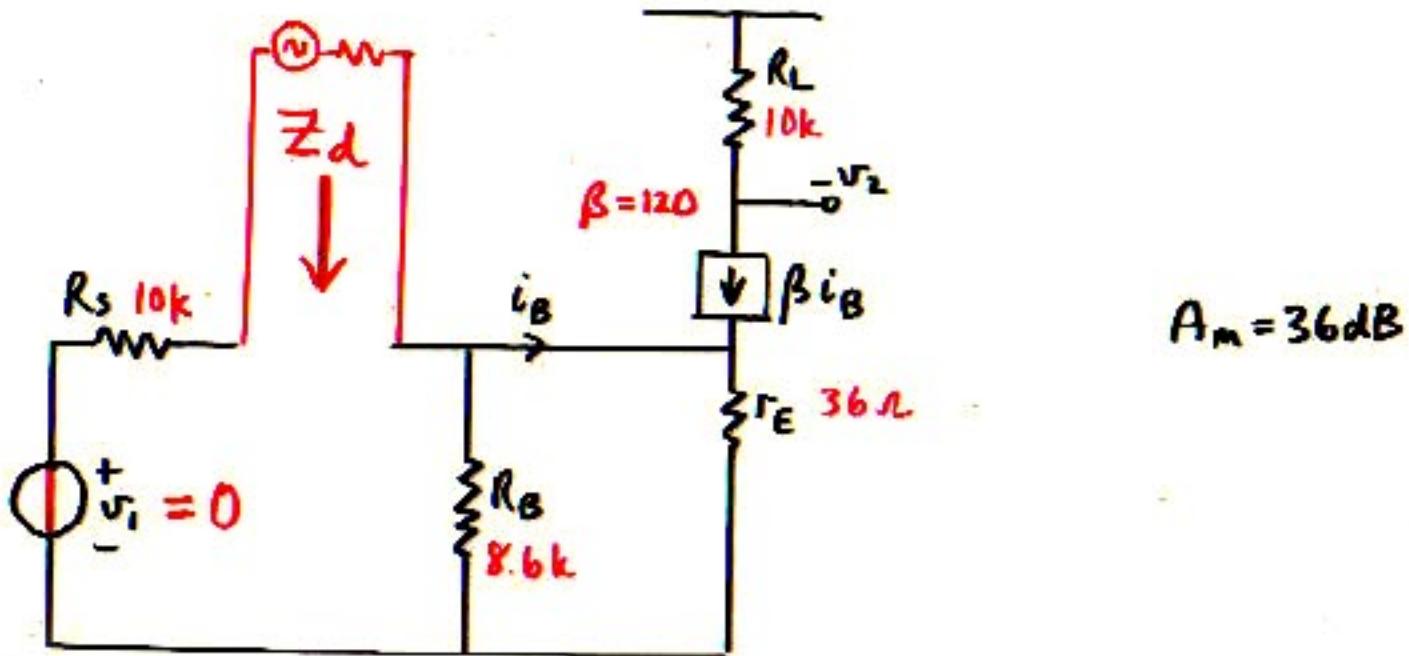


$$A_m = 36 \text{ dB}$$

Step 1.

$$\begin{aligned}
 Z_d &= R_d = R_s + R_B \parallel ((1+\beta)r_E) \\
 &= 10 + 8.6 \parallel (120 \times 0.036) \\
 &= 10 + 8.6 \parallel 4.3 \\
 &= 13k
 \end{aligned}$$

## Exercise Solution

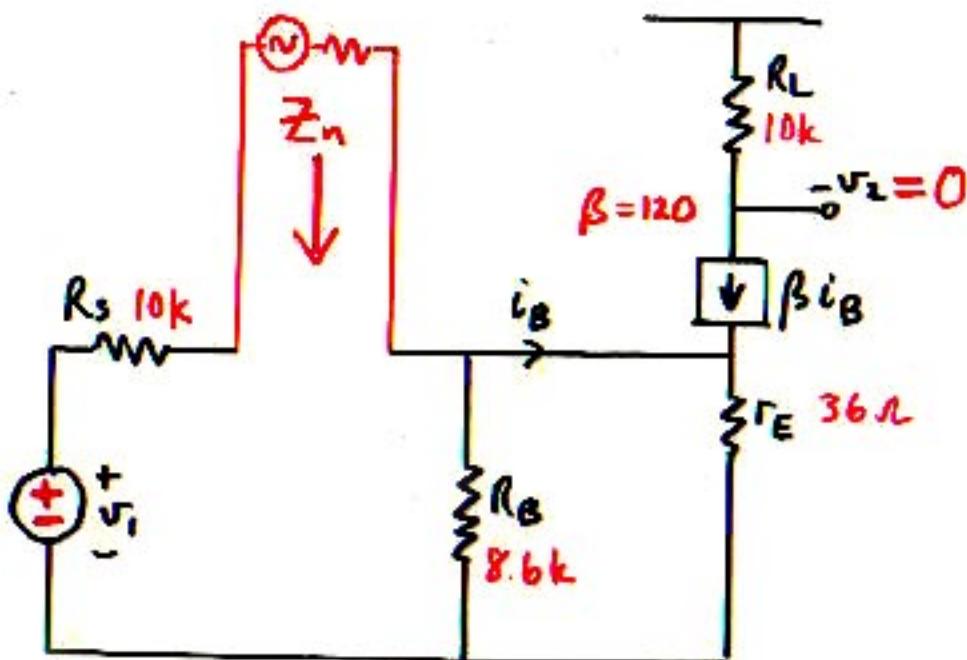

$$A_m = 36 \text{ dB}$$