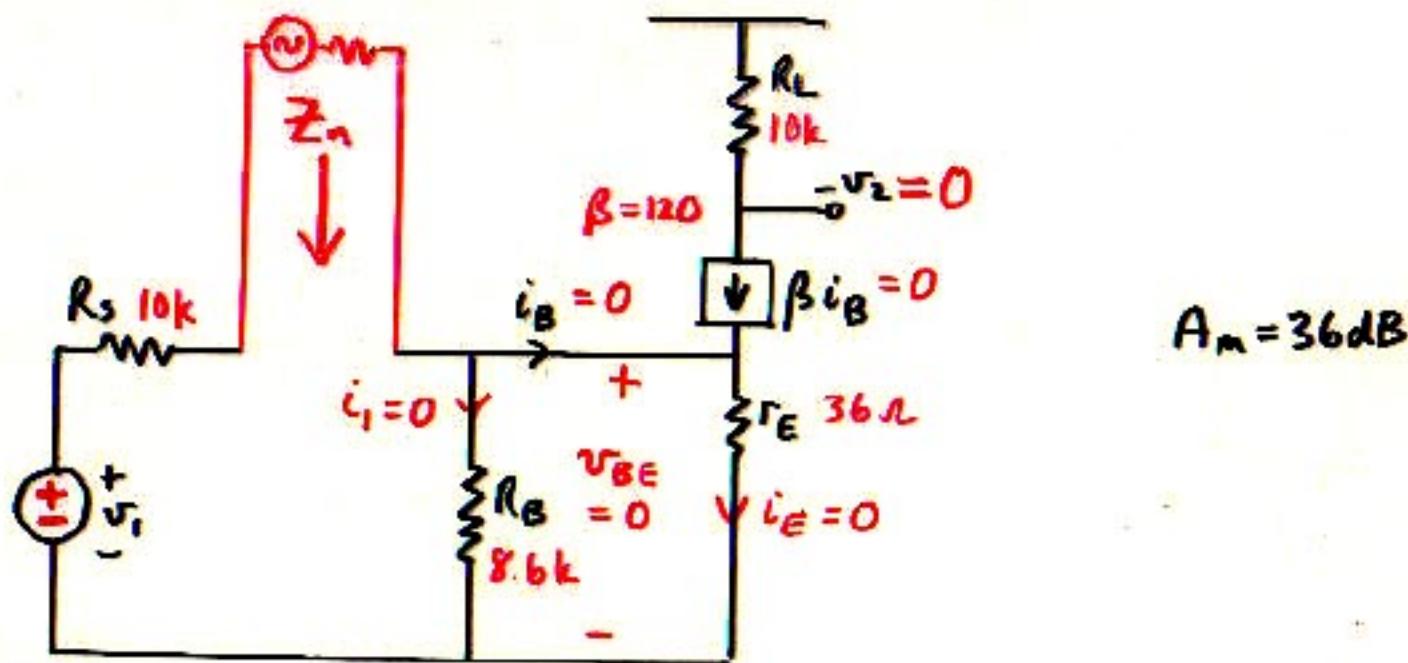



## Exercise Solution



Step 2.

$$Z_n = R_n = \infty$$

## Exercise Solution

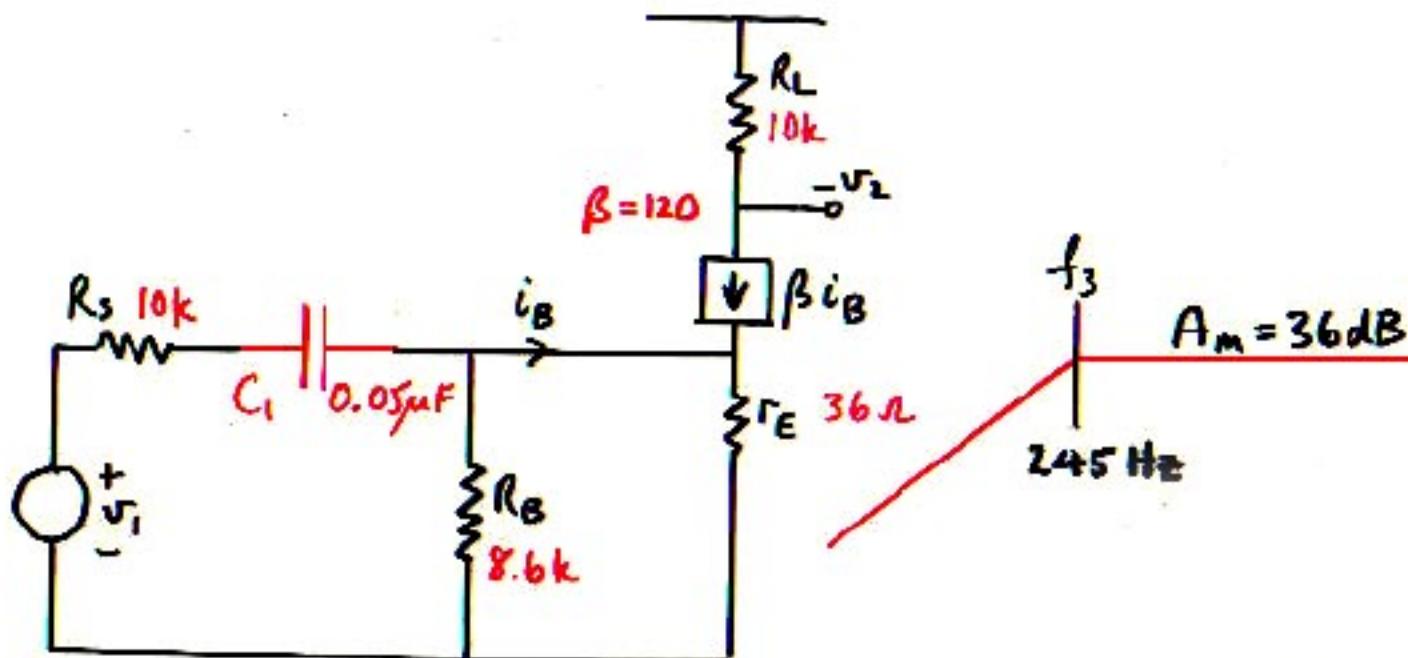

Hence corrected gain in the presence of  $Z \rightarrow 1/sC_1$ , is

$$A = A_m \frac{1 + \frac{Z}{Z_k}}{1 + \frac{Z}{Z_k}} = A_m \frac{1}{1 + \frac{1}{sC_1R_d}} = A_m \frac{1}{1 + \frac{\omega_3}{s}}$$

where

$$\omega_3 = \frac{1}{C_1R_d} \quad f_3 = \frac{159}{0.05 \times 13} = 245\text{Hz}$$

Generalization: Extra Element Theorem - #2

If the reference circuit is purely resistive,  
 $Z_d = R_d$  and  $Z_n = R_n$  are pure resistances.

If, also, the extra element is a pure reactance,  
the Extra Element Theorem correction  
factor gives the corner frequencies  
directly.


### Generalization: Extra Element Theorem - #3

The Extra Element Theorem can profitably be used to divide the analysis of a complicated circuit into successive simpler steps:


Designate one element as "extra," and the circuit without the element as the "reference circuit."  
Calculate the gain of the (simpler) reference circuit, then restore the omitted element by the Extra Element Theorem correction factor.

This is a particularly useful approach when the designated "extra" element is a reactance and the reference circuit is purely resistive.


Exercise : lag-lead network

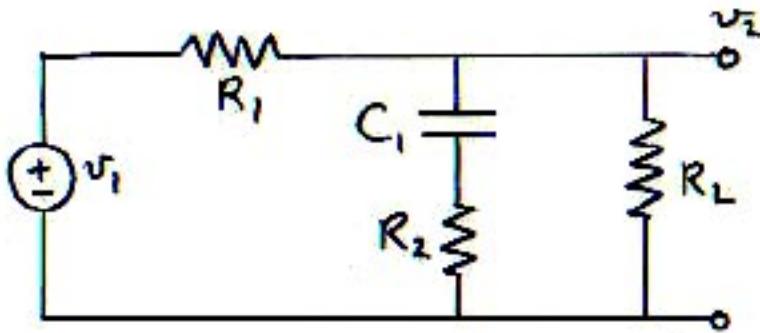

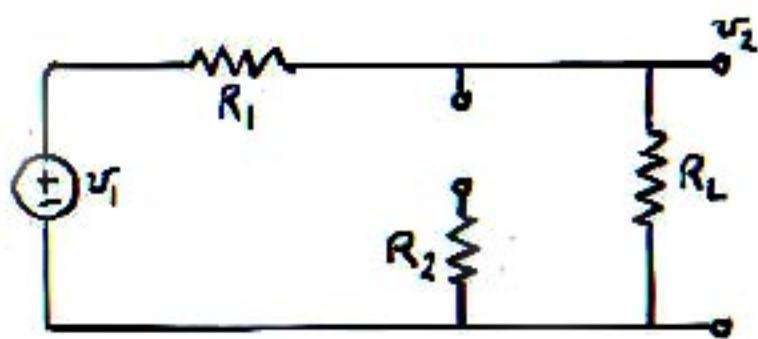Find the transfer function  $A = v_2/v_1$  by designating  $C_1$  as an "extra" element.




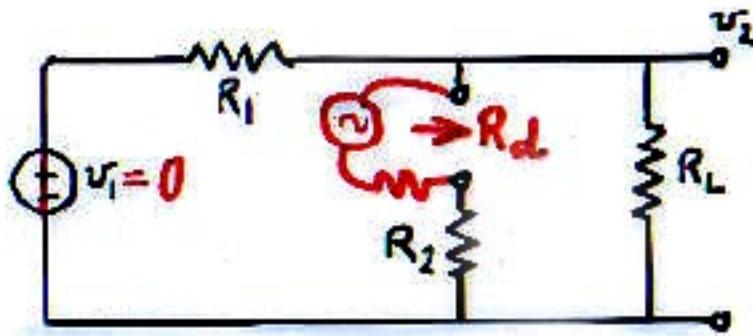
$$\frac{v_2}{v_1} = \frac{R_L}{R_1 + R_L}$$



$$\frac{v_2}{v_1} = \frac{R_L}{R_1 + R_L}$$

$$R_d = R_2 + R_1 \parallel R_L$$

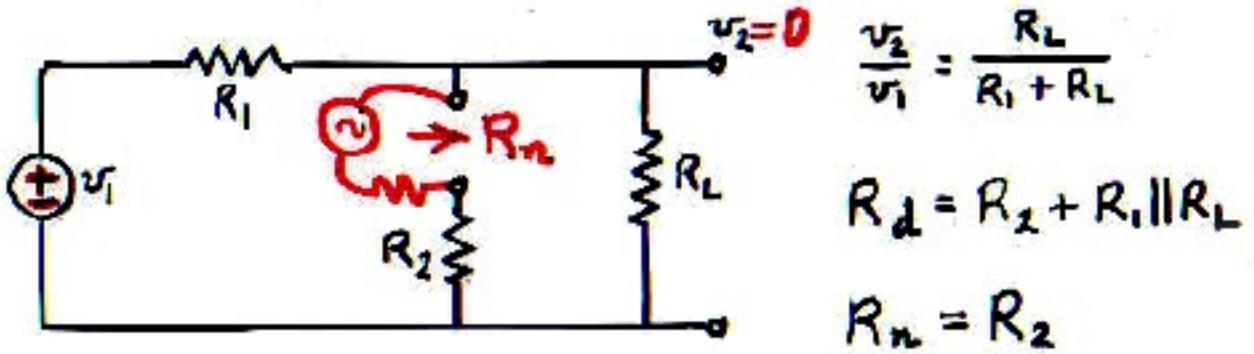

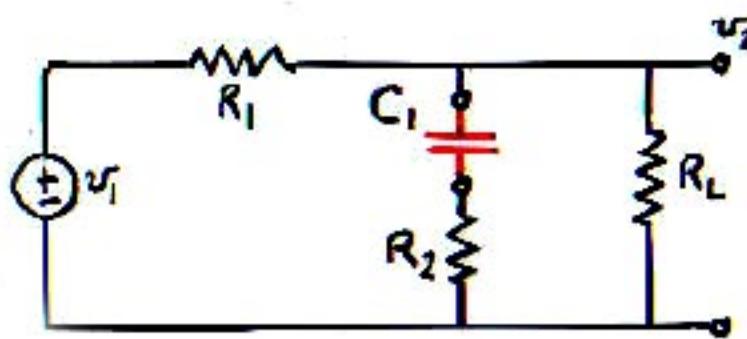

$$\frac{v_2}{v_1} = \frac{R_L}{R_1 + R_L}$$

$$R_d = R_2 + R_1 \parallel R_L$$

$$R_n = R_2$$

$$\frac{v_2}{v_1} = \frac{R_L}{R_1 + R_L} \cdot \frac{1 + sC_1 R_2}{1 + sC_1 (R_2 + R_1 \parallel R_L)}$$


The Extra Element Theorem may be used to find an extra element correction factor for any transfer function of a linear circuit. It is necessary merely to identify the "input" and "output" signals;  $Z_d$  and  $Z_n$  are then calculated as the driving point impedance seen by the extra element with the "input" zero and with the "output" nulled, respectively.

Examples of transfer functions:

- "output"  $\rightarrow$  current drawn from power supply      (a transadmittance)  
    "input"  $\rightarrow$  input voltage
- "output"  $\rightarrow$  output voltage ripple component      (a voltage gain; audio susceptibility of a power supply)  
    "input"  $\rightarrow$  Power Supply Ripple Voltage
- "output"  $\rightarrow$  corresponding driving voltage      (a self-impedance, e.g. input or output impedance)  
    "input"  $\rightarrow$  any driving current

Example: Input impedance  $Z_i$  of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

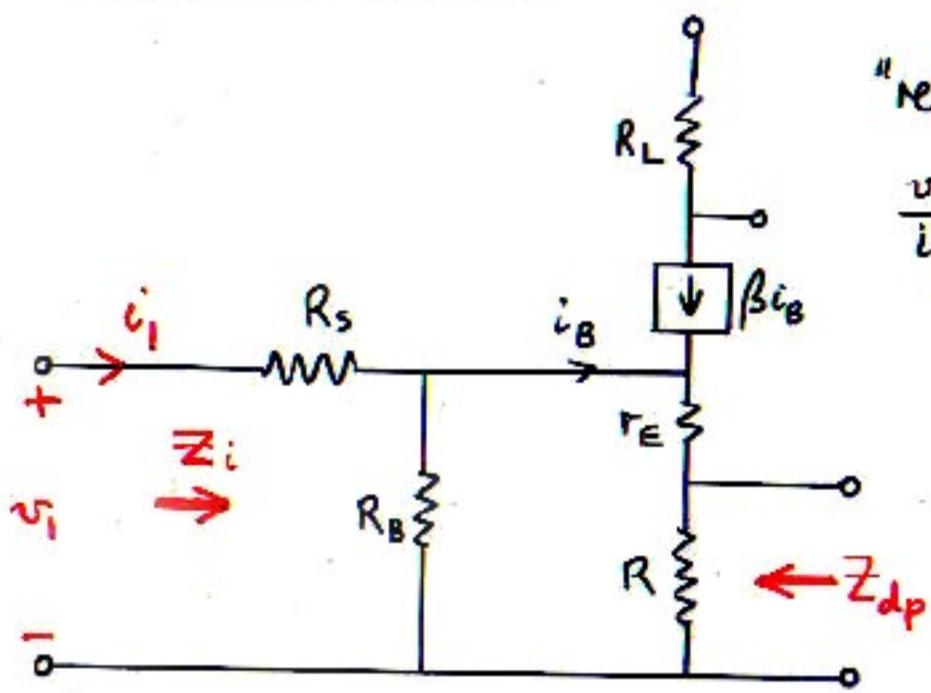


"reference transfer function":

$$\left. \frac{v_o}{i_1} \right|_{Z=0} = Z_i \left|_{Z=0} \right. = R_s + R_B \parallel (1+\beta)(r_E + R)$$

$$Z = \frac{1}{sC_E}$$

Example: Input impedance  $Z_i$  of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

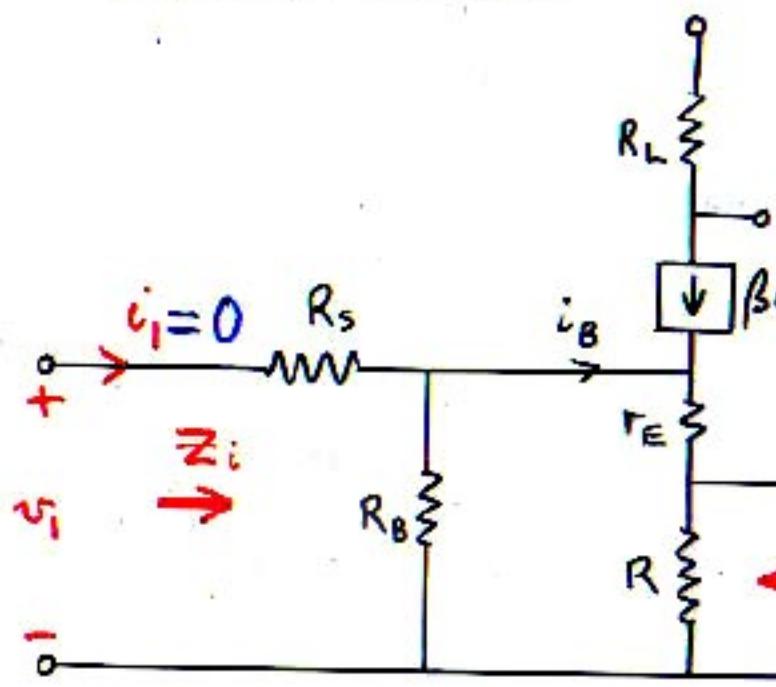

"reference transfer function":


$$\left. \frac{v_o}{i_i} \right|_{Z=0} = Z_i \left|_{Z=0} \right. = R_s + R_B \parallel (1+\beta)(r_e + R)$$

$$Z_d = \frac{1}{sC_2}$$

$$Z_d = Z_{dp} \left. \left( \begin{array}{c} \text{"input"} \\ \text{zero} \end{array} \right) \right. = Z_{dp} \Big|_{i_i=0} = R_d = R \parallel \left( r_e + \frac{R_B}{1+\beta} \right)$$

Example: Input impedance  $Z_i$  of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

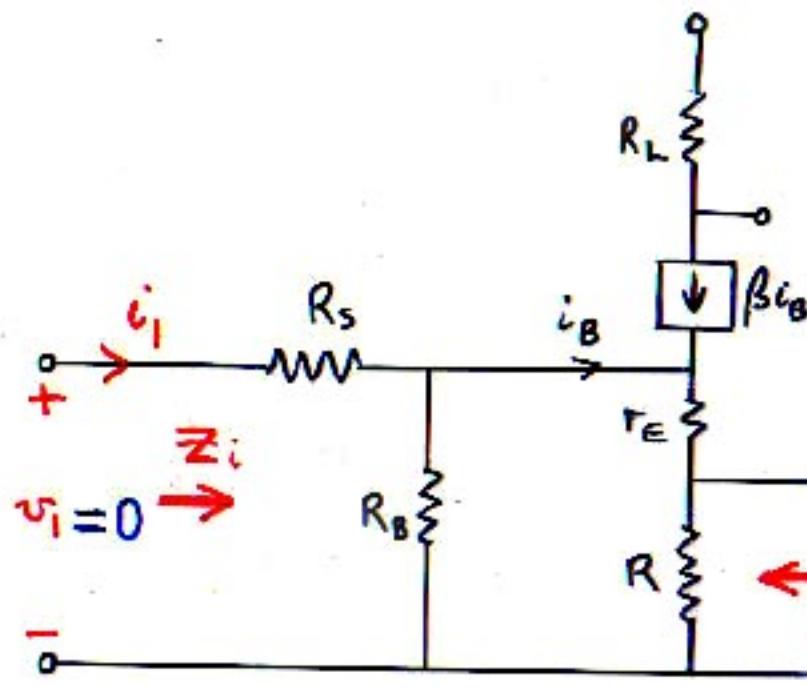

"reference transfer function":


$$\left. \frac{v_i}{i_s} \right|_{Z=\infty} = Z_i \left|_{Z=\infty} \right. = R_s + R_B \parallel (1+\beta)(r_E + R)$$

$$Z_{dp} = Z_n \quad Z = \frac{1}{sC_2}$$

$$Z_n = Z_{dp} \Big| \text{"output nulled"} = Z_{dp} \Big|_{v_o=0} = R_n = R \parallel (r_E + \frac{R_s \parallel R_B}{1+\beta})$$

Example: Input impedance  $Z_i$  of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

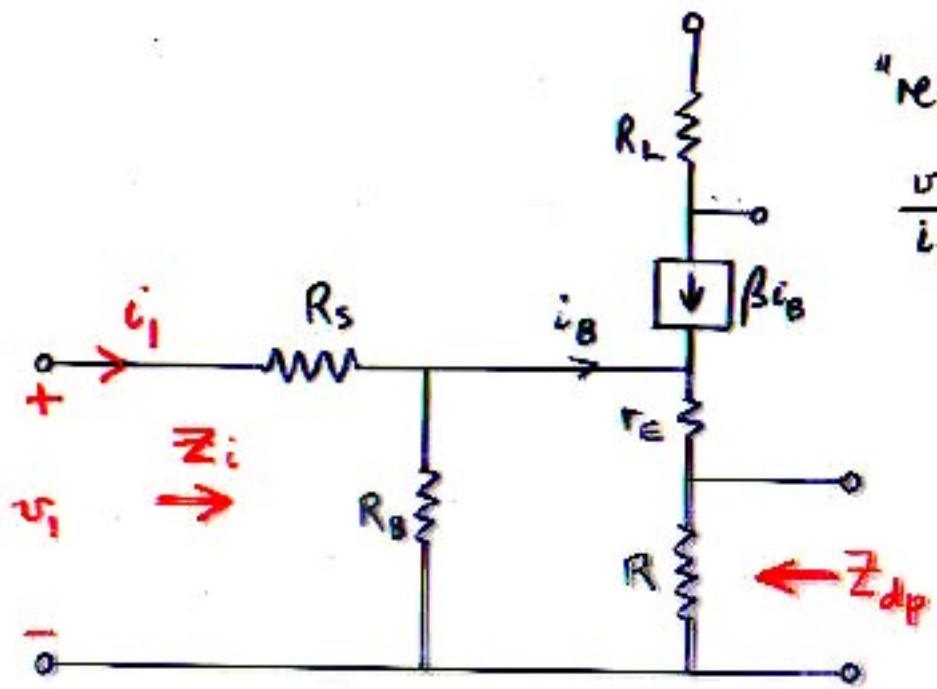

"reference transfer function":


$$\left. \frac{v_i}{i_1} \right|_{Z=\infty} = Z_i \left|_{Z=\infty} \right. = R_s + R_B \parallel (1+\beta)(r_e + R)$$

$$Z = \frac{1}{sC_2}$$

Hence,  $Z_i = [R_s + R_B \parallel ((1+\beta)(r_e + R))] \frac{1 + sC_2 R_n}{1 + sC_2 R_d}$

Example: Input impedance  $Z_i$  of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

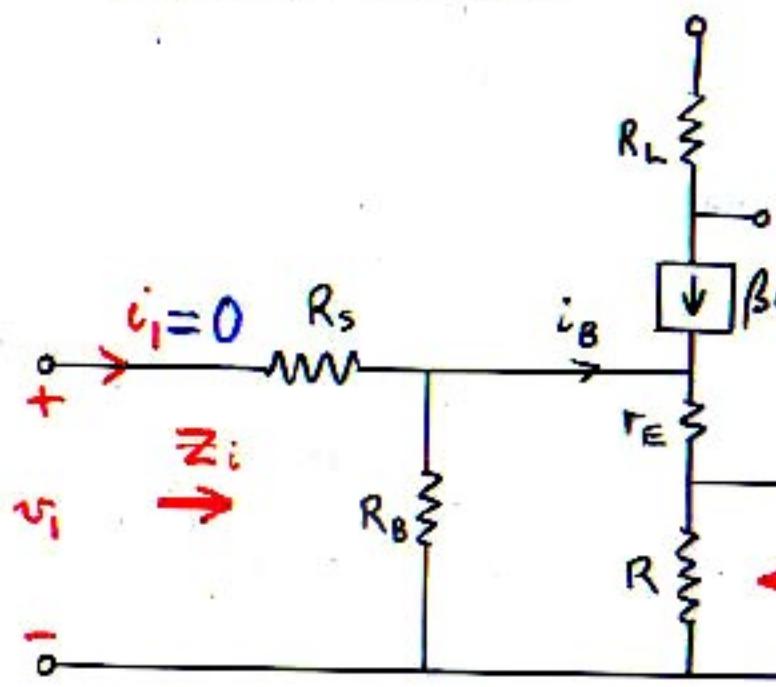


"reference transfer function":

$$\left. \frac{v_o}{i_i} \right|_{Z=0} = Z_i \left|_{Z=0} \right. = R_s + R_B \parallel (1+\beta)(r_e + R)$$

$$Z_d = \frac{1}{sC_2}$$

$$Z_d = Z_{dp} \left. \left( \begin{array}{l} \text{"input"} \\ \text{zero} \end{array} \right) \right. = Z_{dp} \Big|_{i_i=0} = R_d = R \parallel \left( r_e + \frac{R_B}{1+\beta} \right)$$

"Reference circuit":

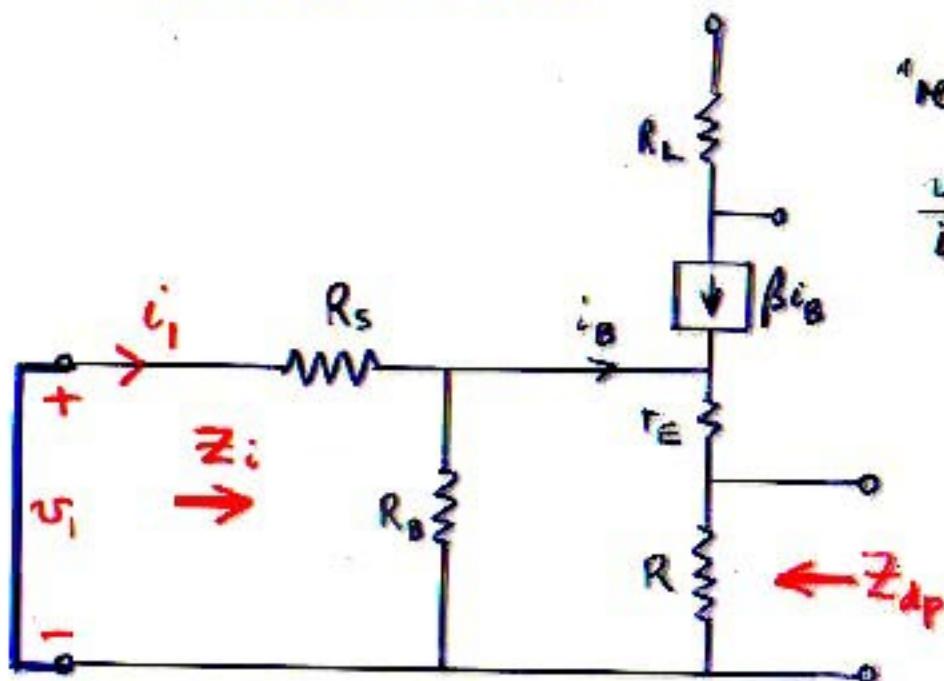


"reference transfer function":

$$\left. \frac{v_i}{i_1} \right|_{z=0} = Z_i \left|_{z=0} \right. = R_s + R_o \parallel (1+\beta)(r_E + R)$$

A circuit symbol for a capacitor, consisting of two parallel lines forming a loop. To the right of the symbol, the equation  $Z = \frac{1}{SC_2}$  is written.


NOTE: In the special case of a self-impedance, nulling the "output" voltage is the same as shorting the "input" current, because the "output" and "input" are at the same node pair.

Example: Lag-lead network

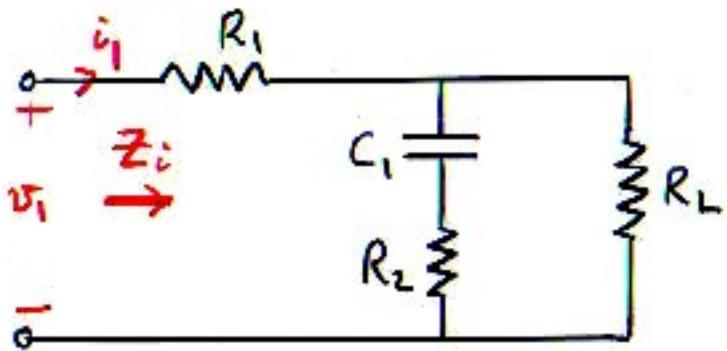

Find the input impedance  $Z_i = v_i / i_1$  by designating  $C_1$  as an "extra" element.


"Reference circuit":

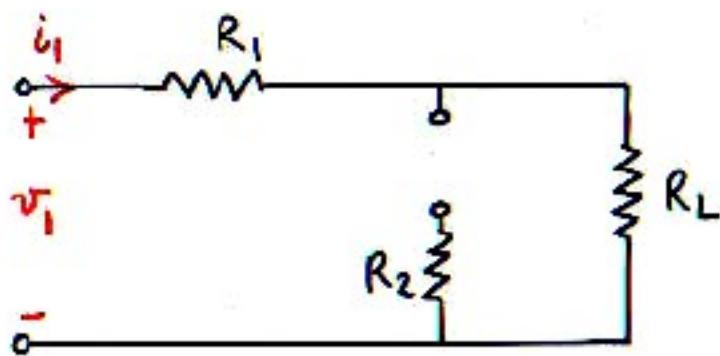

"Reference" input impedance:

$$Z_i|_{z=\infty} = \frac{v_i}{i_1}|_{z=\infty} = R_1 + R_L$$

"Reference circuit:"

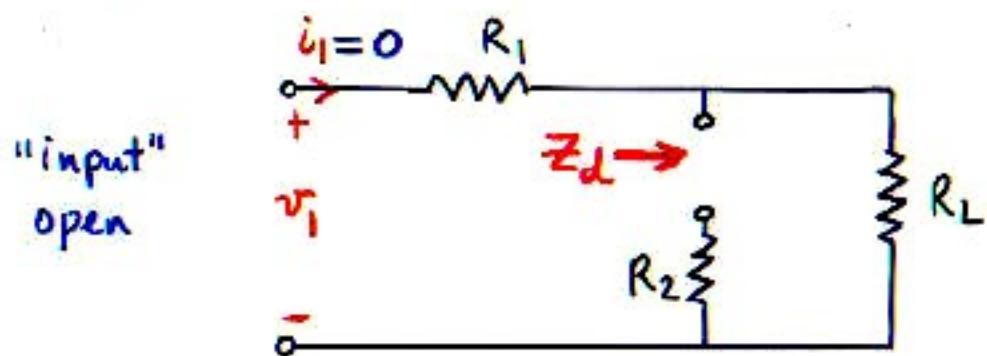


"input"  
open

"Reference" input impedance:

$$Z_i|_{z=\infty} = \frac{v_1}{i_1}|_{z=\infty} = R_1 + R_L$$

$$Z_d = R_d = R_2 + R_L$$

"Reference circuit:"

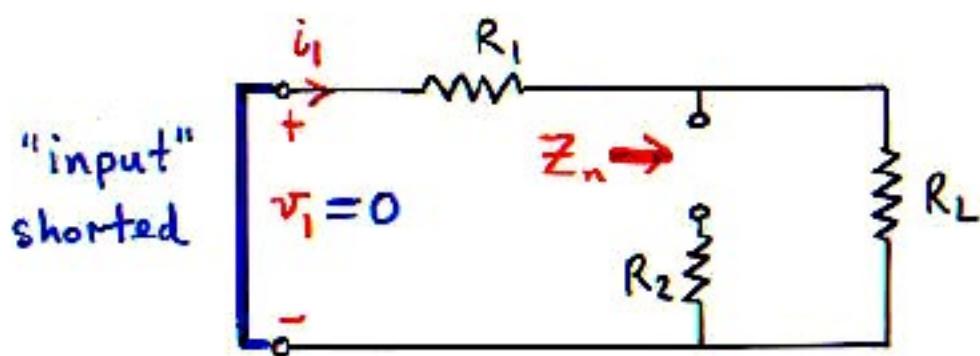

"Reference" input impedance:


$$Z_i|_{z=0} = \frac{v_1}{i_1}|_{z=0} = R_1 + R_L$$

$$Z_n = R_n = R_2 + R_1 \parallel R_L$$


Hence:

$$Z_i = (R_1 + R_L) \frac{1 + sC_1 R_n}{1 + sC_1 R_d}$$


Exercise: Lag-lead network

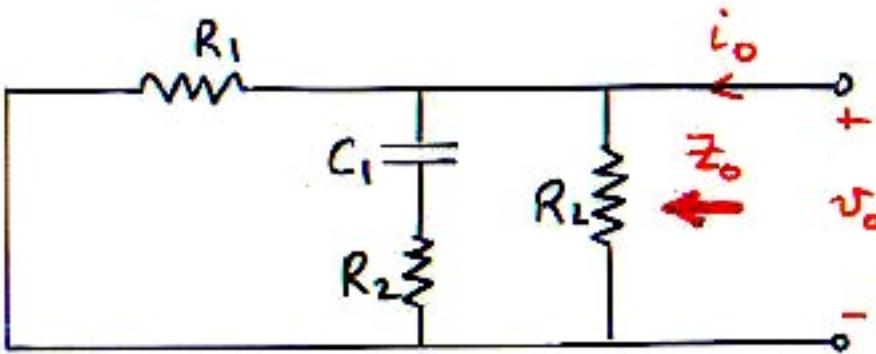

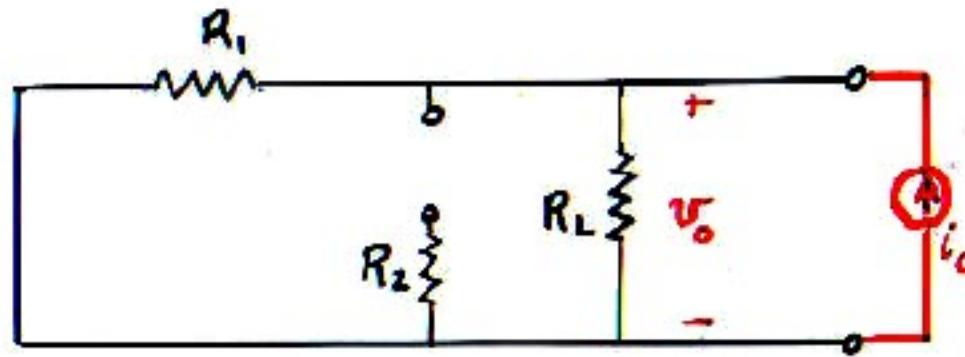Find the output impedance  $Z_o = v_o / i_o$  by designating  $C_1$  as an "extra" element.




$$Z_o \Big|_{Z=\infty} \equiv \frac{v_o}{i_o} \Big|_{Z=\infty} = R_1 \parallel R_L$$

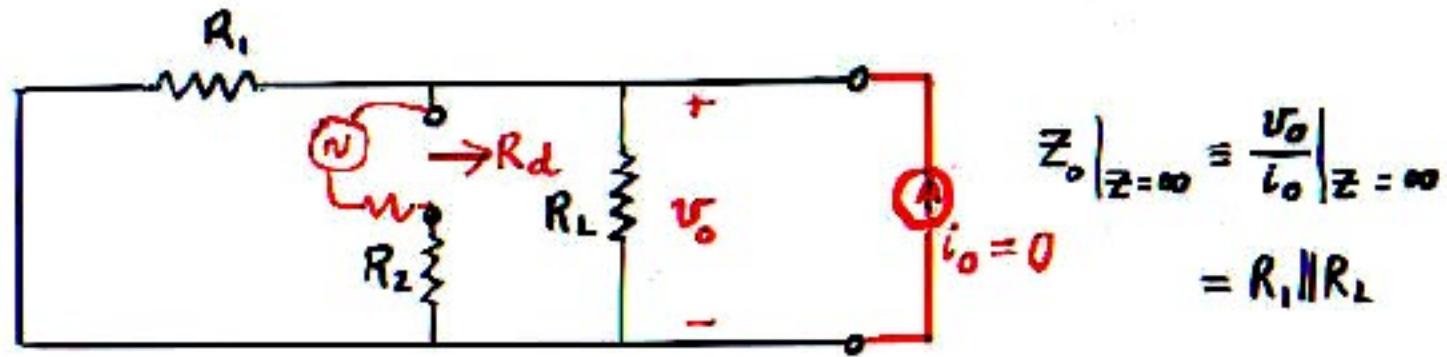

$$\begin{aligned}
 Z_o|_{Z=\infty} &\equiv \frac{v_o}{i_o}|_{Z=\infty} \\
 &= R_1 \parallel R_L
 \end{aligned}$$

$$R_d = R_2 + R_1 \parallel R_L$$

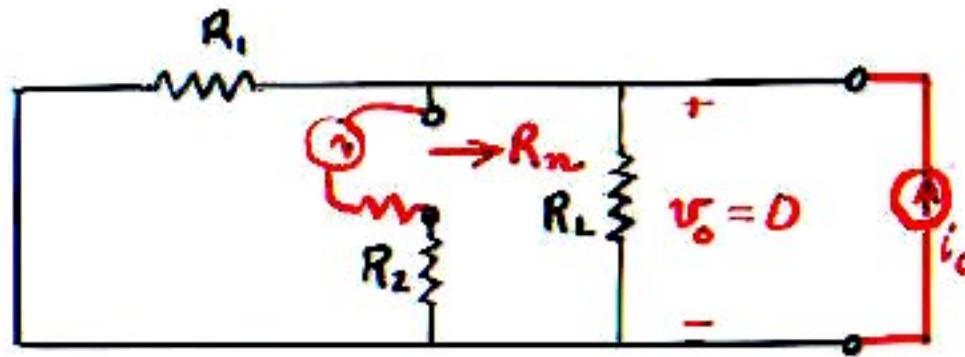

$$Z_0|_{Z=\infty} \equiv \frac{V_0}{i_0}|_{Z=\infty} = R_1 \parallel R_L$$

$$R_d = R_2 + R_1 \parallel R_L$$

$$R_n = R_2$$

With  $C_1$  replaced:

$$Z_0 = R_1 \parallel R_L \frac{1 + s C_1 R_2}{1 + s C_1 (R_2 + R_1 \parallel R_2)}$$

### Generalization: Extra Element Theorem - #4


The Extra Element theorem can be used to find an extra element correction factor for any transfer function;  $Z_d$  and  $Z_n$  are then the driving point impedances seen by the extra element with the "input" zero and with the "output" nulled, respectively.

When the transfer function is a self-impedance, such as the input impedance  $Z_i$  or the output impedance  $Z_o$ , nulling the "output" is the same as shorting the "input," hence


$$Z_d = Z_{dp} \left| \begin{array}{l} \text{"input" zero} \\ \text{---} \\ \text{"input" open} \end{array} \right. = Z_{dp} \left| \begin{array}{l} \text{"input" open} \end{array} \right.$$

$$Z_n = Z_{dp} \left| \begin{array}{l} \text{"output" nulled} \\ \text{---} \\ \text{"input" shorted} \end{array} \right. = Z_{dp} \left| \begin{array}{l} \text{"input" shorted} \end{array} \right.$$

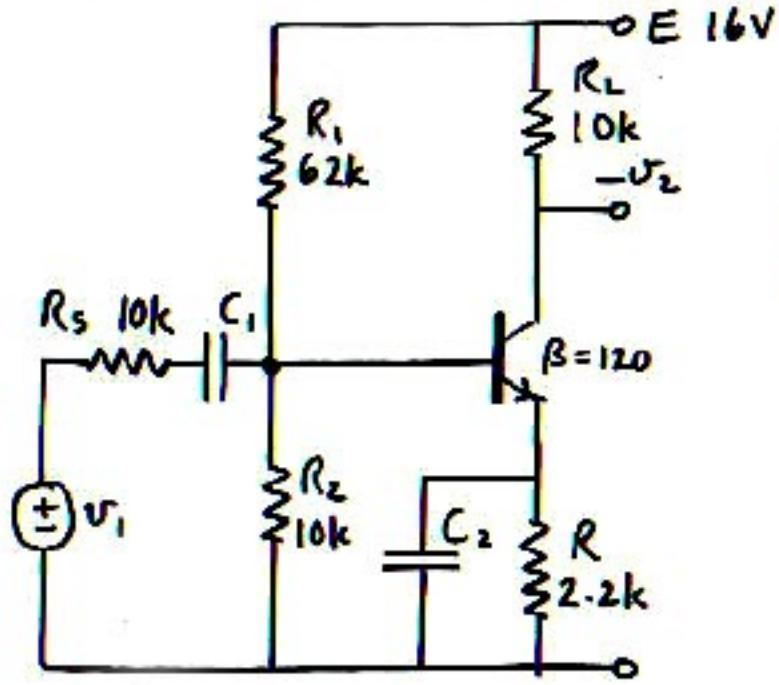
## High-frequency properties of CE amplifier



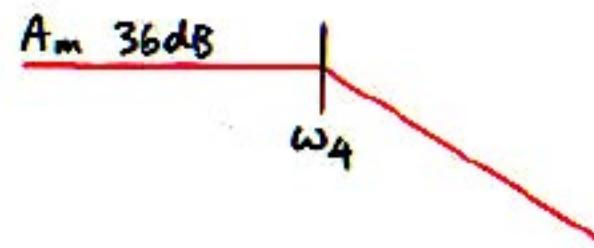Measurement indicates that there is a high-frequency pole  $\omega_4$ :



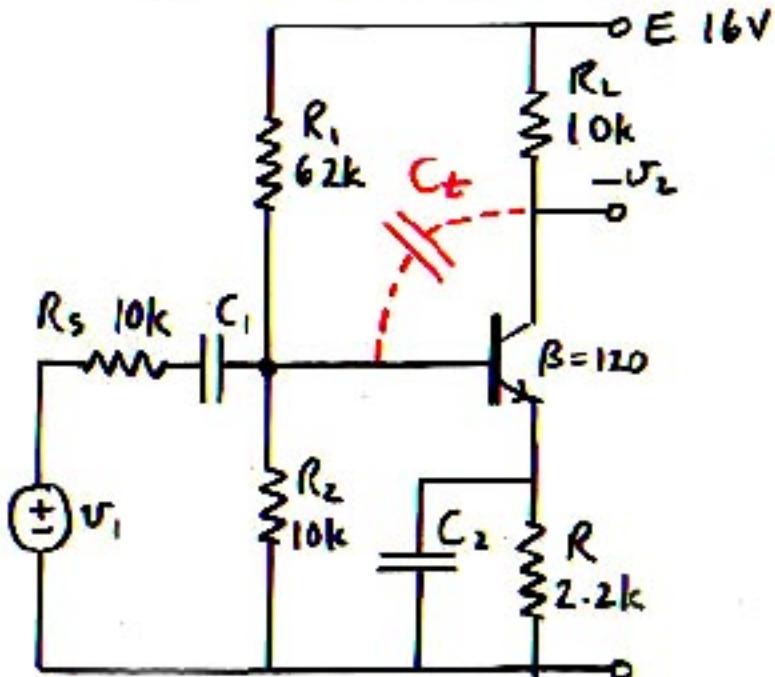
## High-frequency properties of CE amplifier



Measurement indicates that there is a high-frequency pole  $\omega_4$ :


$A_m = 36\text{dB}$

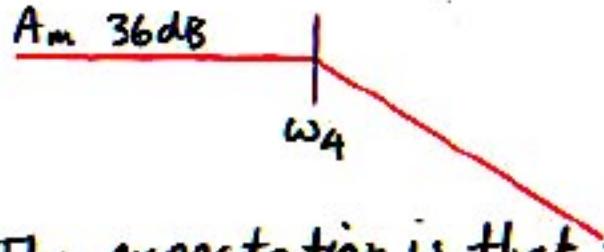


The expectation is that this is caused by the collector-base transition-layer capacitance  $C_t$ .

A typical value is  $C_t = 5\text{pF}$ . The resulting corner frequency with  $R_L = 10k$  is  $159/5 \times 10^{-6} \times 10 = 3.2\text{MHz}$ . Since the actual corner frequency is much lower, there must be a multiplying effect on  $C_t$  resulting from its connection to the transistor base instead of to ground.
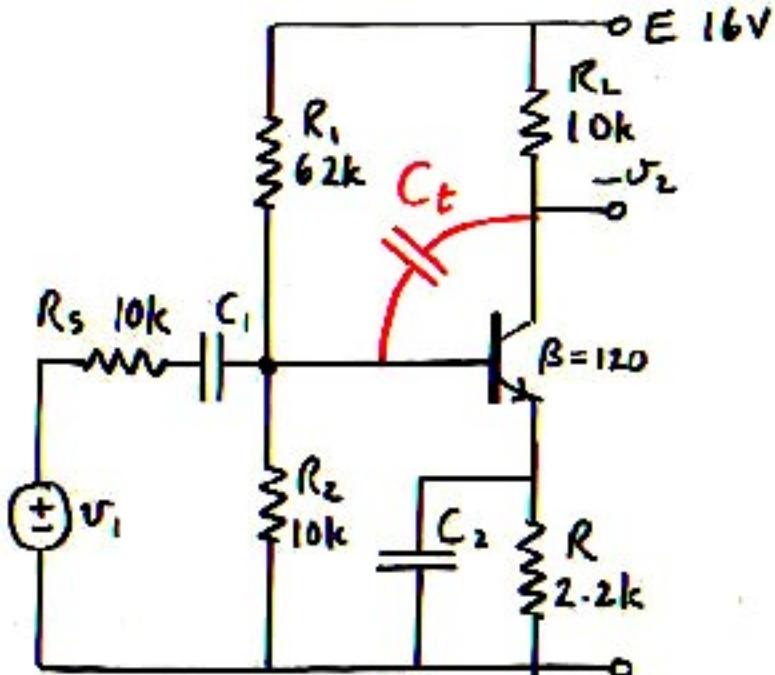
## High-frequency properties of CE amplifier




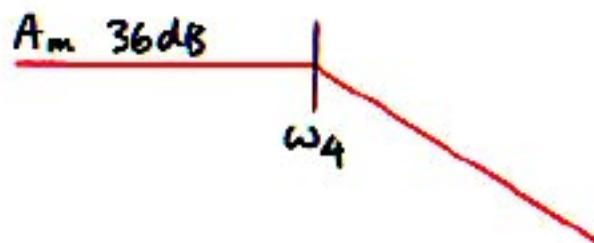Measurement indicates that there is a high-frequency pole  $\omega_4$ :




Since the midband gain  $A_m = 36\text{dB}$  has already been determined, use the Extra Element Theorem to find the correction factor resulting from inclusion of  $Z \rightarrow 1/sC_t$ .

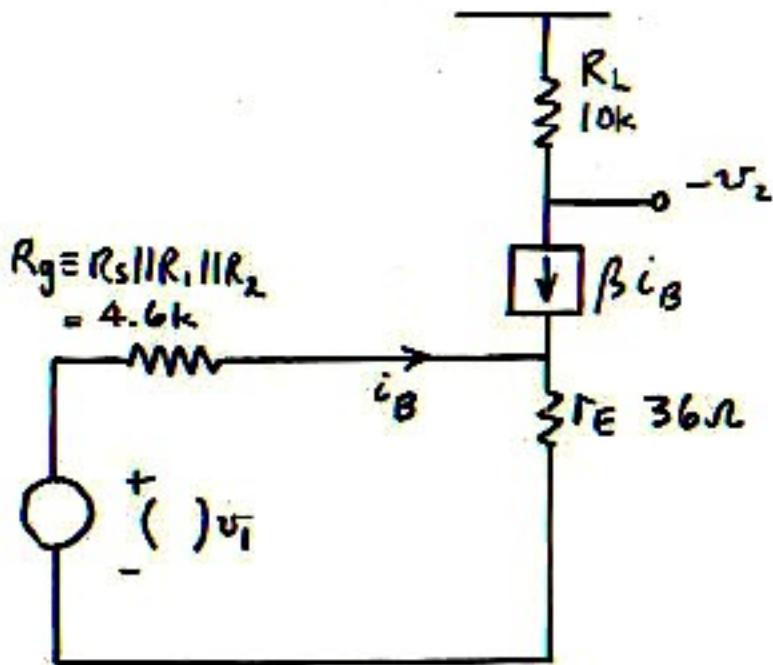Midband model after Thevenin reduction of  $R_s, R_i, R_2$ :




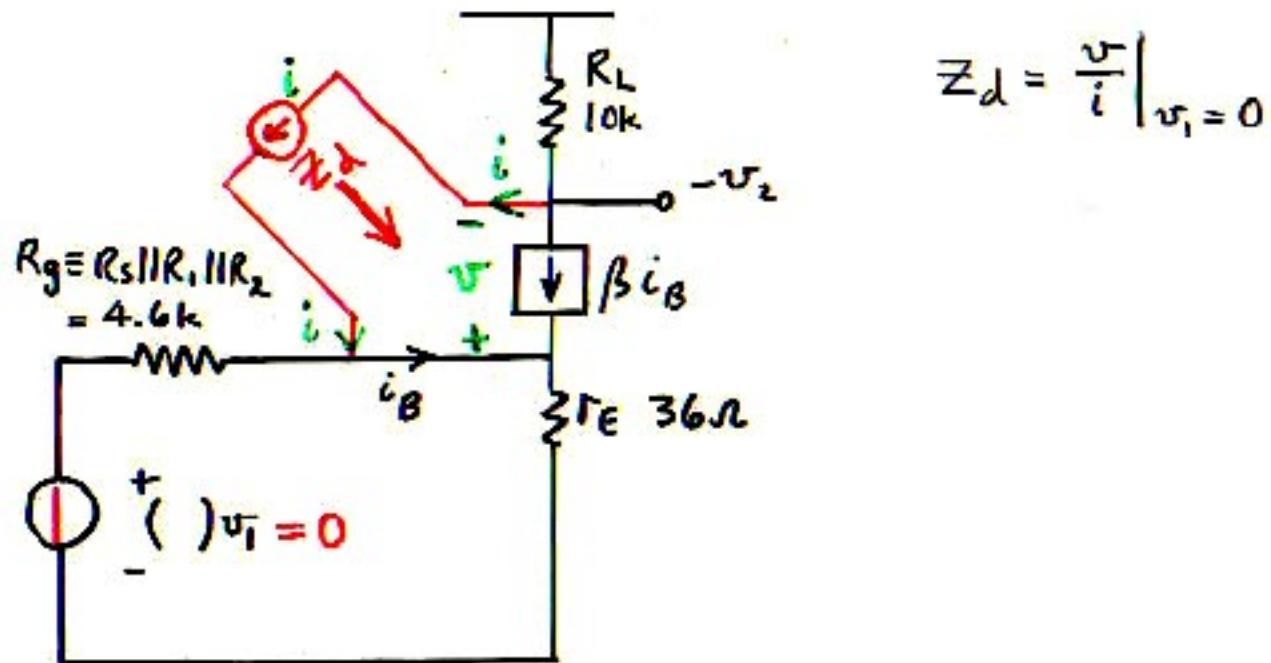Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :




$$Z_d = \frac{v}{i} \Big|_{v_1=0}$$

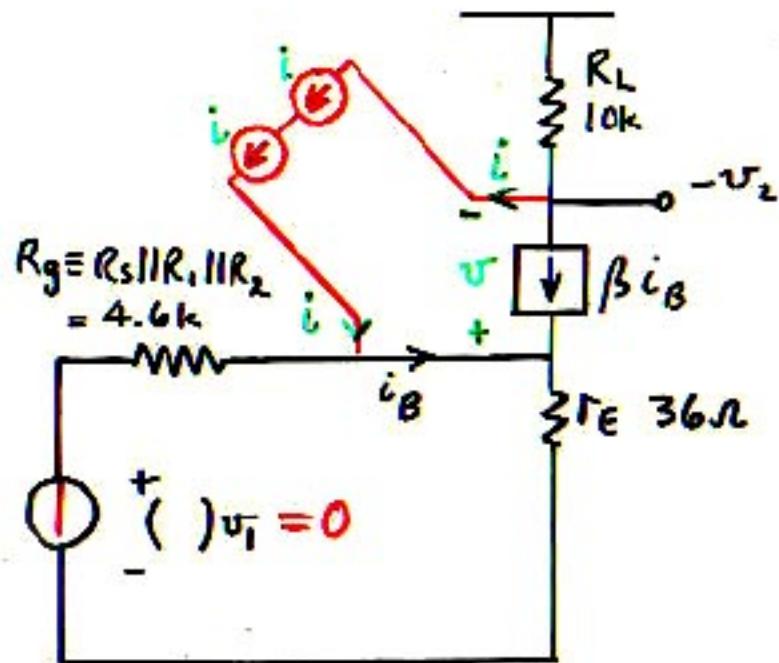Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :



The current generator  $i$  can be divided into two equal current generators in series.

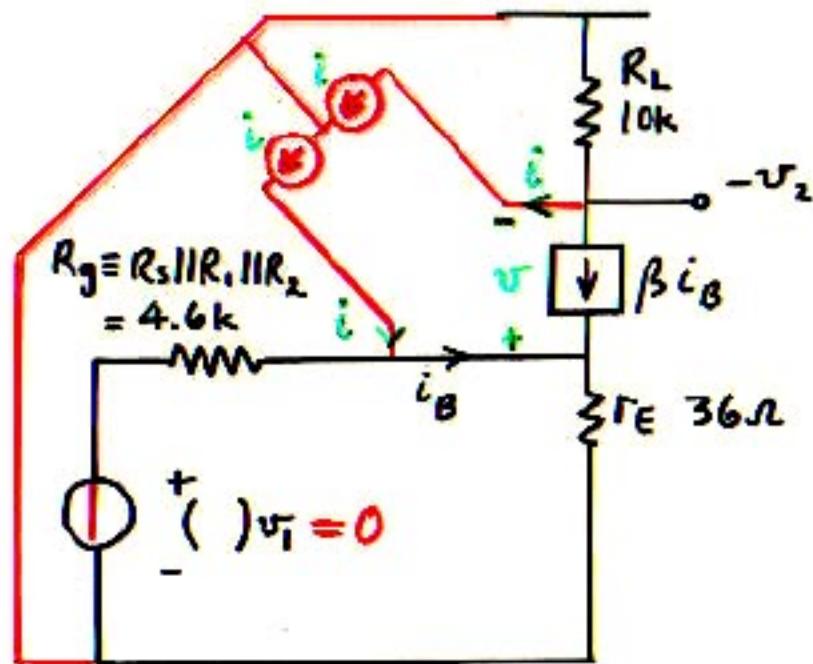
Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :



The current generator  $i$  can be divided into two equal current generators in series.


Since the voltage at the junction of the two current generators  $i$  is immaterial, the junction can be grounded.

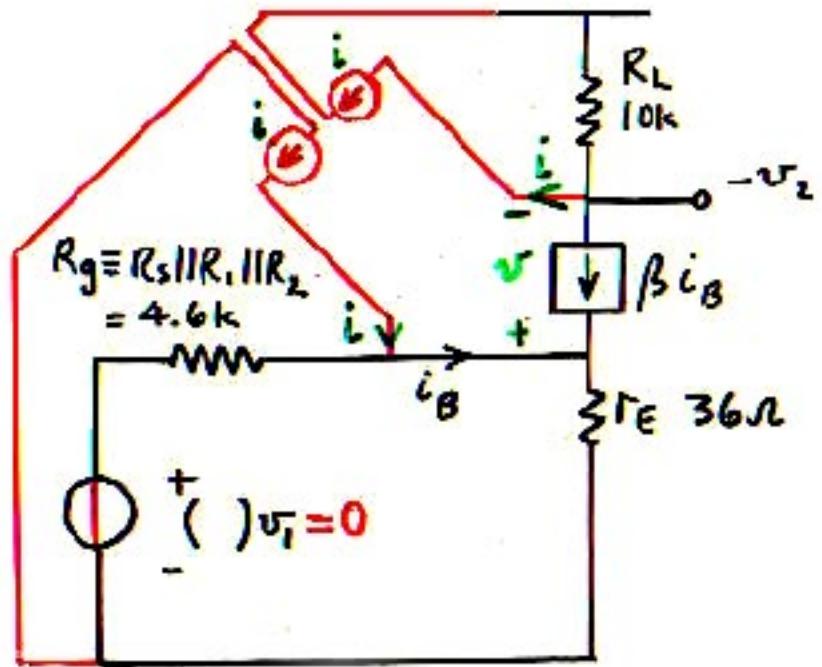Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :



A separate ground can be identified for each current generator  $i$ .

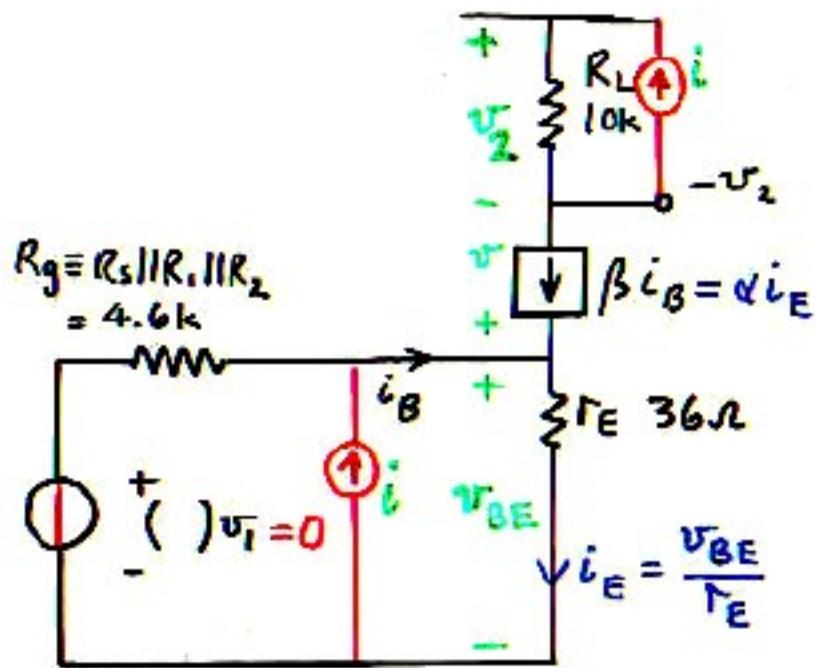Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :



Rearranged diagram.

$$Z_d = R_d = \frac{v}{i} = \frac{v_{BE}}{i} + \frac{v_2}{i}$$

$$v_{BE} = [R_g \parallel (1+\beta)r_E] i$$

$$v_2 = R_L (\alpha i_E + i) = R_L \left( \frac{\alpha}{r_E} v_{BE} + i \right)$$

$$R_d = \frac{v_{BE}}{i} + R_L \left( \frac{\alpha}{r_E} \frac{v_{BE}}{i} + 1 \right)$$

$$R_d = \left( 1 + \frac{\alpha R_L}{r_E} \right) [R_g \parallel (1+\beta)r_E] + R_L = R_L \left[ R_g \parallel (1+\beta)r_E \right] \left[ \frac{1}{R_L} + \frac{\alpha}{r_E} + \frac{1}{R_g \parallel (1+\beta)r_E} \right]$$

$$= R_L \left[ R_g \parallel (1+\beta)r_E \right] \left[ \frac{1}{R_L} + \frac{\beta}{(1+\beta)r_E} + \frac{1}{R_g} + \frac{1}{(1+\beta)r_E} \right]$$


$$= \frac{R_g \parallel (1+\beta)r_E}{R_g \parallel r_E \parallel R_L} R_L = \frac{4.6 \parallel 4.3}{4.6 \parallel 0.036 \parallel 10} R_L = 62 R_L = 620\text{k}$$

Generalization: Floating Current Generator

A floating current generator can be replaced by two separate, equal, grounded current generators.

This is a useful technique in "doing the algebra on the circuit diagram."

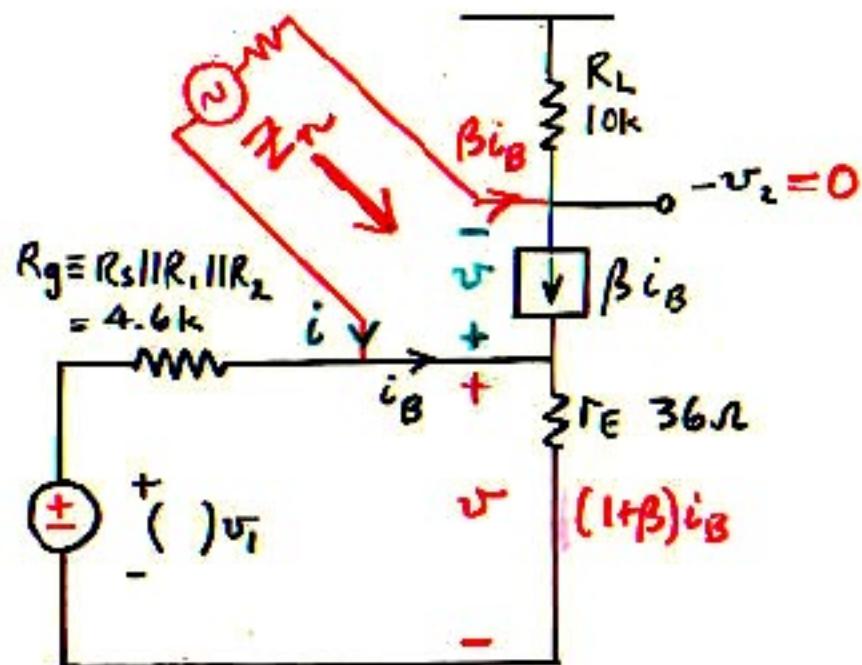
Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :



$$Z_n = R_n = \frac{v}{i} = \frac{(1+\beta)r_E i_B}{-\beta i_B} = -\frac{r_E}{\alpha} = -36\Omega$$

Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :

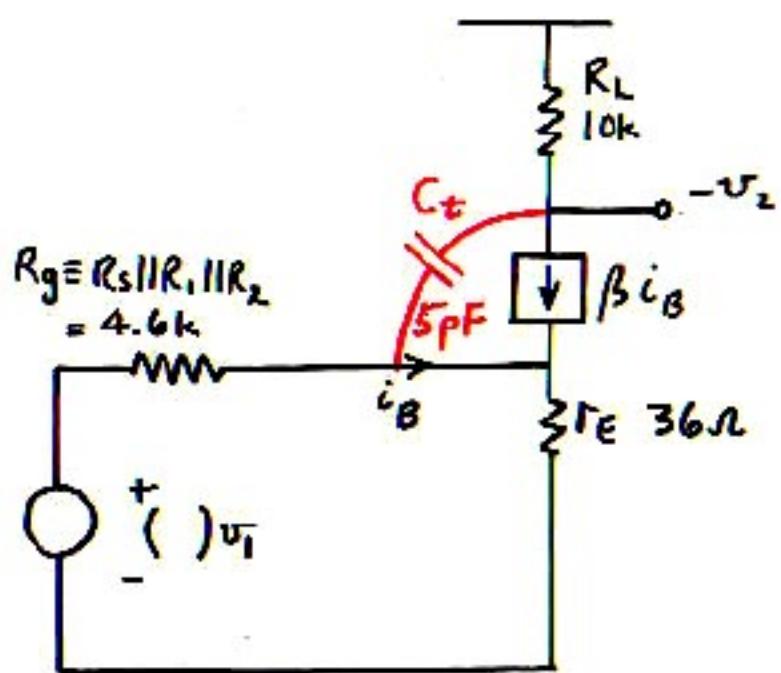Hence corrected gain after inclusion of  $C_t$  is



$$A = A_m \frac{1 + \frac{Z_n}{Z}}{1 + \frac{Z_d}{Z}} = A_m \frac{1 + sC_t + R_n}{1 + sC_t R_d}$$


$$= A_m \frac{1 - \frac{s}{\omega_4}}{1 + \frac{s}{\omega_4}} \quad \text{where}$$

$$\omega_4 \equiv \frac{1}{C_t R_d} \quad f_4 = \frac{159}{5 \times 10^{-6} \times 620} = 51\text{kHz}$$

$$\omega_5 \equiv \frac{1}{C_t R_n} \quad f_5 = \frac{159}{5 \times 10^{-6} \times 0.036} = 880\text{MHz}$$

Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :

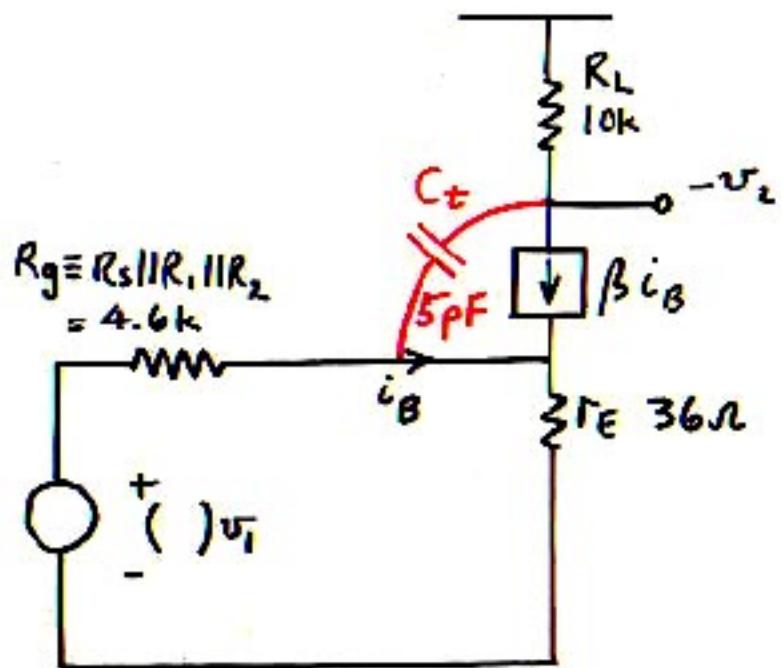Hence corrected gain after inclusion of  $C_t$  is



$$A = A_m \frac{1 + \frac{Z_n}{Z}}{1 + \frac{Z_d}{Z}} = A_m \frac{1 + sC_t R_n}{1 + sC_t R_d}$$

$$= A_m \frac{1 - \frac{s}{\omega_5}}{1 + \frac{s}{\omega_4}} \quad \text{where}$$

$$\omega_4 \equiv \frac{1}{C_t R_d} \quad f_4 = \frac{159}{5 \times 10^{-6} \times 620} = 51\text{kHz}$$

$$\omega_5 \equiv \frac{1}{C_t R_n} \quad f_5 = \frac{159}{5 \times 10^{-6} \times 0.036} = 880\text{MHz}$$


Note that the zero  $\omega_5 = \frac{1}{C_t R_n} = \frac{\alpha}{C_t R_E}$  is negative (right half-plane), and is at a very high frequency unless there is substantial external emitter resistance and/or there is substantial external collector-base capacitance (as often exists).

Note that the pole  $\omega_4 = \frac{1}{C_t R_d} = \frac{1}{C_t R_L} \frac{R_g R_{re} || R_L}{R_g || (1+\beta) r_E}$  is at a much lower frequency than  $\omega_5 = \frac{1}{C_t R_L}$ , and can be ascribed to an effective multiplication of  $C_t$  by a factor


$$m \equiv \frac{R_g || (1+\beta) r_E}{R_g || r_E || R_L} = \frac{R_g || (1+\beta) r_E}{R_g || r_E} \left( 1 + \frac{R_g || r_E}{R_L} \right)$$

$R_g \gg (1+\beta) r_E \rightarrow 1 + \beta$   
 $R_g \ll r_E \rightarrow 1$

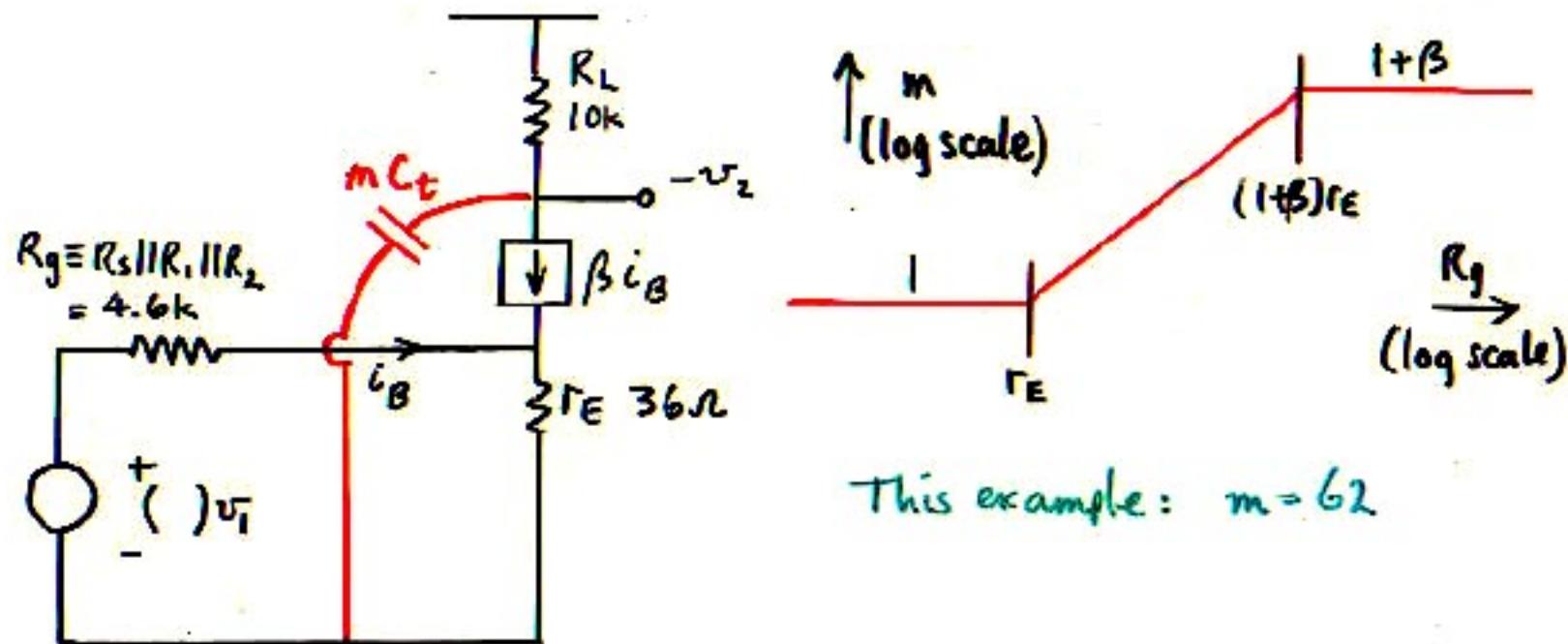Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :



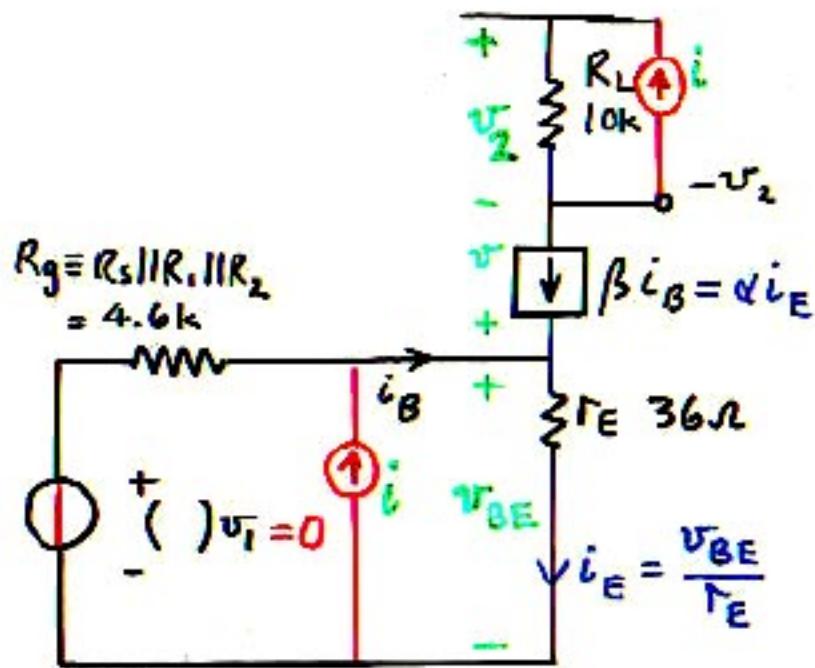Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :



Rearranged diagram.

$$Z_d = R_d = \frac{v}{i} = \frac{v_{BE}}{i} + \frac{v_2}{i}$$

$$v_{BE} = [R_g \parallel (1+\beta)r_E] i$$



$$v_2 = R_L (\alpha i_E + i) = R_L \left( \frac{\alpha}{r_E} v_{BE} + i \right)$$

$$R_d = \frac{v_{BE}}{i} + R_L \left( \frac{\alpha}{r_E} \frac{v_{BE}}{i} + 1 \right)$$

$$R_d = \left( 1 + \frac{\alpha R_L}{r_E} \right) [R_g \parallel (1+\beta)r_E] + R_L = R_L \left[ R_g \parallel (1+\beta)r_E \right] \left[ \frac{1}{R_L} + \frac{\alpha}{r_E} + \frac{1}{R_g \parallel (1+\beta)r_E} \right]$$

$$= R_L \left[ R_g \parallel (1+\beta)r_E \right] \left[ \frac{1}{R_L} + \frac{\beta}{(1+\beta)r_E} + \frac{1}{R_g} + \frac{1}{(1+\beta)r_E} \right]$$
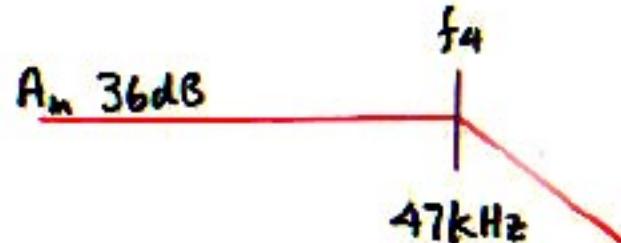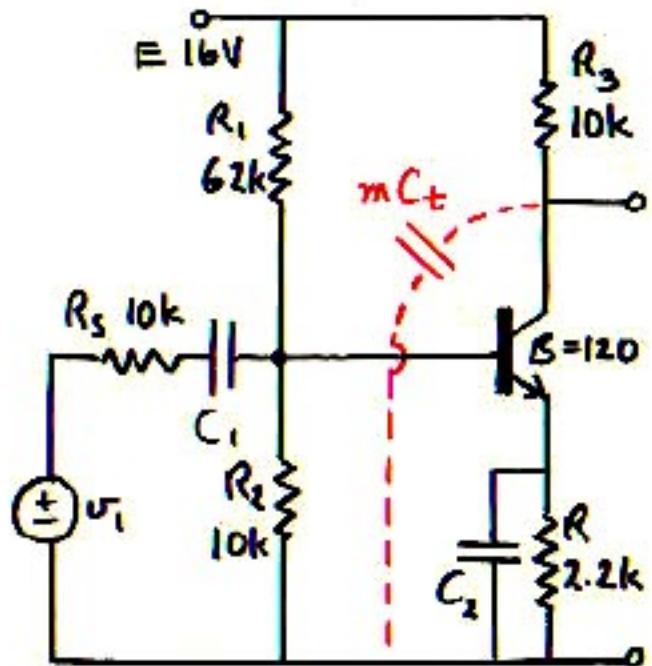
$$= \frac{R_g \parallel (1+\beta)r_E}{R_g \parallel r_E \parallel R_L} R_L = \frac{4.6 \parallel 4.3}{4.6 \parallel 0.036 \parallel 10} R_L = 62 R_L = 620\text{k}$$



By measurement,  $f_4 = 47\text{kHz}$ ; hence


$$mC_t = \frac{159}{0.047 \times 10} = 340\text{pF}$$

So:

$$C_t = 340/62 = 5.5\text{pF}$$

(Note: 13 pF of 10:1 scope probe is negligible)

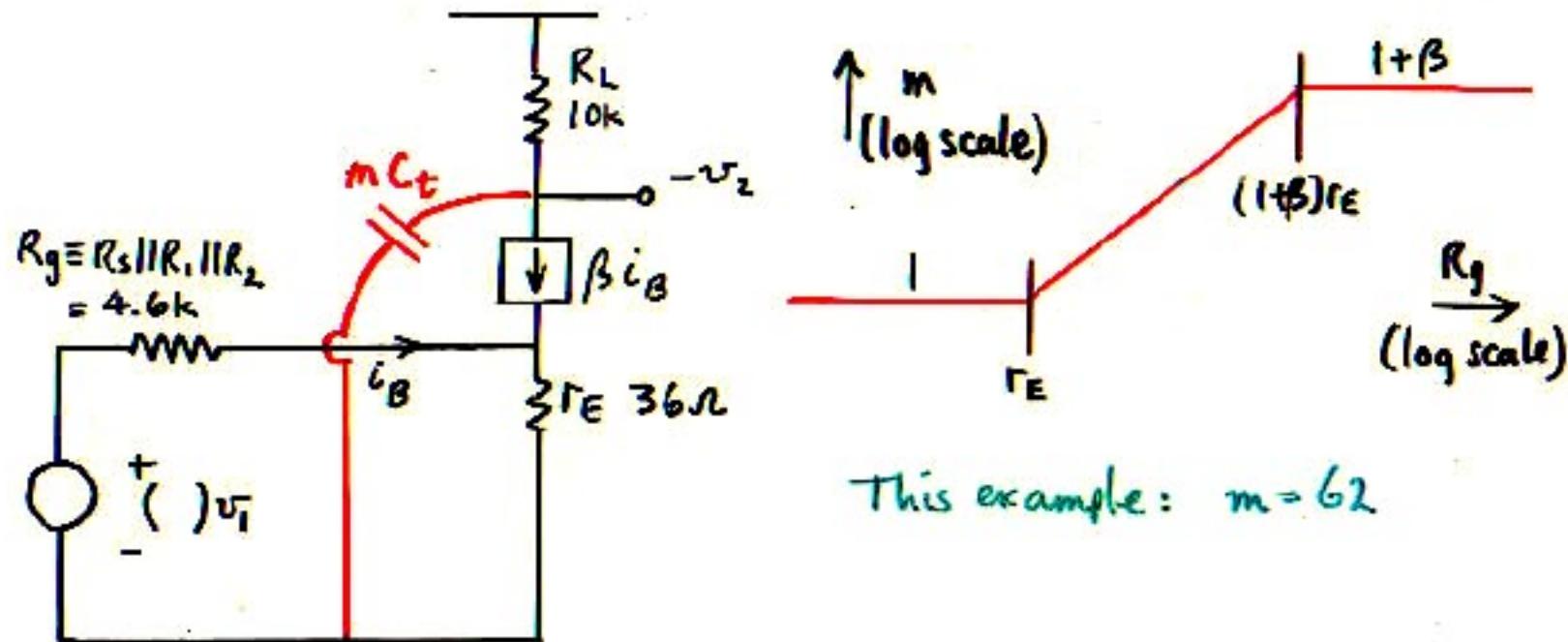Midband model after Thevenin reduction of  $R_s, R_1, R_2$ :



Alternative method for calculation of  $Z_d$

There are two forms of the Extra Element theorem:

$$A = A|_{z=\infty} \frac{1 + \frac{z_n}{z}}{1 + \frac{z_d}{z}} = A|_{z=0} \frac{1 + \frac{z}{z_n}}{1 + \frac{z}{z_d}}$$

where  $A|_{z=0} = \frac{z_n}{z_d} A|_{z=\infty}$

Hence in general

$$\frac{A|_{z=0}}{A|_{z=\infty}} = \frac{z_n}{z_d}$$

It may be easier to find  $A|_{z=0}$ ,  $A|_{z=\infty}$ , and  $z_n$  than to find  $Z_d$  directly.

Example: Addition of collector-base capacitance  $C_t$  to the CE amplifier stage.  $A|_{z=\infty}$  and  $z_n$  were easily found:

$$A|_{z=\infty} = A_m = \frac{R_B}{R_s + R_B} \cdot \frac{\beta R_L}{R_g + (1+\beta) r_E} \quad z_n = R_n = -\frac{r_E}{\alpha}$$

The Extra Element Theorem as derived applies to the correction factor resulting from an extra shunt element.

There is a corresponding form to find the correction factor resulting from an extra series element:

$$\text{reference gain} \downarrow$$

$$\text{gain } |_{Z} = \text{gain } |_{Z=\infty} \frac{1 + \frac{z_n}{Z}}{1 + \frac{z_d}{Z}}$$

$$= \text{gain } |_{Z=\infty} \frac{\frac{z_n}{Z}}{\frac{z_d}{Z}} \frac{\frac{Z}{z_n} + 1}{\frac{Z}{z_d} + 1}$$

$$\text{reference gain} \downarrow$$

$$= \text{gain } |_{Z=0} \frac{1 + \frac{Z}{z_n}}{1 + \frac{Z}{z_d}}$$

$$= \left( \frac{z_n}{z_d} \cdot \text{gain } |_{Z=\infty} \right) \frac{1 + \frac{Z}{z_n}}{1 + \frac{Z}{z_d}}$$

This must be  
the gain when  $Z=0$

Alternative method for calculation of  $Z_d$

There are two forms of the Extra Element theorem:

$$A = A|_{z=\infty} \frac{1 + \frac{z_n}{z}}{1 + \frac{z_d}{z}} = A|_{z=0} \frac{1 + \frac{z}{z_n}}{1 + \frac{z}{z_d}}$$

where  $A|_{z=0} = \frac{z_n}{z_d} A|_{z=\infty}$

Hence in general


$$\frac{A|_{z=0}}{A|_{z=\infty}} = \frac{z_n}{z_d}$$

It may be easier to find  $A|_{z=0}$ ,  $A|_{z=\infty}$ , and  $z_n$  than to find  $Z_d$  directly.


Example: Addition of collector-base capacitance  $C_t$  to the CE amplifier stage.  $A|_{z=\infty}$  and  $z_n$  were easily found:

$$A|_{z=\infty} = A_m = \frac{R_B}{R_s + R_B} \cdot \frac{\beta R_L}{R_g + (1 + \beta) r_E} \quad z_n = R_n = -\frac{r_E}{\alpha}$$

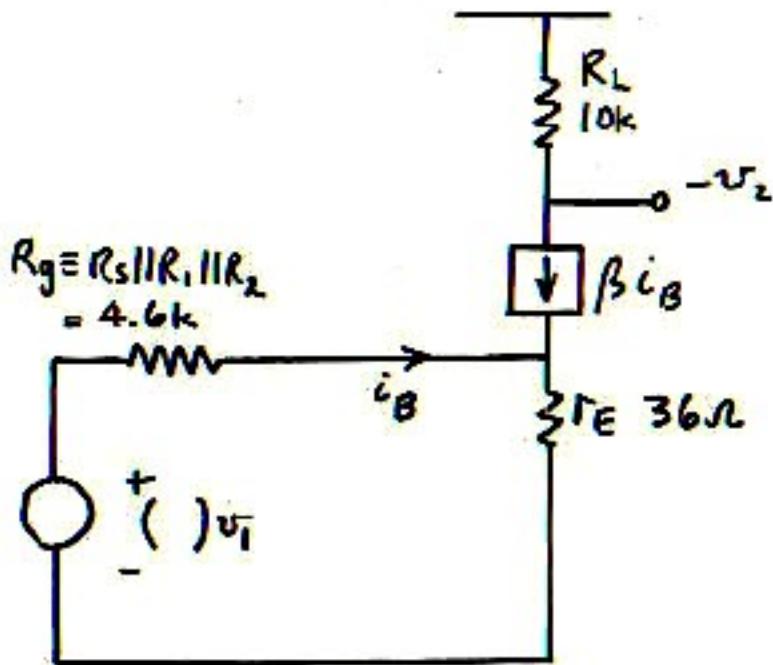Midband model after Thevenin reduction of  $R_s, R_i, R_2$ :



Model for calculation of  $A|_{z=0}$

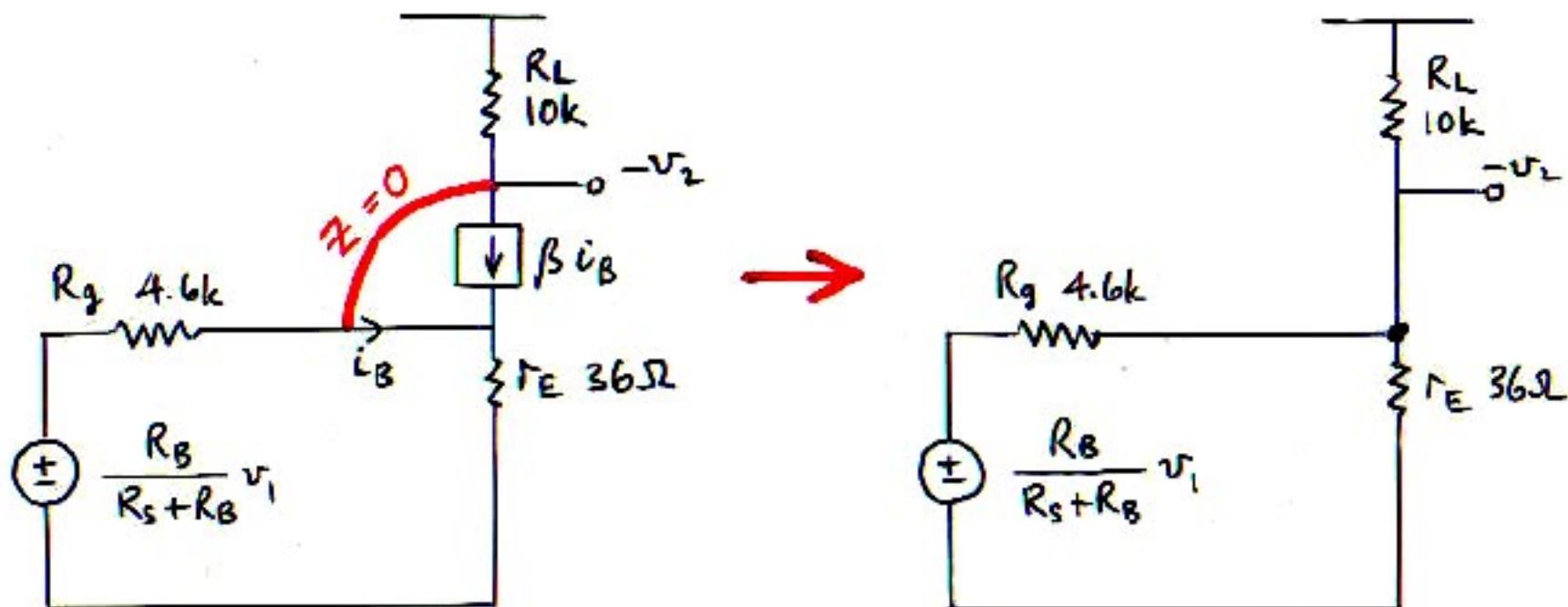

$$A|_{z=0} = -\frac{R_B}{R_s + R_B} \frac{r_E \parallel R_L}{R_g + r_E \parallel R_L} = -\frac{R_B}{R_s + R_B} \frac{R_g \parallel r_E \parallel R_L}{R_g}$$

Hence:

$$Z_d = R_d = R_n \frac{A|_{z=\infty}}{A|_{z=0}} = \frac{r_E}{\alpha} \frac{\beta R_L}{R_g + (1+\beta)r_E} \frac{R_g}{R_g \parallel r_E \parallel R_L} = \frac{R_g \parallel ((1+\beta)r_E)}{R_g \parallel r_E \parallel R_L} R_L$$

This is much easier than was the direct calculation of  $Z_d$ !

### Generalization: Extra Element theorem - #5

The two reference gains and the two driving point impedances are related by:

$$\frac{A|_{z=0}}{A|_{z=\infty}} = \frac{z_n}{z_d}$$

One reference gain is always known or is easily found.  
 $z_n$  is always easier to find than  $z_d$ .

Therefore:

It is often easier to find the other reference gain and to use the above ratio relation for  $z_d$ , than to find  $z_d$  directly.