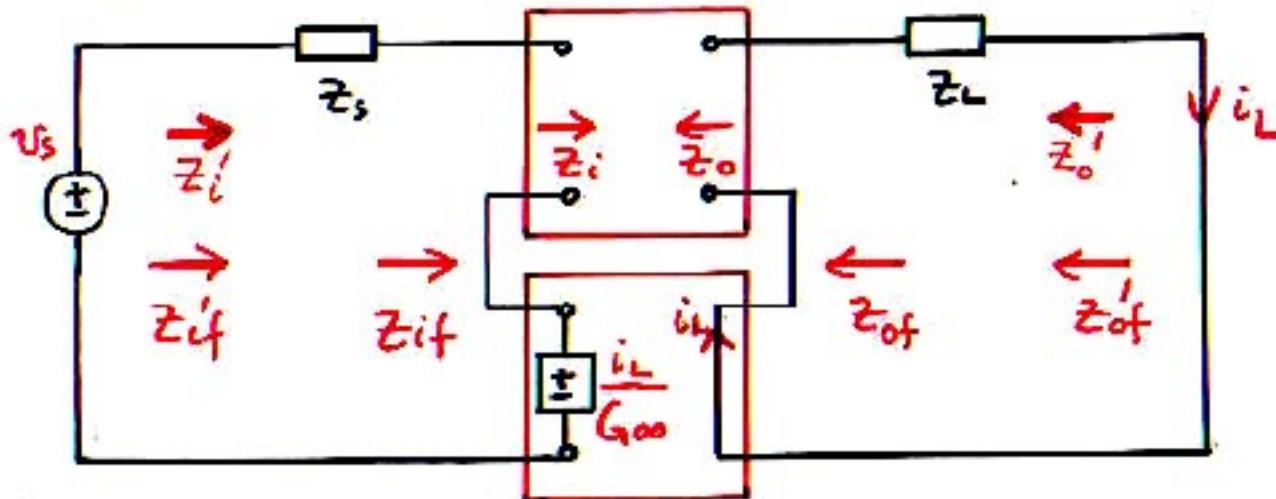


2. Voltage -to -current (Series current feedback)



$$Z'_{of} = \frac{Z_L G |_{Z_L \rightarrow \infty}}{G} = \frac{\frac{Z_L A |_{Z_L \rightarrow \infty}}{1 + T |_{Z_L \rightarrow \infty}}}{\frac{A}{1 + T}} = \frac{Z_L A |_{Z_L \rightarrow \infty}}{A} \cdot \frac{1 + T}{1 + T |_{Z_L \rightarrow \infty}} = Z'_o (1 + T)$$


$$Z'_{of} = Z_o (1 + T |_{Z_L \rightarrow \infty})$$

OR:

$$Z'_{of} = \frac{G_{\infty} \frac{Z_L T |_{Z_L \rightarrow \infty}}{1 + T |_{Z_L \rightarrow \infty}}}{G_{\infty} \frac{T}{1 + T}} = \frac{1 + T}{T} [Z_L T |_{Z_L \rightarrow \infty}]$$

$$Z'_{of} = \frac{1 + T}{T} |_{Z_L \rightarrow 0} [Z_L T |_{Z_L \rightarrow \infty}]$$

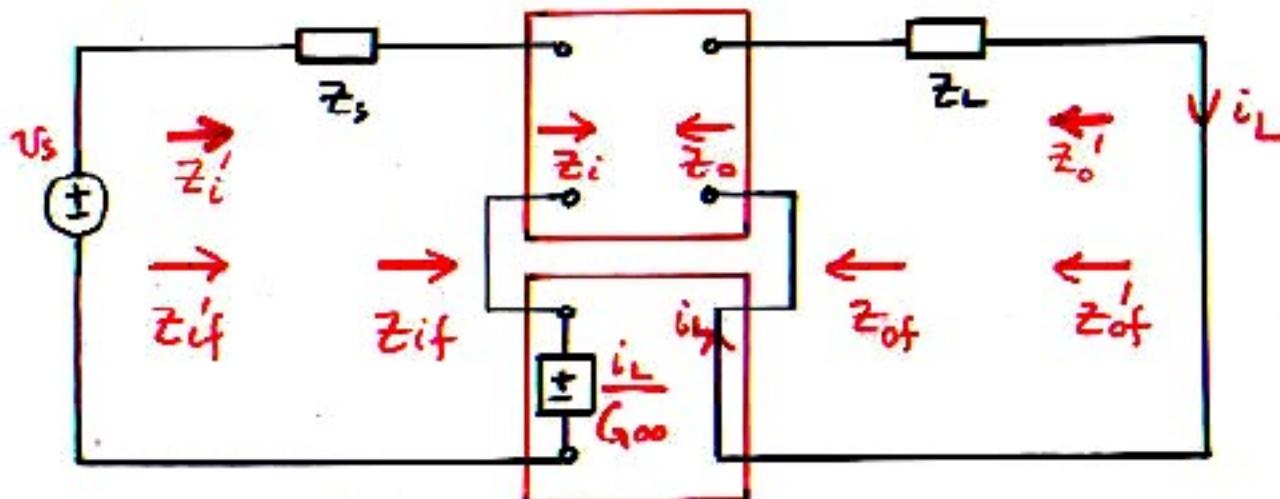2. Voltage -to -current (Series current feedback)



$$Z'_{if} = \frac{Z_s G|_{Z_s \rightarrow \infty}}{G} = \frac{\frac{Z_s A|_{Z_s \rightarrow \infty}}{1 + T|_{Z_s \rightarrow \infty}}}{\frac{A}{1 + T}} = \frac{Z_s A|_{Z_s \rightarrow \infty}}{A} \frac{1 + T}{1 + T|_{Z_s \rightarrow \infty}} = Z'_i (1 + T)$$


$$Z'_{if} = Z_i (1 + T|_{Z_s \rightarrow 0})$$

OR:

$$Z'_{if} = \frac{G_{oo} \frac{Z_s T|_{Z_s \rightarrow \infty}}{1 + T|_{Z_s \rightarrow \infty}}}{G_{oo} \frac{T}{1 + T}} = \frac{1 + T}{T} [Z_s T|_{Z_s \rightarrow \infty}]$$

$$Z'_{if} = \frac{1 + T}{T} \Big|_{Z_s \rightarrow 0} [Z_s T|_{Z_s \rightarrow \infty}]$$

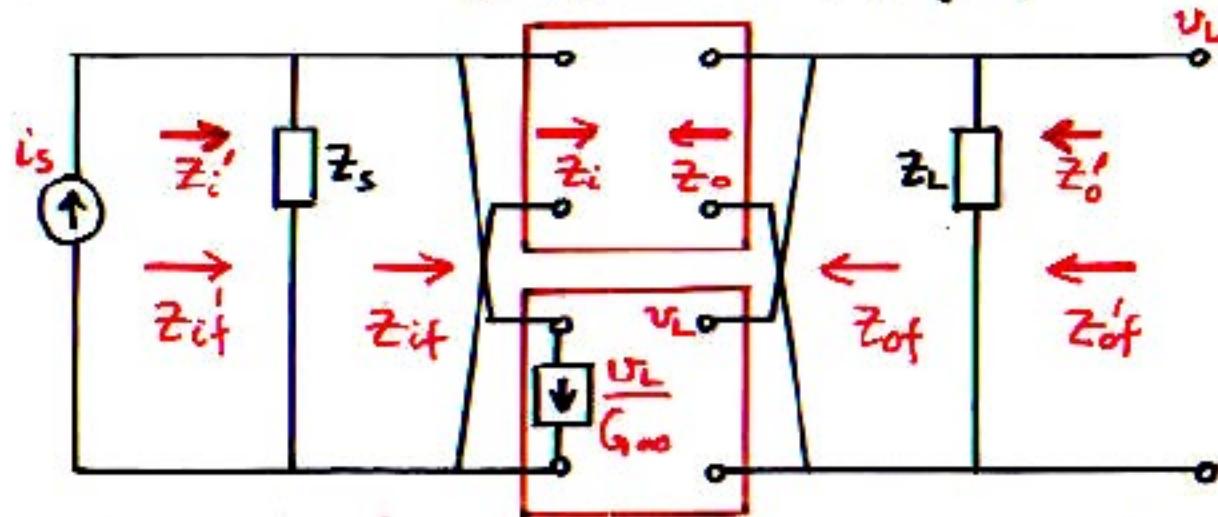3. Current-to-voltage (Shunt voltage feedback)




Ideal feedback path must "sense" output voltage and convert it to a feedback current. Current summing is done in shunt.

$$G = \frac{v_L}{i_s} = \frac{\text{voltage}}{\text{current}} = \frac{A}{1+T} = G_{o\infty} \frac{T}{1+T}$$

where

$$A = \frac{v_L}{i_s} \Big|_{K=1/G_{o\infty}=0}$$

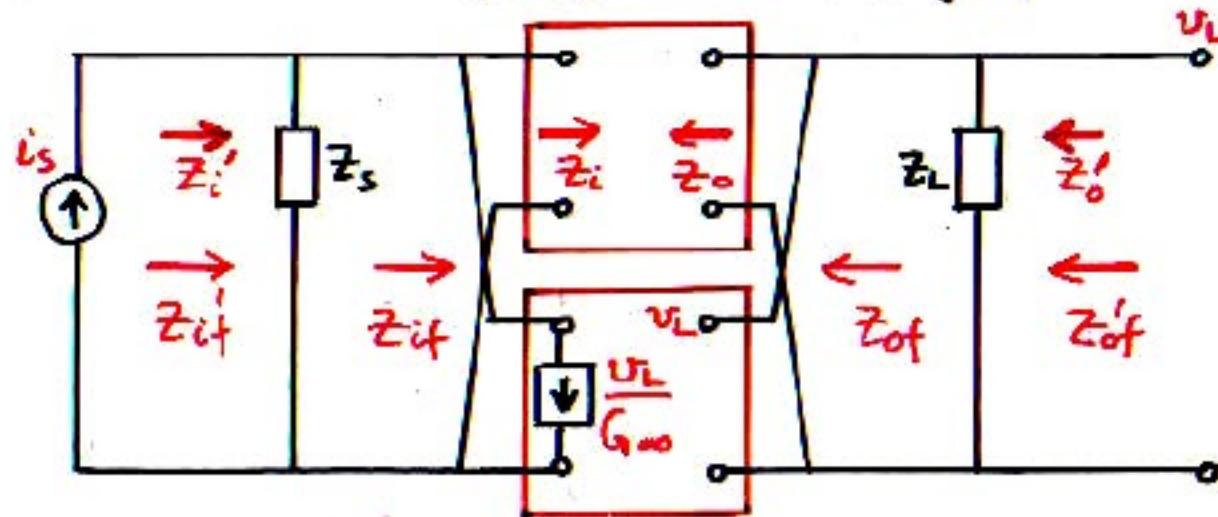3. Current-to-voltage (Shunt voltage feedback)



$$Z_{of}' = \frac{\frac{G}{G|_{z_L \rightarrow 0}}}{\frac{z_L}{z_L|_{z_L \rightarrow 0}}} = \frac{\frac{A}{A|_{z_L \rightarrow 0}} \frac{1}{\frac{1}{1+T|_{z_L \rightarrow 0}}}}{\frac{z_L}{z_L|_{z_L \rightarrow 0}}} = \frac{A}{A|_{z_L \rightarrow 0}} \frac{1+T|_{z_L \rightarrow 0}}{\frac{1}{1+T|_{z_L \rightarrow 0}}} = \frac{z_o'}{1+T}$$


$$Z_{of} = \frac{z_o}{1+T|_{z_L \rightarrow \infty}}$$

OR:

$$Z_{of}' = \frac{\frac{G_\infty \frac{T}{1+T}}{G_\infty \frac{T}{z_L|_{z_L \rightarrow 0}}}}{\frac{1}{1+T|_{z_L \rightarrow 0}}} = \frac{T}{1+T} \left[\frac{z_L}{T} \right]_{z_L \rightarrow 0}$$

$$Z_{of} = \frac{T}{1+T} \left[\frac{z_L}{T} \right]_{z_L \rightarrow \infty}$$

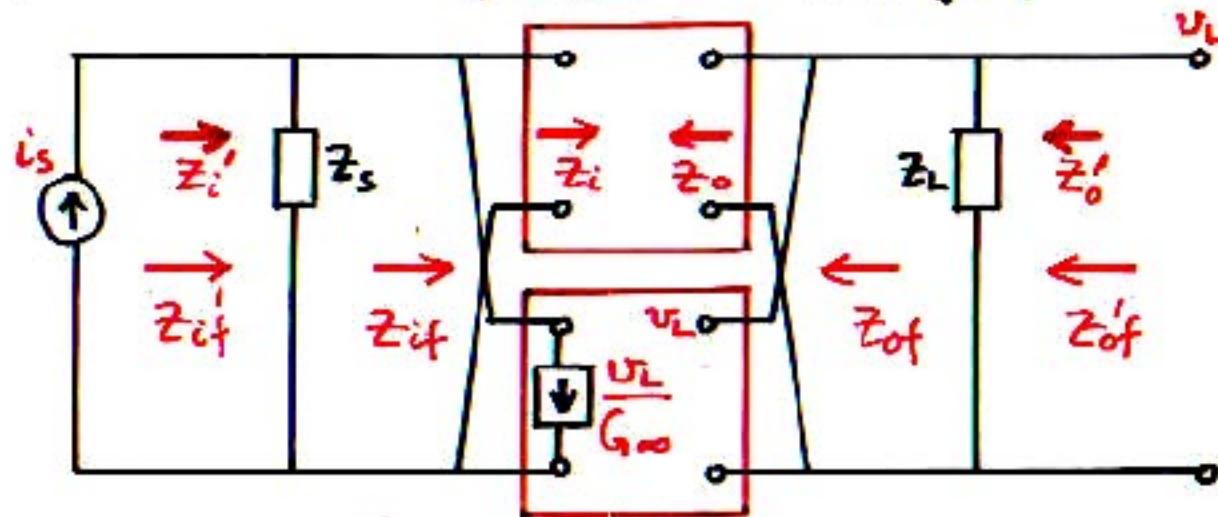3. Current-to-voltage (Shunt voltage feedback)



$$z'_{if} = \frac{G}{\left. \frac{G}{z_s} \right|_{z_s \rightarrow 0}} = \frac{\frac{A}{1+\tau}}{\left. \frac{A}{z_s} \right|_{z_s \rightarrow 0} \left. \frac{1}{1+\tau} \right|_{z_s \rightarrow 0}} = \left. \frac{A}{z_s} \right|_{z_s \rightarrow 0} \frac{1 + \cancel{\tau} z_s \rightarrow 0}{1 + \tau} = \frac{z'_i}{1 + \tau}$$


$$z'_{if} = \frac{z_i}{1 + \tau \left. z_s \right|_{z_s \rightarrow \infty}}$$

OR:

$$z'_{if} = \frac{G_{oo} \frac{\tau}{1 + \tau}}{\left. G_{oo} \frac{\tau}{z_s} \right|_{z_s \rightarrow 0} \left. \frac{1}{1 + \tau} \right|_{z_s \rightarrow 0}} = \frac{\tau}{1 + \tau} \left[\left. \frac{z_s}{\tau} \right|_{z_s \rightarrow 0} \right]$$

$$z'_{if} = \frac{\tau}{1 + \tau} \left. \left[\left. \frac{z_s}{\tau} \right|_{z_s \rightarrow 0} \right] \right|_{z_s \rightarrow \infty}$$

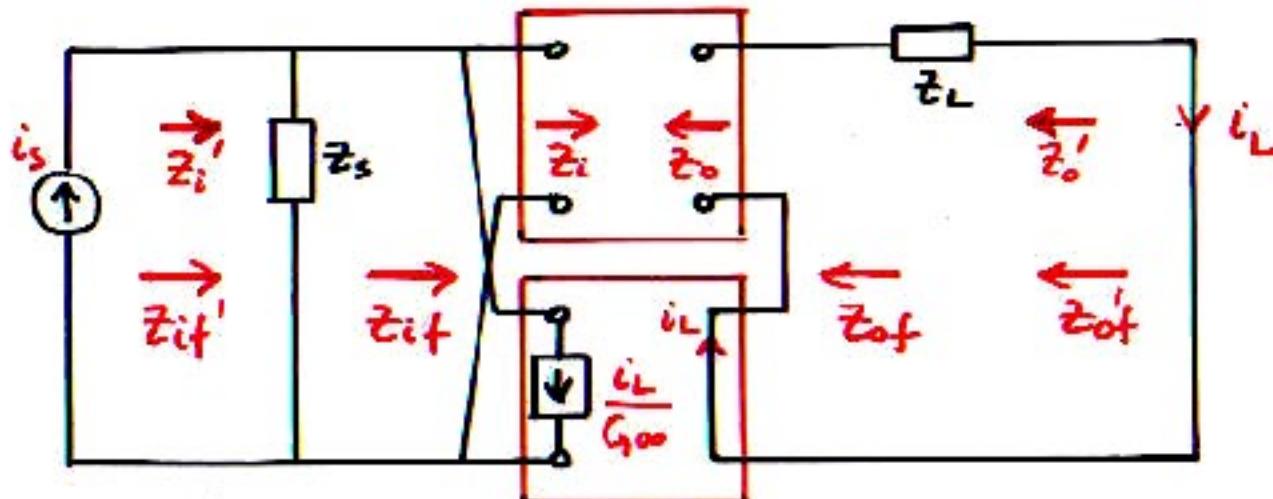4. Current-to-current (shunt current feedback)




Ideal feedback path must "sense" output current and convert it to a feedback current. Current summing is done in shunt.

$$G_i = \frac{i_L}{i_s} = \frac{\text{current}}{\text{current}} = \frac{A}{1+T} = G_{oo} \frac{T}{1+T}$$

where

$$A = \left. \frac{i_L}{i_s} \right|_{K=1/G_{oo}=0}$$

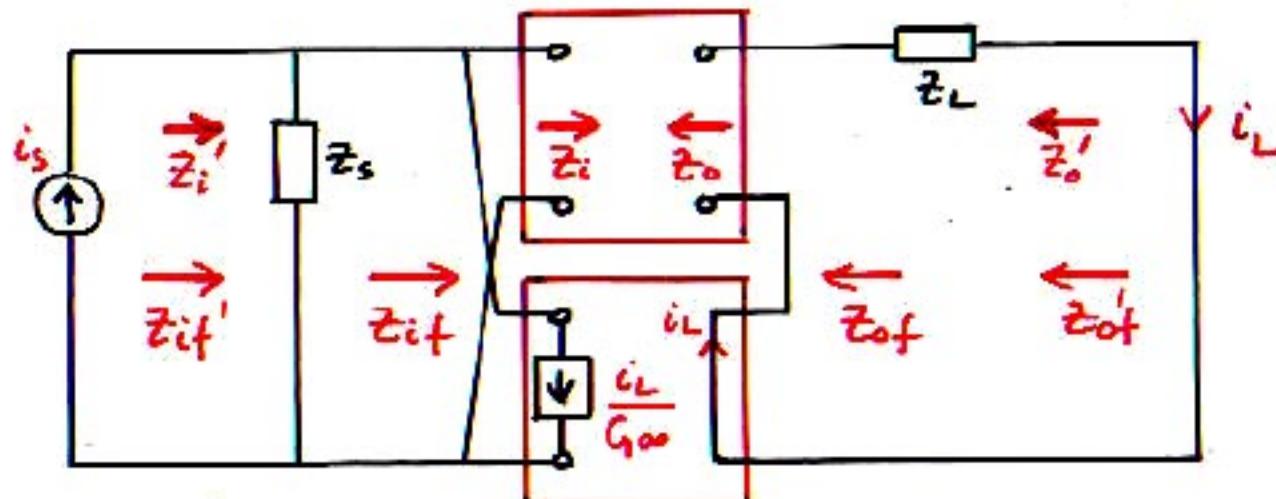4. Current-to-current (shunt current feedback)



$$Z_{of}' = \frac{Z_L G |_{Z_L \rightarrow \infty}}{G} = \frac{\frac{Z_L A |_{Z_L \rightarrow \infty}}{1 + T |_{Z_L \rightarrow \infty}}}{\frac{A}{1 + T}} = \frac{Z_L A |_{Z_L \rightarrow \infty}}{A} \frac{1 + T}{1 + T |_{Z_L \rightarrow \infty}} = Z_o' (1 + T)$$


$$Z_{of} = Z_o (1 + T |_{Z_L \rightarrow \infty})$$

OR:

$$Z_{of}' = \frac{G_\infty \frac{Z_L T |_{Z_L \rightarrow \infty}}{1 + T |_{Z_L \rightarrow \infty}}}{G_\infty \frac{T}{1 + T}} = \frac{1 + T}{T} [Z_L T |_{Z_L \rightarrow \infty}]$$

$$Z_{of} = \frac{1 + T}{T} |_{Z_L \rightarrow 0} [Z_L T |_{Z_L \rightarrow \infty}]$$

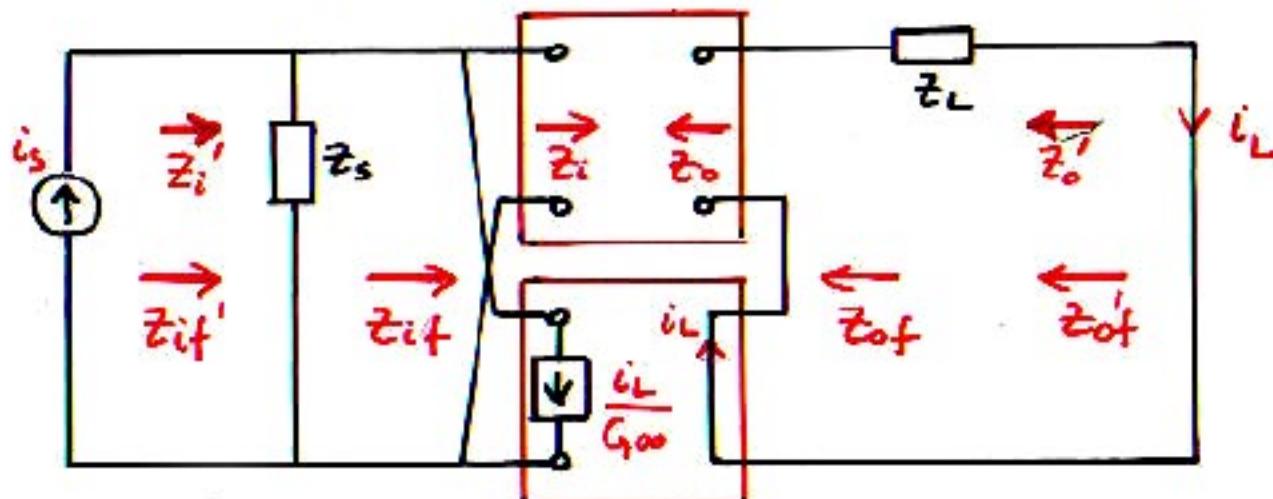4. Current-to-current (shunt current feedback)



$$Z'_{if} = \frac{G}{\left. \frac{G}{z_s} \right|_{z_s \rightarrow 0}} = \frac{\frac{A}{1+T}}{\left. \frac{A}{z_s} \right|_{z_s \rightarrow 0} \left. \frac{1}{1+T} \right|_{z_s \rightarrow 0}} = \frac{A}{\left. \frac{A}{z_s} \right|_{z_s \rightarrow 0}} \frac{1+T \cancel{|}_{z_s \rightarrow 0}}{1+T} = \frac{z'_i}{1+T}$$


$$Z'_4 = \frac{z_i}{1+T \left. \frac{1}{z_s} \right|_{z_s \rightarrow \infty}}$$

OR:

$$Z'_4 = \frac{G_{o0} \frac{T}{1+T}}{\left. G_{o0} \frac{T}{z_s} \right|_{z_s \rightarrow 0} \left. \frac{1}{1+T} \right|_{z_s \rightarrow 0}} = \frac{T}{1+T} \left[\left. \frac{z_s}{T} \right|_{z_s \rightarrow 0} \right]$$


$$Z'_4 = \frac{T}{1+T} \left. \left[\left. \frac{z_s}{T} \right|_{z_s \rightarrow 0} \right] \right|_{z_s \rightarrow \infty}$$

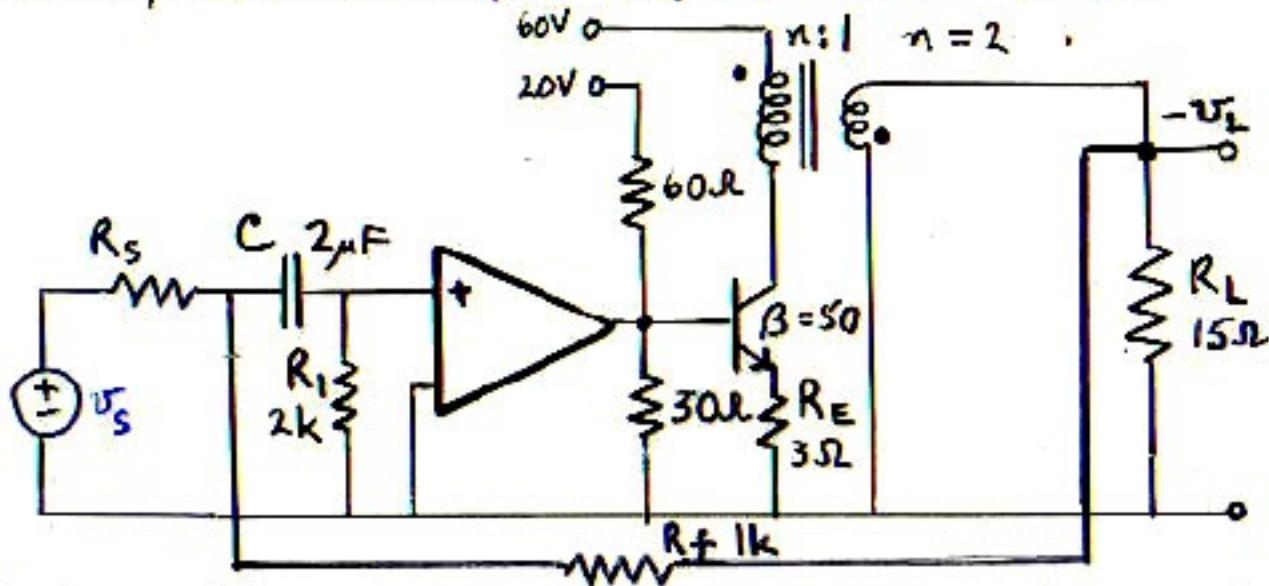Single-ended Class A audio feedback power amplifier, based on the same power stage previously discussed. The driver opamp has a gain $A_1 = A_{10} / (1 + s/\omega_A)$, where $A_{10} = 8\text{dB}$ and $\omega_A = 2\text{kHz}$, and an output impedance of 4.5Ω .




Although the gain is expressed as a voltage ratio, this is really a "Type 3" current-to-voltage feedback amplifier, because the feedback signal is connected at a shunt current-summing junction.

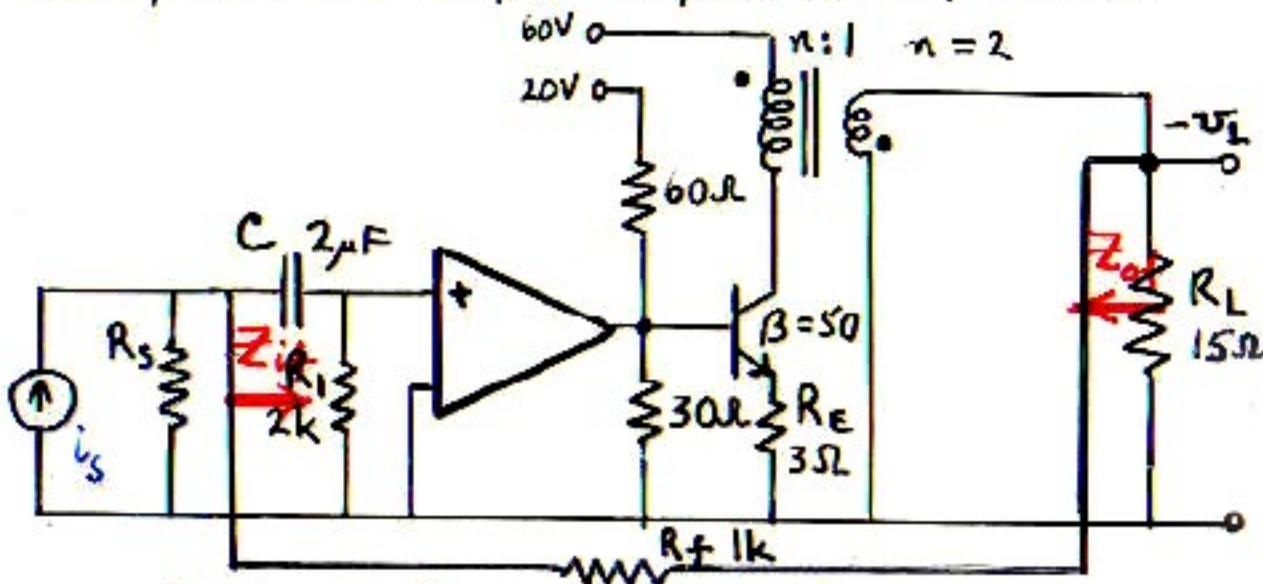Single-ended Class A audio feedback power amplifier, based on the same power stage previously discussed. The driver opamp has a gain $A_1 = A_{1o} / (1 + s/\omega_A)$, where $A_{1o} = 8\text{dB}$ and $\omega_A = 2\text{kHz}$, and an output impedance of 4.5Ω .




Hence, the "inside" output and input impedances Z_{of} and Z_{if} are both lowered by the feedback.

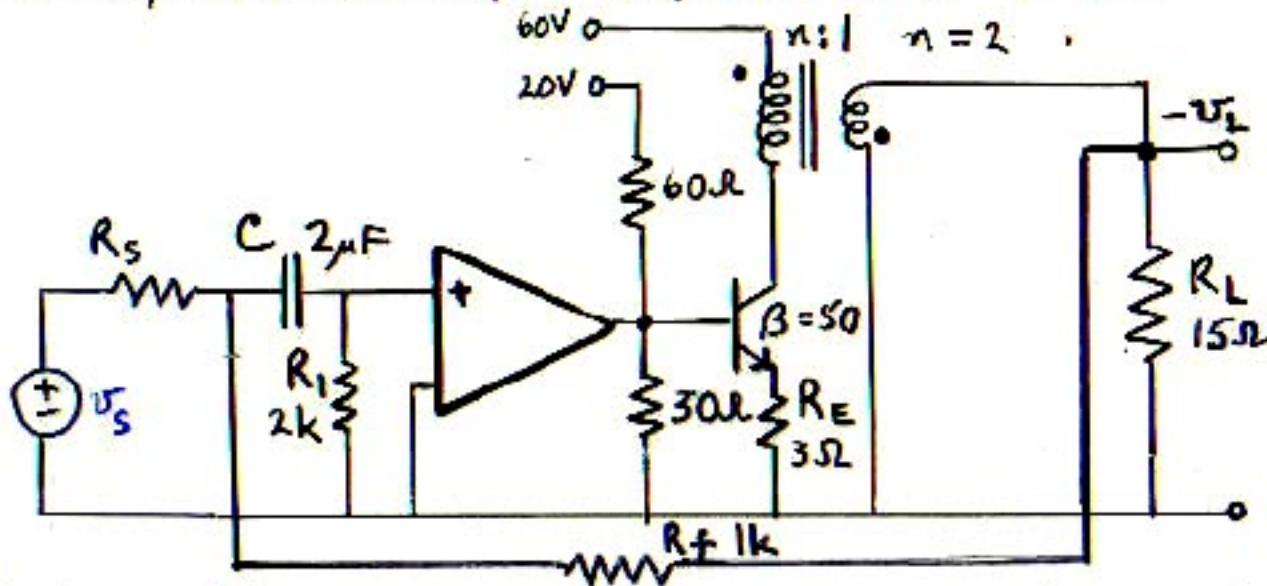Single-ended Class A audio feedback power amplifier, based on the same power stage previously discussed. The driver opamp has a gain $A_1 = A_{10} / (1 + s/\omega_A)$, where $A_{10} = 8\text{dB}$ and $\omega_A = 2\text{kHz}$, and an output impedance of 4.5Ω .




Although the gain is expressed as a voltage ratio, this is really a "Type 3" current-to-voltage feedback amplifier, because the feedback signal is connected at a shunt current-summing junction.

Ac model

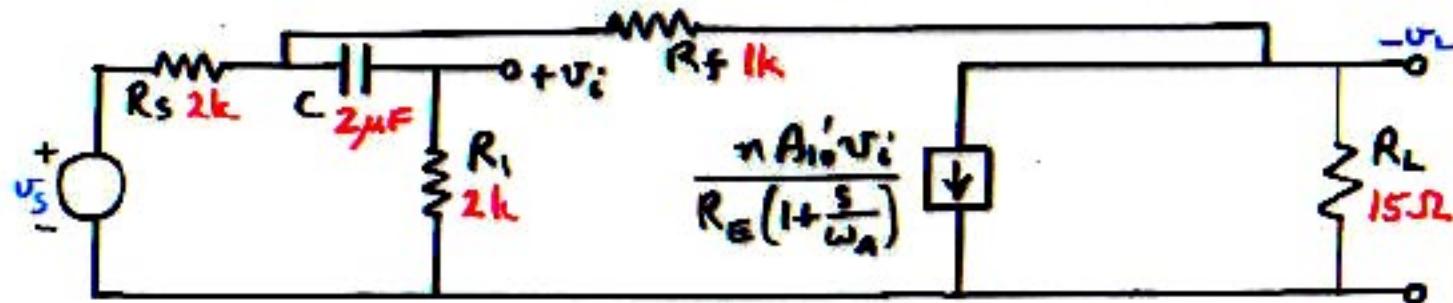

Ac model

Find Z_{of}

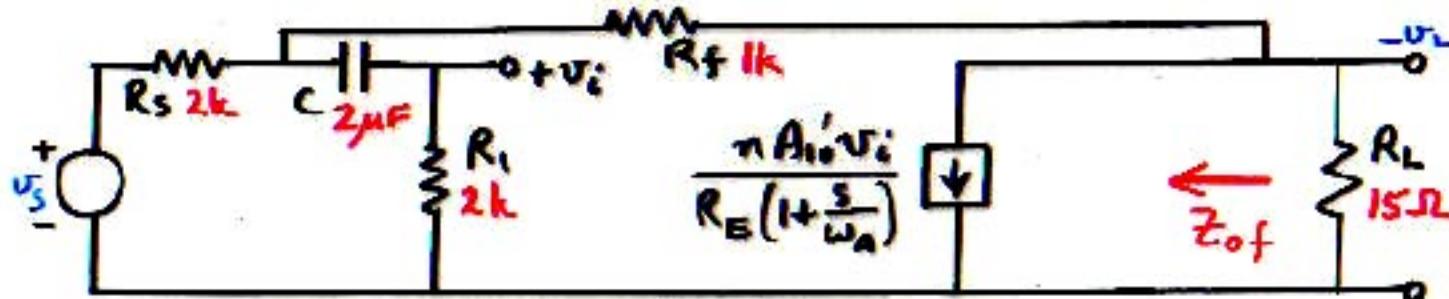

Use $Z_{of} = \frac{T}{1+T} \Big|_{R_L \rightarrow \infty} \left[\frac{R_L}{T} \Big|_{R_L \rightarrow 0} \right]$

where

$$T = T_m \frac{1}{\left(1 + \frac{\omega_2}{s}\right)\left(1 + \frac{s}{\omega_n}\right)}$$

$$T_m = \frac{(R + nR_s || R_1)nA_{10}'R_L}{R_f R_E}$$

$$\omega_2 = \frac{1}{C[R_f || R_s + R_1]}$$

$$\frac{R_L}{T} \Big|_{R_L \rightarrow 0} = \frac{R_f R_E}{(R_f + R_s + R_1) n A_{10}} \left(1 + \frac{\omega_2}{s} \right) \left(1 + \frac{s}{\omega_A} \right)$$


$$T \Big|_{R_L \rightarrow \infty} = \infty, \text{ so } \frac{T}{1+T} \Big|_{R_L \rightarrow \infty} = 1$$

Hence



$$Z_{\text{af}} = R_{\text{af}} \left(1 + \frac{\omega_2}{s} \right) \left(1 + \frac{s}{\omega_A} \right)$$

where

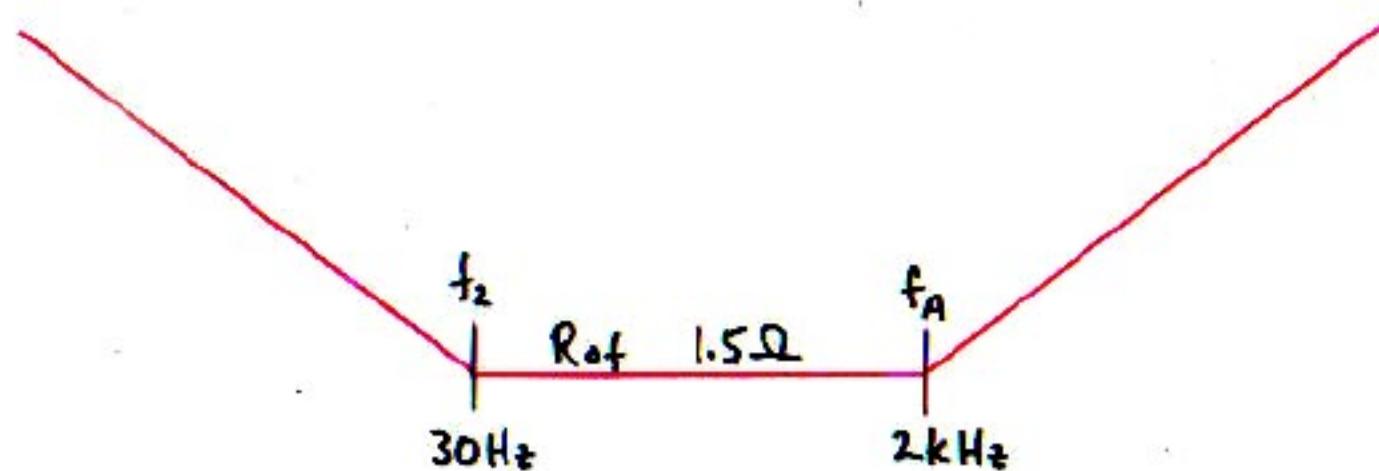
$$R_{\text{af}} = \frac{R_f R_E}{(R_f + R_s + R_1) n A_{10}} = \frac{1 \times 3}{0.5 \times 2 \times 2} = 1.5 \Omega$$



Ac model

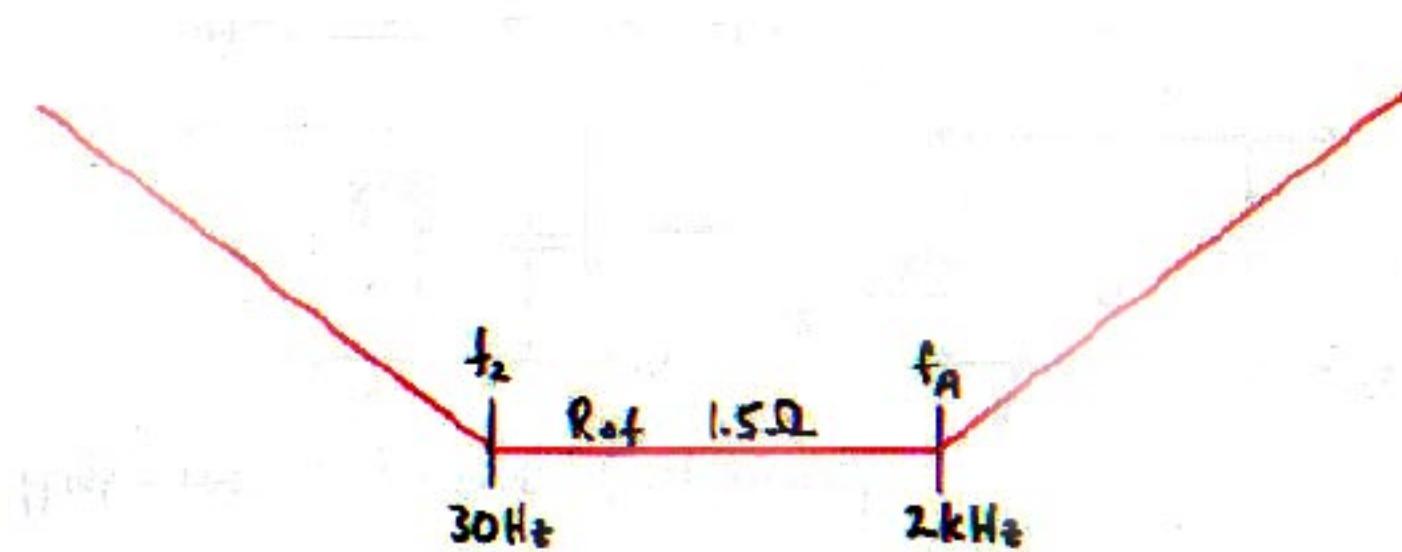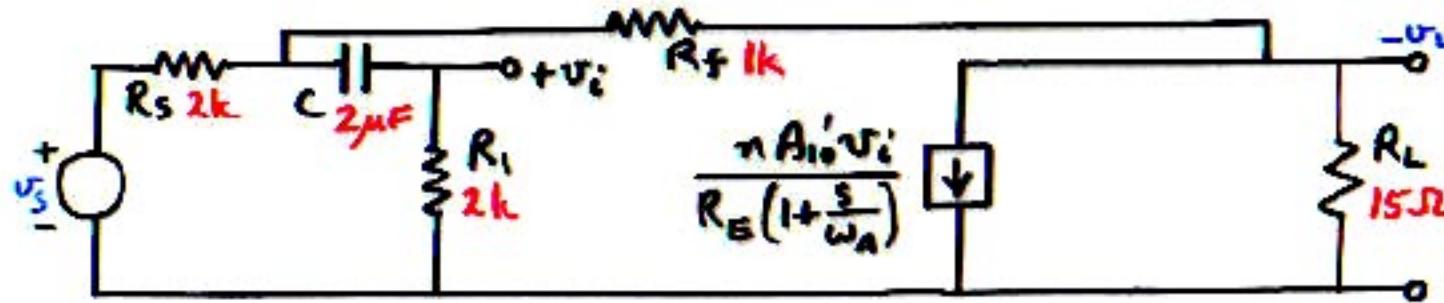

AC model

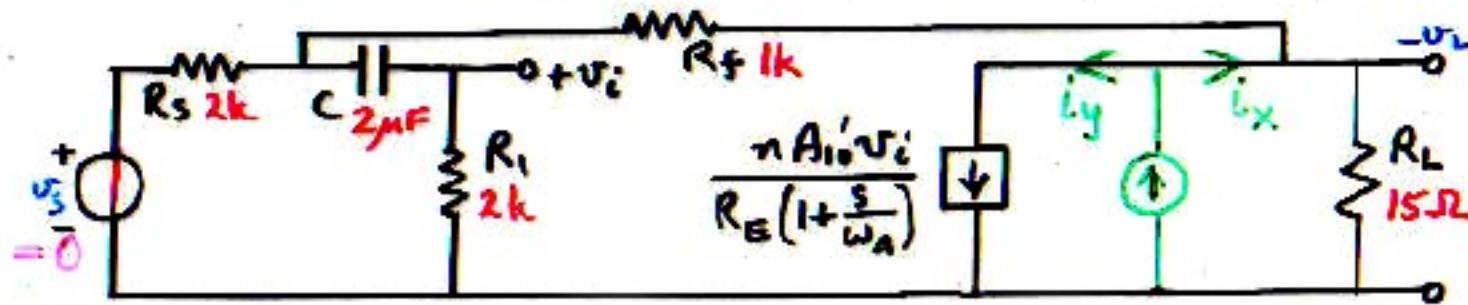


$$T = \left. \frac{i_y}{i_x} \right|_{u_s=0} = \frac{R_L}{R_L + R_f + R_s || R_1 (1 + \frac{\omega_1}{s})} \frac{R_s}{R_s + R_1 (1 + \frac{\omega_1}{s})} \frac{R_1 n A_{10}}{R_g (1 + \frac{s}{\omega_A})}$$

where

$$\omega_1 = \frac{1}{CR_1} \quad f_1 = \frac{159}{2 \times 2} = 40 \text{ Hz}$$

Ac model

Find Z_{of}

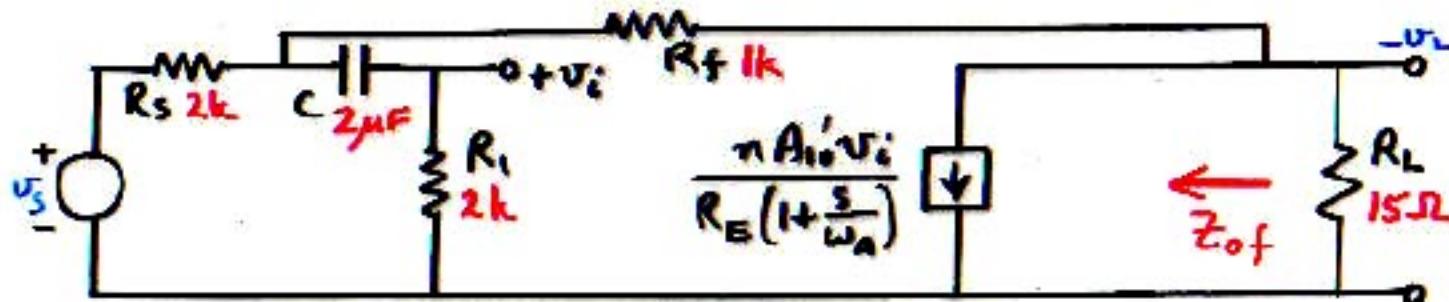


Use $Z_{of} = \frac{T}{1+T} \Big|_{R_L \rightarrow \infty} \left[\frac{R_L}{T} \Big|_{R_L \rightarrow 0} \right]$

where

$$T = T_m \frac{1}{(1 + \frac{\omega_2}{s})(1 + \frac{s}{\omega_n})}$$

$$T_m = \frac{(R + nR_s || R_1)nA_{10}' R_L}{R_f R_E}$$


$$\omega_2 = \frac{1}{C [R_f || R_s + R_1]}$$

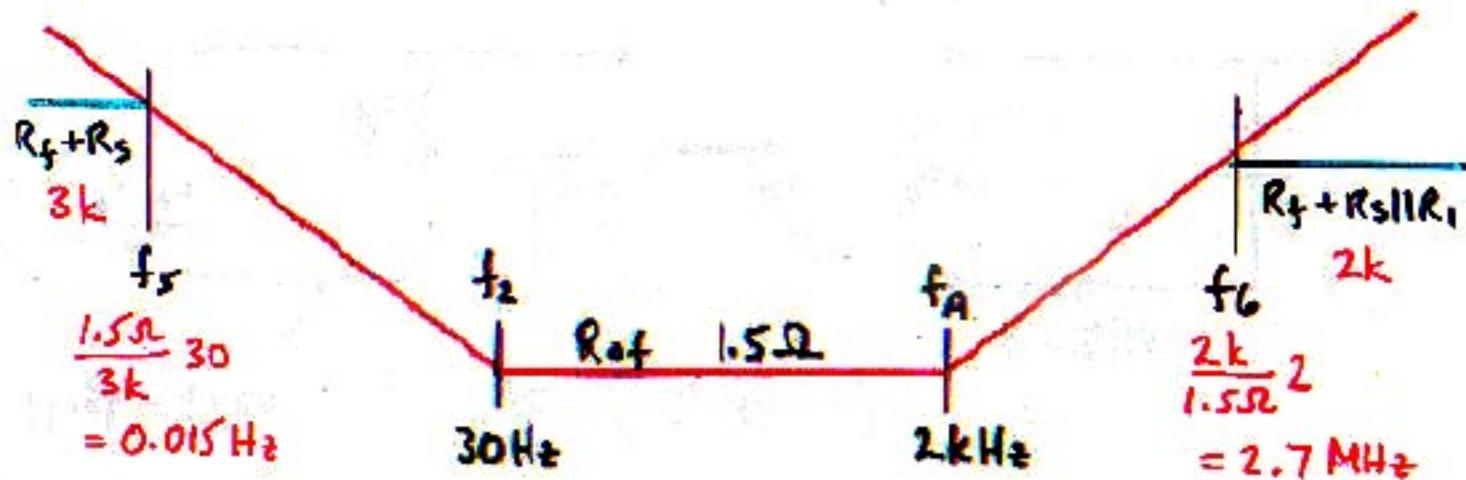

Note from the actual circuit that Z_{af} would limit at both low and high frequencies, because of the loading effect of the feedback path on R_L . This nonideality was ignored in the solution, but could have been included with further complication but no additional difficulty.

Ac model

Find Z_{if}

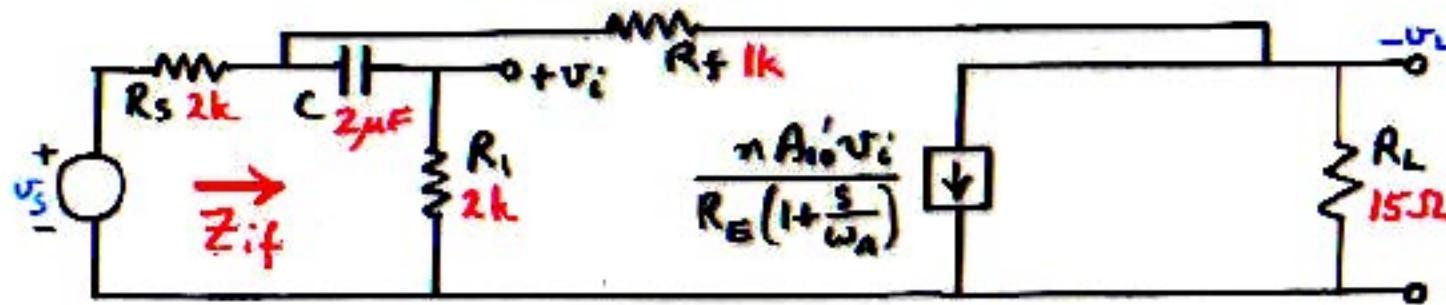

Use $Z_{if} = \frac{T}{1+T} \Big|_{R_s \rightarrow \infty} \cdot \frac{R_s}{T} \Big|_{R_s \rightarrow 0}$

where $D = \frac{T}{1+T} = \frac{T_m}{1+T_m} \frac{1}{\left(1 + \frac{\omega_3}{\omega}\right)\left(1 + \frac{\omega}{\omega_4}\right)}$

$$\omega_3 = \frac{\omega_2}{1+T_m}$$

$$\omega_2 = \frac{1}{C[R_f || R_s + R_i]}$$

$$\omega_4 = (1+T_m)\omega_A$$

$$\left. \frac{R_s}{T} \right|_{R_s \rightarrow 0} = \frac{R_f + R_E}{n A_{10}' R_L} \left(1 + \frac{\omega_2}{s} \right) \left(1 + \frac{s}{\omega_A} \right)$$

where

$$\omega_2 \equiv \omega_2|_{R_s \rightarrow 0} = \frac{1}{C R_i} = \omega_1$$

$$D|_{R_s \rightarrow \infty} = \frac{(R_f + R_i) n A_{10}' R_L}{R_f R_E (1 + T_m|_{R_s \rightarrow \infty})} \frac{1}{\left(1 + \frac{\omega_E}{s} \right) \left(1 + \frac{s}{\omega_q} \right)}$$

where

$$\begin{aligned} \omega_S &\equiv \omega_3|_{R_s \rightarrow \infty} = \frac{\omega_2|_{R_s \rightarrow \infty}}{1 + T_m|_{R_s \rightarrow \infty}} \\ &= \frac{1}{C(R_f + R_i)(1 + T_m|_{R_s \rightarrow \infty})} \end{aligned}$$

$$T_m|_{R_s \rightarrow \infty} = \frac{(R_f + R_i) n A_{10}' R_L}{R_f R_E} = \frac{(112) 2 \times 2 \times 15}{1 \times 3} = 13$$

$$f_S = \frac{159}{2(1+2)(1+13)} = 1.9 \text{ Hz}$$

$$\omega_q \equiv (1 + T_m|_{R_s \rightarrow \infty}) \omega_A$$

$$f_q = 14 \times 2 = 28 \text{ kHz}$$


Hence

$$Z_{if} = \frac{(R_f || R_i) n A_{10} R_L}{R_f R_o (1 + T_m |_{R_s \rightarrow \infty})} \frac{R_f + R_o}{n A_{10} R_L} \frac{(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_A})}{(1 + \frac{\omega_f}{s})(1 + \frac{s}{\omega_A})}$$

$$= R_{if} \frac{(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_A})}{(1 + \frac{\omega_f}{s})(1 + \frac{s}{\omega_A})}$$

$$R_{if} = \frac{R_f || R_i}{1 + T_m |_{R_s \rightarrow \infty}}$$

$$= \frac{1/12}{1/4} = 47 \Omega$$

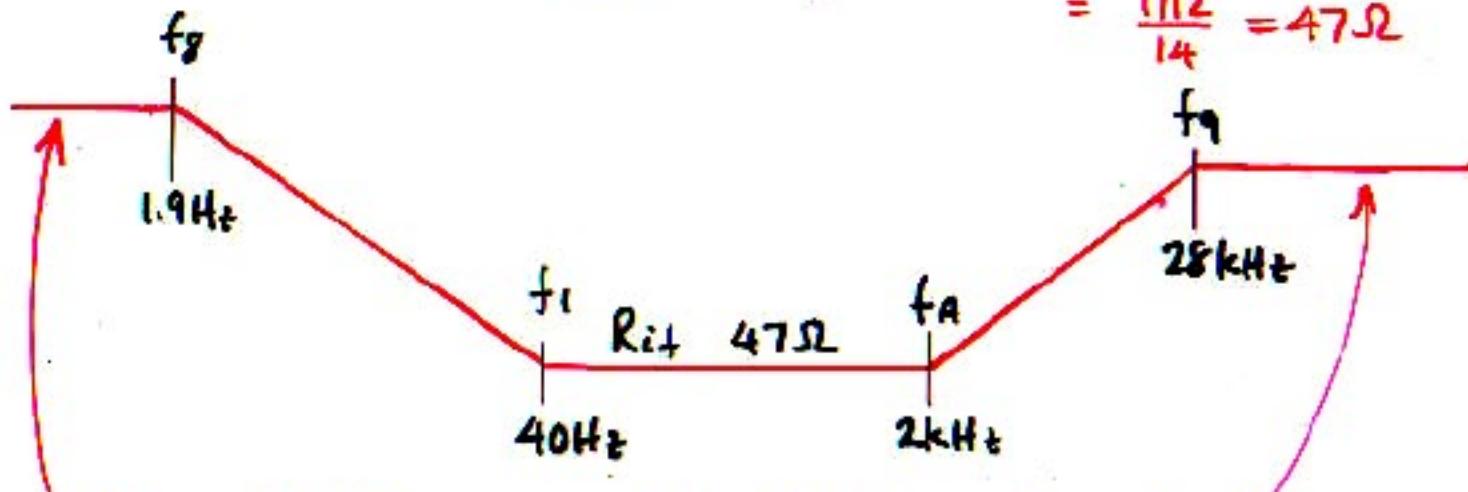

$$R_{if} \frac{\omega_1}{\omega_B} = \frac{R_f || R_i}{1 + T_m |_{R_s \rightarrow \infty}} \frac{C(R_f + R_i)(1 + T_m |_{R_s \rightarrow \infty})}{CR_i}$$

$$= R_f$$

$$= 1k$$


$$R_{if} \frac{\omega_A}{\omega_B} = \frac{R_f || R_i}{1 + T_m |_{R_s \rightarrow \infty}} (1 + T_m |_{R_s \rightarrow \infty})$$

$$= R_f || R_i = 0.67k$$

Example: Distortion

When the open-loop amplifier is delivering full output power at 1kHz, the output stage develops 3% 2nd harmonic and 5% 3rd harmonic distortion. Find the full output power closed-loop total harmonic distortion at 1kHz.

Percentage of each harmonic is reduced by $|1+T|$ at the harmonic frequency.

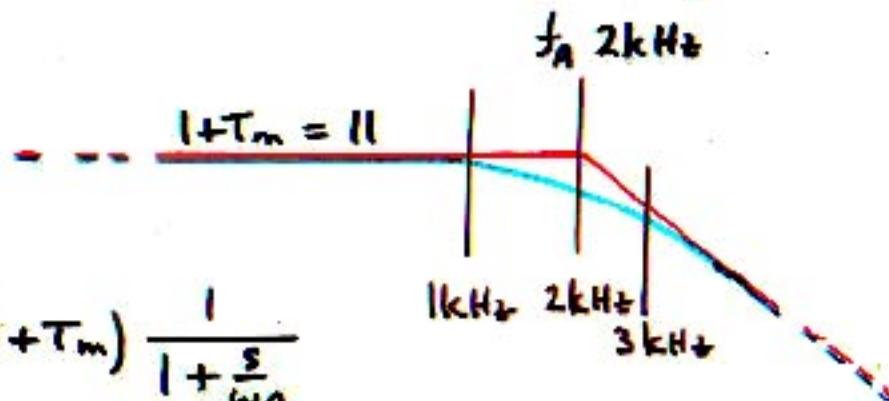

$$1+T = (1+\tau_m) \frac{1}{1 + \frac{s}{\omega_A}}$$

$$|1+T|_{2\text{kHz}} = 11 \sqrt{1 + \left(\frac{2}{2}\right)^2} = \frac{11}{\sqrt{2}} = 7.8$$

$$|1+T|_{3\text{kHz}} = 11 \sqrt{1 + \left(\frac{3}{2}\right)^2} = \frac{11}{\sqrt{3.8}} = 6.1$$

$$\begin{aligned} \text{THD} &= \sqrt{\left(\frac{3\%}{7.8}\right)^2 + \left(\frac{5\%}{6.1}\right)^2} = \sqrt{0.39^2 + 0.82^2} \\ &= 0.91\% \end{aligned}$$

Generalization: Effect of Feedback on Impedances

1. Output impedance is {decreased} by {voltage} feedback from the output.
{increased} by {current}

Input impedance is {increased} by {series} feedback to the input.
{decreased} by {shunt}

2. The "outside" impedances are changed by a factor $(1+T)$

The "inside" impedances are changed by a larger factor.

3. Alternatively, the input and output impedances can be found solely from the loop gain T .

Stability

If the open-loop gain A is stable, the closed-loop gain


$$G = \frac{A}{1+A}$$

is stable if $1+A$ has no roots in the right half-plane (R_{hp}).

By complex variable theory, this implies that a polar plot of $1+A$ must not encircle the origin; or, equivalently, that a polar plot of A must not encircle the $(-1, 0)$ point. (Nyquist Stability Criterion).

Simple cases of the Nyquist plot of loop gain A :


1-pole response:

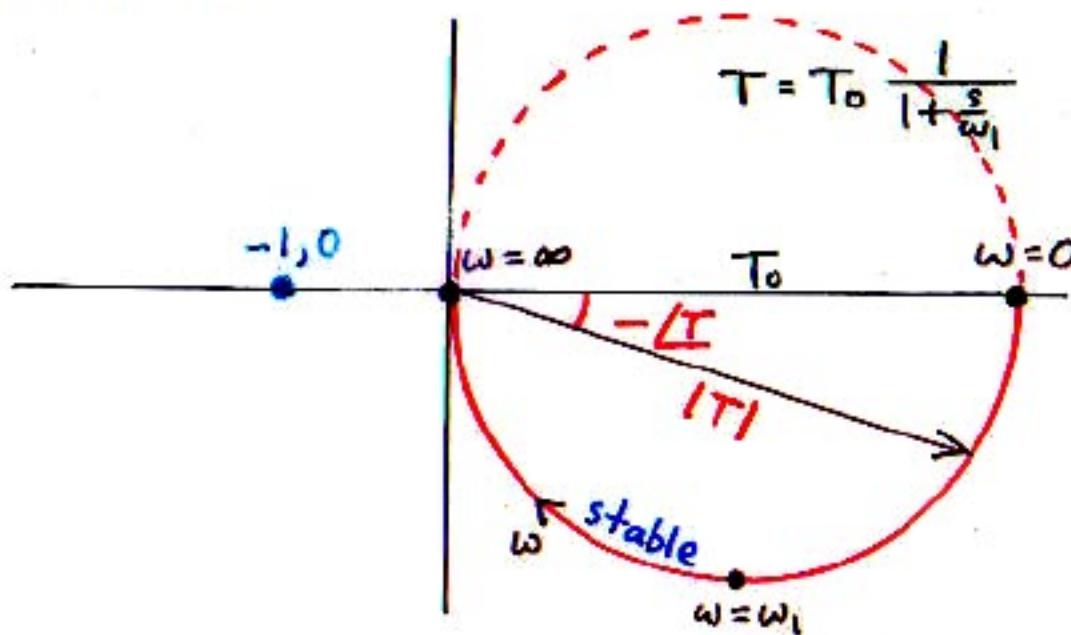

Always stable


2-pole response
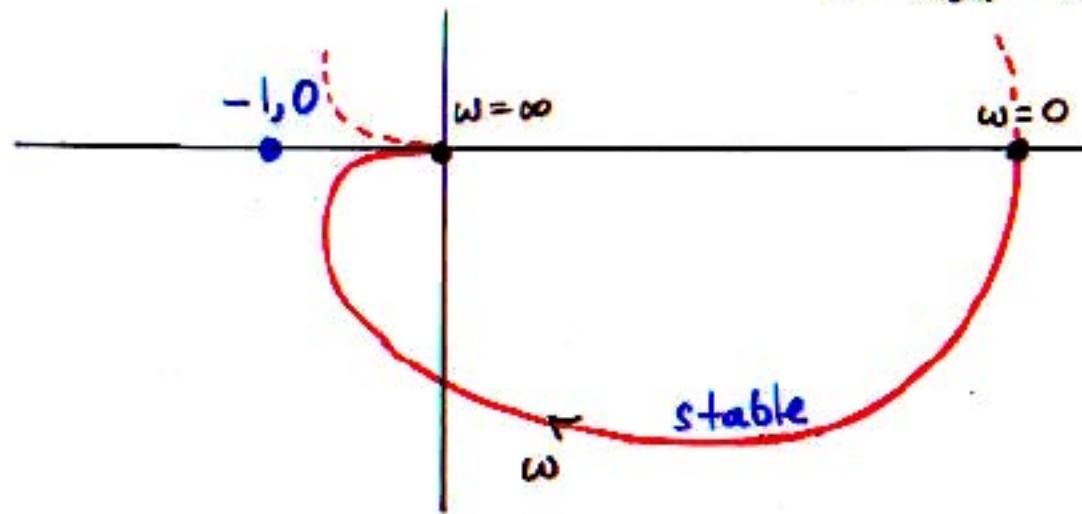
$$T = T_0 \frac{1}{(1 + \frac{\omega}{\omega_1})(1 + \frac{\omega}{\omega_2})}$$




Always stable

3-pole response

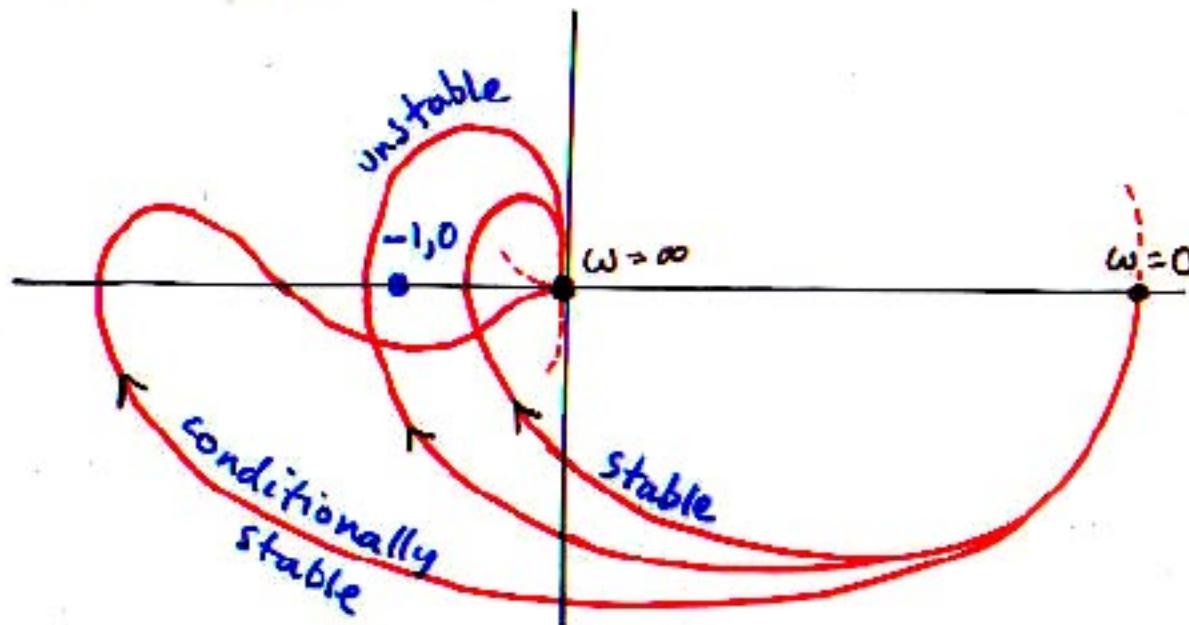

Can be stable or unstable


Stability margins

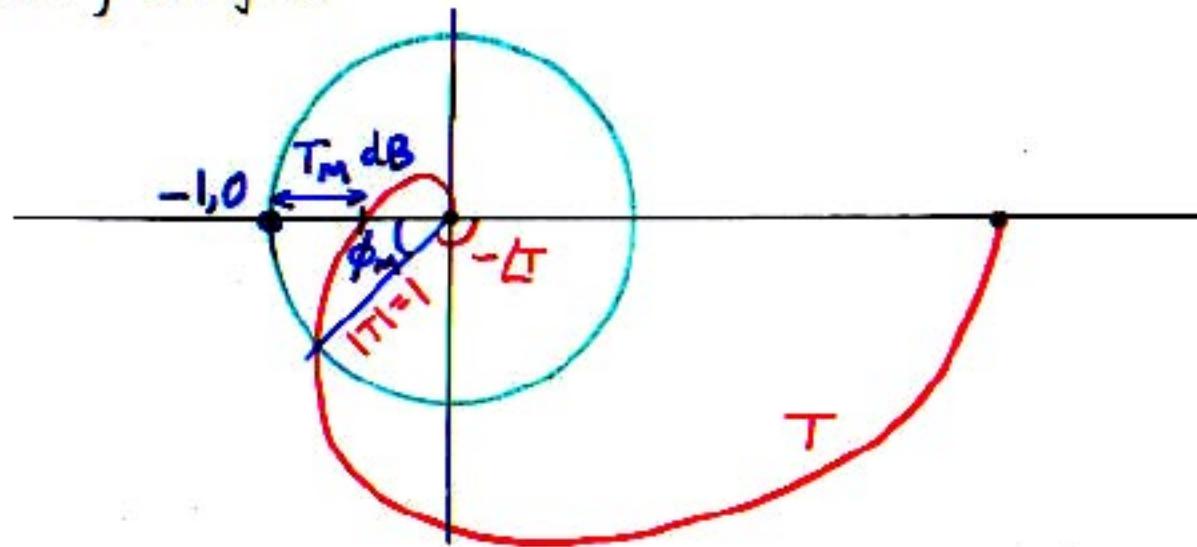


Phase margin $\phi_M = 180^\circ + \angle T$ when $|T| = 1$ (0 dB)
C negative (lag)

Gain margin $T_M \text{ dB} = -T \text{ dB}$ when $\angle T = -180^\circ$

Bode plot:

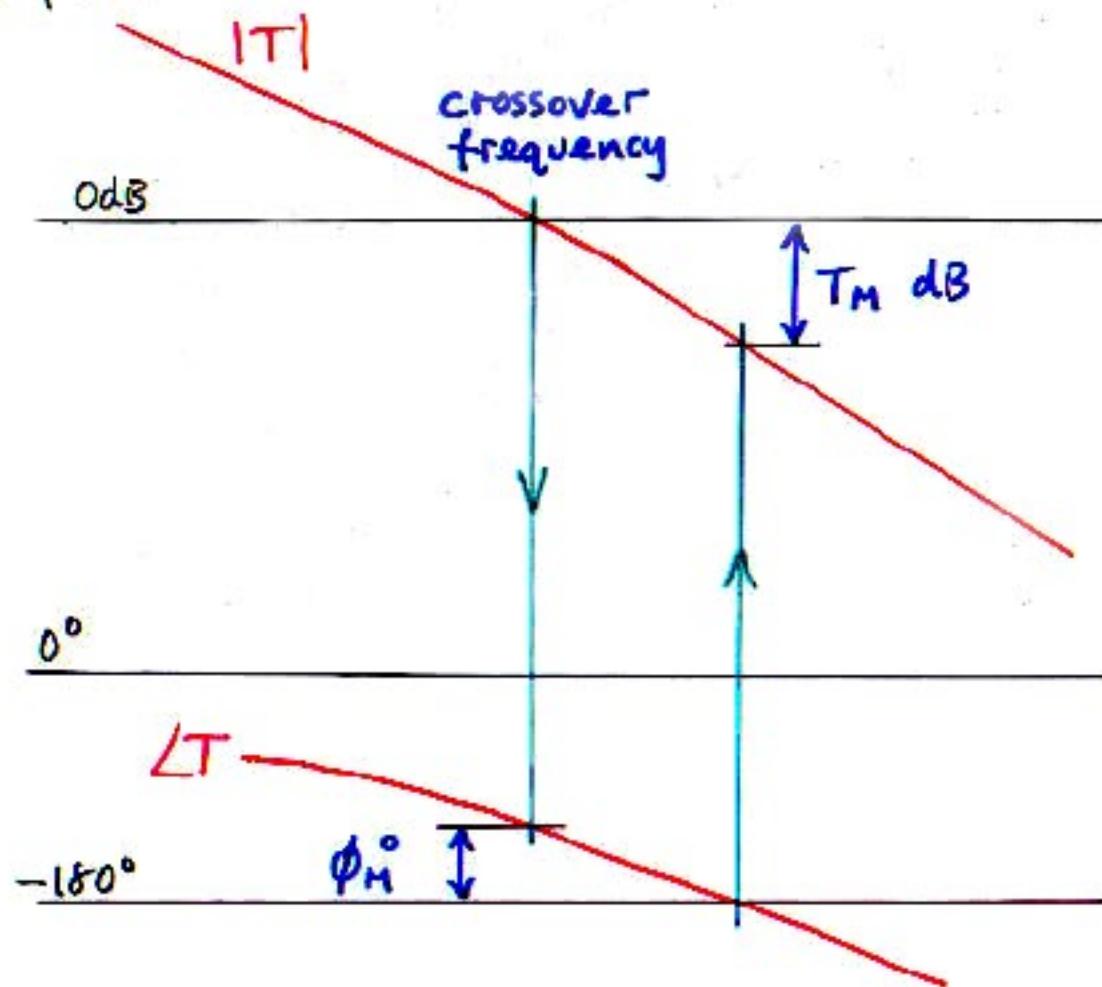


Stability margins

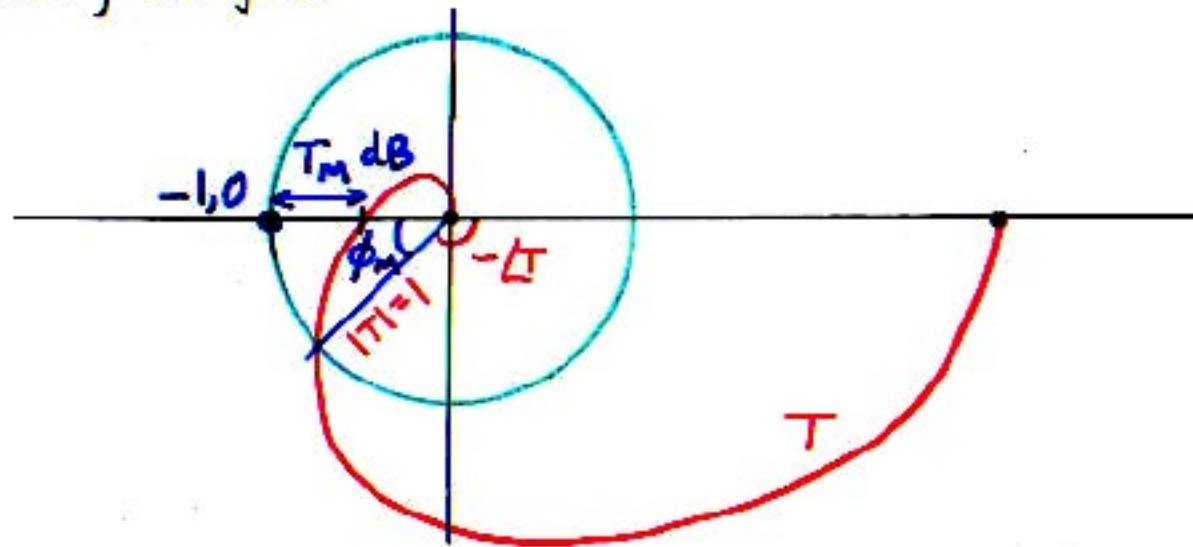

Phase margin $\phi_M = 180^\circ + \angle T$ when $|T| = 1$ (0 dB)
C negative (lag)

Gain margin $T_M \text{ dB} = -T \text{ dB}$ when $\angle T = -180^\circ$


Stability margins

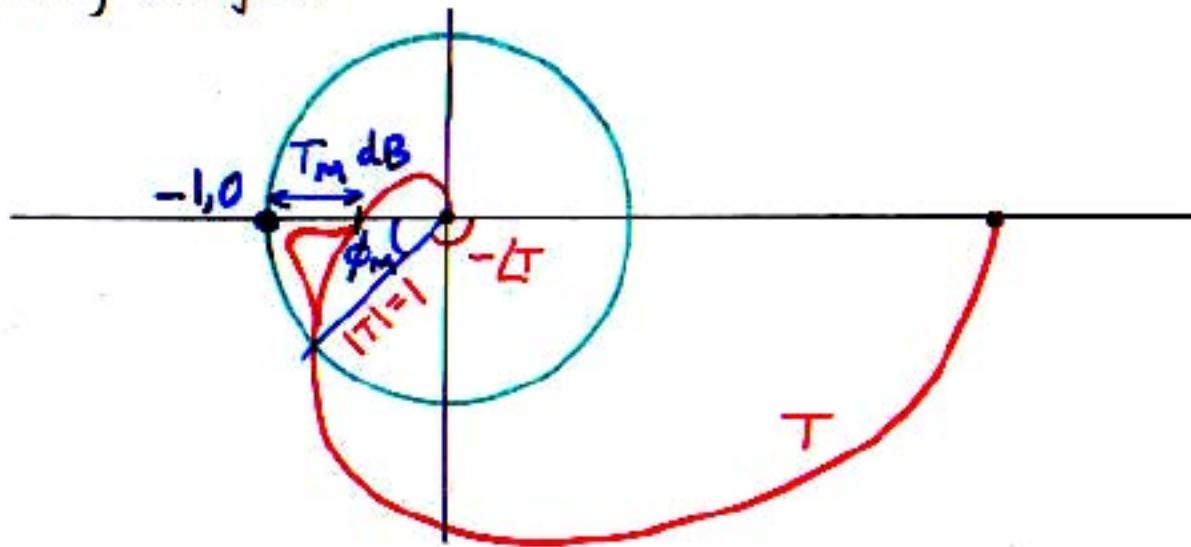

Phase margin $\phi_M = 180^\circ + \angle T$ when $|T| = 1$ (0dB)
C negative (lag)

Gain margin $T_M \text{ dB} = -T \text{ dB}$ when $\angle T = -180^\circ$


Stability margins

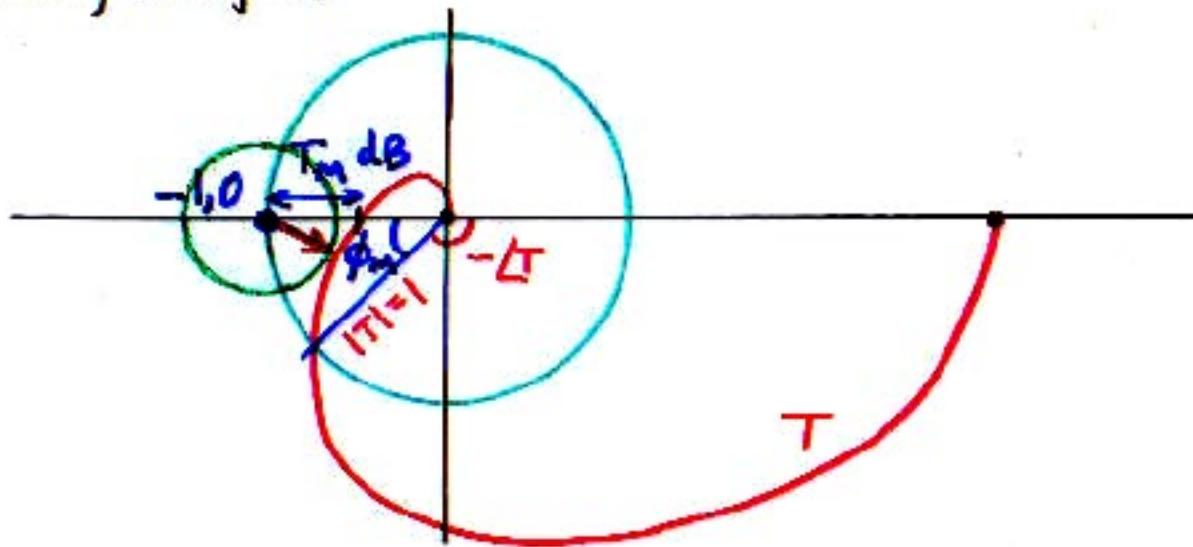


Phase margin $\phi_M = 180^\circ + \angle T$ when $|T| = 1$ (0dB)
C negative (lag)

Gain margin $T_M \text{ dB} = -T \text{ dB}$ when $\angle T = -180^\circ$

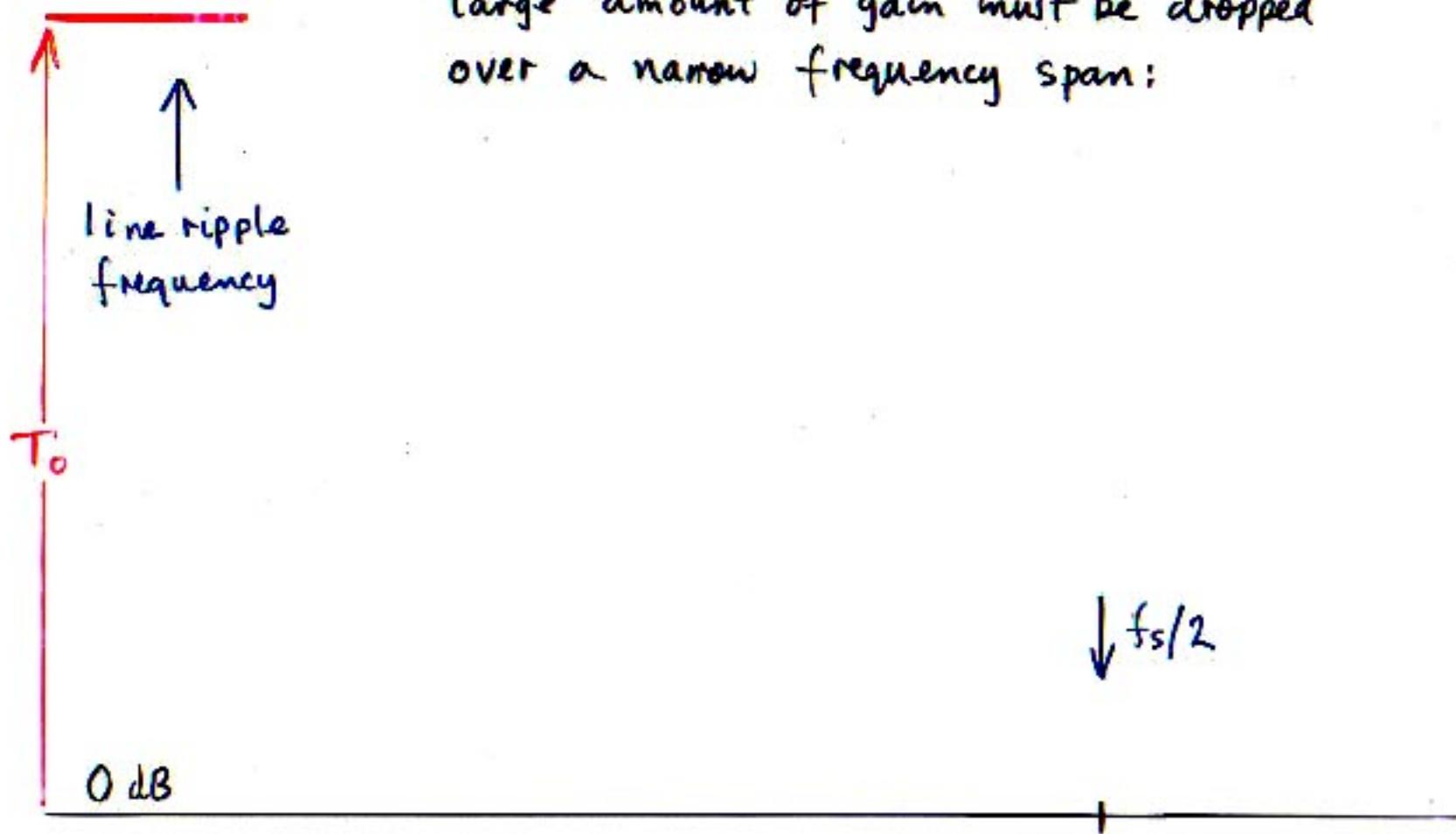
A conditionally stable system may be necessary when a large amount of gain must be dropped over a narrow frequency span:



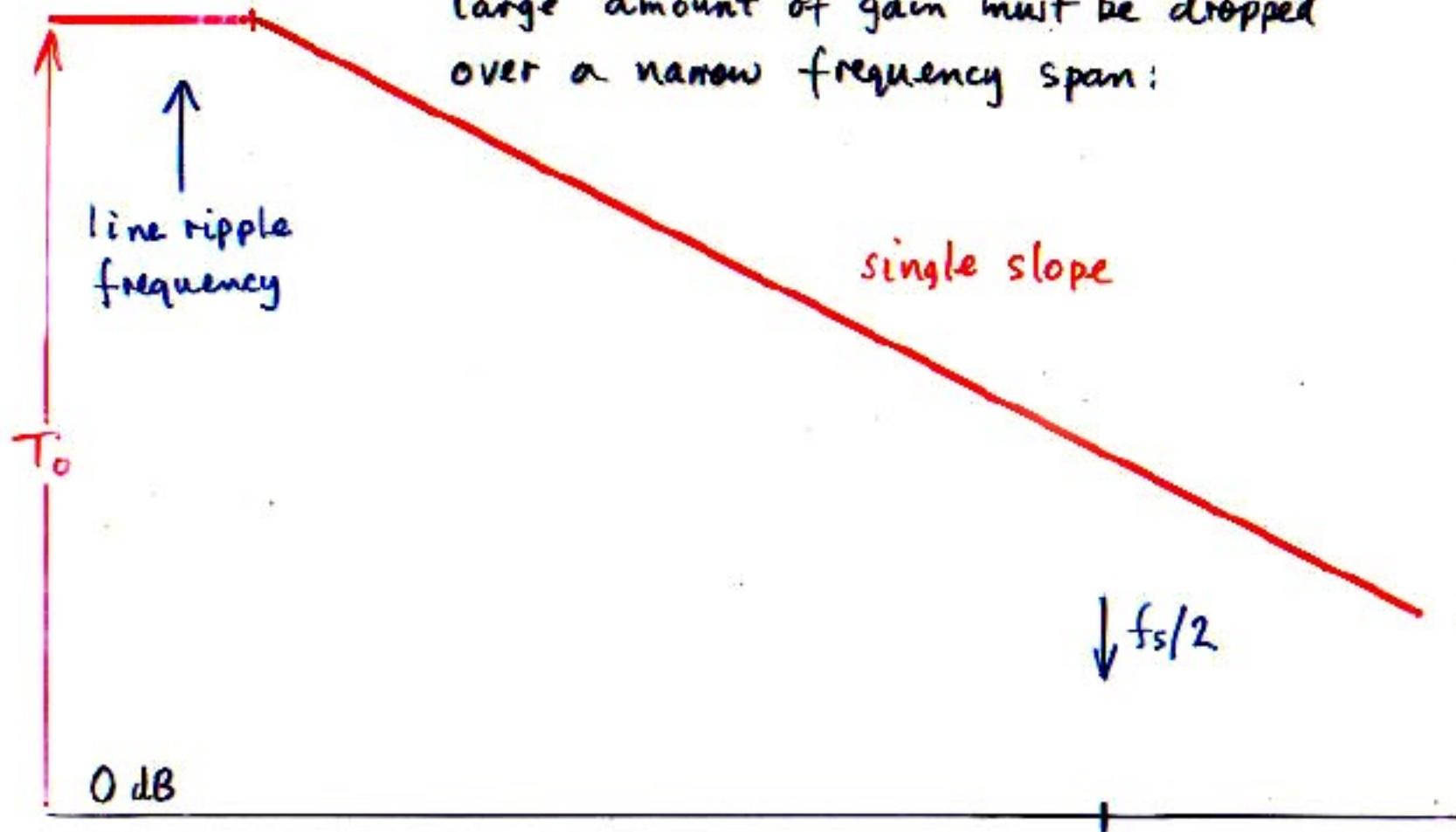A conditionally stable system may be necessary when a large amount of gain must be dropped over a narrow frequency span:



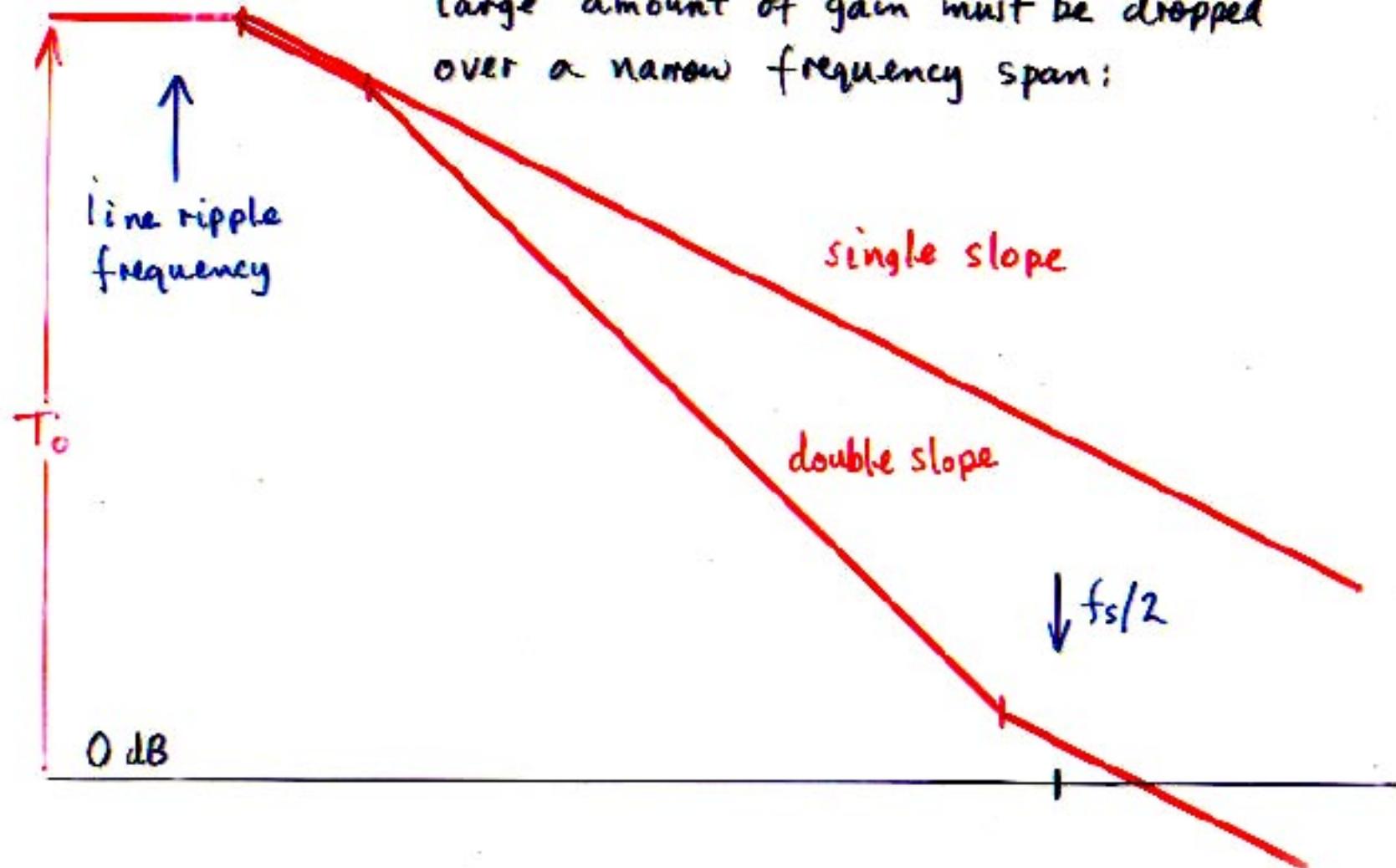A conditionally stable system may be necessary when a large amount of gain must be dropped over a narrow frequency span:



A conditionally stable system may be necessary when a large amount of gain must be dropped over a narrow frequency span:

