
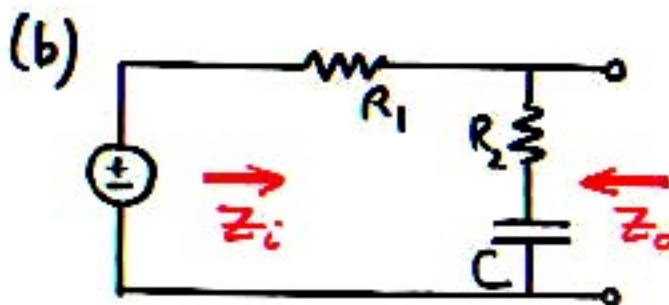


EXERCISE 3.2

SOLUTION


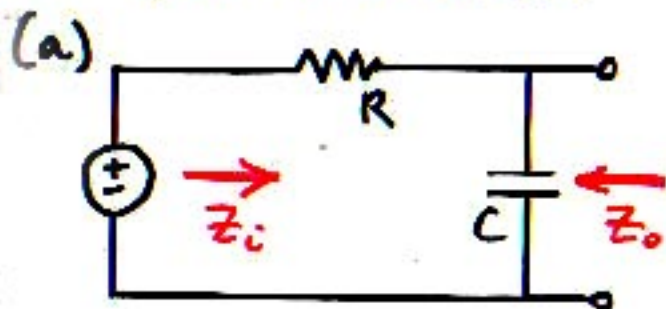
Exercise

Find the input and output impedances Z_i and Z_o in factored pole-zero form, and sketch the magnitude and phase asymptotes, for each of the two networks:



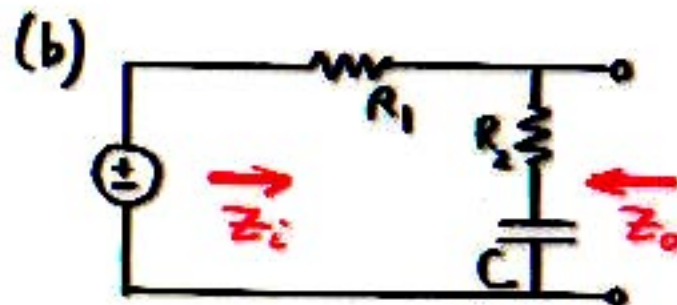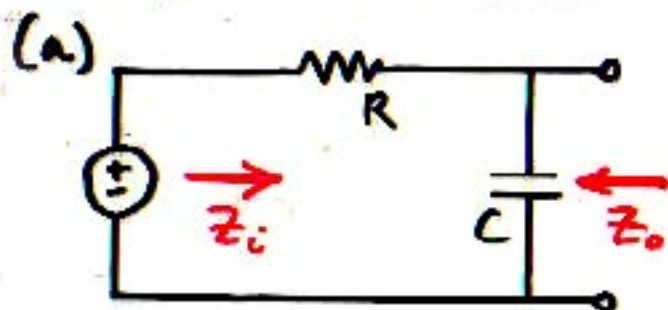
Exercise

Find the input and output impedances Z_i and Z_o in factored pole-zero form, and sketch the magnitude and phase asymptotes, for each of the two networks:



$$\begin{aligned}Z_i &= R + \frac{1}{sC} \\ &= R \left(1 + \frac{\omega_1}{s} \right) \quad \omega_1 \equiv \frac{1}{CR}\end{aligned}$$
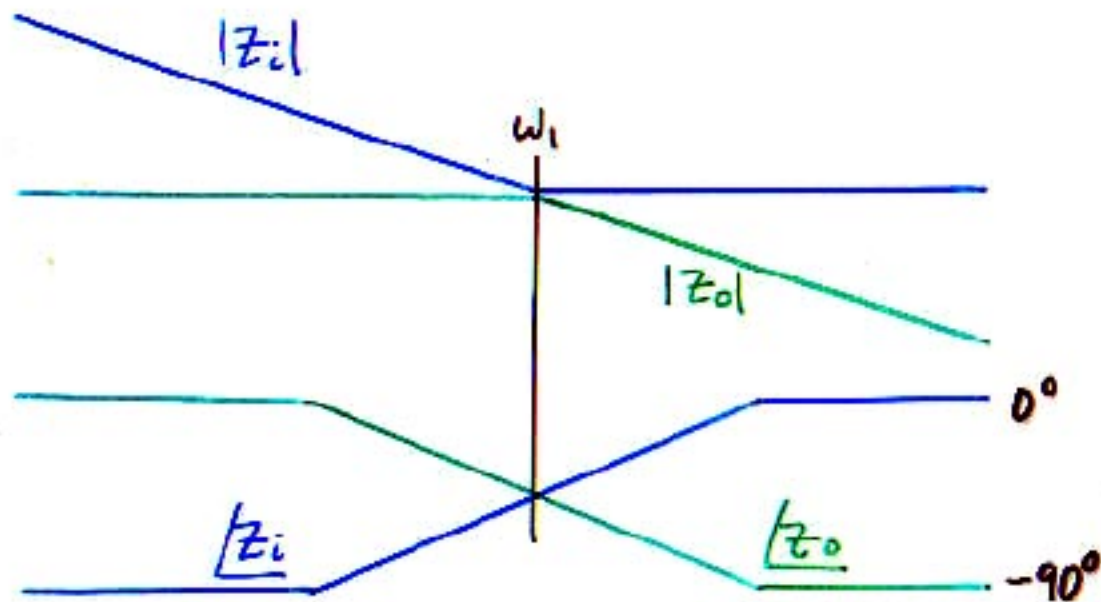
$$\begin{aligned}Z_o &= R \parallel \frac{1}{sC} \\ &= R \frac{1}{1 + \frac{s}{\omega_1}}\end{aligned}$$





$$\begin{aligned}
 Z_i &= R + \frac{1}{sC} \\
 &= R \left(1 + \frac{\omega_1}{s} \right) \quad \omega_1 = \frac{1}{CR}
 \end{aligned}$$

$$\begin{aligned}
 Z_o &= R \parallel \frac{1}{sC} \\
 &= R \frac{1}{1 + \frac{s}{\omega_1}}
 \end{aligned}$$

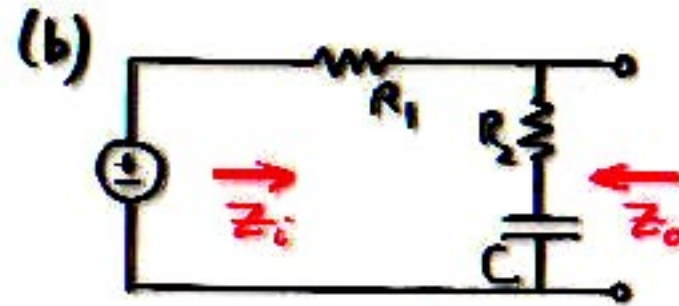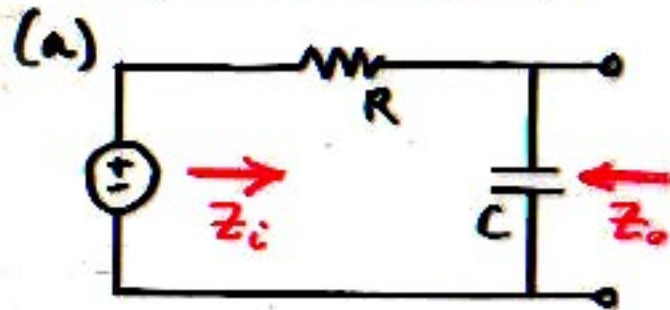
Exercise

Find the input and output impedances Z_i and Z_o in factored pole-zero form, and sketch the magnitude and phase asymptotes, for each of the two networks:



$$\begin{aligned}Z_i &= R_1 + R_2 + \frac{1}{sC} \\ &= (R_1 + R_2) \left(1 + \frac{\omega_3}{s} \right) \\ \omega_3 &\equiv \frac{1}{C(R_1 + R_2)}\end{aligned}$$
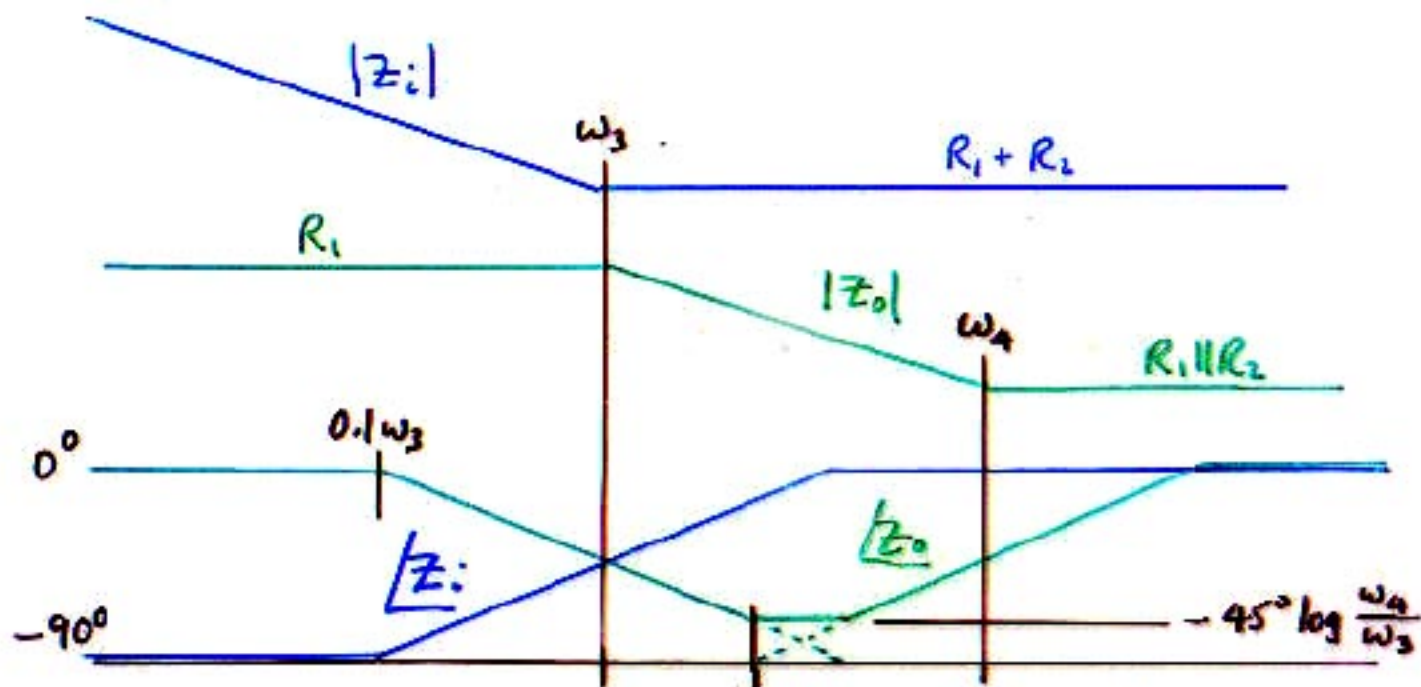
$$\begin{aligned}Z_o &= R_1 \parallel \left(R_2 + \frac{1}{sC} \right) \\ &= (R_1 \parallel R_2) \frac{1 + \frac{\omega_4}{s}}{1 + \frac{\omega_3}{s}} \\ \omega_4 &\equiv \frac{1}{CR_2}\end{aligned}$$



$$Z_i = R_1 + R_2 + \frac{1}{sC}$$

$$= (R_1 + R_2) \left(1 + \frac{\omega_3}{s} \right)$$

$$\omega_3 = \frac{1}{C(R_1 + R_2)}$$

$$Z_o = R_1 \parallel \left(R_2 + \frac{1}{sC} \right)$$

$$= (R_1 \parallel R_2) \frac{1 + \frac{\omega_4}{s}}{1 + \frac{\omega_3}{s}}$$

$$\omega_4 = \frac{1}{CR_2}$$