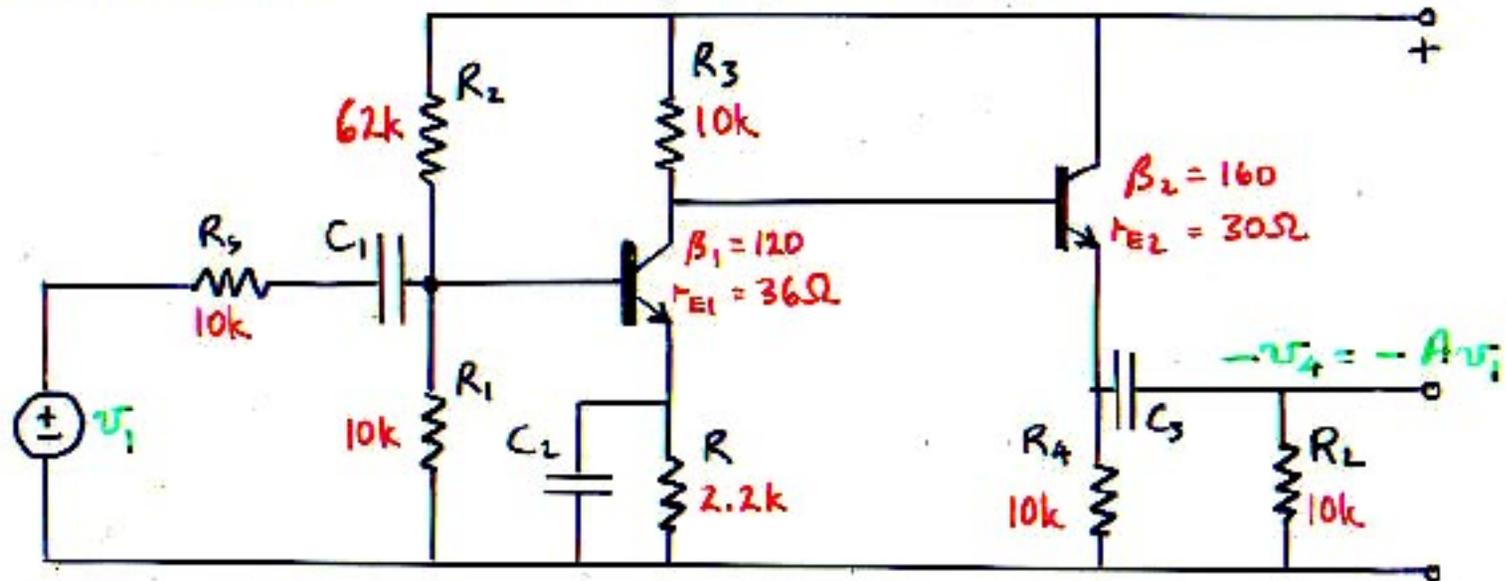


EXERCISE 7.1

SOLUTION


Example

Draw the small-signal equivalent circuit model of the common-emitter — emitter-follower amplifier:



Find the midband gain $A \equiv v_o/v_i$ analytically and numerically.

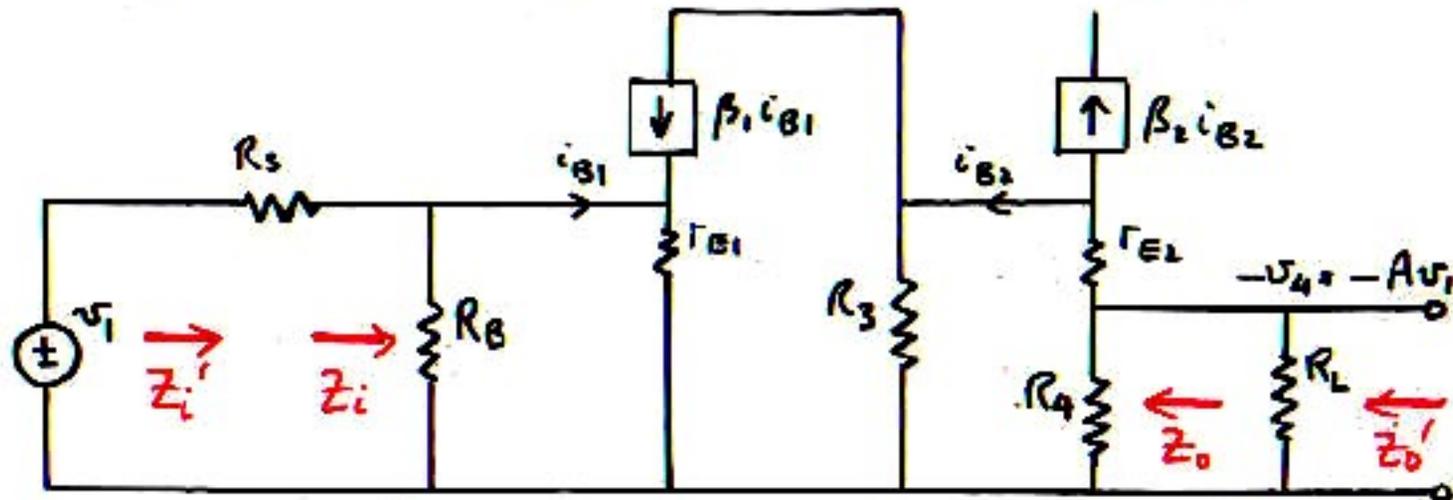
Example: the CE plus emitter follower amplifier



$$A_m = \frac{R_B}{R_B + (1 + \beta_1) r_{e1}} \cdot \frac{\beta_1 R_B}{R_s + R_B \parallel (1 + \beta_1) r_{e1}} \cdot \frac{R_4 \parallel R_L}{R_4 \parallel R_L + r_{E2} + R_3 / (1 + \beta_2)}$$

$K_1 \uparrow$ $K_2 \uparrow$ $K_3 \uparrow$

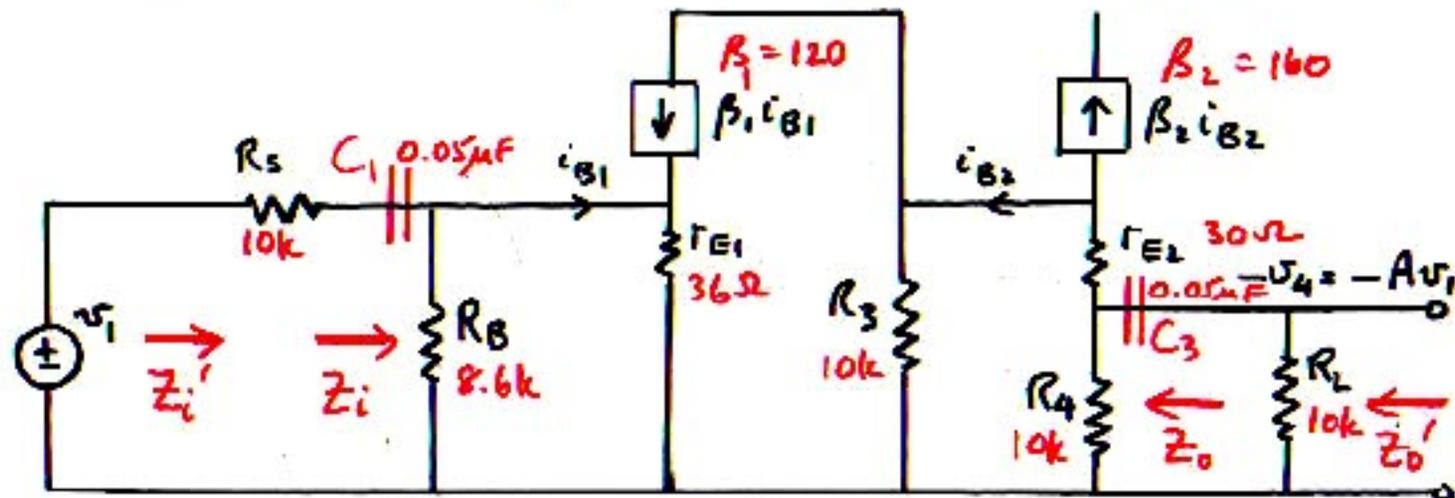Example: the CE plus emitter follower amplifier



$$A_m = \frac{R_B}{R_B + (1 + \beta_1)r_{e1}} \cdot \frac{\beta_1 R_B}{R_s + R_B \parallel (1 + \beta_1)r_{e1}} \cdot \frac{R_4 \parallel R_L}{R_4 \parallel R_L + r_{e2} + R_3 / (1 + \beta_2)}$$

$K_1 \uparrow$ $K_2 \uparrow$ $K_3 \uparrow$

Exercise


Find the gain in factored pole-zero form when the coupling capacitances C_1 and C_3 are included. Evaluate the corner frequencies, and sketch the magnitude asymptotes.

Exercise Solution


$$A = A_m \frac{1}{\left(1 + \frac{\omega_3}{s}\right) \left(1 + \frac{\omega_5}{s}\right)}$$

$$\omega_3 \equiv \frac{1}{C_1 [R_s + R_B \parallel (1 + \beta_1) r_{E1}]} = \frac{159}{0.05 [10 + \underbrace{8.6 \parallel 4.3}_{2.9}]} = 240 \text{ Hz}$$
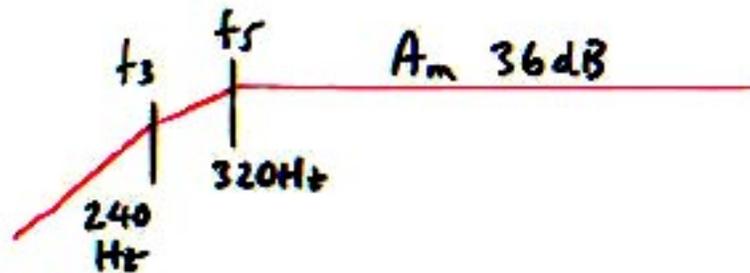
$$\omega_5 \equiv \frac{1}{C_3 \left[r_{E2} + \frac{R_3}{1 + \beta_2} \parallel (R_4 + R_L) \right]} = \frac{159}{0.05 [(0.03 + 0.06) \parallel 10 + 10]} = 320 \text{ Hz}$$



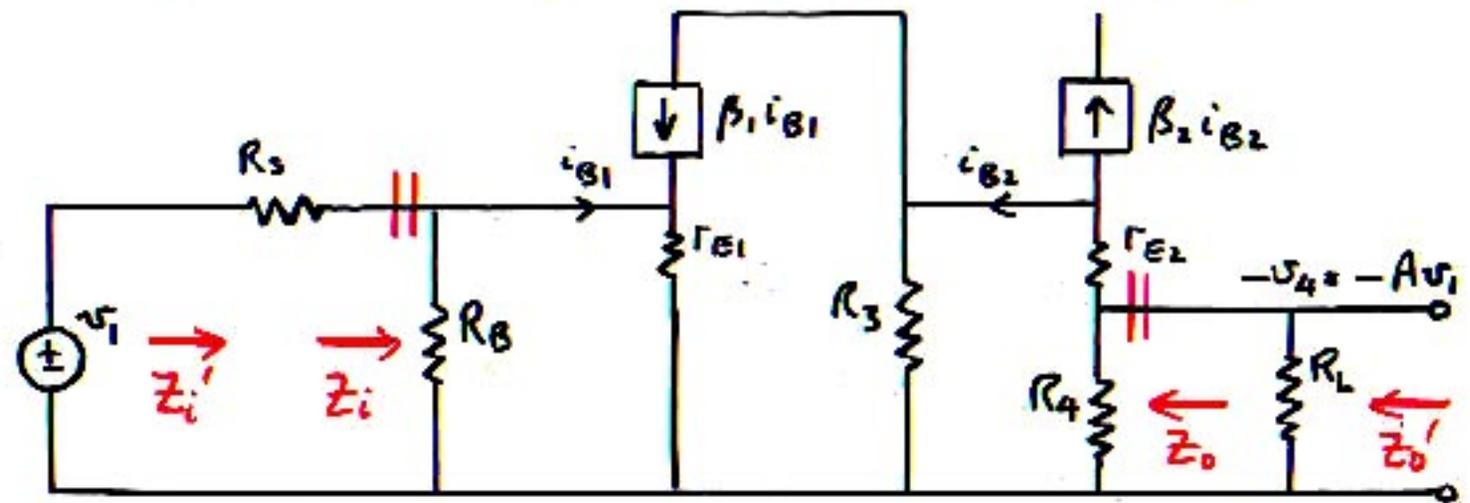Example: the CE plus emitter follower amplifier



$$A_m = \frac{R_B}{R_B + (1 + \beta_1)r_{E1}} \cdot \frac{\beta_1 R_3}{R_s + R_B \parallel (1 + \beta_1)r_{E1}} \cdot \frac{R_4 \parallel R_L}{R_4 \parallel R_L + r_{E2} + R_3 / (1 + \beta_2)}$$

$K_1 \uparrow$ $K_2 \uparrow$ $K_3 \uparrow$

Exercise

Find the impedances z_o' , z_i' , z_o , z_i in factored pole-zero form in the presence of C_1 and C_3

Exercise Solution

$$Z_o' = \frac{A}{\frac{A}{R_L} \Big|_{R_L \rightarrow 0}} = R_{om}' \frac{1}{1 + \frac{w_5}{s}} \Big|_{R_L \rightarrow 0}$$

$$= R_{om}' \frac{1 + \frac{w_5}{s} \Big|_{R_L \rightarrow 0}}{1 + \frac{w_5}{s}}$$

$$Z_o = R_{om} \frac{1 + \frac{w_5}{s} \Big|_{R_L \rightarrow \infty}}{1 + \frac{w_5}{s} \Big|_{R_L \rightarrow \infty}} = R_{om} \left(1 + \frac{w_5}{s} \Big|_{R_L \rightarrow 0} \right)$$

$$Z_i' = \frac{R_s A \Big|_{R_s \rightarrow \infty}}{A}$$

$$= R_{im}' \frac{1}{1 + \frac{w_3}{s} \Big|_{R_s \rightarrow \infty}} = R_{im}' \left(1 + \frac{w_3}{s} \right)$$

$$Z_i = R_{im} \left(1 + \frac{w_3}{s} \Big|_{R_s \rightarrow 0} \right)$$


$$w_3 = \frac{1}{C_1 [R_s + R_B \parallel (1 + \beta_1) r_{E1}]}$$

$$w_5 = \frac{1}{C_3 \left[\left(r_{E2} + \frac{R_3}{1 + \beta_2} \right) \parallel R_4 + R_L \right]}$$

$$w_5 \Big|_{R_L \rightarrow 0} = \frac{1}{C_3 \left[\left(r_{E2} + \frac{R_3}{1 + \beta_2} \right) \parallel R_4 \right]}$$

$$w_3 \Big|_{R_s \rightarrow 0} = \frac{1}{C_1 [R_B \parallel (1 + \beta_1) r_{E1}]}$$

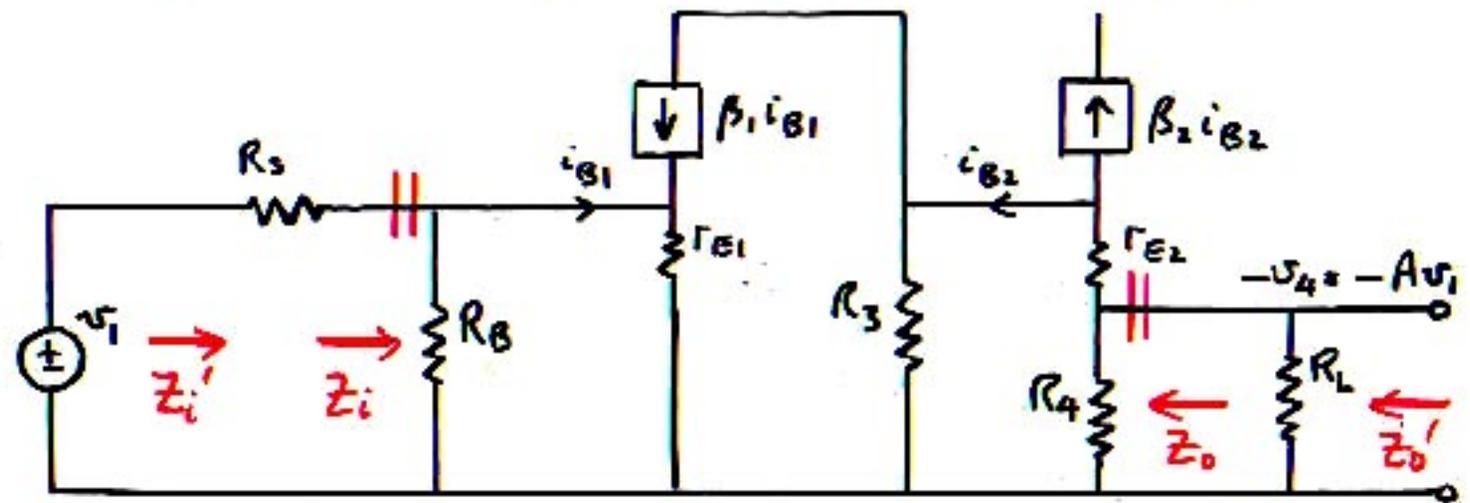Example: the CE plus emitter follower amplifier



$$A_m = \frac{R_B}{R_B + (1 + \beta_1)r_{E1}} \cdot \frac{\beta_1 R_3}{R_s + R_B \parallel (1 + \beta_1)r_{E1}} \cdot \frac{R_4 \parallel R_L}{R_4 \parallel R_L + r_{E2} + R_3 / (1 + \beta_2)}$$

$K_1 \uparrow$ $K_2 \uparrow$ $K_3 \uparrow$

Exercise

Find the impedances z_o' , z_i' , z_o , z_i in factored pole-zero form in the presence of C_1 and C_3